

Computing $\overline{v_i^2}$ (short-circuit inputs and equate)

CKT W/N.S.

$$v_o = v_{ia} \frac{R_f}{R_f + R_e} + i_{ia} \frac{R_f R_e}{R_f + R_e} + \frac{R_f}{R_f + R_e} v_e + \frac{R_e}{R_f + R_e} v_f$$

(Resolve the circuit)

Making $R = R_f || R_e$ and adding the thermal contributions

$$\overline{v_i^2} = \overline{v_{ia}^2} + \underbrace{i_{ia}^2 R^2}_{\text{usually negligible}} + \underbrace{4KTR}_{\text{Thermal noise of } R_f || R_e}$$

Amplifier noise


Thermal noise of $R_f || R_e$

usually negligible

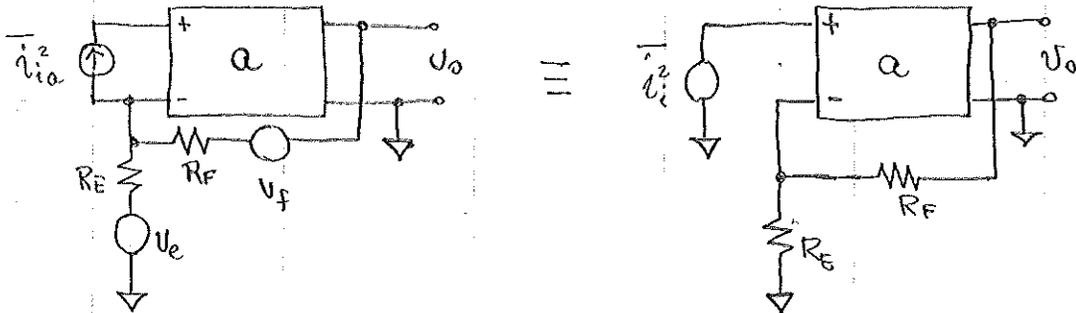13-782 500 SHEETS FULLER SQUARE
42-381 50 SHEETS EYEGLASS SQUARE
42-382 100 SHEETS EYEGLASS SQUARE
42-383 200 SHEETS EYEGLASS SQUARE
42-384 500 SHEETS EYEGLASS SQUARE
42-385 1000 SHEETS EYEGLASS SQUARE
42-386 200 SHEETS WHITE SQUARE
42-387 500 SHEETS WHITE SQUARE
42-388 1000 SHEETS WHITE SQUARE
42-389 200 SHEETS WHITE SQUARE
42-390 500 SHEETS WHITE SQUARE
42-391 1000 SHEETS WHITE SQUARE
42-392 200 SHEETS WHITE SQUARE
42-393 500 SHEETS WHITE SQUARE
42-394 1000 SHEETS WHITE SQUARE
42-395 200 SHEETS WHITE SQUARE
42-396 500 SHEETS WHITE SQUARE
42-397 1000 SHEETS WHITE SQUARE
42-398 200 SHEETS WHITE SQUARE
42-399 500 SHEETS WHITE SQUARE
42-400 1000 SHEETS WHITE SQUARE
Made in U.S.A.



Computing $\overline{i_i^2}$ (Open ckt inputs and equate)




$$i_{ia} = i_i$$

v_e and v_f are not amplified in this case and the contribution of the current source is the same in both cases.




Thus, the input noise current is unaffected by the presence of feedback.

- Also applies for any series feedback at input.
 $R_f \rightarrow \infty \Rightarrow R \Rightarrow R_e$

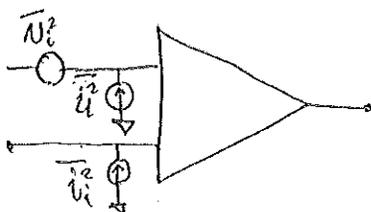OpAmps are considered 3-port devices and use a different circuit.



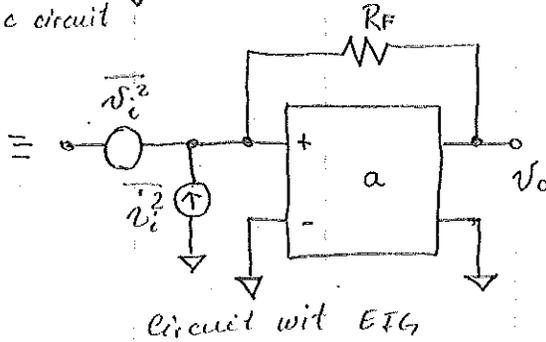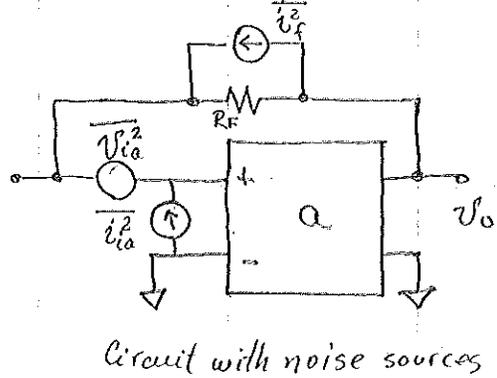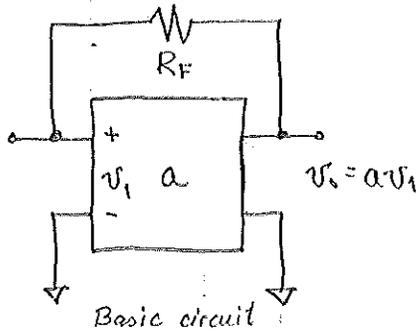As a second practical case, consider a shunt-shunt feedback



Finding i_i : Open-ckt input and solve for v_o & equate

$$v_{o1} = i_i R_F \quad v_{o2} = v_{ia} \quad v_{o3} = i_f R_F \quad \text{in ckt's: } v_o = i_i R_F$$

Thus $i_i R_F = v_{ia} R_F + v_{ia} + i_f R_F \therefore i_i = v_{ia} + \frac{v_{ia}}{R_F} + i_f$

Assuming independence:

$$\overline{i_i^2} = \overline{i_{ia}^2} + \frac{\overline{v_{ia}^2}}{R_F^2} + 4KT \frac{1}{R_F}$$

\uparrow Amplifier current noise
 \uparrow Attenuated amplifier noise (negligible)
 \uparrow Thermal noise in R_F

Finding v_i : Short-ckt input and solve for v_o & equate:

Note that all current sources are shorted and $\overline{v_i^2} = \overline{v_{ia}^2}$

- In this case, the feedback has no effect on the voltage input noise.
- This second case readily applies to op-amps, because connecting one input to GND makes op-amp a two-port device
- When analyzing a BJT, these results justify ignoring $C_\mu \Rightarrow$ Behaves as shunt feedback and has no thermal noise component. The second term would become $\overline{v_{ia}^2} / |Z_F|^2$ with Z_F the impedance of C_μ , very large at practical frequencies, justifying the term as negligible


12-782 500 SHEETS FILLER 5 SQUARE
 42-381 50 SHEETS GVE-BASE 5 SQUARE
 42-382 100 SHEETS GVE-BASE 5 SQUARE
 42-383 100 SHEETS GVE-BASE 5 SQUARE
 42-384 100 SHEETS GVE-BASE 5 SQUARE
 42-385 100 RECYCLED WHITE 5 SQUARE
 42-386 200 RECYCLED WHITE 5 SQUARE
 Made in U.S.A.

Noise Figure: Specifies noise performance in ckt. or device.

- Usage limited to circuits with resistive source impedance

Noise figure: $F = \frac{\text{Input SNR}}{\text{Output SNR}}$ in dB $(10 \log_{10})$

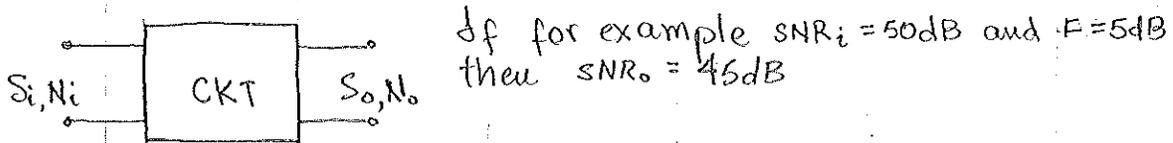- F measures the SNR degradation caused by the circuit



Assume S & N represent the signal & noise power in a ckt.

$$F = \frac{S_i}{N_i} \cdot \frac{N_o}{S_o} \quad **$$

Assuming an ideal noiseless amplifier, all noise will come from the source resistance @ input. If the amplifier has gain G

$$S_o = G S_i \quad \text{and} \quad N_o = G N_i \Rightarrow F = 1 = 0 \text{dB}$$

However, decomposing F as in **, $F = \frac{N_o}{G N_i}$ resulting

$$F = \frac{\text{Total output noise}}{\text{Output noise due to source resistance}}$$

F is specified for a small bandwidth around some $f \gg \Delta f$: Spot noise figure

Noise Temperature: (T_n)

The temperature at which the source resistance R_s must be held such that the noise output in the circuit due to R_s equals the noise output due to the complete circuit.

- Useful for noise measures in very-low-noise amplifiers where $F \approx 1$

12-782
42-381
42-382
42-383
42-999
43-000

