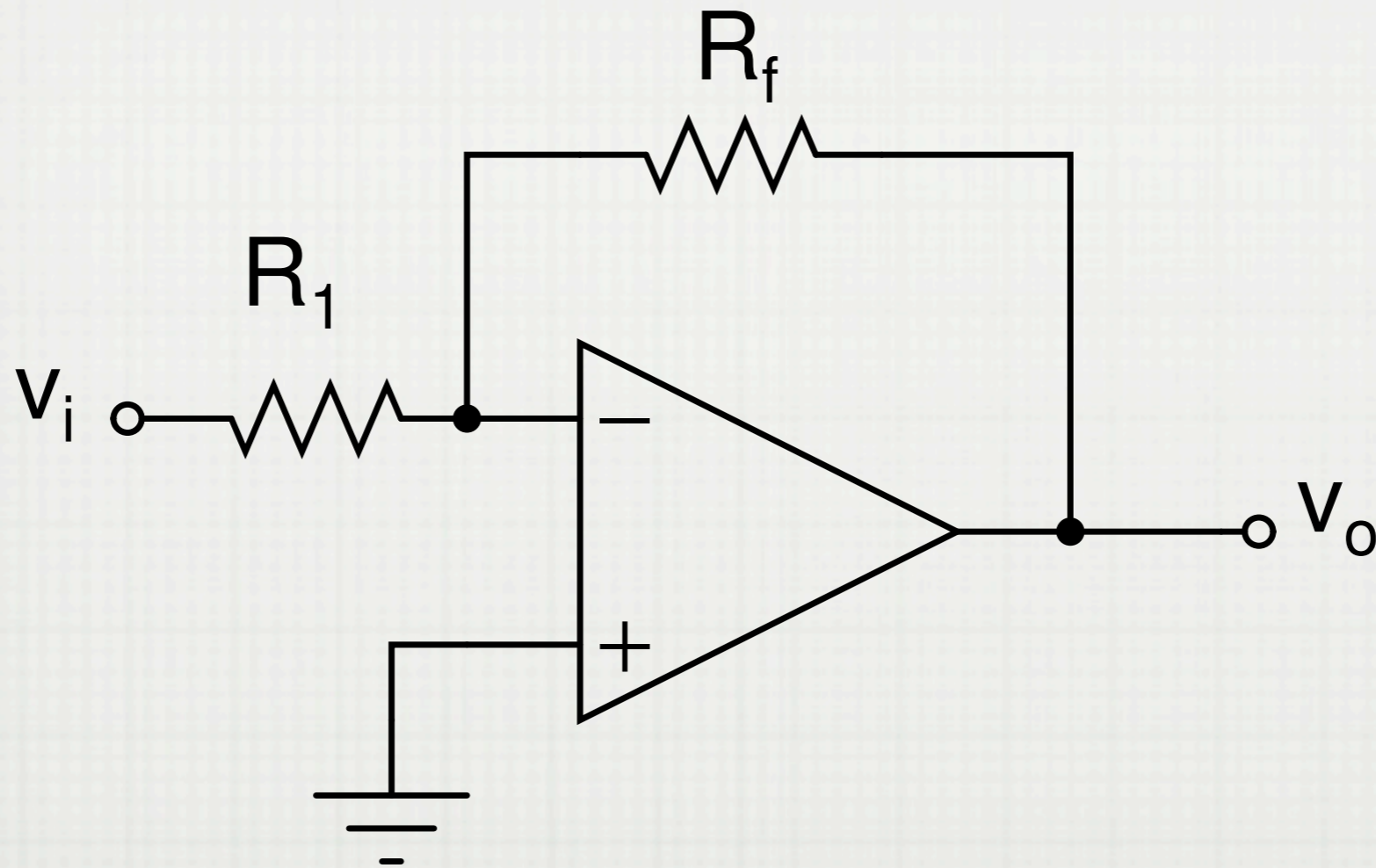


# OP-AMP APPLICATIONS

INEL 4202 - ELECTRONICS II


# INVERTING AMPLIFIER

---




# NON-INVERTING AMPLIFIER

---

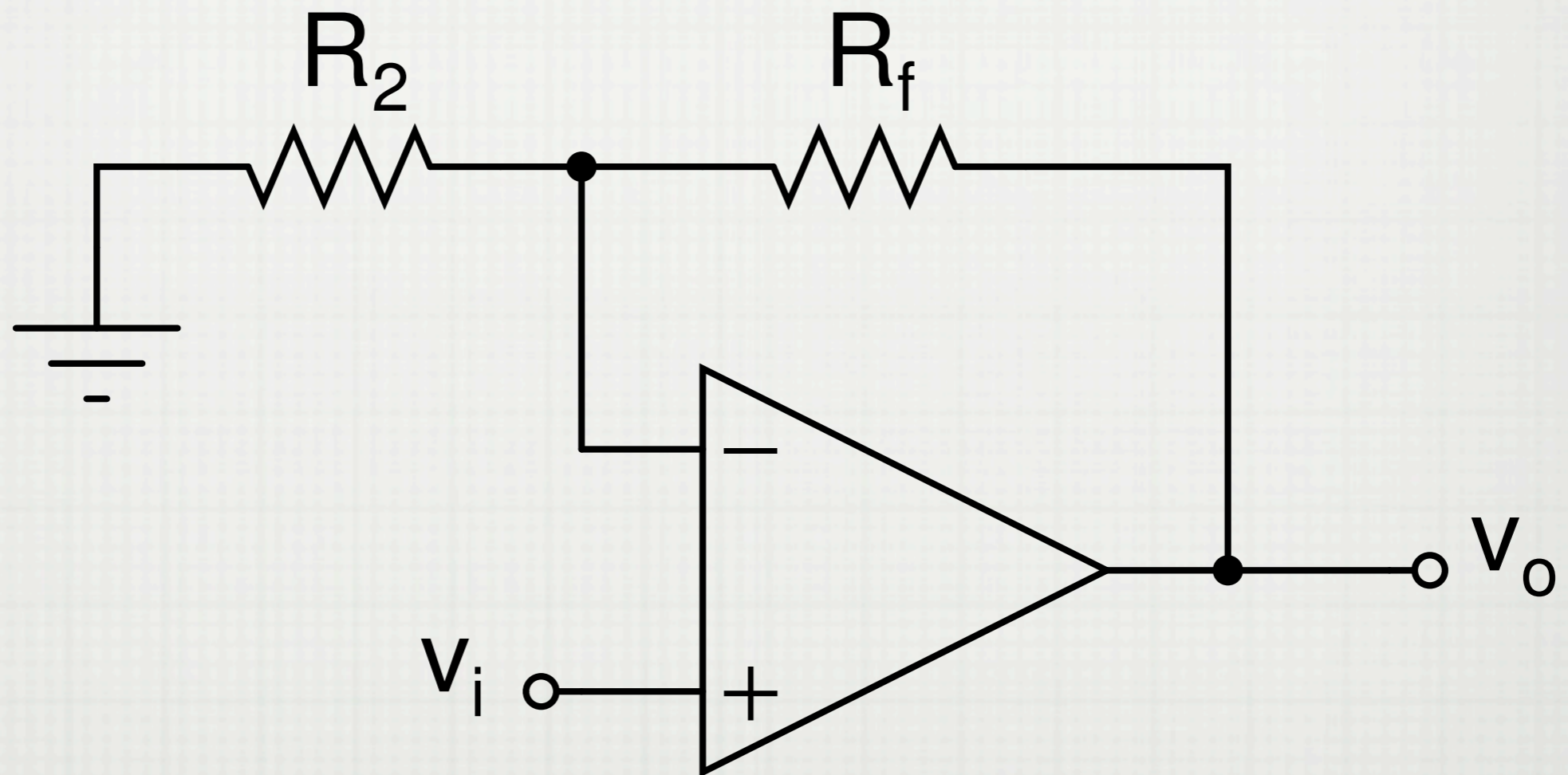


# BUFFER AMPLIFIER

---

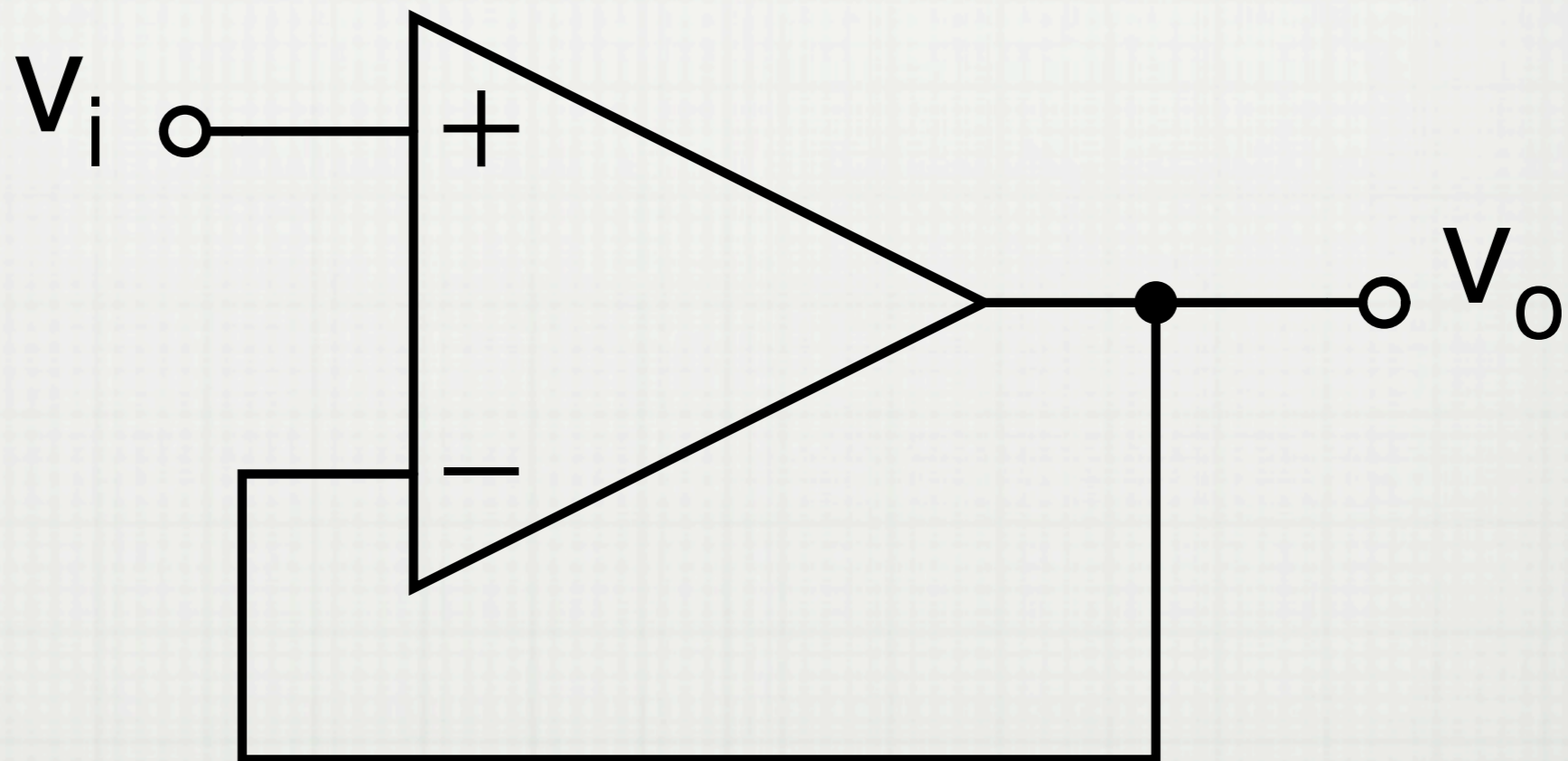


# SUMMING AMPLIFIER

---

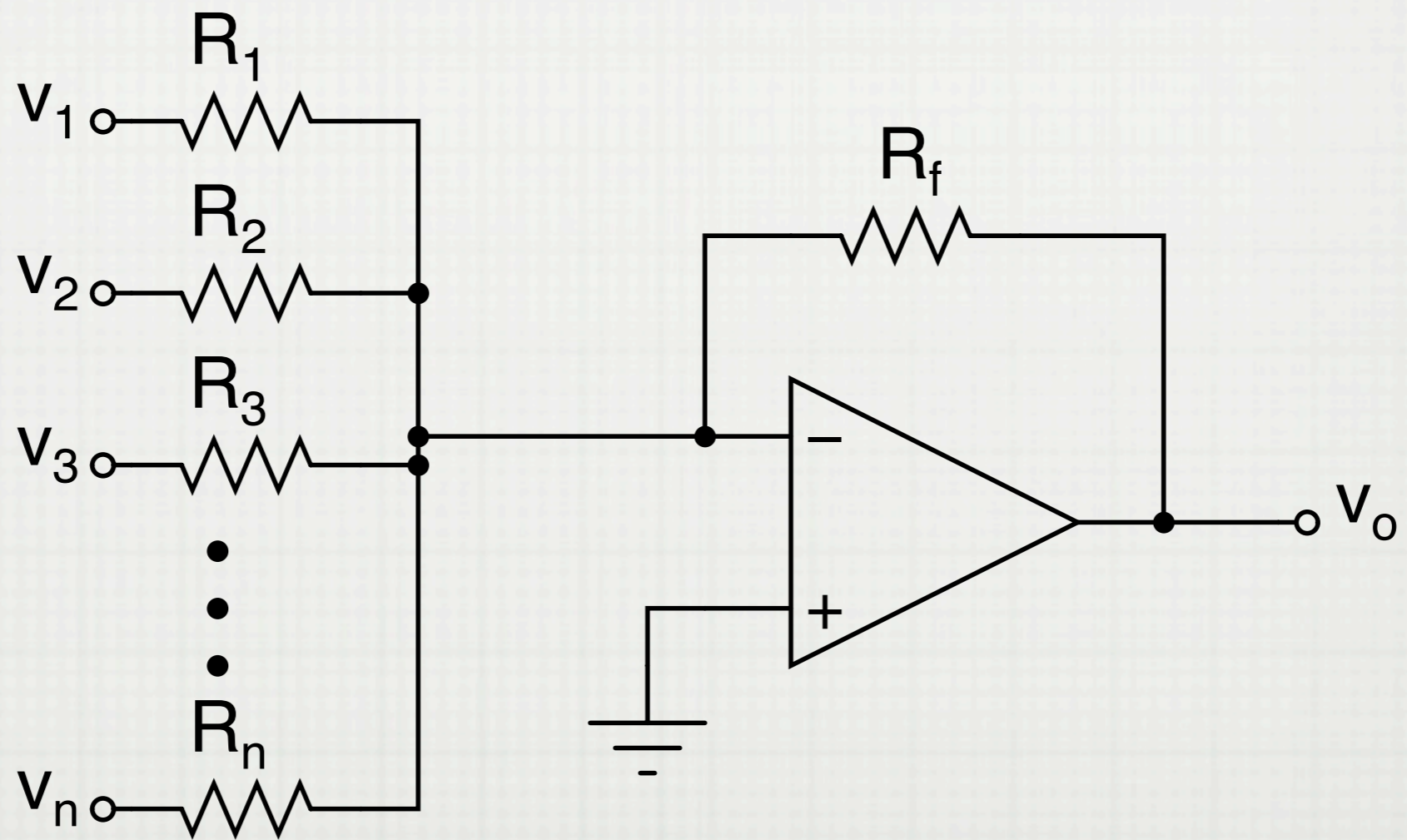


# DIFFERENCE AMPLIFIER

---

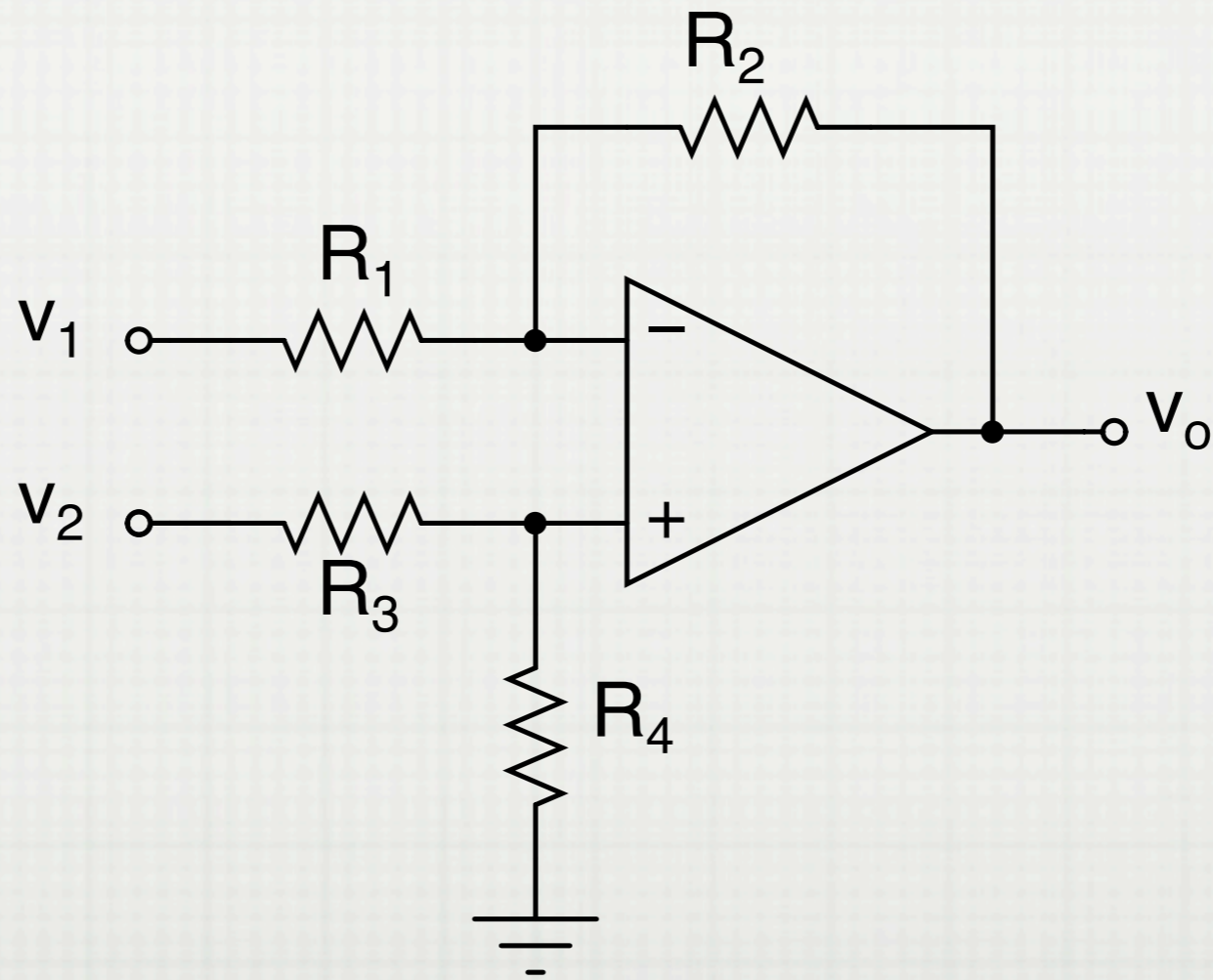


# I-V CONVERTER

---

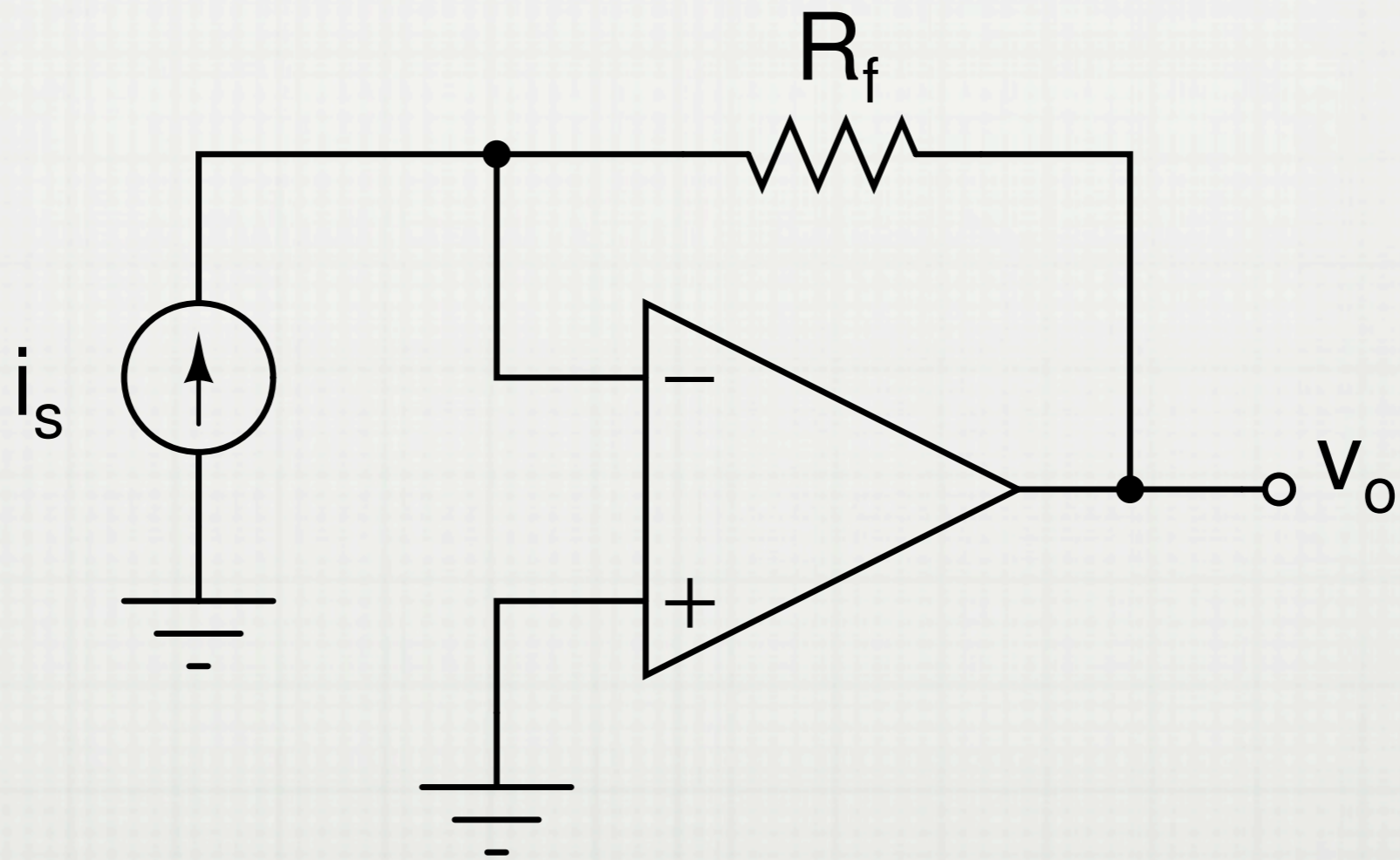


# V-I CONVERTER

---

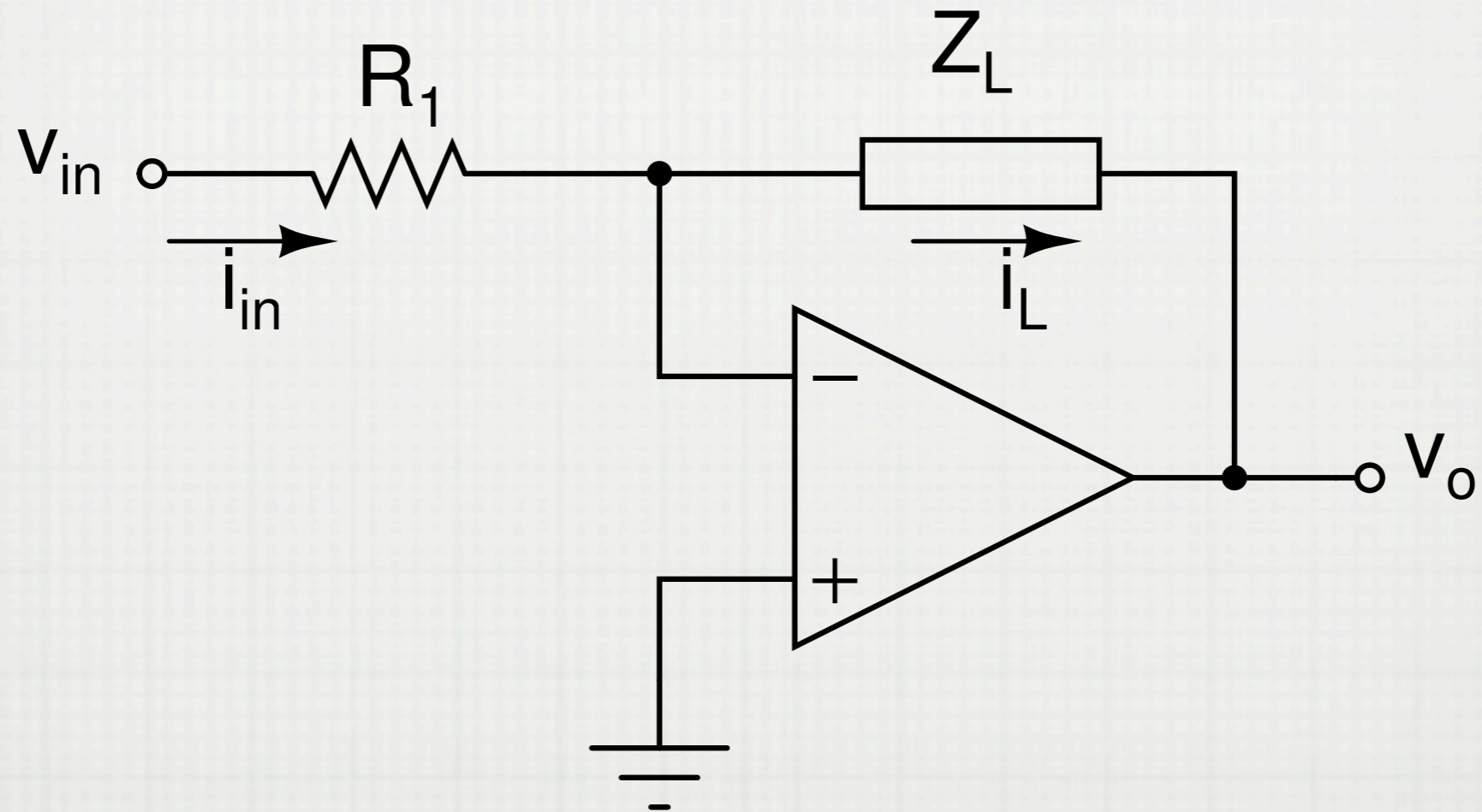


# INTEGRATOR

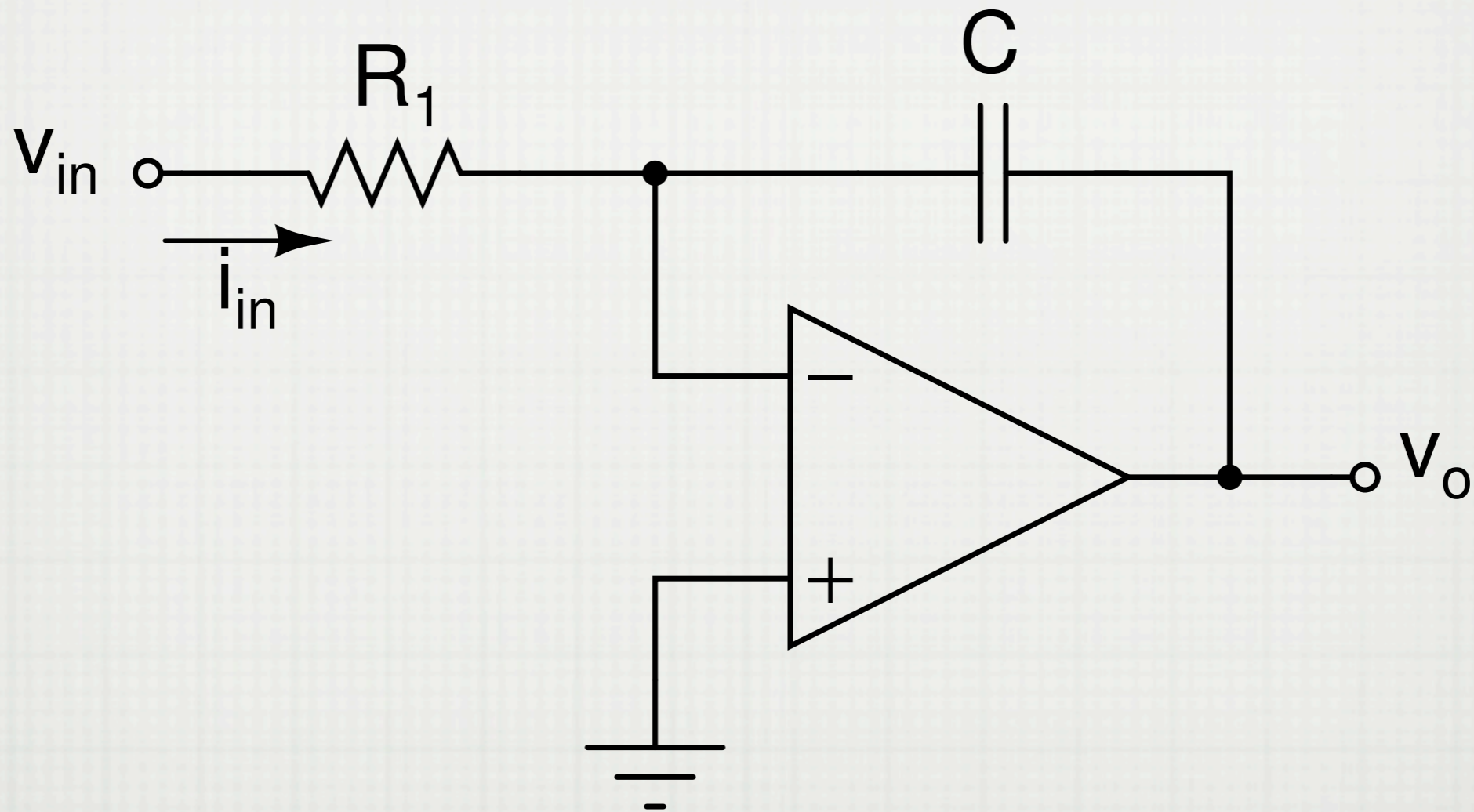


# LOW-PASS FILTER

---

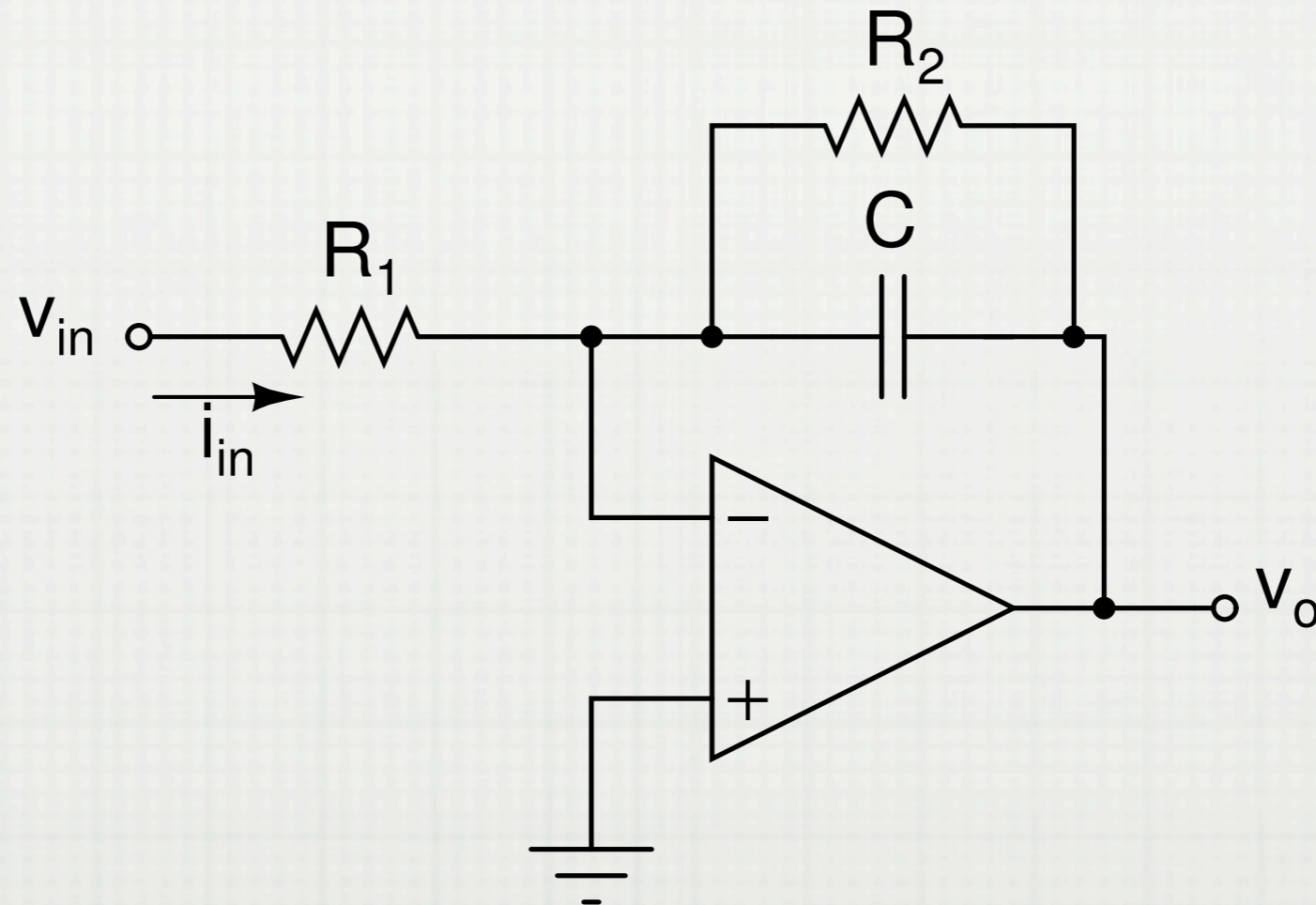


# DIFFERENTIATOR

---

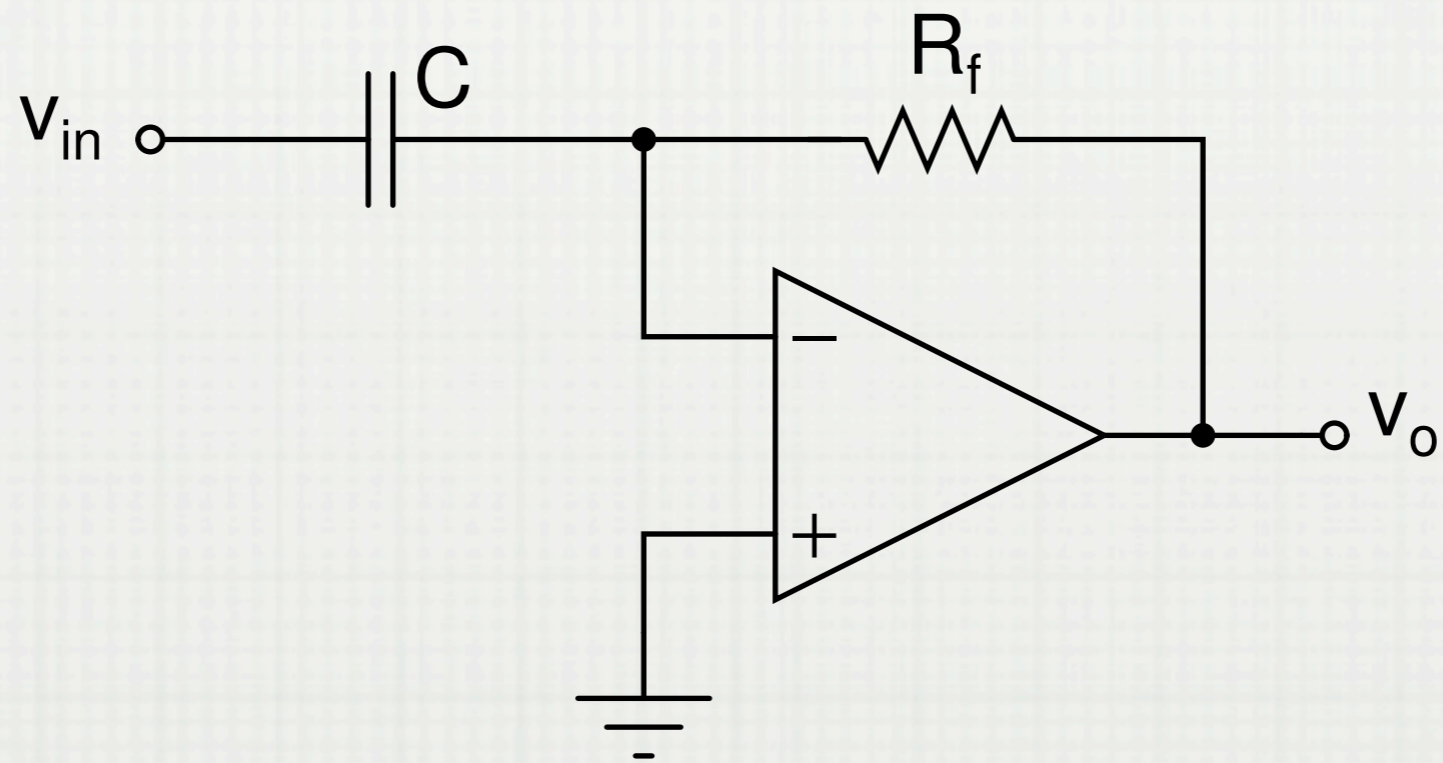


# HIGH-PASS FILTER

---

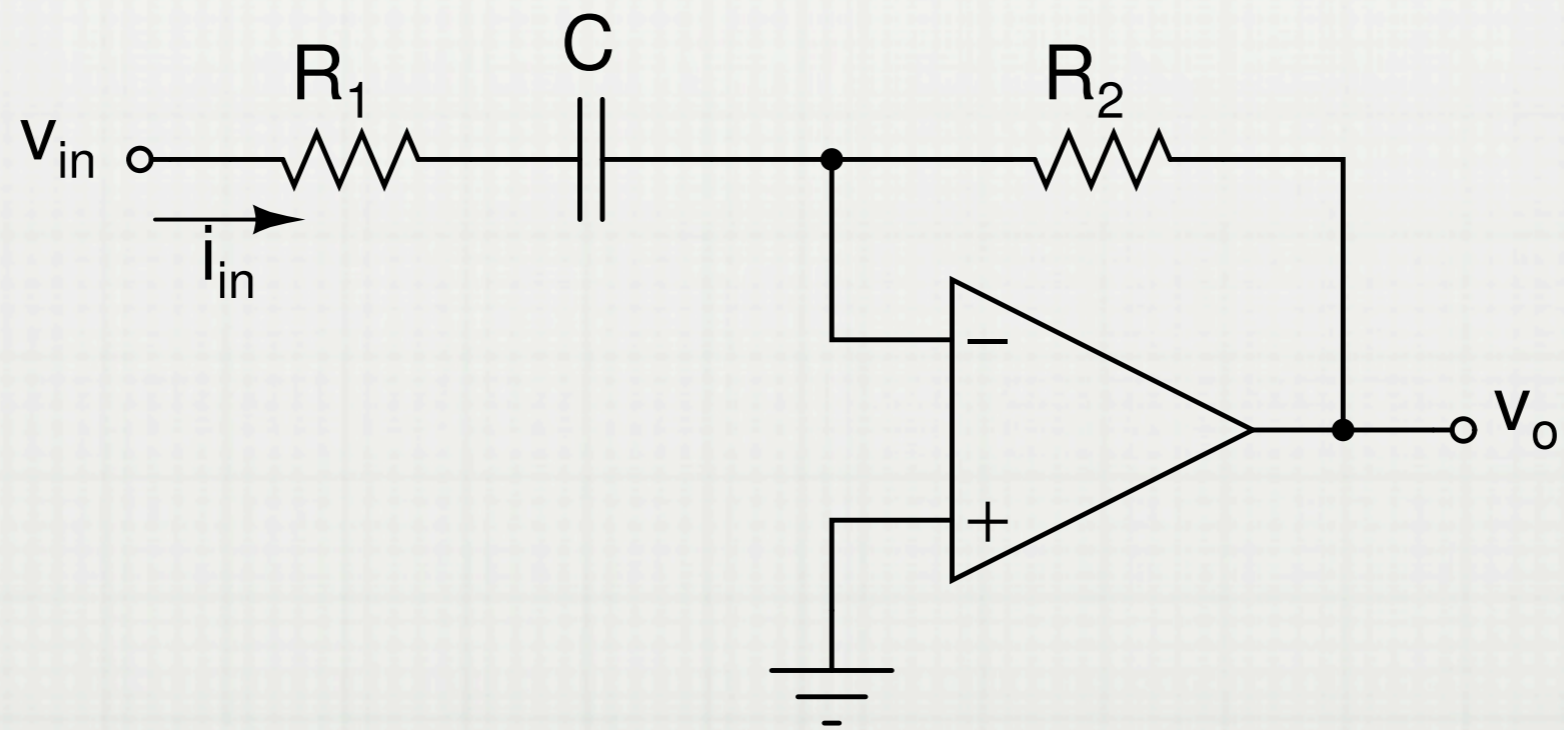


# PRECISION RECTIFIER

---

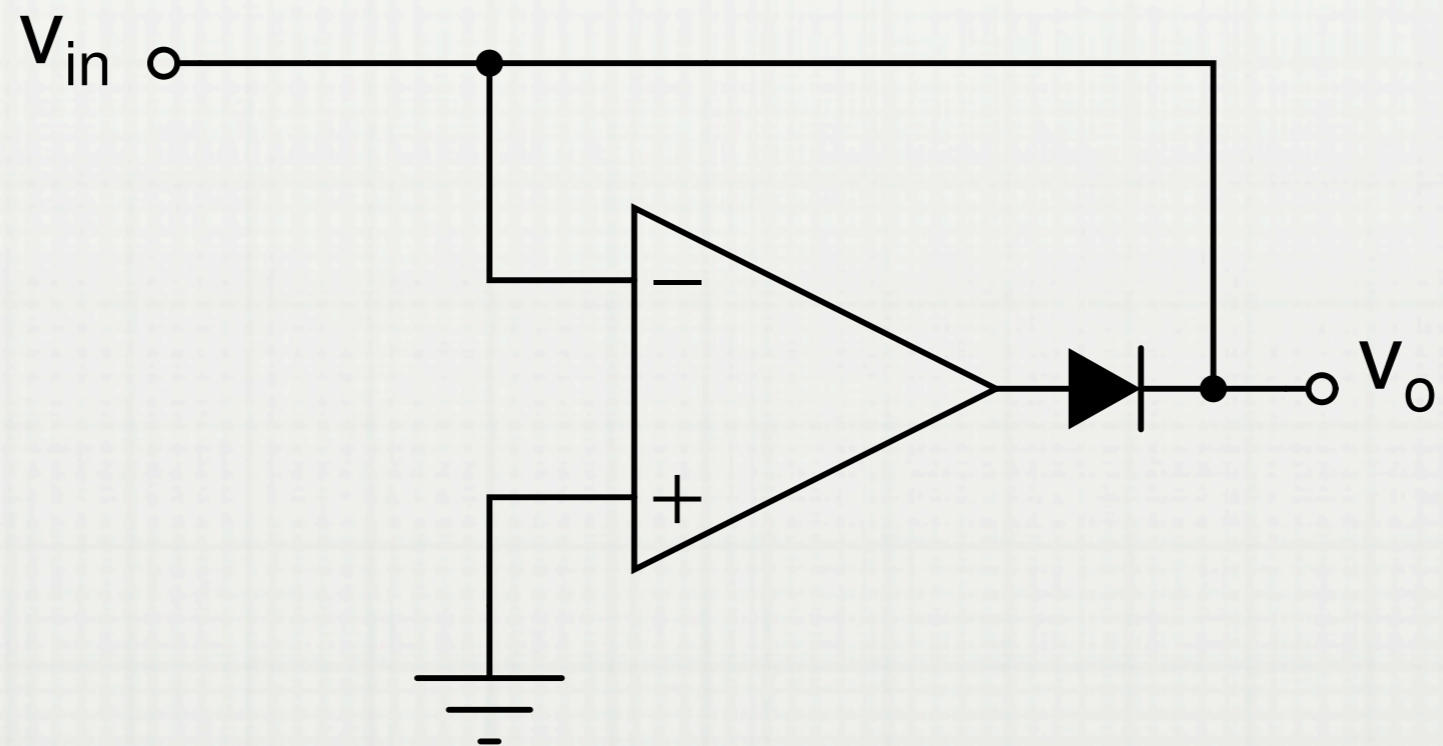


# SIMPLE LOG CONVERTER

---

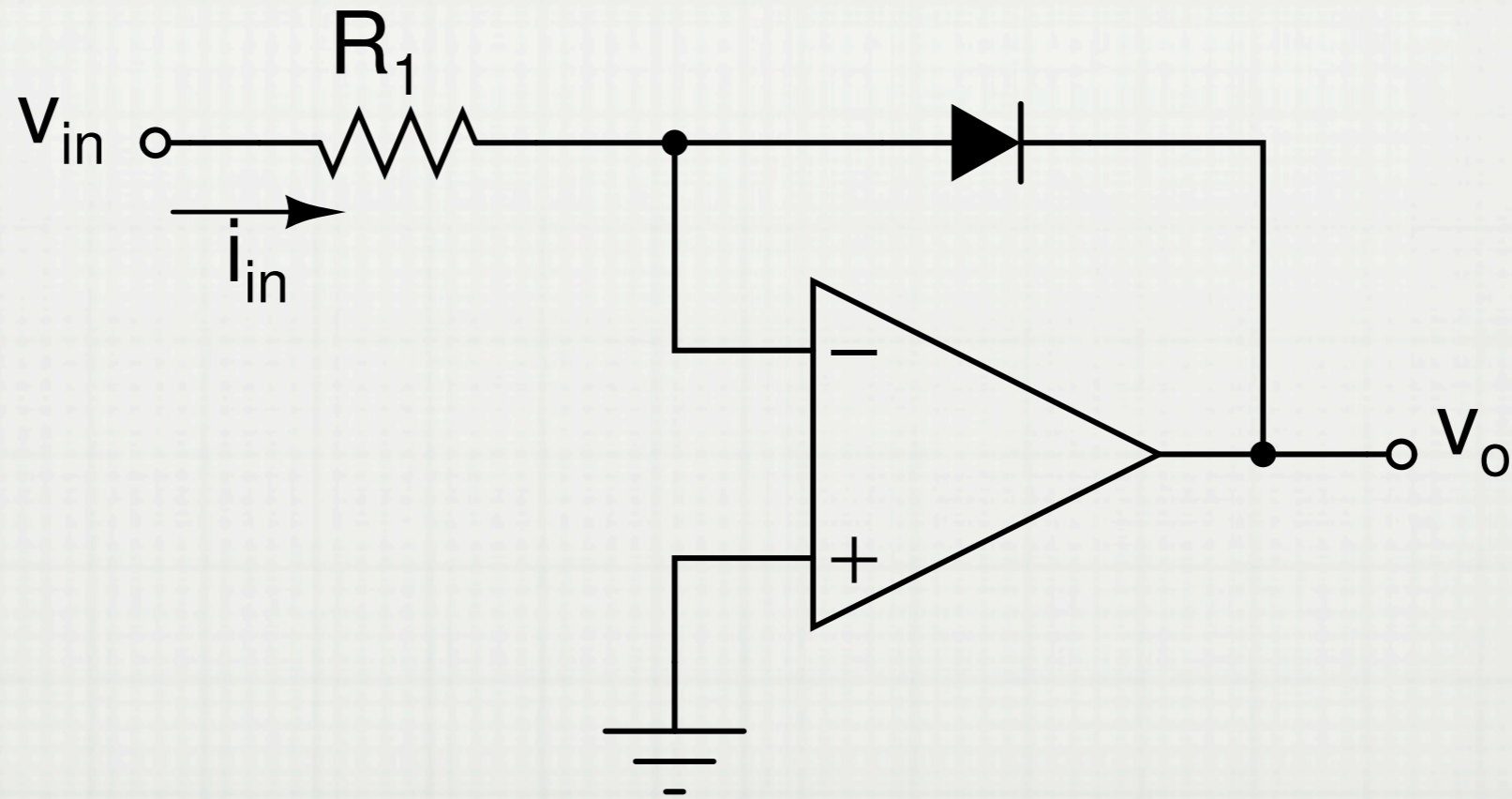


# ANTILOG CONVERTER


---

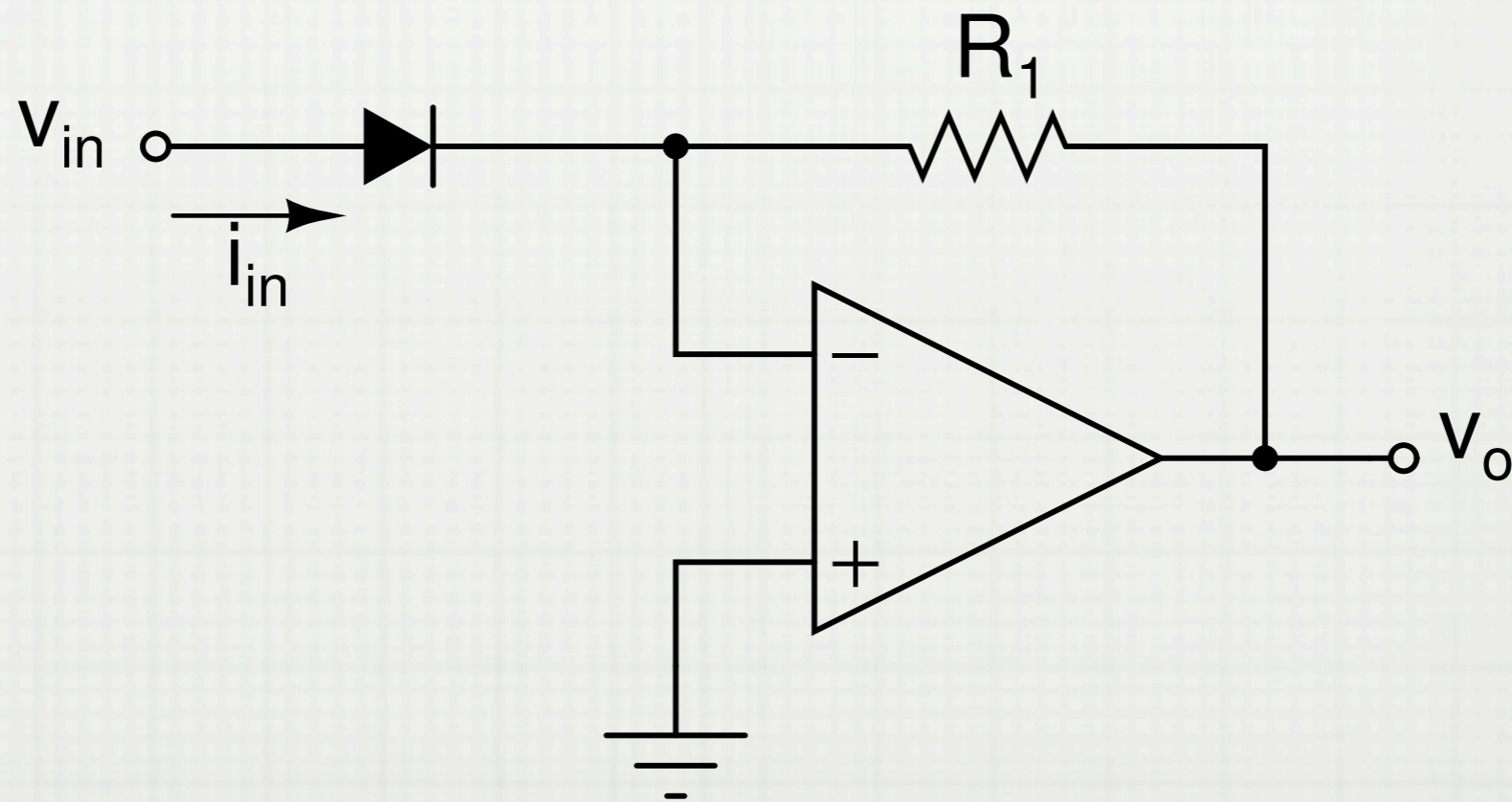


# COMPARATOR

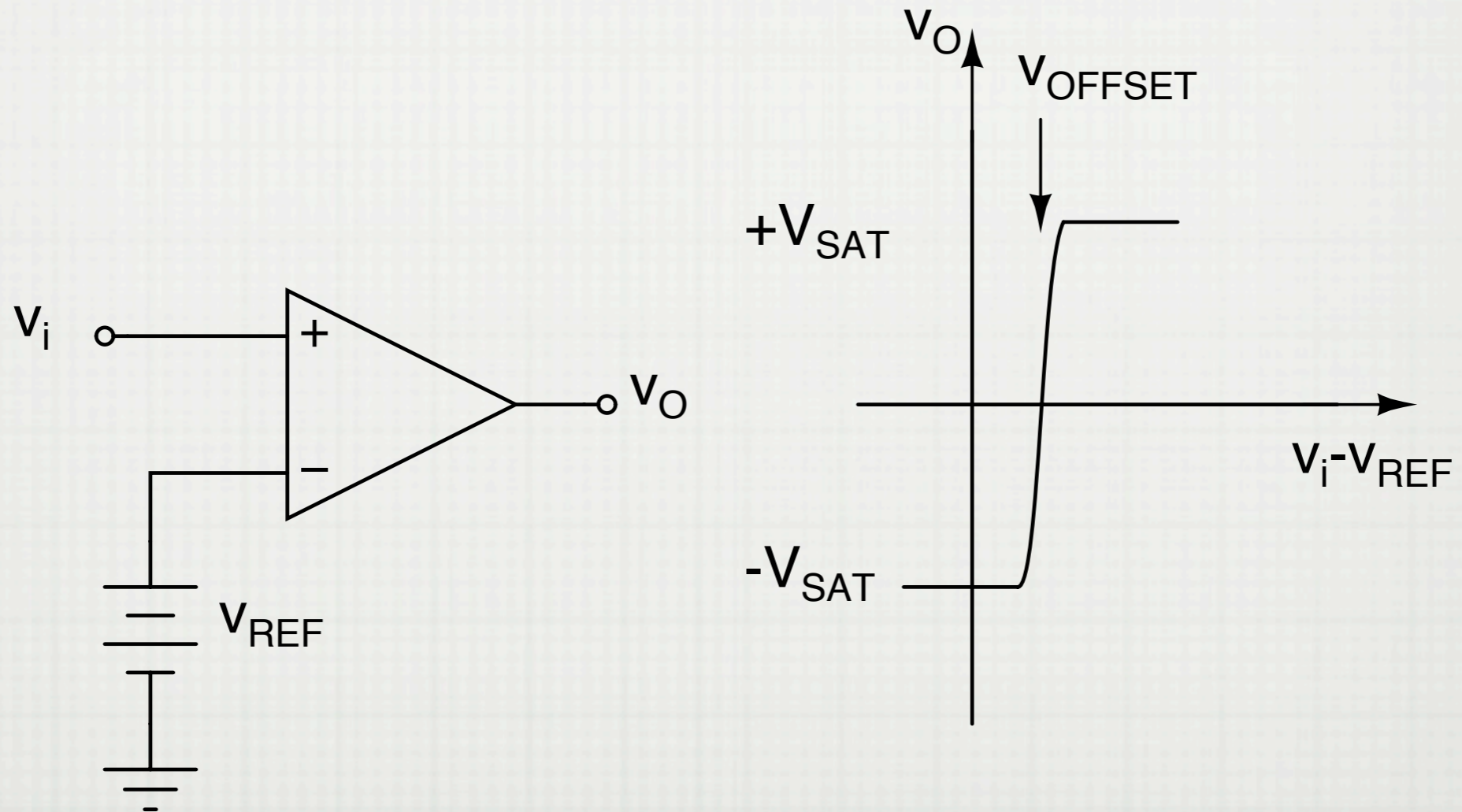


# ZERO-CROSSING DETECTOR

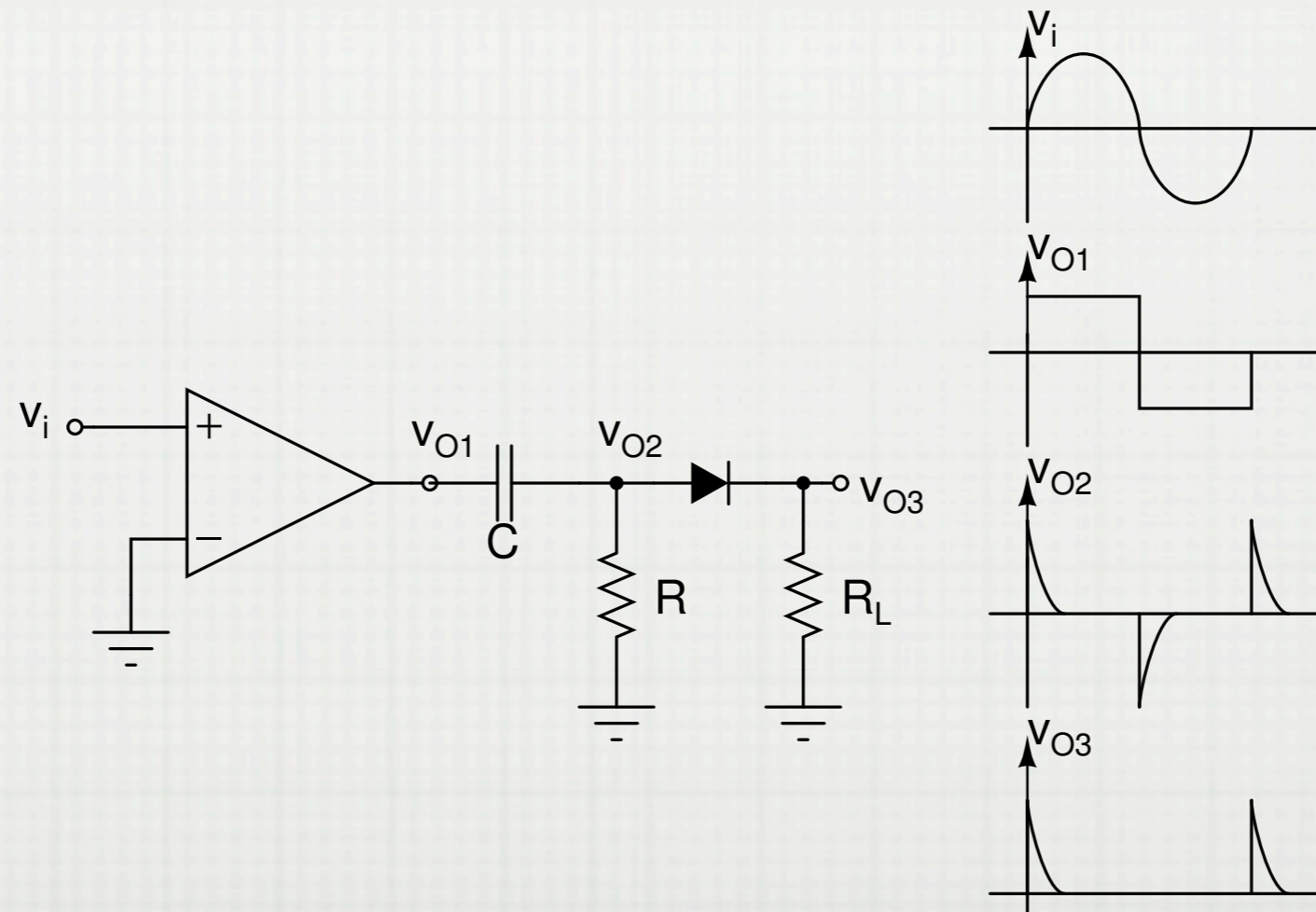


# SQUARE-WAVE GENERATOR

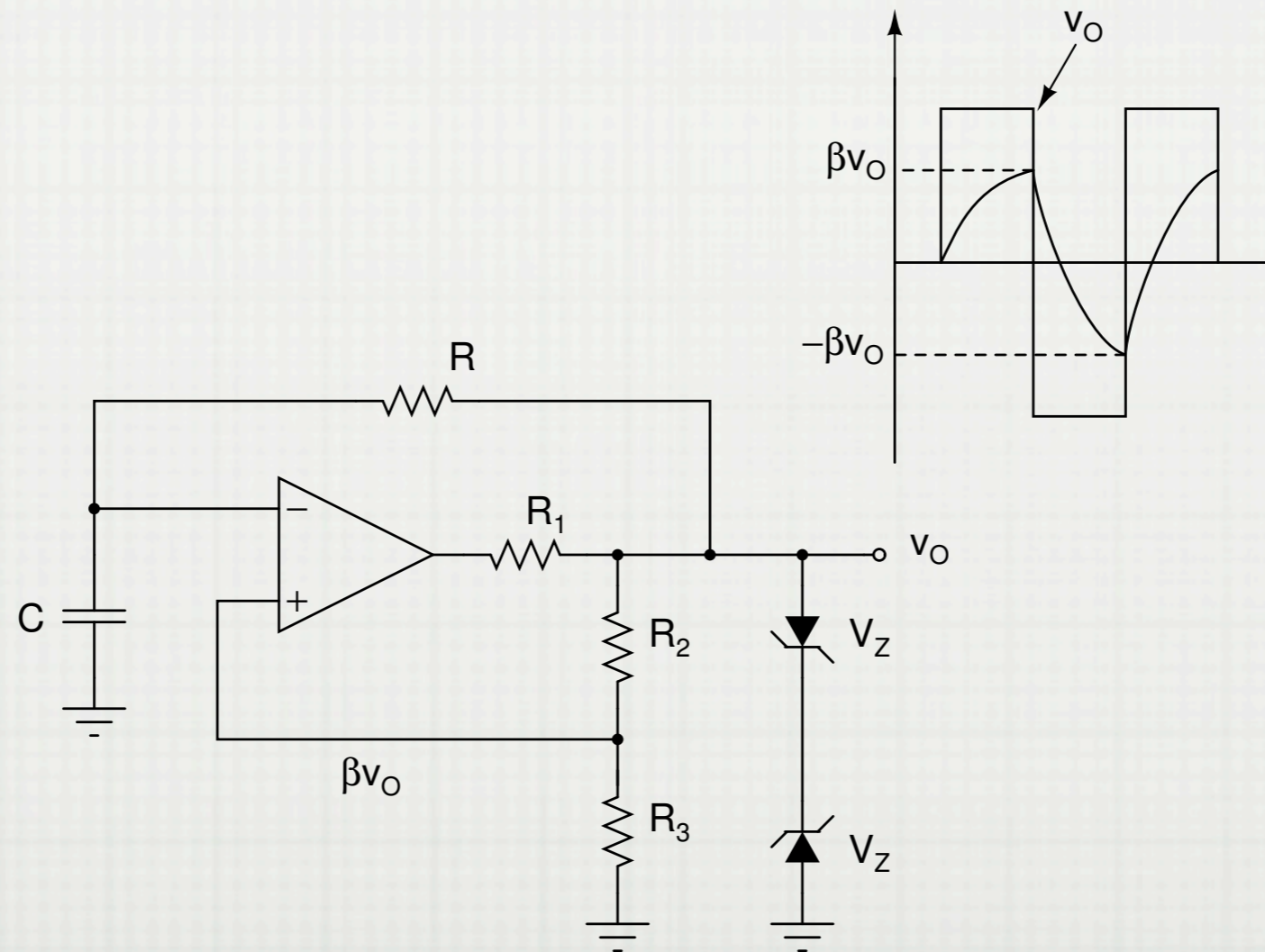

# HOWLAND CURRENT PUMP

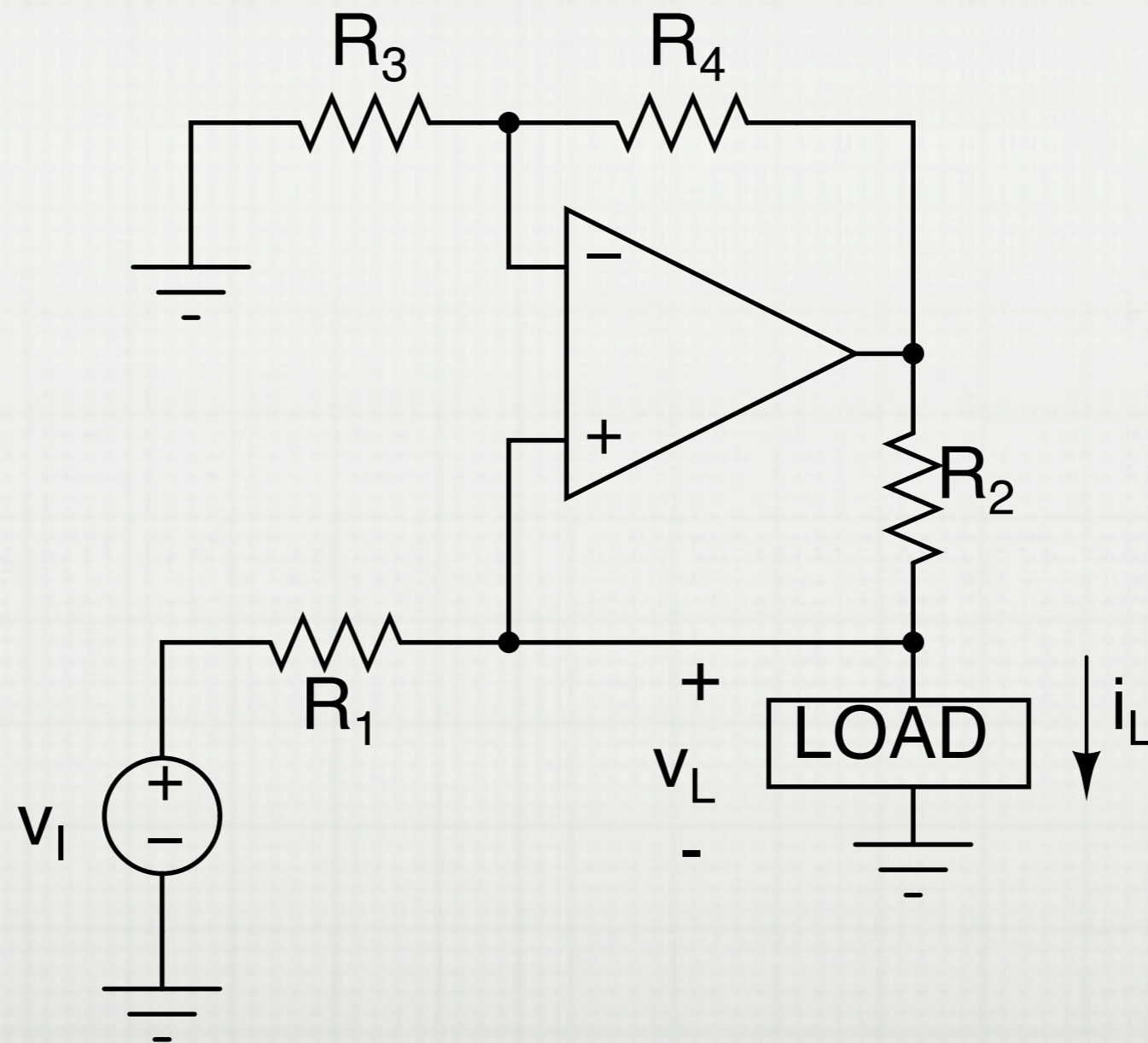


# FLOATING LOAD V-TO-I

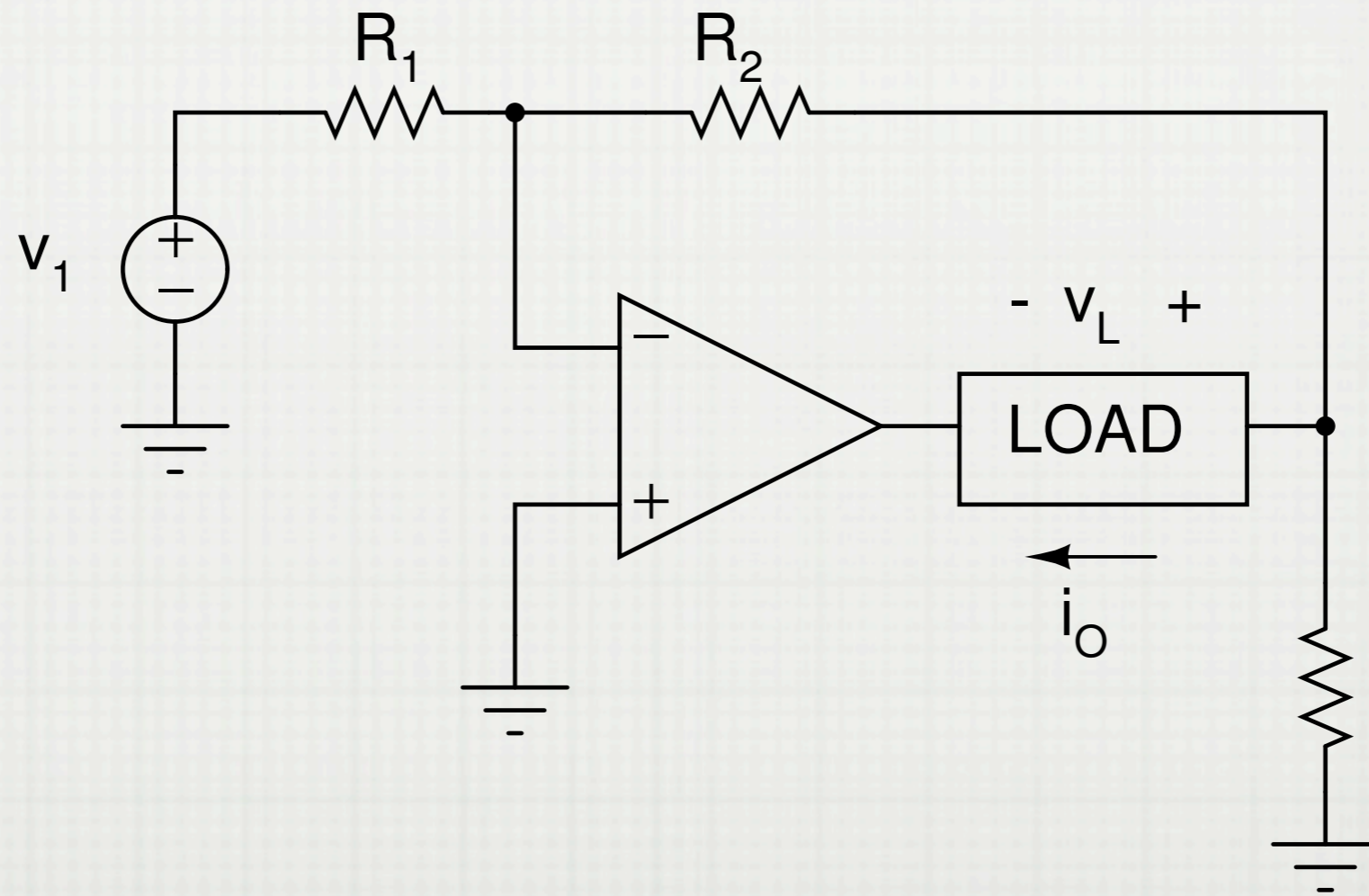


# GROUNDING-LOAD CURRENT AMP

---

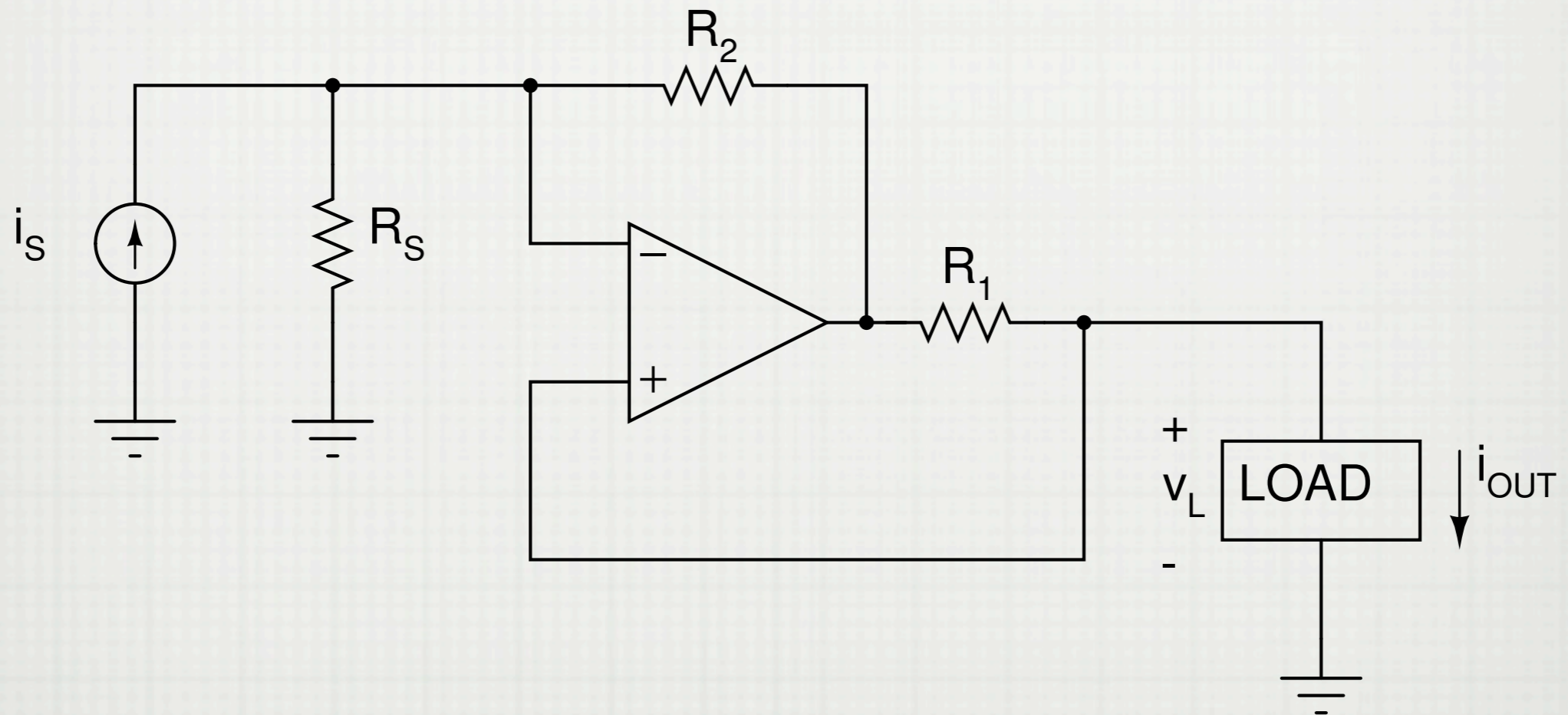


# INSTRUMENTATION AMPLIFIER

---

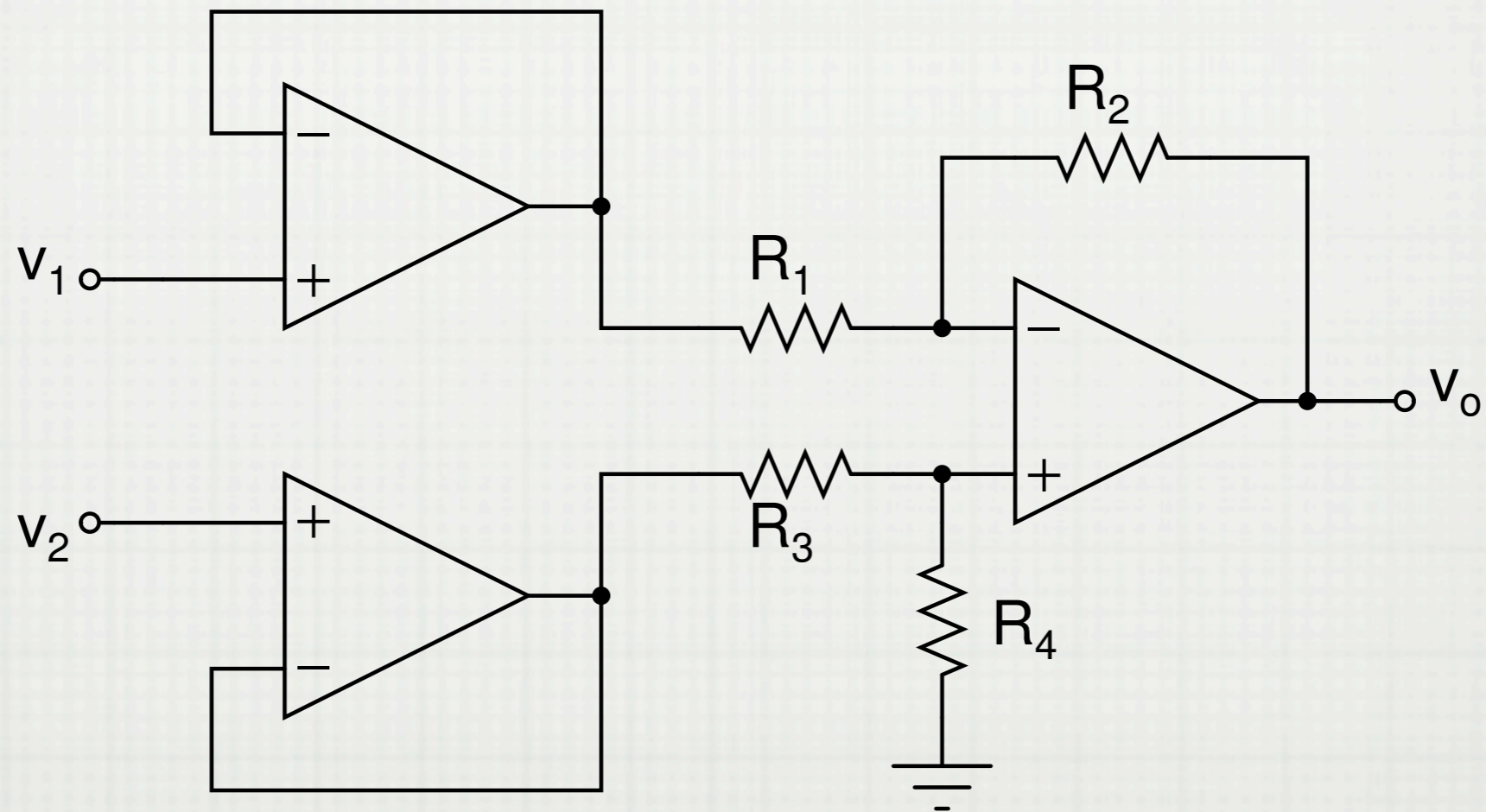

# TRIPLE-OPAMP IA

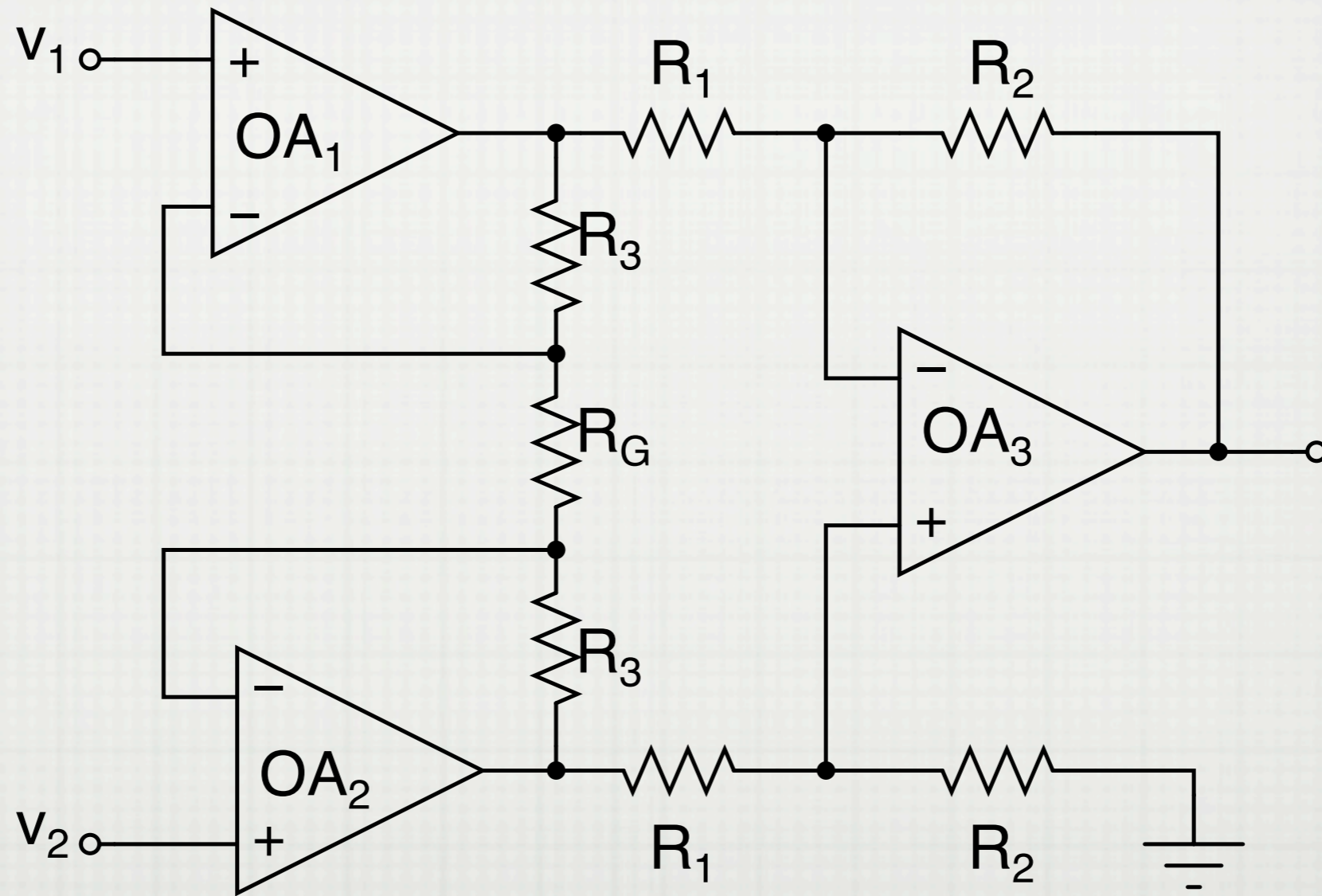

# DUAL-OPAMP IA WITH VARIABLE GAIN

---

