

Electrical and Computer Engineering Department
University of Puerto Rico - Mayaguez, P.R.
Electronics II - INEL 4202 - Spring 2002 - Exam 1B - Prof. Manuel Toledo
THERE ARE THREE PROBLEMS - WORK CLEARLY OR LOOSE POINTS

1. An amplifier have a single low-frequency pole at $f_L = 10Hz$, and two high-frequency poles at $f_{h1} = 1MHz$ and $f_{h2} = 2MHz$. The amplifier's gain for intermediate frequencies is 60dB. The low-frequency zero is located at the origin.


- (a) Write an expression for the amplifier's gain has a function of the complex frequency s , valid for low-, mid- and high-frequencies. (15 points)
- (b) Find the high-frequency effective 3dB frequency. (10 points)

$$(a) \quad A_v(s) = 1000 \frac{s}{s+20\pi} \frac{2\pi \times 10^6}{s+2\pi \times 10^6} \frac{4\pi \times 10^6}{s+4\pi \times 10^6}$$

$$(b) \quad f_{3dB} = \frac{1}{\frac{1}{10^6 \text{ Hz}} + \frac{1}{2 \times 10^6 \text{ Hz}}} = 667 \text{ kHz}$$

2. For the circuit shown below, assume that the operating point current is $i_{CQ} = 0.5\text{mA}$ and $\beta_0 = 100$.


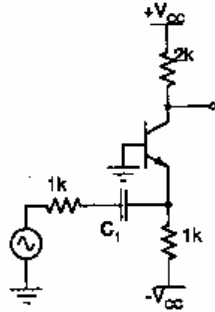
- (a) select C_1 such that the amplifier's low-frequency pole is located at 100 radians per second. (20 points)
- (b) find the high-frequency pole due to $C_\pi = 10\text{pF}$ by replacing the transistor with its equivalent model and analyzing the resulting circuit. (25 points)



$$(a) C_1 \text{ zero } 1\text{k} + 1\text{k} \parallel \frac{1}{g_m} = 1\text{k} + 1\text{k} \parallel \frac{\frac{1}{2} \text{ mA}}{25 \text{ mV}} = 1\text{k} + 1\text{k} \parallel 50\Omega = 1047.2 \Omega$$

$$\therefore 100 (1047.2 \Omega) = 1/C_1$$

$$C_1 = 9.6 \mu\text{F}$$

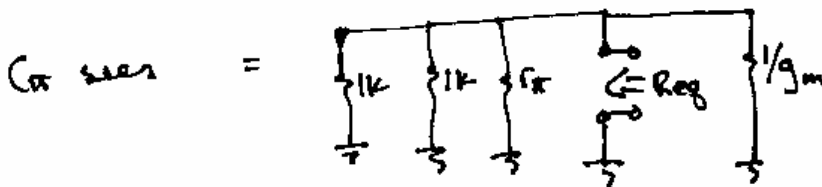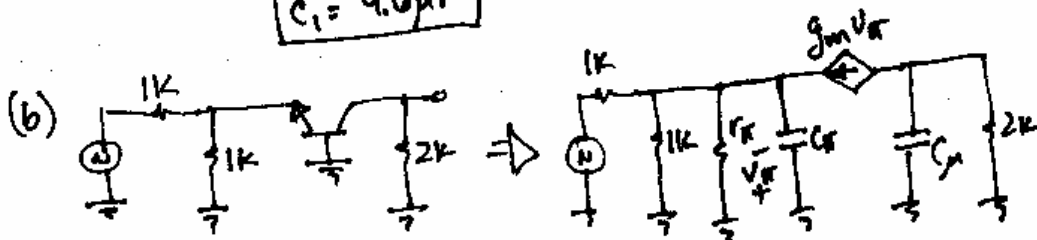


$$R_{eq} = \frac{1}{g_m} \parallel \frac{1\text{k}}{1\text{k}} \parallel \frac{1\text{k}}{1\text{k}} \parallel r_\pi = 50\Omega \parallel 5\text{k} \parallel 500\Omega = 45\Omega$$

$$\omega_H = \frac{1}{10^{-11} \text{ F} \times 45 \Omega} = 2.22 \times 10^9 \text{ rps.}$$

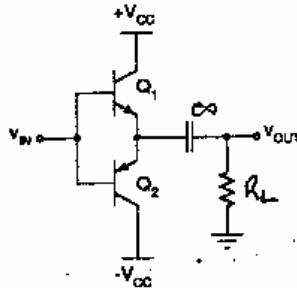3. For the power stage shown below, let $V_{CC} = 6V$ and $R_L = 4\Omega$. If the input is a sinusoid with 4.5V peak amplitude, find

- the output power P_L ; (5 points)
- the average power drawn from each supply; (5 points)
- the efficiency obtained at this output voltage; (5 points)
- the peak current supplied by v_{IN} assuming that $\beta_{NPN} = \beta_{PNP} = 50$; (5 points)
- the maximum power that each transistor must be capable of dissipating safely, assuming that the output level can assume any value. (10 points)



$$(a) V_{L\text{peak}} \approx 4.5V - 0.7V = 3.8V$$

$$P_L = \frac{V_{L\text{peak}}^2}{2R_L} = \frac{3.8^2}{2(4\Omega)} = 1.805W$$

$$(b) i_{C\text{AVG}} = \frac{V_{L\text{peak}}/R_L}{\pi} = \frac{3.8/4\Omega}{\pi} = 0.3A$$

$$P_{DC} = V_{CC} i_{C\text{AVG}} = 6V(0.3A) = 1.81W$$

$$(c) \eta = \frac{P_L}{2P_{DC0}} = \frac{1.805W}{2(1.81W)} \times 100\% = 50\%$$

$$(d) i_{C\text{peak}} = 3.8V/4\Omega = 0.95A$$

$$i_{m\text{peak}} = \frac{i_{C\text{peak}}}{\beta} = \frac{0.95A}{50} = 19mA$$

(e) max. power is dissipated when $V_{L\text{peak}} = \frac{2V_{CC}}{\pi} = 3.8V$
 \therefore that's above case $\Rightarrow P_D = 0.9W$

Electrical and Computer Engineering Department
University of Puerto Rico - Mayaguez, P.R.
Electronics II - INEL 4202 - SPRING 2002 - Exam 1A - Prof. Manuel Toledo
THERE ARE FOUR PROBLEMS - WORK CLEARLY OR LOOSE POINTS

1. A common-source amplifier is constructed with a $10\mu\text{F}$ bypass capacitor in parallel with a $1\text{k}\Omega$ resistor, both connected to the FET's source terminal. The equivalent resistance "seen" by the bypass capacitor is 100Ω . At high frequencies there is a single pole located at 1MHz . If the amplifier's mid-band gain is 80dB , find an expression for the amplifier's gain as a function of the complex frequency s , valid for low-, mid- and high-frequencies. (25 points)

$$\omega_z = \frac{1}{1\text{k} \times 10\mu\text{F}} = 10^2 \text{ rps}$$

$$\omega_{pL} = \frac{1}{100 \times 10\mu\text{F}} = 10^3 \text{ rps}$$


$$\omega_H = 2\pi \times 10^6 \text{ rps}$$

$$A_{\text{mid}} = 80 \text{ dB} = 10^4 \text{ v/v}$$

$$A_v(s) = -10^4 \frac{s+10^2}{s+10^3} \frac{2\pi \times 10^6}{s+2\pi \times 10^6}$$

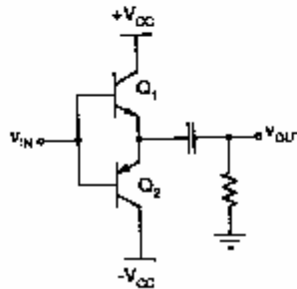2. The transistors in the class-B power amplifier shown below dissipate an average power of 10W each, when their peak collector current is 1A. Assuming sinusoidal output and $R_L = 10\Omega$, find

- the output power P_L ; (5 points)
- the average power drawn from each supply; (5 points)
- the efficiency obtained at this peak current; (5 points)
- the value of V_{CC} being used; (5 points)
- the maximum power that each transistor must be capable of dissipating safely, assuming that the output level can assume any value. (10 points)



$$(a) P_L = I_{RMS}^2 R_L = \left(\frac{1}{\sqrt{2}}\right)^2 (10\Omega) = 5W$$

$$(b) i_{AVE DC} = \frac{I_A}{\pi}; P_{DC} = 2V_{CC} i_{AVE DC} = P_L + 2P_D = 25W$$

$$(c) \eta = \frac{5W}{25W} \times 100\% = 20\%$$

$$(d) P_{DC} = 2V_{CC} i_{AVE DC} = 25W$$

$$V_{CC} = \frac{25W}{2(1A/\pi)} = 39V$$

(e) P_{max} occur when $V_{\text{out}} = \frac{2V_{\text{cc}}}{\pi} = 25\text{V}$
for this voltage $P_L = \frac{25\text{V}^2}{2(10\Omega)} = 31.25\text{W}$


$$P_{\text{DC}} = 2(39\text{V}) \frac{25\text{V}}{10\Omega \times \pi} = 62\text{W}$$

$$P_D = \frac{1}{2} (62 - 31.25\text{W}) = 15.4\text{W}$$

or use the formula from class $P_{\text{max}} = \frac{V_{\text{cc}}^2}{\pi^2 R_L}$


3. For the circuit shown below, find

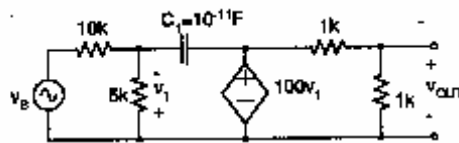- (a) the pole frequency applying Miller's theorem; (10 points)
 (b) the pole frequency by analyzing the circuit directly (this is, not using Miller's theorem) (25 points)
 (c) an expression for the voltage gain $A_v(s) = \frac{v_{out}}{v_s}$ as a function of complex frequency s , valid for mid- and high-frequencies. (10 points)



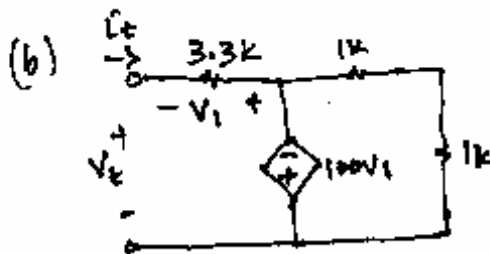(a) $k = -100 \text{ V/V}$; $C_{in} = 101 \times 10^{-11} \text{ F} = 1.01 \text{ nF}$
 $C_{in} \text{ "seen" } 5\text{k} \parallel 10\text{k} = 3.3\text{k}\Omega$

$$\therefore \omega_p = \frac{1}{3.3\text{k} \times 101 \times 10^{-11} \text{ F}} = \boxed{297 \text{ krps}}$$



$$-v_1 = (3.3\text{k}) i_t$$

$$i_t = \frac{v_s + 100v_1}{3.3\text{k}}$$

$$i_t (3.3\text{k}) = v_s = 100(3.3\text{k} i_t)$$

$$R_{eq} = \frac{v_s}{i_t} = 101(3.3\text{k}) = 337\text{k}\Omega$$

$$\omega_p = \frac{1}{337\text{k}\Omega \times 10^{-11} \text{ F}} = \boxed{297 \text{ krps}}$$

(c) $A_{mid} = v_{out}/v_s$; $v_{out} = \frac{1}{2}(100v_1)$
 $= \frac{1}{2}(100) \left(\frac{-5}{15} v_s \right)$

$$\therefore A_{mid} = -16.7 \text{ V/V}$$

$$A_v(s) = -16.7 \text{ V/V} \frac{297 \text{ krps}}{s + 297 \text{ krps}}$$