

NAME:


KEY

STUDENT NO.:

University of Puerto Rico
 Electrical and Computer Engineering Department
 INE1, 4202 - Electronics II - Fall 2002 - Exam 2a - Prof. M. Toledo
 THERE ARE THREE PROBLEMS - BE CLEAR OR LOOSE POINTS

1. For the amplifier shown below, assume an ideal opamp.

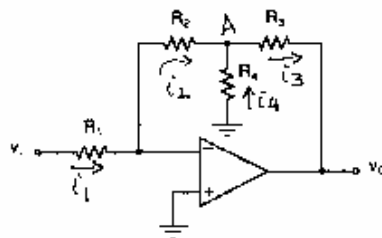- (a) Derive an expression for $A_v \approx v_o/v_i$ in terms of R_1, R_2, R_3 and R_4 ; (25 points)
 (b) Find $A_v = v_o/v_i$ if $R_1 = R_2 = 1k\Omega, R_3 = 10k\Omega$ and $R_4 = 20k\Omega$; (5 points)



$$(a) \quad i_1 = i_2 = \frac{v_i}{R_1} \Rightarrow v_A = -i_2 R_2 = -\frac{R_2}{R_1} v_i$$

$$i_4 = -v_A/R_4 = +\frac{R_2}{R_1} \frac{v_i}{R_4}$$

$$i_3 = i_2 + i_4 = +\frac{v_i}{R_1} + \frac{R_2}{R_1} \frac{v_i}{R_4} = \frac{v_i}{R_1} \left(1 + \frac{R_2}{R_4} \right)$$

$$v_o = v_A - R_3 i_3 = -\frac{R_2}{R_1} v_i - v_i \frac{R_3}{R_1} \left(1 + \frac{R_2}{R_4} \right)$$

$$\boxed{\frac{v_o}{v_i} = -\frac{R_2}{R_1} \left[1 + \frac{R_3}{R_2} \left(1 + \frac{R_2}{R_4} \right) \right]}$$

$$(b) \quad \frac{v_o}{v_i} = -\frac{10k}{1k} \left[1 + \frac{1}{10} \left(1 + \frac{10}{20} \right) \right] = \boxed{-11.5/V}$$

I switched R_3 & R_4 in the diagram by mistake. You can see that if $R_3 = 20k$ and $R_4 = 1k$, you get $A_v \approx -10 \left(1 + \frac{20}{10} [1 + 10] \right) = -230/V$ with moderate resistance values (less thermal noise).


Ex 2a

NAME:


STUDENT NO.:

2. For the amplifier shown in problem 1, assume that the opamp can be represented with the model shown below, with $r_d = 10k\Omega$, $a = 10^4 V/V$ and $r_o = 100\Omega$.

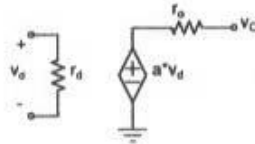- (a) Identify the type of feedback being used. (10 points)
- (b) Draw a diagram of the feedback network. (10 points)
- (c) Find the feedback network's R_{11} , R_{22} and β as defined in lecture. (10 points)
- (d) Draw a diagram of the non-feedback amplifier that must be analyzed to properly use the feedback method discussed in lecture. (10 points)
- (e) Find the non-feedback amplifier gain that must be used in the feedback method discussed in lecture. (10 points)



(a) voltage-sampling, current-mixing

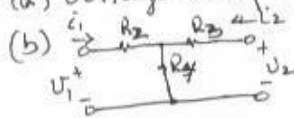


(c) $R_{11} = v_1/i_1 | v_2=0 = R_2 + \frac{R_3 R_4}{R_4 + R_4} = 952\Omega$ (with $10,952\Omega$ written above)

$R_{22} = v_2/i_2 | v_1=0 = R_3 + R_2 || R_4 = 7.67k\Omega$

$\beta = i_1/v_2 | v_1=0 = \frac{-1}{R_{22}} \frac{R_4}{R_2 + R_4} = \frac{-1}{11.5k\Omega} = -8.7 \times 10^{-5} V$

(d)

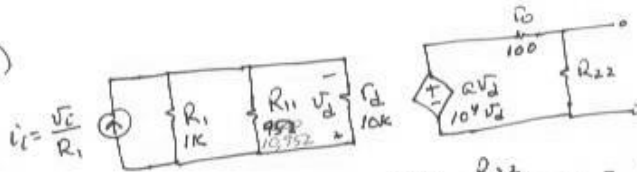

(e) $A = \frac{v_o}{i_i} = R_M \Rightarrow v_o = 10^4 v_d \frac{R_{22}}{R_{22} + r_o} = 9871 v_d$

$v_d = -i_i (R_1 || R_{11} || r_d) = -465\Omega \times i_i$

$\therefore v_o = -i_i \times 4.59M\Omega \Rightarrow R_M = -4.59M\Omega$ (with $8.3M\Omega$ written below)