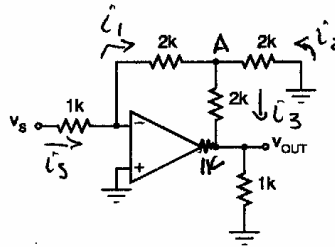


Name: Clave Student No.: _____

Electrical and Computer Engineering Department
 University of Puerto Rico - Mayaguez, P.R.
 Electronics II - INEL 4202 - SPRING 2002 - Exam 2A - Prof. Manuel Toledo
 THERE ARE FOUR PROBLEMS - WORK CLEARLY OR LOOSE POINTS

1. Find $A_v = v_{out}/v_s$ for the amplifier shown below. Assume that the opamp is ideal. (30 points)



$$v_{out} = v_A - i_3(2k)$$

$$v_A = -i_1(2k) = -2k \left(\frac{v_s}{1k} \right) = -2v_s$$


$$i_2 = \frac{v_A}{2k} = -\frac{v_s}{1k} \quad ; \quad i_3 = i_1 + i_2 = \frac{2v_s}{1k}$$

$$\therefore v_{out} = -2v_s - \frac{2v_s(2k)}{1k} = -6v_s$$

$$A_v = v_{out}/v_s = -6 \text{ V/V}$$

2. The opamp in problem 1 has an input resistance (between the + and - terminals) $r_d = 10k\Omega$, open-loop voltage gain $A_{OL} = 10^4 V/V$, and zero output resistance. Use feedback theory to determine the voltage gain v_{out}/v_s . (50 points)

shunt-shunt feedback

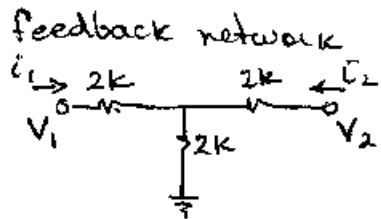


$$R_{11} = 3k$$

$$R_{22} = 3k$$

$$\beta = -\frac{1}{3k} \frac{1}{2} = -\frac{1}{6k}$$

$$= -1.67 \times 10^{-4}$$

Non-feedback amp.

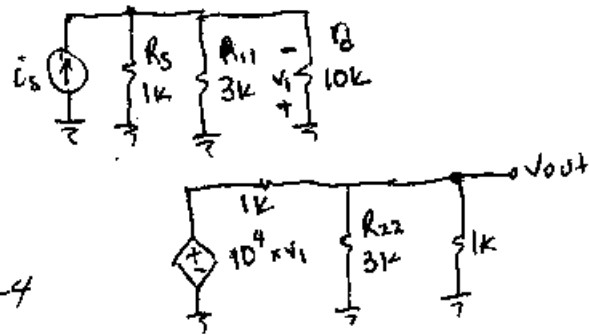

$$R_m = \frac{v_o}{i_s} = \frac{3k \parallel 1k}{1k + 3k \parallel 1k} \cdot 10^4 \cdot (-10k) \cdot \frac{3k \parallel 1k}{10k + 3k \parallel 1k}$$

$$= (0.47)(-10^8)(0.07) = -3.3 M\Omega$$

$$R_{MF} = \frac{-3.3 M\Omega}{1 + (-3.3 M\Omega)(-1/6k\Omega)} = -5989 \Omega = \frac{v_o}{i_s}$$

$$A_v = \frac{v_o}{v_s} = \frac{v_o}{i_s R_s} = \frac{R_{MF}}{R_s} = \frac{-5989 \Omega}{1000 \Omega} = \boxed{-5.989 V/V}$$

3. An amplifier with d.c. gain $A_0 = 10^4$ and poles at 10Hz and 1000Hz is used in a feedback configuration. Find the feedback gain A_f if the phase margin is $\phi_m = 45^\circ$. (20 points)

d.c.
 $\phi_m = 45^\circ$; $\therefore L(1000\text{Hz}) = 0\text{ dB} = 1\text{ V/V} = A\beta$
 at 1000Hz $A = 80\text{ dB} - 2(20\text{ dB}) - 3\text{ dB}$
 $= 37\text{ dB} = 70.8\text{ V/V}$

Assuming
voltage-voltage

$$\therefore \beta = \frac{1}{70.8} = 0.014$$

Then

$$A_f = \frac{A_0}{1 + \beta A_0} = \frac{10^4}{1 + 10^4/70.8}$$

$$A_f = 70.3\text{ V/V}$$

or

↑
 or 40 dB
 $= 100$ if
 3 dB are
 neglected
 then
 $\beta = \frac{1}{100}$
 $A_f = \frac{10^4}{1 + 10^4/100}$
 $= \frac{10^4}{1 + 10^2} = \frac{10^4}{101}$
 $= 99$
 ↑
 O.K. too