

NAME:

STUDENT NO.:

University of Puerto Rico
Electrical and Computer Engineering Department
INEL 4202 - Electronics II - Spring 2001 - Exam 2b - Prof. M. Toledo
THERE ARE THREE PROBLEMS - BE CLEAR OR LOOSE POINTS

1. An ideal voltage amplifier with $A_v = 4000$, $R_i = 100\Omega$ and $R_o = 100k\Omega$ is connected in a negative feedback loop. The feedback network is ideal and has a $\beta = 0.01$. Find A_{vf} , R_{if} and R_{of} . Assume ideal source and load. (30 points)

$$D = 1 + (0.01)(4000) = 41$$

$$A_{vf} = \frac{4000}{41} = 97.6$$


$$R_{if} = D R_i = 41(100) = 4.1k\Omega$$

$$R_{of} = \frac{R_o}{D} = \frac{100k}{41} = 2.44k\Omega$$

NAME:

STUDENT NO.:

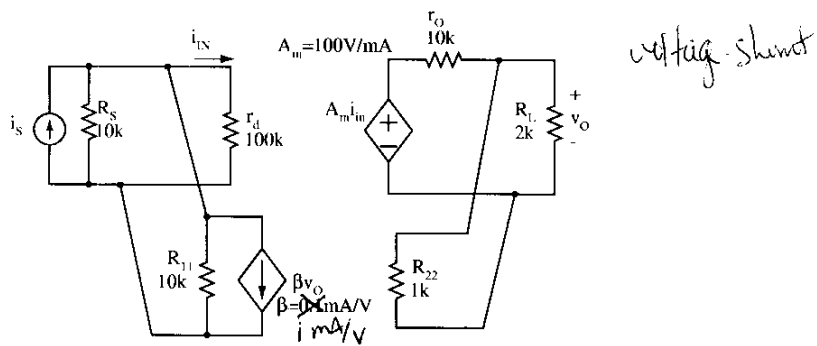2. The sketch below shows a model of a negative feedback amplifier. Find A_f , R_{if} and R_{of} . Specify the appropriate units for A_f , if any. All resistors are expressed in ohms, with k denoting kilo. (40 points)



$$R_o = 2k \parallel 1k \parallel 10k = 625 \Omega$$

$$R_i = 10k \parallel 10k \parallel 100k = 4.76k$$

$$R_M = \left(100 \frac{V}{mA}\right) \left(\frac{1}{10k}\right) \frac{625}{4.76k} \frac{5k}{105k} = 2.27 \frac{V}{mA} = 297 \Omega$$

$$D = 1 + \beta R_M = 1 + (0.2) (2.27) = 1.297$$

$$R_{of} = \frac{R_o}{D} = \frac{625 \Omega}{1.297} = 482 \Omega \rightarrow R_{of} = 482 \Omega$$

$$R_{if} = \frac{R_i}{D} = \frac{4760}{1.297} = 3.66k \Omega = R_{if}$$


$$A_{mf} = \frac{R_M}{D} = \frac{2.27}{1.297} \frac{V}{mA} = 1.75 \frac{V}{mA}$$

$$= \frac{.297}{1.297} = 0.23 \frac{V}{mA} = A_{mf}$$

NAME:

STUDENT NO.:

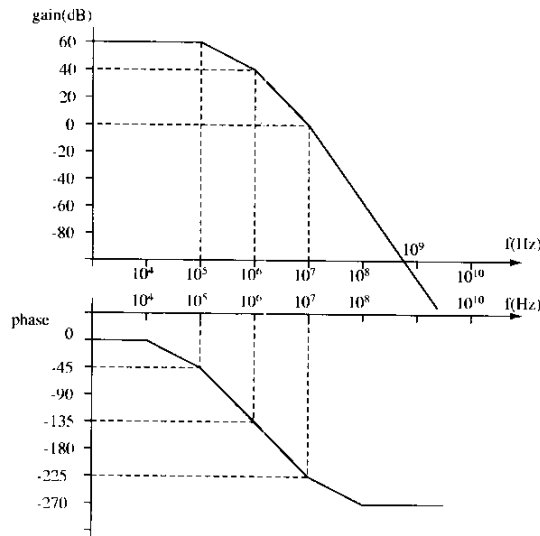3. The following diagram shows the bode plot of the gain A of a non-feedback amplifier, which will be used in a negative feedback amplifier. The non-feedback amplifier dc-gain is 60 dB and has poles at 10^5 , 10^6 and 10^7 Hz. Find
- the phase and gain margins if the negative feedback's $\beta = 0.01$. (15 points)
 - the new first pole's frequency if the pole-shifting technique is used to compensate the amplifier for a 45° phase margin with the feedback network's $\beta = 1$. (15 points)



(a) $20 \log \frac{1}{\beta} = 40 \text{ dB} \Rightarrow \phi_{m1} = 45^\circ ; G_m \approx +20 \text{ dB}$

(b) $20 \log \frac{1}{\beta} = 0 \text{ dB} \rightarrow$ gain at 2nd pole must be reduced by 40 dB \rightarrow 1st pole must be moved 2 decades down

$$\boxed{f_p = 10^3 \text{ Hz}}$$