

NAME:


STUDENT NO.:

University of Puerto Rico
Electrical and Computer Engineering Department
INEL 4202 - Electronics II - Spring 2000 - Exam 2 - Prof. M. Toledo


THERE ARE FOUR PROBLEMS - BE CLEAR OR LOOSE POINTS

#4 is a bonus problem. Exam is 85 pts. in total (+bonus)

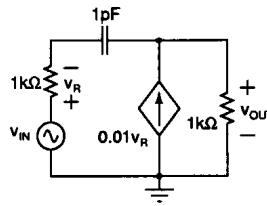1. Use the open-circuit time constant method to estimate the high-frequency pole for the following circuit. Do not use the Miller approximation. (25 pts)



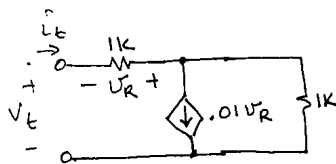Shortening the source, the cap "sees" the following circuit



Applying a test source and KVL on the external loop gives

$$v_t = i_t(1k) + [i_t - (0.01)v_R]1k$$

$$v_R = -i_t(1k)$$


$$\therefore \frac{v_t}{i_t} = 1k + [1 + (0.01)(1k)]1k = 12k$$

$$\omega_H = \frac{1}{1pF \times 12k\Omega} = 8.3 \times 10^7 \text{ rps}$$


NAME:

STUDENT NO.:

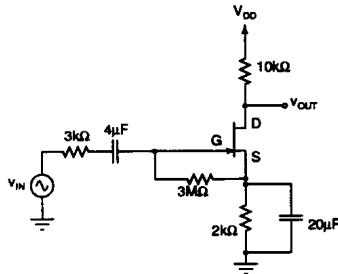
2. Use the short circuit time constant method to estimate the dominant low-frequency pole for the circuit below. The transistor has $g_m = 5.6 \times 10^{-3} \text{ A/V}$. (25 pts)



Replace FET with low-freq. model to get

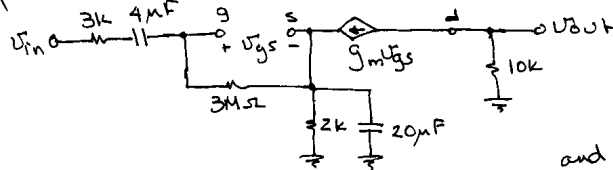


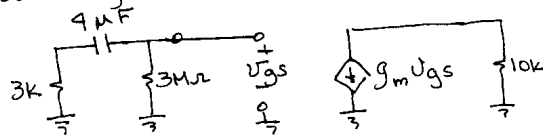\Rightarrow 1st consider the $4\mu\text{F}$ cap. Short the $20\mu\text{F}$ and the independent source to obtain the following circuit




$\therefore 4\mu\text{F}$ "sees" $3003\text{k}\Omega$ and $\omega_{L1} = \frac{1}{4\mu\text{F}(3003\text{k})} = 0.08 \text{ rps}$

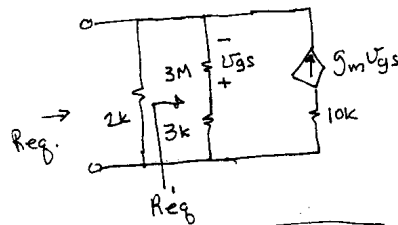\Rightarrow Now let's look at the $20\mu\text{F}$ cap.




$R_{eq} = 2\text{k} \parallel R'_{eq}$

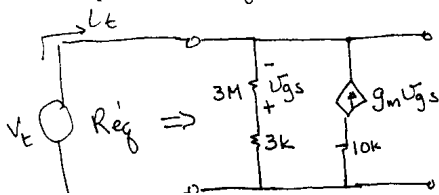


$v_{gs} = -\frac{3\text{M}}{3003\text{k}} v_t$

$i_t = \frac{v_t}{3003\text{k}} - g_m v_{gs}$

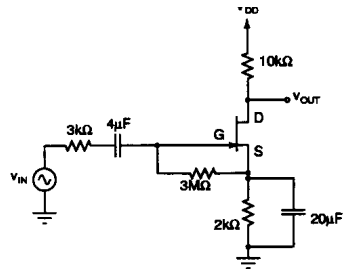$= v_t \left(\frac{1}{3003\text{k}} + 5.6 \times 10^{-3} \frac{\text{A}}{\text{V}} \frac{3\text{M}}{3003\text{k}} \right)$




Replace FET with low-freq. model to get

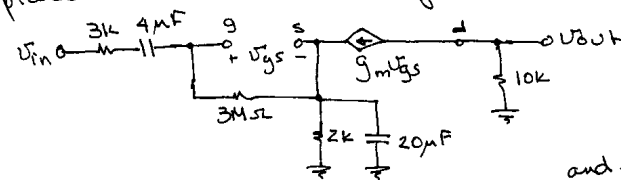



and the independent source.

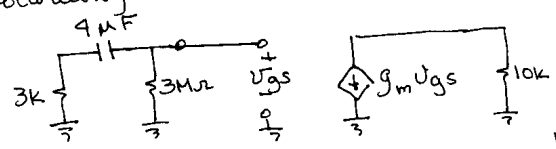⇒ 1st consider the 4μF cap. Short the 20μF to obtain the following circuit



∴ 4μF "sees" 3003kΩ and $\omega_{L1} = \frac{1}{4\mu F (3003k)} = .08 \text{ rps}$

⇒ Now let's look at the 20μF cap.

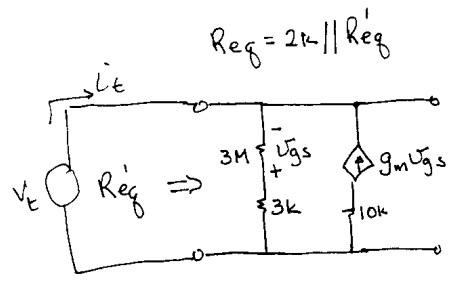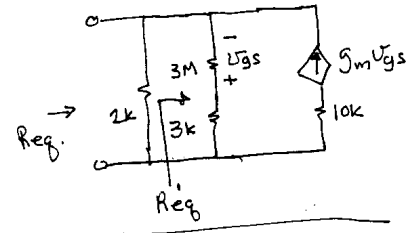

$R_{eq} = 2k \parallel R'_{eq}$

$v_{gs} = - \frac{3M}{3003k} v_t$

$i_t = \frac{v_t}{3003k} - g_m v_{gs}$

$= v_t \left(\frac{1}{3003k} + 5.6 \times 10^{-3} \frac{A}{V} \frac{3M\Omega}{3003k\Omega} \right)$

∴ $\frac{v_t}{i_t} = R'_{eq} = 178.7\Omega$

∴ $R_{eq} = 2k \parallel 178.7 = 164\Omega$


and $\omega_{L2} = \frac{1}{(20\mu F)(164\Omega)} = 304 \text{ rps} = \text{dominant pole}$

NAME:

STUDENT NO.:

3. The circuit shown below has identical transistors biased at 0.5 mA. Parameters are $r_b = 120\Omega$, $r_\pi = 15k\Omega$, $V_A = 180V$, $C_\pi = 40pF$ and $C_\mu = 4pF$.

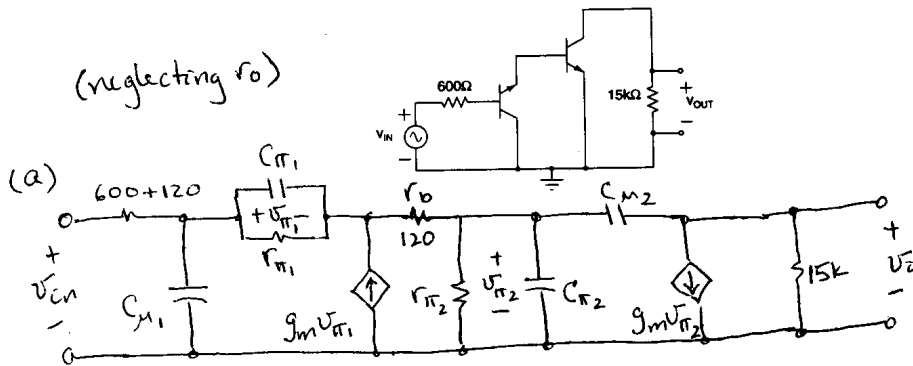
- (a) Draw the high-frequency equivalent circuit. (10 pts)
- (b) Determine the upper half-power frequency for the amplifier. (25 pts)



(b) 2nd stage \rightarrow use Miller's theorem


$$g_m = \frac{I_C}{V_T} = \frac{0.5 \text{ mA}}{25 \text{ mV}} = 0.02 \text{ A/V} \Rightarrow A_M = -g_m R_L = -300$$

$$C_{in} = (1 - A_M) C_{\mu_2} = 301 (4 \text{ pF}) = 1204 \text{ pF}$$

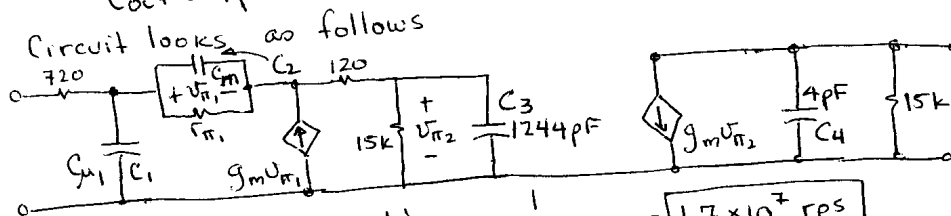
$$C_{out} \approx 4 \text{ pF}$$


$$C_4 \text{ "sees" } 15k \Rightarrow \omega_{H4} = \frac{1}{4 \text{ pF} (15k)} = 1.7 \times 10^7 \text{ rps}$$

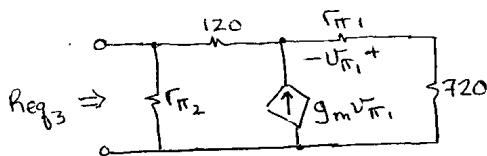
$C_3 = C_{in} + C_{\pi_2} = 1244 \text{ pF}$ see the following circuit (after shortening the input source and opening C_1 & C_2)



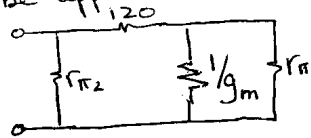Since $r_{\pi_1} = 15k \gg 720\Omega$ this can be approximated to



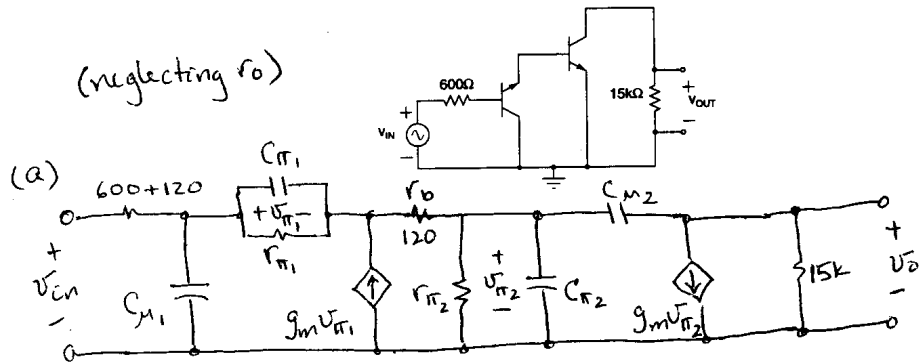- (a) Draw the high-frequency equivalent circuit. (10 pts)
 (b) Determine the upper half-power frequency for the amplifier. (25 pts)




(b) 2nd stage \rightarrow use Miller's theorem

$$g_m = \frac{I_c}{V_T} = \frac{0.5 \text{ mA}}{25 \text{ mV}} = 0.02 \text{ A/V} \Rightarrow A_M = -g_m R_L = -300$$

$$C_{in} = (1 - A_M) C_{\pi 2} = 301 (4 \text{ pF}) = 1204 \text{ pF}$$


$$C_{out} \approx 4 \text{ pF}$$

Circuit looks as follows

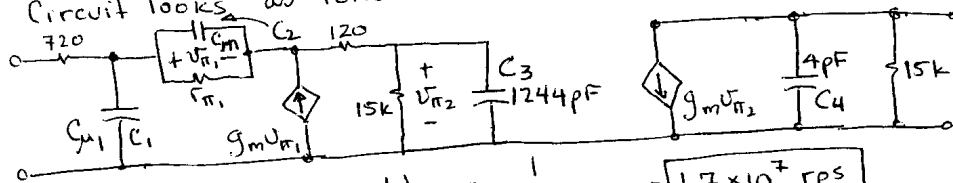


$$C_4 \text{ "sees" } 15k \Rightarrow \omega_{H4} = \frac{1}{4 \text{ pF} (15k)} = 1.7 \times 10^7 \text{ rps}$$

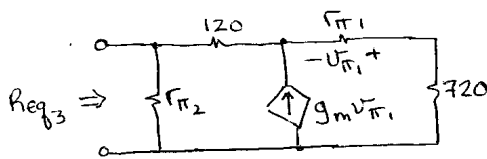$C_3 = C_{in} + C_{\pi 2} = 1244 \text{ pF}$ see the following circuit (after shortening the input source and opening C_1 & C_2)



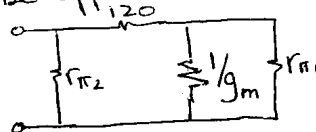Since $r_{\pi 1} = 15k \gg 720\Omega$ this can be approximated to




$$\therefore R_{eq3} = r_{\pi 2} \parallel \left[120 + \left(\frac{1}{0.02} \parallel 15k \right) \right]$$

$$= 15k \parallel [170] = 168\Omega$$

$$\therefore \omega_{H3} = \frac{1}{(168)(1244 \text{ pF})} = 4.79 \times 10^6 \text{ rps}$$

Now let's look at the 1st stage

$C_{\pi 1}$ sees 720Ω in parallel with

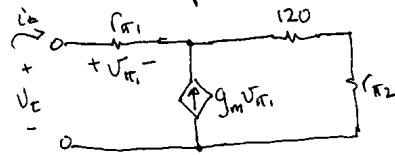

KVL in the external loop gives

$$V_t = i_t r_{\pi 1} + (i_t + g_m V_{\pi 1})(r_{\pi 2} + 120)$$


$$V_{\pi 1} = i_t r_{\pi 1}$$

$$\begin{aligned} \therefore \frac{V_t}{i_t} = R_{eq}' &= r_{\pi 1} + (1 + g_m r_{\pi 1})(r_{\pi 2} + 120) \\ &= 15k + (1 + 0.02 \times 15k)(15120\Omega) \\ &= 4.57 \times 10^6 \Omega \end{aligned}$$

$\therefore C_{\pi 1}$ sees $720 \parallel 4.57 \times 10^6 \approx 720$


and $\omega_{H, \mu 1} = \frac{1}{(4pF)(720\Omega)} = 3.5 \times 10^8 \text{ rps}$

Finally $C_{\pi 1}$ sees,

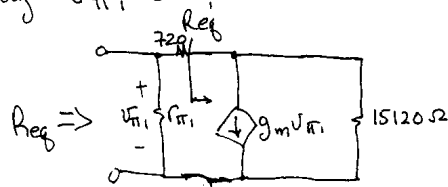

$$R_{eq}' = 15k \parallel R_{eq}$$

to find R_{eq}'

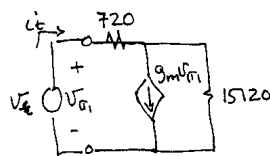

$$V_{\pi 1} = V_t$$

$$V_t = i_t (720) + (i_t - g_m V_t) 15120$$

$$V_t (1 + 0.02 \times 15120) = i_t (15120 + 720)$$

$$R_{eq}' = \frac{V_t}{i_t} = \frac{15840}{303.4} = 52.2 \Omega$$

$$R_{eq} = 15k \parallel 52.2 = 52 \Omega$$

$$\omega_{H, \pi 1} = \frac{1}{(40pF)(52\Omega)} = 4.8 \times 10^8 \text{ rps}$$

$\therefore \omega_{H, \mu 1} = 3.5 \times 10^8 \text{ rps}$ and $4.8 \times 10^8 \text{ rps}$


∴ the 4 poles are 1.7×10^7 rps, 4.7×10^6 rps, 3.5×10^8 rps and 4.8×10^8 rps

Since there is no dominant pole, we use the effective pole


$$\omega_H = \frac{1}{\frac{1}{4.8 \times 10^8} + \frac{1}{3.5 \times 10^8} + \frac{1}{4.7 \times 10^6} + \frac{1}{1.7 \times 10^7}} = \boxed{3.6 \times 10^6} \left\{ \begin{array}{l} \text{final} \\ \text{answer!} \end{array} \right.$$

bonus problem

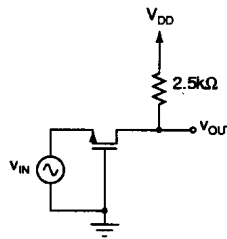4. Estimate the mid-band gain and write down an expression for the gain as a function of frequency for the transistor amplifier shown below. Use $g_m = 10 \text{ mA/V}$ and $C_{gs} = C_{gd} = 4 \text{ pF}$. (15 pts)



Replace transistor with model

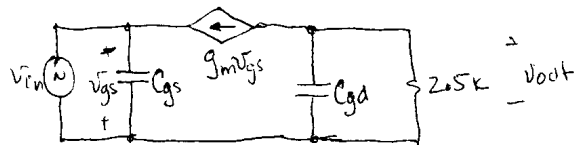

Since there is no Thevenin resistance in the source, C_{gs} "sees" a short circuit and thus its corresponding pole is at infinity (i.e. does not count). C_{gd} "sees" $2.5 \text{ k}\Omega$. Thus

$$\omega_H = \frac{1}{(4 \text{ pF})(2.5 \text{ k}\Omega)} = 10^8 \text{ rps}$$

The mid-band gain can be obtained from the ~~eq~~ above equivalent circuit, with the caps replaced by open circuits. From the diagram,

$$v_{in} = -v_{gs}$$

$$v_{out} = -g_m v_{gs} (2.5 \text{ k}\Omega)$$

$$\therefore \frac{v_{out}}{v_{in}} = A_{mid} = g_m (2.5 \text{ k}\Omega) = 25$$

Finally,

$$A_v(s) = 25 \frac{10^8}{s + 10^8}$$