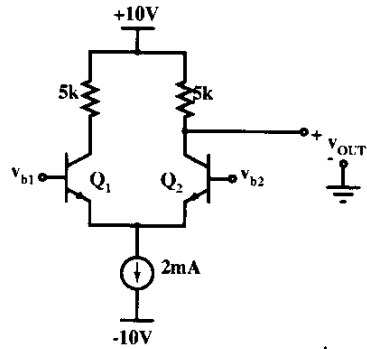


NAME: key

STUDENT NO.:

University of Puerto Rico
Electrical and Computer Engineering Department
INEL 4202 - Electronics II - Spring 2001 - Exam 3a - Prof. M. Toledo
THERE ARE FOUR PROBLEMS - BE CLEAR OR LOOSE POINTS
Use $\beta = 100$ when needed.

1. For the differential amplifier shown below, find
- (a) the voltage gain $A_v = v_{out1}/v_{b1}$ when the base of Q_2 is grounded. (15 points)
 - (b) the quiescent point collector-to-emitter voltages for Q_1 and Q_2 . (15 points)
(HINT: this should be calculated with both bases grounded)
 - (c) the input resistance. (15 points)



(a) $A_v = +\frac{1}{2} g_m R_c$; $g_m = \frac{I_c}{V_T} = \frac{1\text{mA}}{25\text{mV}} = \frac{1}{25} \text{ S}$
 $A_v = \frac{1}{2} \left(\frac{1}{25} \right) (5000) = \boxed{100}$


(b) $V_E = -0.7\text{V}$
 $V_C = 10\text{V} - 1\text{mA}(5\text{k}) = 5\text{V}$ } $V_{CE} = 5.7\text{V}$

(c) $R_{in} = 2r_{\pi} = 2\beta/g_m = 2(100)/\frac{1}{25}\text{S} = \boxed{5\text{k}\Omega}$

NAME:

STUDENT NO.:

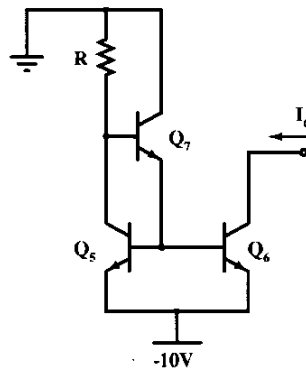2. The circuit shown below will implement the constant current source for the diagram shown in problem 1. Find R such that $I_O = 2\text{mA}$. Assume all transistors have equal areas and very large β . (15 points)



$$I_{\text{ref}} = \frac{10\text{V} - 1.4\text{V}}{R} = \frac{8.6\text{V}}{R} = 2\text{mA}$$

$$R = \frac{8.6\text{V}}{2\text{mA}} = \boxed{4.3\text{k}\Omega}$$

NAME:

STUDENT NO.:


3. The circuit shown in problem 1 uses the current mirror shown in problem 2 to implement the constant current source. Find the gain $A_{CM} = v_{out1}/v_{CM}$, obtained when a common voltage v_{CM} is applied to both v_{b1} and v_{b2} , if all transistors exhibit an early voltage of 100V. (10 points)

$$A_{CM} \approx \frac{1}{2} \frac{R_C}{R_{TAIL}}$$

$$R_{TAIL} \approx r_{OQ6} = \frac{V_A}{I_{C6}} = \frac{100V}{2mA} = \frac{50}{100} k\Omega$$

$$A_{CM} = \frac{1}{2} \frac{5k}{\frac{50}{100}} = \boxed{0.5} \quad \boxed{.05}$$

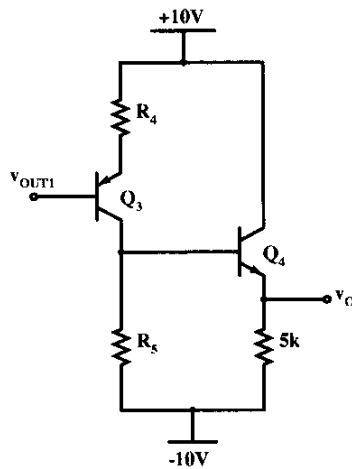4. The circuit shown below will be connected to the output of the differential stage shown in problem 1. Find
- R_4 and R_5 such that transistor Q_3 is biased at approximately 5mA and the quiescent output voltage (when both inputs are grounded) is zero. (10 points)
 - the overall gain of the amplifier. (10 points)
 - the approximate output resistance of the amplifier. (10 points)



$$(a) \left. \begin{array}{l} V_{B3} = V_{C2} = 5\text{V} \\ V_{E3} = 5.7\text{V} \end{array} \right\} V_{R4} = 4.3\text{V} \Rightarrow R_4 = \frac{4.3\text{V}}{5\text{mA}} = \boxed{860\Omega}$$

$$V_{E4} = 0\text{V} \Rightarrow V_{B4} = V_{C3} = +0.7\text{V} \Rightarrow V_{R5} = 10.7\text{V}$$

$$R_5 = \frac{10.7}{5\text{mA}} = \boxed{2.14\text{k}\Omega}$$

$$(b) A_{VQ3} \approx -\frac{2.14\text{k}\Omega}{860\Omega} = -2.5$$

stage 2 loading on stg. 1 = $\frac{101(860)}{5\text{k} + 101(860)} = \boxed{0.95}$

$$A_{VQ4} \approx 1 \quad \therefore A_{V\text{total}} = 100(0.95)(-2.5)(1) = \boxed{-238}$$

$$(c) R_{out} = 5\text{k} \parallel \frac{r_{R4} + R_5}{\beta + 1}$$

$$I_{C4} \approx \frac{10\text{V}}{5\text{k}} = 2\text{mA} \Rightarrow r_{R4} = \frac{100(25\text{mV})}{2\text{mA}} = 1.25\text{k}$$

$$R_{out} = 5\text{k} \parallel \frac{1.25\text{k} + 2.14\text{k}}{101} = 5\text{k} \parallel 34 \approx \boxed{34\Omega}$$