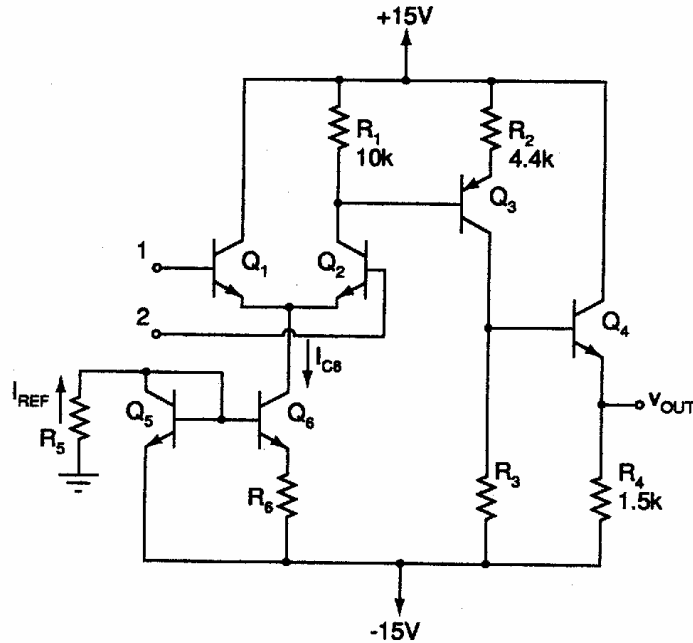


Electrical and Computer Engineering Department
 University of Puerto Rico - Mayaguez, P.R.
 Electronics II - INEL 4202 - SPRING 2002 - Exam 3B - Prof. Manuel Toledo
THIS EXAM CONTAINS 15 BONUS POINTS - WORK CLEARLY OR LOOSE POINTS

The transistors in the amplifier shown below have $\beta = 100$. Base currents can be neglected in your analysis.



1. Assuming $R_5 = 50k\Omega$, $R_3 = 10k\Omega$, $R_6 = 0$, and that the area of Q_6 equals 5 times the area of Q_5 , find:
 - (a) the differential gain $A_d = \frac{v_{OUT}}{v_1 - v_2}$ (50 points)
 - (b) the input resistance R_{in} seen by differential signals between terminals 1 and 2. (25 points)
 - (c) the output resistance R_{out} at the output terminal. (25 points)
2. Assuming $I_{C6} = 1mA$, select R_3 so that $v_{OUT} \approx 0V$ when $v_1 = v_2 = 0V$. (15 points)

1. (a) To find the gain, we need to determine the bias currents.

$$I_{REF} = \frac{15 - 7}{R_5} = \frac{14.3V}{50K} = 286 \mu A$$

$$I_{C6} = 5 \times I_{REF} = 1.43 \text{ mA}$$

$$I_{C2} = \frac{1}{2} I_{C6} = 0.715 \text{ mA}$$

$$\therefore V_{C2} = 15 - 10K(0.715 \text{ mA}) = 7.85V$$

$$I_{C3} = \frac{15V - (V_{C2} + 7)}{4.4K\Omega} = \frac{15 - (7.85 + 7)}{4.4K} = 1.47 \text{ mA}$$

$$\therefore V_{B4} = -15 + (1.47 \text{ mA})(R_3) = -15 + (1.47 \text{ mA})(10K) = -0.37V$$

$$I_{B4} = \frac{V_{B4} - 7 + 15}{1.5K} = 9.3 \text{ mA}$$

From this we can find the g_m 's

$$g_{m2} = \frac{0.715 \text{ mA}}{25 \text{ mV}} = 0.0286 \text{ A/V}$$

$$g_{m3} = \frac{1.47 \text{ mA}}{25 \text{ mV}} = 0.0588 \text{ A/V}$$

$$g_{m4} = \frac{9.3 \text{ mA}}{25 \text{ mV}} = 0.372 \text{ A/V}$$

The load at the collector of C_2 is

$$R_{C2} = R_2 \parallel (R_3 + (\beta+1)4.4K) \\ = 10K \parallel \left[\frac{100(25)}{1.47} + 101(4.4K) \right] = 9.78K\Omega$$

$$\therefore \frac{V_{C2}}{V_1 - V_2} = + \frac{1}{2} g_{m2} R_{C2} = \frac{1}{2} (0.0286 \text{ A/V})(9.78K\Omega) = 140 \text{ V/V}$$

$$\frac{V_{c3}}{V_{c2}} = \frac{-g_{m3} R_{c3}}{1 + g_{m3} R_2}$$

$$R_{c3} = R_3 \parallel (r_{\pi 3} + 101 \times 1.5k\Omega) = 10k \parallel \left(\frac{100}{.372} + 151.5k \right)$$

$$= 10k \parallel (151.8k\Omega) = 9.38k\Omega \quad \leftarrow$$

$$\frac{V_{c3}}{V_{c2}} = \frac{- .0588 \times 9.38k\Omega}{1 + .0588 \times 4.4k} = -2.12 V/V \quad \leftarrow$$

$$\frac{V_{out}}{V_{c3}} = \frac{+g_{m4} R_4}{1 + g_{m4} R_4} = \frac{.372(1500)}{1 + .372 \times 1500} = 0.998 \quad \leftarrow$$

$$A_d = (+140 V/V)(-2.12 V/V)(.998 V/V) = \boxed{-296.3 V/V} \quad \leftarrow$$

$$(b) R_{in} = 2r_{\pi} = 2 \times \frac{100}{g_{m2}} = 2 \times \frac{100}{.0286 A/V} = \boxed{7k\Omega}$$

$$(c) R_{out} = 1.5k \parallel \frac{r_{\pi 4} + R_3}{101} = 1.5k \parallel \frac{\frac{100}{.372} + 10k\Omega}{101} = \boxed{95.2\Omega}$$

(2) if $I_{C6} = 1mA$, $I_{C2} = .5mA$, $V_{C2} = 10V$; $I_{C3} = \frac{15 - 10.7}{7.4k} = .98mA$
 For $V_{out} = 0$, $V_{C3} = +0.7V$; $\therefore R_3 = \frac{15.7V}{.98mA} = \boxed{16k\Omega}$

(3) Widlar Current Source

$$I_0 R_M = V_T \ln\left(\frac{I_{REF}}{I_0}\right); \quad I_{REF} = 2mA \Rightarrow R_5 = \frac{14.3V}{2mA} = \boxed{7.15k\Omega}$$

$$R_6 = \frac{25mV}{1mA} \ln(2) = 17.3\Omega$$