

Name: Key

Student No: _____

Electrical and Computer Engineering Department
University of Puerto Rico - Mayaguez, P.R.
Electronics II - Fall 1999 - Third Exam (b) - Prof. Manuel Toledo

EACH PROBLEM IS 25 POINTS
BE CLEAR AND WELL ORGANIZED OR LOOSE POINTS

1. A 3-pole feedback amplifier has a dc gain of 10^4 . All three open-loop poles are located at $f = 1\text{MHz}$. Find the maximum feedback β for which the amplifier is stable.

You may find the following two formulas useful:

- the number of decades between frequencies f_1 and f_2 is $n = |\log \frac{f_2}{f_1}|$
- the phase at frequency f_2 due to a pole at f_1 is $-\tan^{-1}(\frac{f_2}{f_1})$.

Let f_2 be the freq. at which total phase $= -180^\circ$

Since each pole contributes -60° at f_2 ,

$$-60^\circ = -\tan^{-1}\left(\frac{f_2}{1\text{MHz}}\right)$$

$$f_2 = 1.73\text{MHz}$$

At this freq.

$$|A(f=1.73\text{MHz})| = \left| \frac{10^4}{\left(j\frac{1.73\text{MHz}}{1\text{MHz}} + 1\right)^3} \right| = \frac{10^4}{\left(\sqrt{1.73^2 + 1^2}\right)^3} = 1253.3$$

Since we want this to become 0dB

$$\frac{1}{\beta} = 1253.3$$

and

$$\boxed{\beta \approx 8 \times 10^{-4}}$$


Name: _____

Student No: _____

2. For the circuit shown below, the transistor's $\beta = 50$, $r_{\pi} = 2k\Omega$, $r_b = 0$ and $r_o = \infty$. Find


- type of feedback
- feedback network's β
- current gain of the amplifier without feedback, but taking into account the loading due to the feedback network
- current gain of feedback amplifier (do not approximate to $1/\beta$)

(a) current-shunt

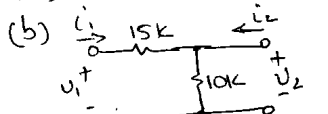(b) 


$$g_{12} = \frac{i_i}{i_o} \Big|_{v_i=0} = \frac{-10k}{10k+15k}$$

$$= -10/25$$

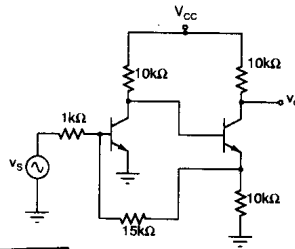

Since $i_o = -i_2 \Rightarrow \beta = -g_{12} = 10/25$

(c) $g_{11} = \frac{i_i}{v_i} \Big|_{i_2=0} = 1/25k\Omega$; $g_{22} = \frac{v_o}{i_2} \Big|_{v_i=0} = 10k \parallel 15k = 6k\Omega$

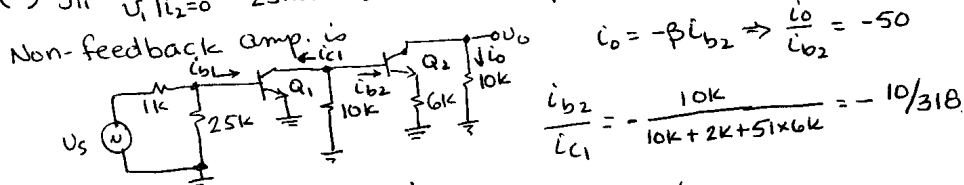

$$\frac{i_{c1}}{i_{b1}} = \beta = 50 ; \frac{i_{b1}}{i_s} = \frac{25k}{2k+25k} = 25/27$$

$$A_i = i_o/i_s = \frac{i_o}{i_{b2}} \frac{i_{b2}}{i_{c1}} \frac{i_{c1}}{i_{b1}} \frac{i_{b1}}{i_s} = (-50) \left(\frac{-10}{318} \right) (50) \left(\frac{25}{27} \right) = 72.8 = A_i$$

(d) $A_{if} = \frac{A_i}{1 + \beta A_i} = \frac{72.8}{1 + \frac{10}{25}(72.8)} = 2.42 = A_{if}$

Name: _____

Student No: _____

3. For a shunt feedback amplifier, $R_{if} = 110\Omega$, $R_{of} = 26k\Omega$, $A_f = 20$, and $\omega_{L,f} = 10\text{rad/s}$. For the associated non-feedback amplifier, $R_o = 2k\Omega$ and $\omega_H = 10^4\text{rad/s}$.

(a) Find the non-feedback amplifier R_i , A and ω_L .

(b) What's the feedback's network β ?

(c) Changing a resistor from $10k\Omega$ to $11k\Omega$ changes A_f from 20 to 21. Determine the value of A when the resistor is $11k\Omega$. (HINT: Use sensitivity analysis.)

(a) We can find D from R_{of}/R_o (notice that, since $R_{of} > R_o$, we know that the amp. is current-shunt)

$$D = \frac{26k\Omega}{2k\Omega} = 13$$

Thus, $A = A_f D = 20(13) = 260$

$$R_i = D R_{if} = 13(110\Omega) = 1.43k\Omega$$

$$\omega_L = D \omega_{L,f} = 13(10\text{rad/sec}) = 130\text{rad/sec}$$

(b) $D = 1 + \beta A = 13 = 1 + \beta(260)$

$$\beta = \frac{13-1}{260} = \frac{12}{260} = \frac{6}{130} = \frac{3}{65} = 0.046$$

(c) $S_R^{A_f} = \frac{S_R^A}{D} \rightarrow S_R^A = D S_R^{A_f} = (13) \frac{\Delta A_f/A_f}{\Delta R/R} = 13 \frac{1/20}{1k/10k} = 6.5$

$$\therefore 6.5 = \frac{\Delta A/A}{\Delta R/R} \rightarrow \frac{\Delta A}{A} = 6.5 \frac{1k}{10k} = .650$$

$$\Delta A = .65(260) = 169$$

and ~~new~~ $A = 260 + 169 = 429$ when $R = 11k$

Name: _____

Student No: _____

4. A feedback amplifier displays a transresistance gain $R_{Mf} = 10^5 \Omega$, $R_{if} = 10 \Omega$ and $R_{of} = 10 \Omega$. The feedback type is voltage-shunt with $\beta = 0.9 \times 10^{-5}$.

- Determine the current and voltage gains of the feedback amplifier.
- Find the transresistance gain R_M , input resistance R_i and output resistance R_o of the non-feedback amplifier.
- Determine the current and voltage gains of the non-feedback amplifier.

$$(a) \underline{A_{if}} = \frac{i_o}{i_s} = \frac{v_o/R_{of}}{i_s} = \frac{v_o}{i_s} \frac{1}{R_{of}} = R_{MF} \frac{1}{R_{of}} = \frac{10^5 \Omega}{10 \Omega} = \boxed{10^4}$$

$$\underline{A_{vf}} = \frac{v_o}{v_s} = \frac{v_o}{i_s R_{if}} = \frac{1}{R_{if}} R_{MF} = \frac{10^5 \Omega}{10 \Omega} = \boxed{10^4}$$

(b) From table,

$$R_{mf} = R_M/D = R_M/(1 + \beta R_M)$$

$$R_{MF} + \beta R_M R_{MF} = R_M$$

$$R_{MF} = (1 - \beta R_M) R_M$$

$$R_M = \frac{R_{MF}}{1 - \beta R_{MF}} = \frac{10^5}{1 - (0.9 \times 10^{-5})(10^5)} = \frac{10^5}{.1} = \boxed{10^6}$$

$$D = 1 + (0.9 \times 10^{-5})(10^6) = 10$$

$$\therefore R_{if} = R_i/D ; R_i = D R_{if} = \boxed{100 \Omega}$$

$$R_{of} = R_o/D ; R_o = D R_{of} = \boxed{100 \Omega}$$

$$(c) A_i = \frac{i_o}{i_s} = \frac{v_o/R_o}{i_s} = \frac{R_M}{R_o} = \frac{10^6}{100} = \boxed{10^4}$$

$$A_o = \frac{v_o}{v_s} = \frac{v_o}{i_s R_i} = \frac{R_M}{R_i} = \boxed{10^4}$$