

Name: KEY

Student No: \_\_\_\_\_

Electrical and Computer Engineering Department  
University of Puerto Rico - Mayaguez, P.R.  
Electronics II - Spring 2000 - Third Exam - Prof. Manuel Toledo  
BE CLEAR AND WELL ORGANIZED OR LOOSE POINTS

1. A non-feedback amplifier with voltage gain  $A_V = 1,000 \pm 100$  is available. It is necessary to have a voltage-series feedback amplifier whose voltage gain varies by no more than  $\pm 0.1\%$ .
- (a) Find the  $\beta$  of the feedback network. (5 pts)
  - (b) Determine the gain of the feedback amplifier. (5 pts)

(a) variability of non-feedback amp =  $\frac{100}{1000} \times 100\% = 10\%$

$\therefore D = \frac{10\%}{0.1\%} = 100 = 1 + \beta A$


Since  $A = 1000$

$\beta = \frac{99}{1000} = 0.099$


(b)  $A_{VF} = \frac{A_V}{D} = \frac{1000}{100} = 10 = A_{VF}$

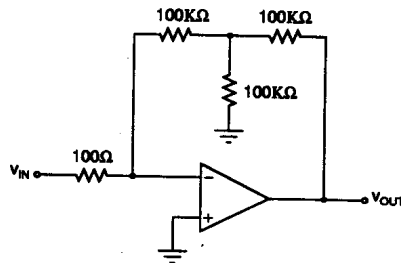2. In the amplifier shown below, voltage-shunt feedback is being employed. The active element is an opamp, with open-loop voltage gain  $A_{OL} = 10^4$ , output resistance  $R_{out} = 1k\Omega$ , and input resistance is  $R_d = 10k\Omega$ .

- Find the feedback network's  $\beta$ , and the 11 and 22 parameters that correspond to the type of feedback being used. (5 pts)
- Find the non-feedback amplifier's gain, input resistance  $R_i$  and output resistance  $R_o$  that should be used to apply feedback theory. (10 pts) (HINT: REPLACE OPAMP BY ITS TWO-PORT NETWORK MODEL)
- Use feedback theory to find the feedback amplifier's voltage gain  $A_{vf} = \frac{v_{OUT}}{v_{IN}}$ , input resistance  $R_{if}$  and output resistance  $R_{of}$ . (10 pts)



(a) feedback is voltage-shunt - y model

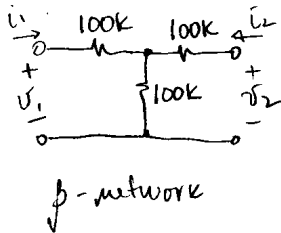


$$y_{11} = \frac{i_1}{v_1} \Big|_{v_2=0} = \frac{1}{150k}$$

$$y_{22} = \frac{i_2}{v_2} \Big|_{v_1=0} = \frac{1}{150k}$$

$$y_{12} = \frac{i_1}{v_2} \Big|_{v_1=0} = -\frac{1}{150k} \frac{100k}{200k}$$


$$y_{12} = -3.33 \times 10^{-6} \text{ A/V} = \beta$$

(b)

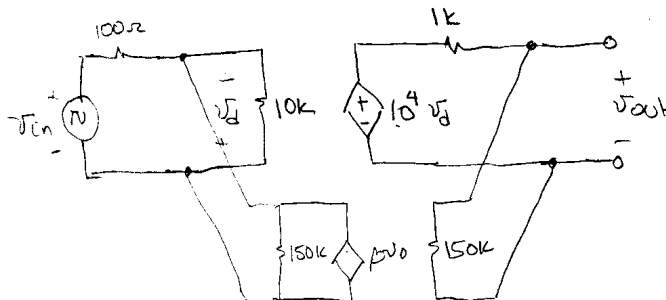

Student No: \_\_\_\_\_

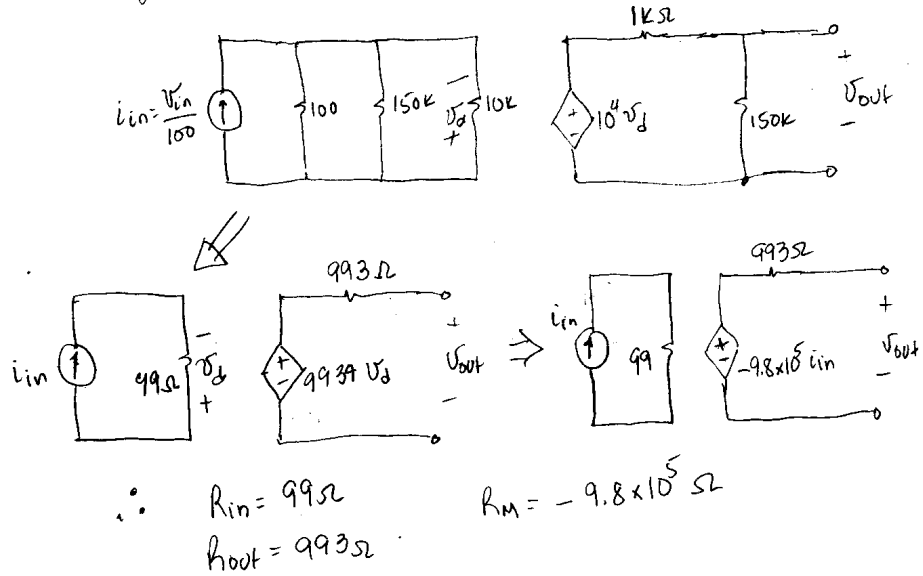Setting the feedback  $\beta$  to zero and noticing that the required gain is a transresistance,



(c)  $D = 1 + \beta R_M = 1 + (-3.33 \times 10^6)(-9.8 \times 10^5 \Omega) = 4.26$

$R_{MF} = \frac{-9.8 \times 10^5 \Omega}{4.26} = -2.3 \times 10^5 \Omega = \frac{v_{out}}{i_{in}} = \frac{v_{out}}{v_{in}/100 \Omega}$

$\therefore A_{VF} = \frac{v_{out}}{v_{in}} = \frac{R_{MF}}{100} = \boxed{-2.3 \times 10^4}$


$R_{if} = \frac{R_i}{D} = \frac{99}{4.26} \Omega = \boxed{23.2 \Omega = R_{if}}$

$R_{of} = \frac{R_o}{D} = \frac{993}{4.26} = \boxed{233.1 \Omega = R_{of}}$

Student No: \_\_\_\_\_

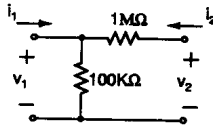3. A FET non-feedback amplifier has a voltage gain  $A_V = +g_m R_D$ . When the amplifier is operating at 25 degrees Celsius (room temperature), the nominal values for  $g_m$  and  $R_D$  are  $10\text{mA/V}$  and  $10\text{K}\Omega$ , respectively. While  $g_m$  drops with increasing temperature at a rate of approximately 0.5% per degree Celsius, the resistance increases at about  $10\Omega$  per degree Celsius.

If the following circuit is used to establish voltage-series feedback,



determine

- the  $\beta$  of the feedback network (5 pts)
- the temperature sensitivity of the non-feedback amplifier's voltage gain (5 pts)
- the temperature sensitivity of the feedback amplifier's voltage gain (5 pts)

$$(a) \quad \beta = \left. \frac{v_1}{v_2} \right|_{i_1=0} = \frac{100\text{K}\Omega}{1100\text{K}\Omega} = \boxed{\frac{1}{11}}$$

$$(b) \quad S_T^{A_V} = \frac{T}{A} \frac{dA}{dT} \approx \frac{T}{A} \frac{\Delta A}{\Delta T}$$

at  $25^\circ\text{C}$ ,  $A_V = (10\text{mA/V})(10\text{K}\Omega) = 100$

at  $26^\circ\text{C}$ ,  $A_V(26^\circ) = (10\frac{\text{mA}}{\text{V}} \times 0.995) \times (10010\Omega)$

$A_V(26^\circ) = 99.6$

$$S_T^{A_V} \approx \frac{25}{100} \frac{(99.6 - 100)}{(26 - 25)} = -0.1 = \boxed{-10\%}$$

$$(c) \quad S_T^{A_{Vf}} = \frac{S_T^{A_V}}{D} \quad ; \quad D = 1 + \beta A = 1 + \left(\frac{1}{11}\right)(100) = 10.09$$

$$\therefore S_T^{A_{Vf}} = \frac{-10\%}{10.09} \approx \boxed{-1\%}$$

Name: \_\_\_\_\_

Student No: \_\_\_\_\_

4. (BONUS) Draw a schematic diagram of a circuit that approximates the feedback amplifier described in problem 3. (5 pts)

Since  $A_v = +g_m R_D$ , the amplifier must be common-gate. A possible implementation would be:

