

Name: \_\_\_\_\_

Student No: \_\_\_\_\_


Electrical and Computer Engineering Department  
University of Puerto Rico - Mayaguez, P.R.  
Electronics II - Summer 1999 - Third Exam - Prof. Manuel Toledo  
**EACH PROBLEM IS 20 POINTS**

1. An amplifier with poles at  $300\text{kHz}$  and  $3\text{MHz}$  is made into a voltage-series feedback amplifier by subtracting 10 % of the output voltage to its input. Assume that the effect of the feedback network on the original amplifier midband gain  $A_v$  is negligible. What is the voltage gain  $A_v$  if the phase margin is 45 degrees?.

Name: \_\_\_\_\_

Student No: \_\_\_\_\_

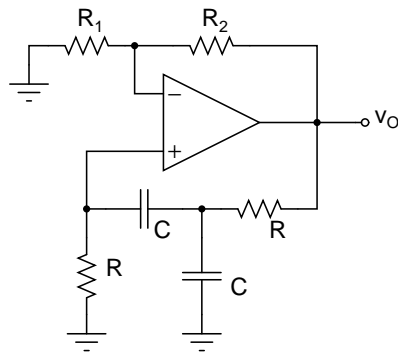2. For the oscillator shown below, derive an expression for the frequency of oscillation in terms of  $R$  and  $C$ . What minimum value of  $\frac{R_2}{R_1}$  is required for oscillations to be maintained?



Name: \_\_\_\_\_

Student No: \_\_\_\_\_

Name: \_\_\_\_\_

Student No: \_\_\_\_\_

3. Design a class B amplifier capable of delivering 25 watts to a 10 ohms load. Your design should specify minimum power supply rated voltage, current and power, as well as the dissipation requirements for the PNP and NPN power transistors. Your design must work for output signal levels lower than the maximum.

Name: \_\_\_\_\_

Student No: \_\_\_\_\_

4. Design a 680kHz Wein-bridge oscillator. Use an ideal op-amp as your active element. Find suitable values for all passive components. Draw the schematic diagram.

Name: \_\_\_\_\_

Student No: \_\_\_\_\_

5. A transistor is operating in an ideal class B amplifier with a  $1k\Omega$  load. A d.c. meter in the collector circuit reads an average current of 10 mA. How much signal power is being delivered to the load?