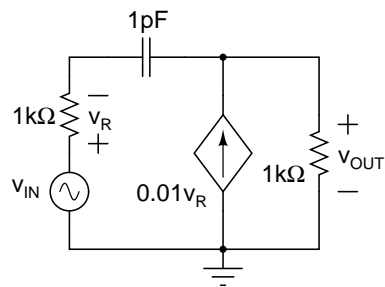


NAME:

STUDENT NO.:

University of Puerto Rico  
Electrical and Computer Engineering Department  
INEL 4202 - Electronics II - Spring 2000 - Exam 2 - Prof. M. Toledo  
THERE ARE FOUR PROBLEMS - BE CLEAR OR LOOSE POINTS


1. Use the open-circuit time constant method to estimate the high-frequency pole for the following circuit. Do not use the Miller approximation. (25 pts)



NAME:

STUDENT NO.:

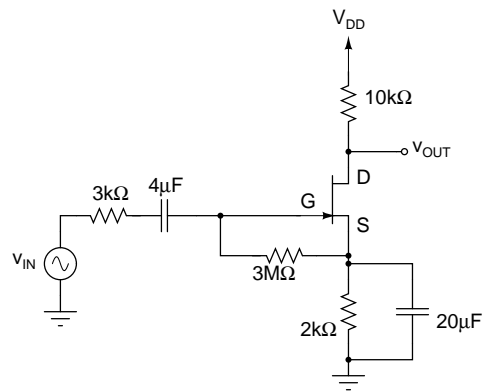2. Use the short circuit time constant method to estimate the dominant low-frequency pole for the circuit below. The transistor has  $g_m = 5.6 \times 10^{-3}$  A/V. (25 pts)




NAME:

STUDENT NO.:

3. The circuit shown below has identical transistors biased at 0.5 mA. Parameters are  $r_b = 120\Omega$ ,  $r_\pi = 15k\Omega$ ,  $V_A = 180V$ ,  $C_\pi = 40pF$  and  $C_\mu = 4pF$ .

(a) Draw the high-frequency equivalent circuit. (10 pts)

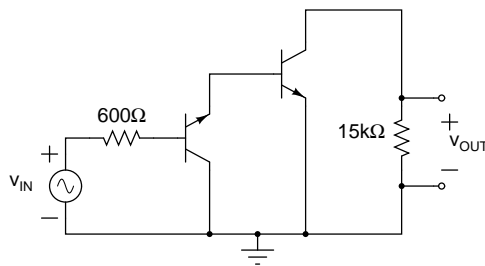(b) Determine the upper half-power frequency for the amplifier. (25 pts)



NAME:

STUDENT NO.:

4. Estimate the mid-band gain and write down an expression for the gain as a function of frequency for the transistor amplifier shown below. Use  $g_m = 10\text{mA/V}$  and  $C_{gs} = C_{gd} = 4\text{pF}$ . (15 pts)

