

University of Puerto Rico - ECE Department
INEL 4202 - Electronics II - Summer 2001 - Exam 2 Solutions - Prof. M. Toledo

1. For a current-mixing feedback amplifier, $R_{if} = 110\Omega$, $R_{of} = 26k\Omega$, $A_f = 20$, and $\omega_{L,f} = 10rad/s$. For the associated non-feedback amplifier, $R_o = 2k\Omega$ and $\omega_H = 10^4rad/s$.
- (a) Find the non-feedback amplifier R_i , A and ω_L . (10 pts)
 (b) What's the feedback's network β ? (10 pts)

ANSWER

- (a) Since $R_{of} > R_o$, the amplifier must sample current. Thus,

$$D = 1 + \beta A = \frac{R_{of}}{R_o} = \frac{26k\Omega}{2k\Omega} = 13$$

Since the feedback is current-mixing, $R_{if} = R_i/D$ and

$$R_i = D \times R_{if} = 13 \times 110\Omega = 1430\Omega$$

$$A = D \times A_f = 20 \times 13 = 260A/A$$

$$\omega_L = D \times \omega_{LF} = 13 \times 10rad/s = 130rad/s$$

- (b)

$$D = 1 + \beta \times A$$

$$\beta = \frac{D - 1}{A} = \frac{13 - 1}{260} \approx 0.046$$

2. A feedback amplifier displays a transresistance gain $R_{Mf} = 10^5\Omega$, $R_{if} = 10\Omega$ and $R_{of} = 10\Omega$. The feedback type is voltage-sampling, current-mixing with $\beta = 0.9 \times 10^{-5}$. The source's Thevenin resistance is $R_s = v_s/i_s = 1k\Omega$ and $R_L = v_o/i_o = 2k\Omega$.
- (a) Determine the current and voltage gains, $A_{vf} = v_o/v_s$ and $A_{if} = i_o/i_s$ respectively, of the feedback amplifier. (10 pts)
 (b) Find the transresistance gain $R_M = v_o/i_s$, input resistance R_i and output resistance R_o of the non-feedback amplifier. (10 pts)
 (c) Determine the current and voltage gains of the non-feedback amplifier. (10 pts)

ANSWER

- (a)

$$R_{Mf} = \frac{v_o}{i_s} = \frac{i_o R_L}{i_s} = R_L A_{if}$$

Thus

$$A_{if} = R_{Mf}/R_L = 10^5\Omega/2k\Omega = 50A/A$$

Also since

$$R_{Mf} = \frac{v_o}{i_s} = \frac{v_o}{v_s/R_s} = R_s A_{vf}$$

then

$$A_{vf} = \frac{R_{Mf}}{R_s} = 100V/V$$

(b) From $R_{Mf} = \frac{R_M}{1 + \beta \times R_M}$,

$$R_M = \frac{R_{Mf}}{1 - \beta \times R_{Mf}} = \frac{10^5}{1 - (0.9 \times 10^{-5})(10^5)} = 10^6 \Omega$$

The improvement factor is $D = 1 + \beta R_M = 1 + (0.9 \times 10^{-5})(10^5) = 10$ and


$$R_i = D \times R_{if} = 100 \Omega$$

$$R_o = D \times R_{of} = 100 \Omega$$

(c) $A_i = R_M/R_L = 500 A/A$; $A_v = R_M/R_s = 1000 V/V$

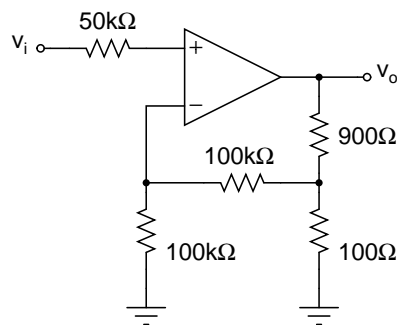
3. In the amplifier shown below, voltage-sampling, voltage-mixing feedback is employed. The active element is an opamp, for which the open-loop gain is 10^5 , the output resistance is $R_O = 1 k\Omega$, and the input resistance is $R_i = 100 k\Omega$.

- Find the feedback network's β , R_{11} and R_{22} . (10 pts)
- Replace the opamp with its two-port network equivalent circuit and draw the resulting non-feedback amplifier diagram, including the loading effects of the feedback network. (10 pts)
- Find the non-feedback amplifier's voltage gain A_v , input resistance R_i and output resistance R_o that should be used to apply feedback theory. (10 pts)
- Use feedback theory to find the feedback amplifier's voltage gain A_{vf} , input resistance R_{if} and output resistance R_{of} . (10 pts)



ANSWER

(a) The feedback network is

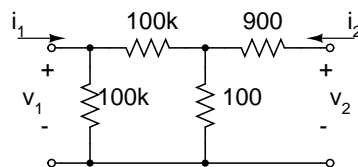


Using formulae for voltage-voltage feedback from the table

$$\beta = \frac{1}{2} \frac{50k \parallel 100}{900 + 50k \parallel 100} \approx 0.05$$

$$R_{11} = (900 \parallel 100 + 100k) \parallel 100k = 50k\Omega$$

$$R_{22} = 900 + (100k + 100k) \parallel 100 \approx 1k\Omega$$

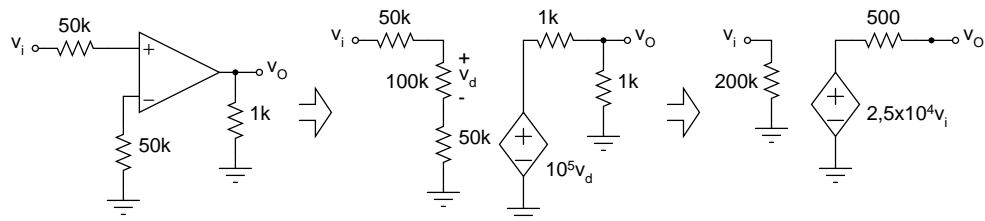(b) Replacing the feedback network by R_{11} and R_{22} we obtain the non-feedback amplifier, which can be simplified as follows:



(c) From the above schematic,

$$A_v = 2.5 \times 10^4 V/V$$

$$R_i = 200k$$

$$R_o = 500$$

(d) Now we can apply feedback theory to obtain

$$D = 1 + (0.05)(2.5 \times 10^4) = 1251$$


$$A_{vf} = \frac{2.5 \times 10^4}{D} \approx 20V/V$$

$$R_{if} = D \times R_i = 250.2M\Omega$$

$$R_{of} = R_o/D = 0.4\Omega$$

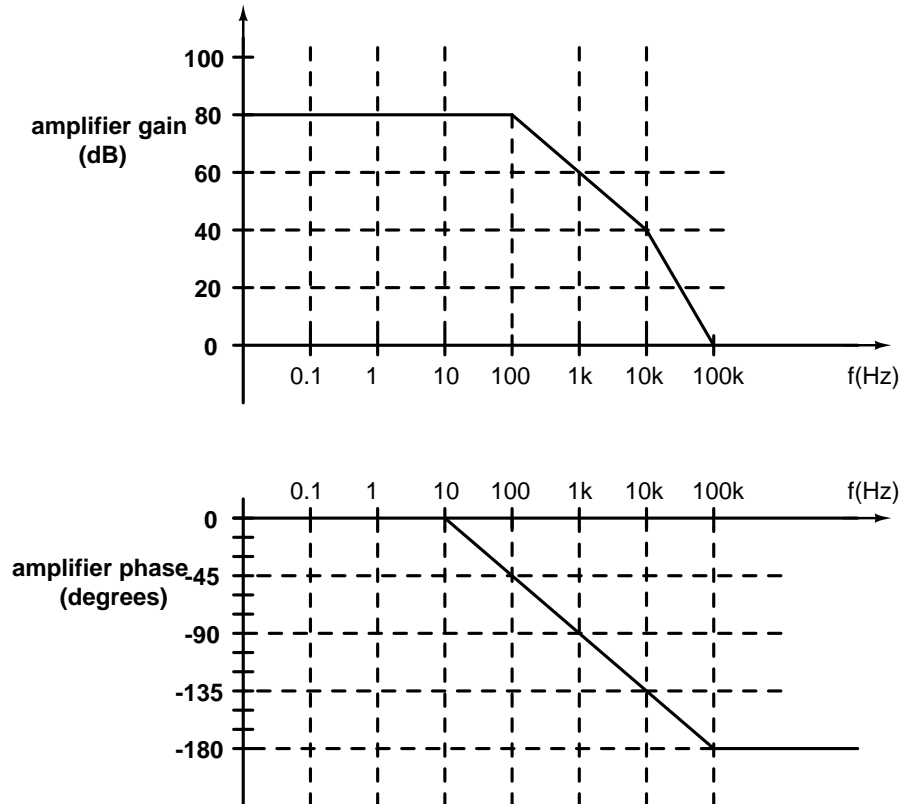4. Shown below is the frequency response for the voltage gain of a non-feedback amplifier. The response shows poles at 100Hz and 10kHz.


- Determine the approximate value of the feedback network's β that will yield a phase margin of 60 degrees. (10 pts)
- Use the pole shifting technique to find the position of the lowest frequency pole that would compensate the amplifier to have a 45° phase margin when $\beta = .1$. (10 pts)



ANSWER


- About $20 \log 1/\beta = 45 \text{ dB}$, or $\beta \approx 0.0056$.
- The phase is about 135° at 10 kHz . At this frequency, the gain is 40 dB . We must reduce this gain to $20 \log 1/\beta = 20 \log 10 = 20 \text{ dB}$, i.e. by 20 dB . Thus, we need to move the first pole down by one decade, to 10 Hz .

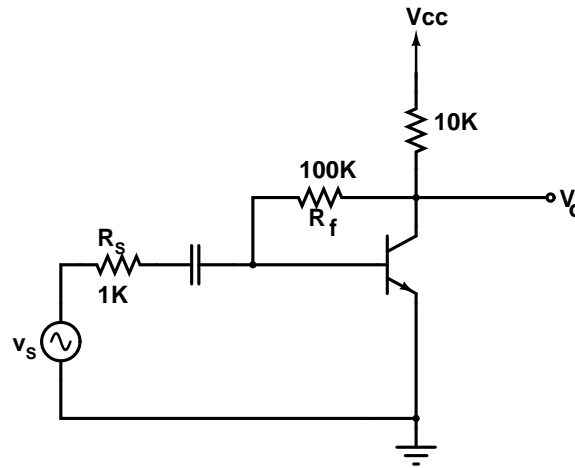5. In the following amplifier, voltage-sampling, current-mixing feedback is used. Find the feedback amplifier transresistance, R_{mf} . Assume that the capacitor is a short circuit at the operating frequency. Use $\beta = 100$ and $r_\pi = 2k\Omega$. (15 pts)



ANSWER

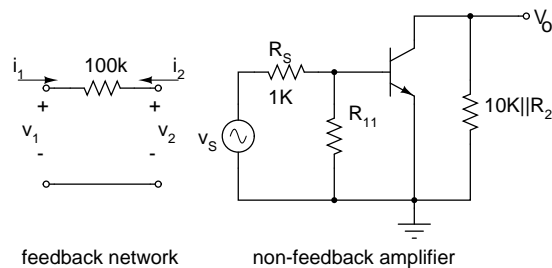To solve the problem, we must first find the non-feedback amplifier that incorporates the feedback's network resistive loads. The feedback network is shown on the left of the following figure:



From the table's formulae,

$$R_{11} = \frac{v_1}{i_1} \Big|_{v_2=0} = 100k\Omega$$

$$R_{22} = \frac{v_2}{i_2} \Big|_{v_1=0} = 100k\Omega$$

and

$$\beta = \frac{i_1}{v_2} \Big|_{v_1=0} = -\frac{1}{100k\Omega}$$

Now we can calculate the gain from the schematic shown on the right in the above figure. Using the formulae included in the exam's formula sheet,

$$A_v = -g_m R_c \frac{R_{in}}{R_{in} + R_s} = -\frac{100}{2k\Omega} (10k \parallel 100k) \frac{100k \parallel 2k}{100k \parallel 2k + 1k} = -301$$

Using this result, we can find the transresistance

$$R_M = \frac{v_o}{i_s} = \frac{v_o}{v_s/R_s} = R_s A_v = -301k\Omega$$

Finally,

$$R_{Mf} = \frac{R_M}{1 + \beta \times R_M} = \frac{-301k\Omega}{4.01} = -75k\Omega$$