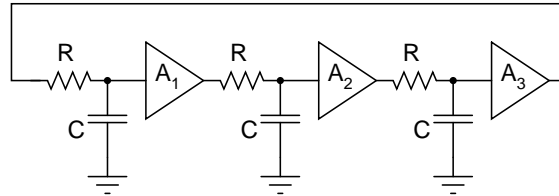


NAME:


STUDENT NO.:

University of Puerto Rico  
Electrical and Computer Engineering Department  
INEL 4202 - Electronics II - Summer 2001 - Exam 4 - Prof. M. Toledo  
THERE ARE THREE PROBLEMS + 5 BONUS POINTS FOR CLARITY

1. The oscillator shown below uses three ideal amplifiers that exhibit infinite input resistance and zero output resistance. Find the frequency of oscillation and a condition that the product of the gains  $A_1 A_2 A_3$  must satisfy for the circuit to work as an oscillator. (30 points)



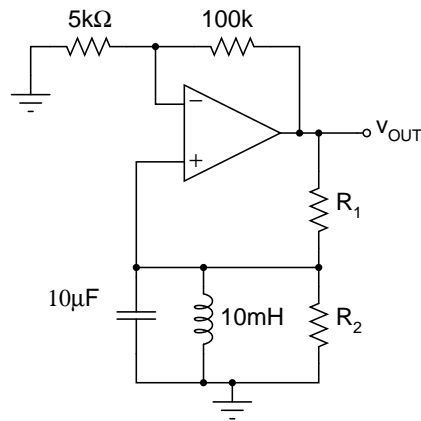2. For the oscillator shown, find the frequency of oscillation and the maximum value of  $R_1$  required for oscillations if  $R_1 + R_2 = 10k\Omega$ . (35 points)



3. For the ideal class B push-pull amplifier shown below, assume that the input is sinusoidal. Determine (35 points)
- (a) the maximum signal power
  - (b) the power dissipation in each transistor when the output power is maximum,
  - (c) the efficiency if the output voltage is half of the maximum possible without saturating either transistor,
  - (d) the maximum power dissipation at each transistor for an arbitrary amplitude input, and
  - (e) the efficiency of the amplifier when transistors dissipate this maximum power.

