
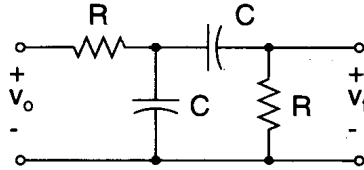


Electronics II - Extra Practice Problems - Sinusoidal Oscillators

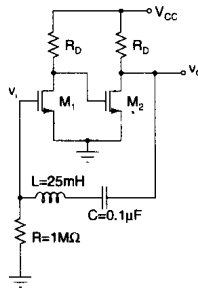
1. The following circuit is used as the phase-shifting network for a two-stage FET oscillator. Find the circuit's beta, $\beta(s) = \frac{v_f}{v_o}$. Determine the frequency of oscillation and the gain required from the amplifier. (30 points)




2. Design a 680kHz Wein-bridge oscillator. Use an ideal op-amp as your active element.
3. For the oscillator circuit shown below, the two transistors have $g_m = 1.6mA/V$. Each part below is 5 points.
- Draw a diagram of the phase shift network.
 - Find $\beta(s) = \frac{v_i}{v_o}$ from the diagram drawn in part (a).
 - Determine the loop gain, $A(s)\beta(s)$. HINT: THE GAIN WILL DEPEND ON THE PHASE SHIFT NETWORK.
 - Apply the Barkhausen Criterion to find the frequency of oscillation.
 - Find the minimum value of R_D that would satisfy the Barkhausen Criterion.



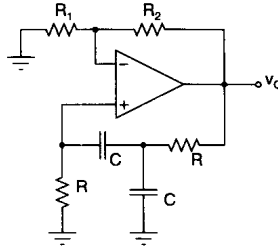
4. For the oscillator shown below, derive an expression for the frequency of oscillation in terms of R and C . What minimum value of $\frac{R_2}{R_1}$ is required for oscillations to be maintained?



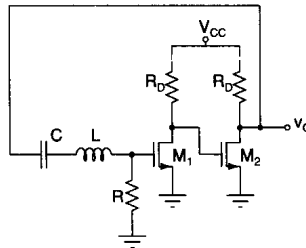
5. For the oscillator shown below, derive an expression for the frequency of oscillation in terms of R , L and C . Find an expression, in terms of g_m , R_D and R , that must be satisfied in order to have sustained oscillations.



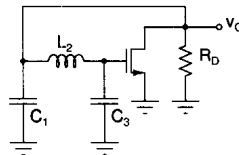6. For the Colpitts oscillator shown below, find values for L_2 , C_3 and R_D appropriate to produce sustained oscillations at 100kHz if $C_1 = 10\text{nF}$. Use $g_m = 1\text{mA/V}$.



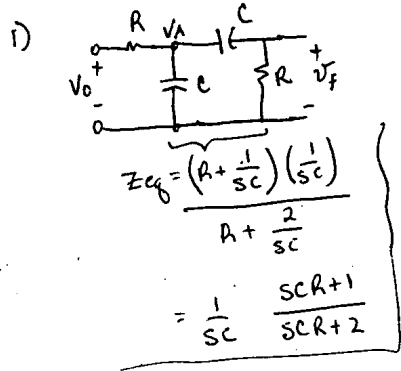Extra Practice Problems - Sinusoidal Oscillators



$$V_F = \frac{R}{R + \frac{1}{sC}} V_A = \frac{sCR}{sCR + 1} V_A$$

$$\frac{V_A}{V_0} = \frac{Z_{eq}}{Z_{eq} + R} = \frac{sCR + 1}{sC(sCR + 2) \left(R + \frac{sCR + 1}{sC(sCR + 2)} \right)}$$



$$= \frac{sCR + 1}{s^2 C^2 R^2 + 2sCR + sCR + 1} = \frac{sCR + 1}{s^2 C^2 R^2 + 3sCR + 1}$$

$$\beta = \frac{V_F}{V_0} = \frac{V_F}{V_A} \frac{V_A}{V_0} = \frac{sCR}{s^2 C^2 R^2 + 3sCR + 1}$$

To satisfy the Barkhausen Criterion: $s^2 C^2 R^2 + 1 = 0$
 $-\omega^2 C^2 R^2 + 1 = 0 \Rightarrow \omega_r = \frac{1}{RC}$

at $\omega = \omega_r$, $\beta = \frac{1}{3}$; \therefore amplifier gain ≥ 3

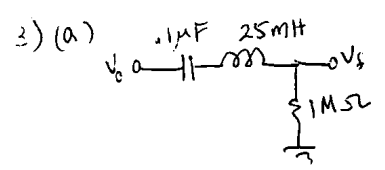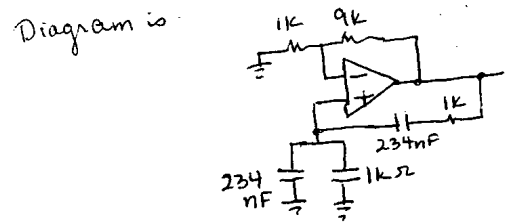2) From book/class notes, $\omega = \frac{1}{RC}$; $1 + \frac{R_2}{R_1} \geq 3$
 for $\omega = 2\pi \times 690 \text{ kHz}$, let $R = 1 \text{ k}\Omega$; $C = 0.234 \mu\text{F}$
 Set gain to 10 $\frac{R_2}{R_1} = 9$; let $R_1 = 1 \text{ k}\Omega$, $R_2 = 9 \text{ k}\Omega$



b)

$$\beta = \frac{1 \text{ M}\Omega}{1 \text{ M}\Omega + \frac{1}{(0.1 \mu\text{F})s} + (25 \text{ mH})s}$$

$$= \frac{0.1s}{2.5 \times 10^{-9} s^2 + 0.1s + 1}$$

$$= \frac{sCR}{s^2 + (4 \times 10^7)s + 40 \times 10^7} = \frac{sCR}{s^2 + sCR + 1}$$

$$c) Z_p = R + sL + \frac{1}{sC} \quad Z_D = R_D \parallel Z_p = \frac{R_D (R + sL + \frac{1}{sC})}{R_D + R + sL + \frac{1}{sC}}$$

$$Z_D = \frac{R_D (s^2 LC + sCR + 1)}{s^2 LC + (R + R_D)s + 1}$$

$$\text{gain} = (-g_m R_D) (-g_m Z_D) = g_m^2 R_D^2 \frac{s^2 LC + sCR + 1}{s^2 LC + (R + R_D)s + 1}$$

$$\text{gain} \times \beta = g_m^2 R_D^2 \frac{sRC}{s^2 LC + (R + R_D)s + 1}$$

$$d) s^2 LC + 1 = 0; \quad -\omega_c^2 LC + 1 = 0; \quad \omega_c = \frac{1}{\sqrt{LC}}$$

$$\omega_c = \frac{1}{\sqrt{1 \text{ mH} \times 1 \mu\text{F}}} = \frac{1}{\sqrt{10^{-6}}} = 100,000 \text{ r/s}$$

$$e) \text{gain} \times \beta \text{ at } \omega = \omega_c = g_m^2 R_D^2 \frac{R}{R + R_D} > 1$$

$$(1.6 \times 10^{-3})^2 R_D^2 \frac{10^6}{10^6 + R_D} > 1$$

$$2.56 R_D^2 - R_D - 10^6 > 0$$

$$R_D = \frac{+1 \pm \sqrt{1 - (2.56)(-10^6)}}{2(2.56)} \geq \boxed{313 \Omega}$$

4) Feedback network is the same than problem's 1.

$$\dots 1 + \frac{R_2}{R_1} \geq 1 \rightarrow R_2/R_1 \geq 2$$

5) Same as problem. 3.

$$6) \beta = \frac{\frac{1}{sC_3}}{sL_2 + \frac{1}{sC_3}} = \frac{1}{s^2 L_2 C_3 + 1}$$

$$Z_D = R_D \parallel \frac{1}{sC_1} \parallel (sL_2 + \frac{1}{sC_3})$$

$$= \frac{1}{\frac{1}{R_D} + sC_1 + \frac{sC_3}{s^2 L_2 + 1}}$$

$$Z_D = \frac{s^2 L_2 C_3 + 1}{\left(\frac{1}{R_D} + sC_1\right) (s^2 L_2 C_3 + 1) + sC_3}$$

$$= \frac{R_D (s^2 L_2 C_3 + 1)}{(sC_1 R_D + 1) (s^2 L_2 C_3 + 1) + sR_D C_3}$$

$$= \frac{R_D (s^2 L_2 C_3 + 1)}{s^3 R_D L_2 C_1 C_3 + sC_1 R_D + s^2 L_2 C_3 + sR_D C_3}$$

$$= \frac{R_D (s^2 L_2 C_3 + 1)}{s^3 R_D L_2 C_1 C_3 + sR_D (C_1 + C_3) + s^2 L_2 C_3 + 1}$$

$$Z_D = \frac{R_D (s^2 L_2 C_3 + 1)}{s^3 R_D L_2 C_1 C_3 + sR_D (C_1 + C_3) + s^2 L_2 C_3 + 1}$$

$$\text{gain} = -g_m Z_D = \frac{-g_m R_D (s^2 L_2 C_3 + 1)}{s^3 R_D L_2 C_1 C_3 + s^2 L_2 C_3 + s R_D (C_1 + C_3) + 1}$$

$$\beta \times \text{gain} = \frac{-g_m R_D}{s^3 R_D L_2 C_1 C_3 + s^2 L_2 C_3 + s R_D (C_1 + C_3) + 1}$$

$$s^2 R_D L_2 C_1 C_3 + R_D (C_1 + C_3) = 0$$

$$+ \omega_r^2 R_D L_2 C_1 C_3 = R_D (C_1 + C_3)$$

$$\omega_r = \sqrt{\frac{C_1 + C_3}{R_D L_2 C_3 C_1}}$$

$$C_1 = 10 \text{ nF}$$

$$\omega_r = \sqrt{\frac{10 \text{ nF} + C_3}{R_D L_2 C_3 (10 \text{ nF})}}$$

$$\text{set } C_3 = 1 \text{ nF}$$

$$\omega_r = \sqrt{\frac{11 \text{ nF}}{10^{-17} R_D L_2}} = 10^5$$

$$\frac{10^{-17} R_D L_2}{11 \times 10^{-9}} = 10^{-10}$$

$$R_D L_2 = \frac{11 \times 10^{-9} \times 10^{-10}}{10^{-17}} = 11$$

$$\text{set } L_2 = 1 \text{ mH}$$

$$R_D = 110 \Omega$$