

NAME: KEY

STUDENT NO.:

University of Puerto Rico
Electrical and Computer Engineering Department
INEL 4202 - Electronics II - Exam 4 - Prof. M. Toledo
25 POINTS EACH PROBLEM - BE CLEAR OR LOOSE POINTS

1. The sketch below shows a sinusoidal oscillator. The transistor transconductance is g_m .

- (a) Find an expression for the frequency of oscillation, ω_r , in terms of C , and L .
- (b) Apply Barkhausen amplitude criterion to find an expression, in terms of g_m , C , R and R_D , that the circuit gain should satisfy for sustained oscillations.

(a)


Let

$$X_L = \omega L$$

$$X_C = -\frac{1}{\omega C}$$

Then

$$\beta = \frac{R}{R + j(X_L + X_C)}$$

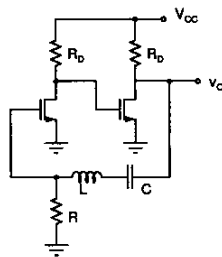

$$Z_{\beta} = R + j(X_L + X_C)$$

and

$$Z_D = R_D \parallel Z_{\beta} = \frac{R_D [R + j(X_L + X_C)]}{R_D + R + j(X_L + X_C)}$$

$$\text{gain} = g_m^2 R_D Z_D = g_m^2 R_D^2 \frac{R + j(X_L + X_C)}{R_D + R + j(X_L + X_C)}$$

$$\beta \times \text{gain} = g_m^2 R_D^2 \frac{R}{R_D + R + j(X_L + X_C)}$$

Since numerator is real, denominator should also be real (phase criterion). Thus

$$X_L = -X_C = \omega L = \frac{1}{\omega C} \Rightarrow \boxed{\omega_r = \frac{1}{\sqrt{LC}}}$$

(b) at $\omega = \omega_r$

$$\boxed{A_v \beta = g_m^2 R_D^2 \frac{R}{R_D + R} \geq 1}$$

NAME:

STUDENT NO.:


3. Design a low-pass, fourth order Butterworth filter with a cutoff frequency of 5000Hz. Use cascaded Sallen-Key and first order stages, as needed. The filter's d.c. gain should be 0dB. $B_4(s) = (s^2 + 0.765s + 1)(s^2 + 1.847s + 1)$.

$$\frac{1}{RC} = 2\pi \times 5K \rightarrow \text{Set } R = 1k\Omega; C = 31.8nF \approx 32nF$$

We need two Sallen-key stages

stage 1: $3 - A_v = 0.765 \Rightarrow 1 + \frac{R_2}{R_1} = 2.235$; Select $R_1 = 1k$
 $R_2 = 1235\Omega$

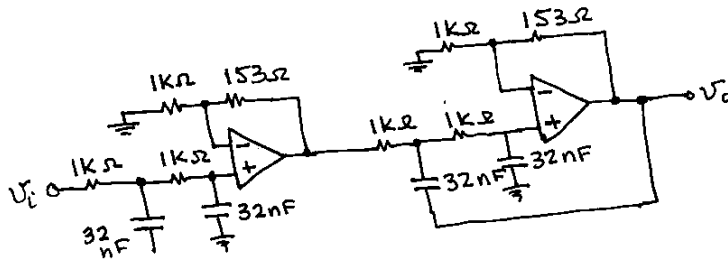
stage 2: $3 - A_v = 1.847 \Rightarrow \frac{R_2}{R_1} = 0.153$; Select $R_1 = 1k$
 $R_2 = 153\Omega$



NAME:

STUDENT NO.:

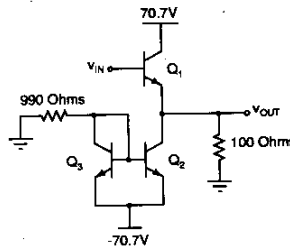2. In the sketch shown below, the area of transistor Q_2 is 10 times the area of transistor Q_3 . Find the efficiency of the amplifier if the peak output voltage is maintained at $\frac{1}{2}V_{CC}$. Determine the required power rating for Q_1 if this output voltage level is always maintained.



$$P_{DC} = \frac{2V_{CC}^2}{R_L} = \frac{2(5000)}{100} = 100W \quad \leftarrow \text{(this neglects power dissipated in } 990\Omega \text{ of } Q_3)$$

$$P_{Load} = \frac{\left(\frac{1}{2}V_{CC}\right)^2}{2R_L} = \frac{1}{8} \frac{V_{CC}^2}{R_L} = \frac{1}{8} \frac{5000}{100} = 6.25W$$

$$\therefore \eta = \frac{6.25W}{100W} \times 100\% = \boxed{6.25\%}$$

$$P_{c.s.} = P_{DQ_2} = (70.7)(I_{EE})$$

$$I_{EE} = 10 \frac{70.7 - 0.7V}{990\Omega} = 0.707A \Rightarrow P_{c.s.} \approx 50W$$

$$P_{DQ_1} = 100W - 50W - 6.25W = \boxed{43.75W}$$

If we take into account the energy dissipated in the 990 Ω resistor and Q_3 , then

$$P_{DC} = 100W + (70.7mA)^2(990\Omega) + (70.7mA)(0.7V) \approx 105W$$

$$\text{and } \eta = \frac{6.25W}{105W} \times 100\% = \boxed{5.95\%}$$