


Name: _____

Student No: _____

Electrical and Computer Engineering Department
University of Puerto Rico - Mayaguez, P.R.
Electronics II - Spring 1999 - Final Exam - Prof. Manuel Toledo

1. For the oscillator circuit shown below, the two transistors have $g_m = 1.6 \text{ mA/V}$. Each part below is 5 points.

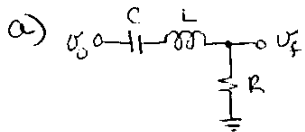
- (a) Draw a diagram of the phase shift network.
- (b) Find $\beta(s) = \frac{v_f}{v_o}$ from the diagram drawn in part (a).
- (c) Determine the loop gain, $A(s)\beta(s)$. HINT: THE GAIN WILL DEPEND ON THE PHASE SHIFT NETWORK.
- (d) Apply the Barkhausen Criterion to find the frequency of oscillation.
- (e) Find the minimum value of R_D that would satisfy the Barkhausen Criterion.



b)

$$\frac{v_f}{v_o} = \frac{R}{R + sL + \frac{1}{sC}} = \beta(s)$$
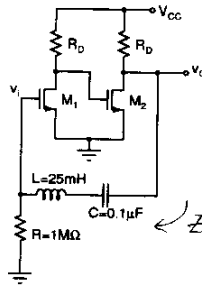
$$\beta(s) = \frac{sCR}{s^2LC + sCR + 1}$$



c)

$$A_{v1} = -g_m R_D ; A_{v2} = -g_m R_D // Z \Rightarrow A_v = g_m^2 R_D^2 \frac{Z}{Z + R_D}$$

$$Z = sL + \frac{1}{sC} + R = \frac{s^2LC + sCR + 1}{sC}$$

$$\therefore A_v = g_m^2 R_D^2 \frac{s^2LC + sCR + 1}{s^2LC + sCR + 1 + sCRD} = g_m^2 R_D^2 \frac{s^2LC + sCR + 1}{s^2LC + sC(R + R_D) + 1}$$

Using $\beta(s)$ from (b)

$$A_v \beta = g_m^2 R_D^2 \frac{sCR}{s^2LC + sC(R + R_D) + 1}$$

d) Real part of denominator must vanish $\Rightarrow -\omega^2LC + 1 = 0$
 $\therefore \omega = \frac{1}{\sqrt{LC}}$



e) Using ω from (d) and $A\beta$ from c

$$g_m^2 R_D^2 R / (R + R_D) = g_m^2 R_D (R_D // R) \geq 1 \Rightarrow \text{Solving for } R_D \text{ gives } R_D \geq 624 \Omega$$


Name: _____

Student No: _____

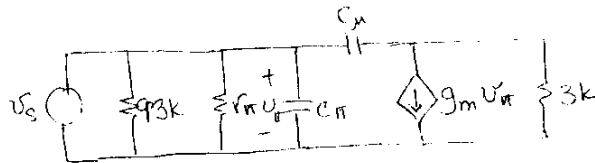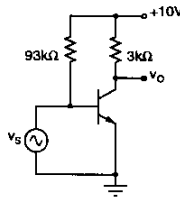3. Determine the high cutoff angular frequency, ω_H , for the following circuit. The input voltage source is ideal. HINT: YOU DON'T NEED β TO ANSWER THE QUESTION. DRAW THE AC EQUIVALENT CIRCUIT WITH THE TRANSISTOR REPLACED WITH ITS MODEL AND THINK. (25 points)



Using miller theorem

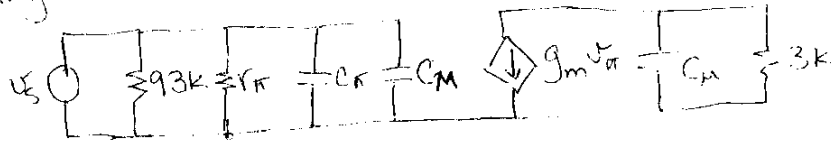

Since there is no resistor in series with v_s , C_π & C_μ can be charged instantly and do not affect the frequency response. Thus



$$\omega_H = \frac{1}{3k C_\mu}$$

Name: _____

Student No: _____

4. The sketch shown below is a diagram of a feedback amplifier. HINT: FEEDBACK TYPE IS CURRENT-SHUNT.

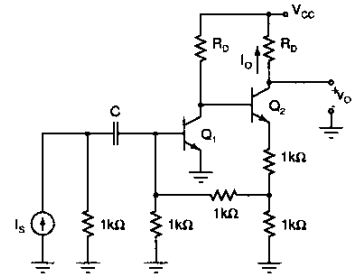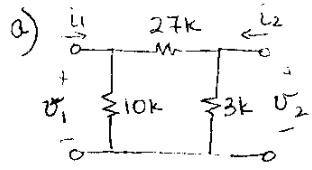- (a) Draw a diagram of the feedback network. (5 points)
- (b) Find the feedback's network β . (5 points)
- (c) Estimate an approximate value of the feedback amplifier's gain. HINT: ASSUME THAT THE NON-FEEDBACK AMPLIFIER GAIN IS VERY LARGE. (5 points)
- (d) Draw a diagram of the non-feedback amplifier, including the loading effects of the feedback network. Include numeric values for the resistors. Do not replace the transistors by their model. (10 points)



b) $\beta = g_{12} = \frac{i_1}{i_2} \Big|_{v_1=0}$

short v_1 , then

$$i_1 = -i_2 \frac{3k}{10k + 3k} = -0.5 i_2$$

$\therefore \beta = -0.5$ (the minus sign makes the feedback negative)

c) $A_f \approx \frac{1}{\beta} = +2$

d) To draw the diagram, we must find g_{11} and g_{22}

$$g_{11} = \frac{i_1}{v_1} \Big|_{i_2=0} = \frac{1}{10k} + \frac{1}{27k} = 0.138 \text{ mS}$$

$$g_{22} = \frac{v_2}{i_2} \Big|_{v_1=0} = 3k \parallel 27k = 2.7k \approx 2.7k \parallel 500\Omega$$

