

# STABILITY

INEL 4202 - Fall 2012 - M.Toledo  
ECE Dept. UPRM

# Stability

## Basics

- Basic feedback equation:

$$A_f(s) = \frac{a(s)}{1 + \beta(s)a(s)}$$

Thus, feedback moves the poles of the amplifier's transfer function.

- Poles of  $A_f$  are roots of  $1 + \beta a$ . Thus, feedback moves the poles of the amplifier's transfer function.
- The idea is to determine information about the stability of  $A_f$  from the loop gain  $T(s) = \beta(s)a(s)$ .

## Nyquist Theorem

Let  $\omega_{180^\circ}$  be the frequency at which the loop gain's phase angle is  $-180^\circ$ . If

$$|T(j\omega_{180^\circ})| = |\beta(j\omega_{180^\circ})A(j\omega_{180^\circ})| > 1$$

then the amplifier is unstable. Otherwise, it is stable.

Nyquist theorem allows us to answer questions about the stability of  $A_f$  by analyzing the loop gain  $\beta A$ .

## Phase and Gain Margin

- Gain margin: decibels below zero of  $|T(j\omega_{180^\circ})|$ .
- Phase margin: degrees above  $-180^\circ$  at the frequency  $\omega_{0dB}$  at which  $|T(j\omega_{0dB})| = 1$ , or 0 db.

$$\phi_m = 180 + \angle T(j\omega_{0dB})$$

Note that  $\angle T(j\omega_{0dB})$  is usually negative.

- The amplifier is unstable if the gain and phase margins are negative. If the margins are positive or zero the amplifier is *stable* or *marginally stable*, respectively.



$$A_{dB} = 20 \log A$$

$$\frac{A_0}{1 + j \frac{f}{f_p}}$$

$f/f_p$	$\phi$
0.1	$5.7^\circ$
1	$45^\circ$
10	$84.3^\circ$

1 decada =  $10 \cdot \text{frec.}$

1 octava =  $2 \cdot \text{frec}$

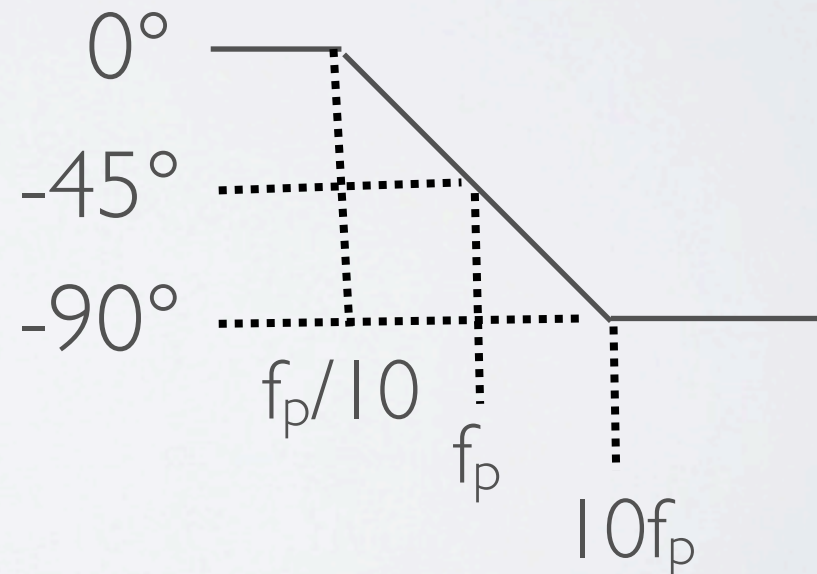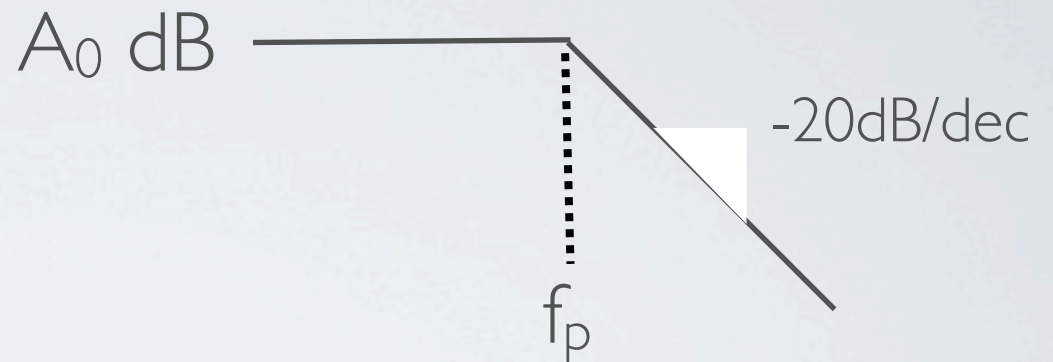

An amplifier with dc gain equal to  $1000\text{V/V}$  will be used in a feedback configuration. The amplifier transfer function displays single poles at  $1\text{kHz}$  and  $10\text{kHz}$ . Find the phase margin  $\Phi_m$  if the circuit will use a feedback network with  $\beta = 1/2$ .

A (dB)



6dB

70kHz

1 kHz

10 kHz

100 kHz

1 MHz

## Geometrical analysis

- Crossover at  $\sim 70\text{kHz}$
- phase =  $-\arctan(70) - \arctan(7) = -171$  degrees
- Phase margin = 9 degrees

Exact solution: express  $f$  in kHz and

solve	$\frac{1000 \times 0.5}{\sqrt{1 + f^2} \sqrt{1 + \left(\frac{f}{10}\right)^2}} = 1$
-------	---


to get  $f = 70.35\text{kHz}$ . Then proceed as in geometrical analysis.

12.65 A 3-pole amplifier has a loop gain given by

$$T(f) = \frac{10^5 \times \beta}{\left(1 + j \frac{f}{5 \times 10^2}\right) \left(1 + j \frac{f}{10^4}\right)^2}$$

(a) determine the frequency  $f_{180}$  at which the phase is -180 degrees. (b) At  $f_{180}$  determine the value of  $\beta$  such that  $|T(f_{180})| = 1$ .

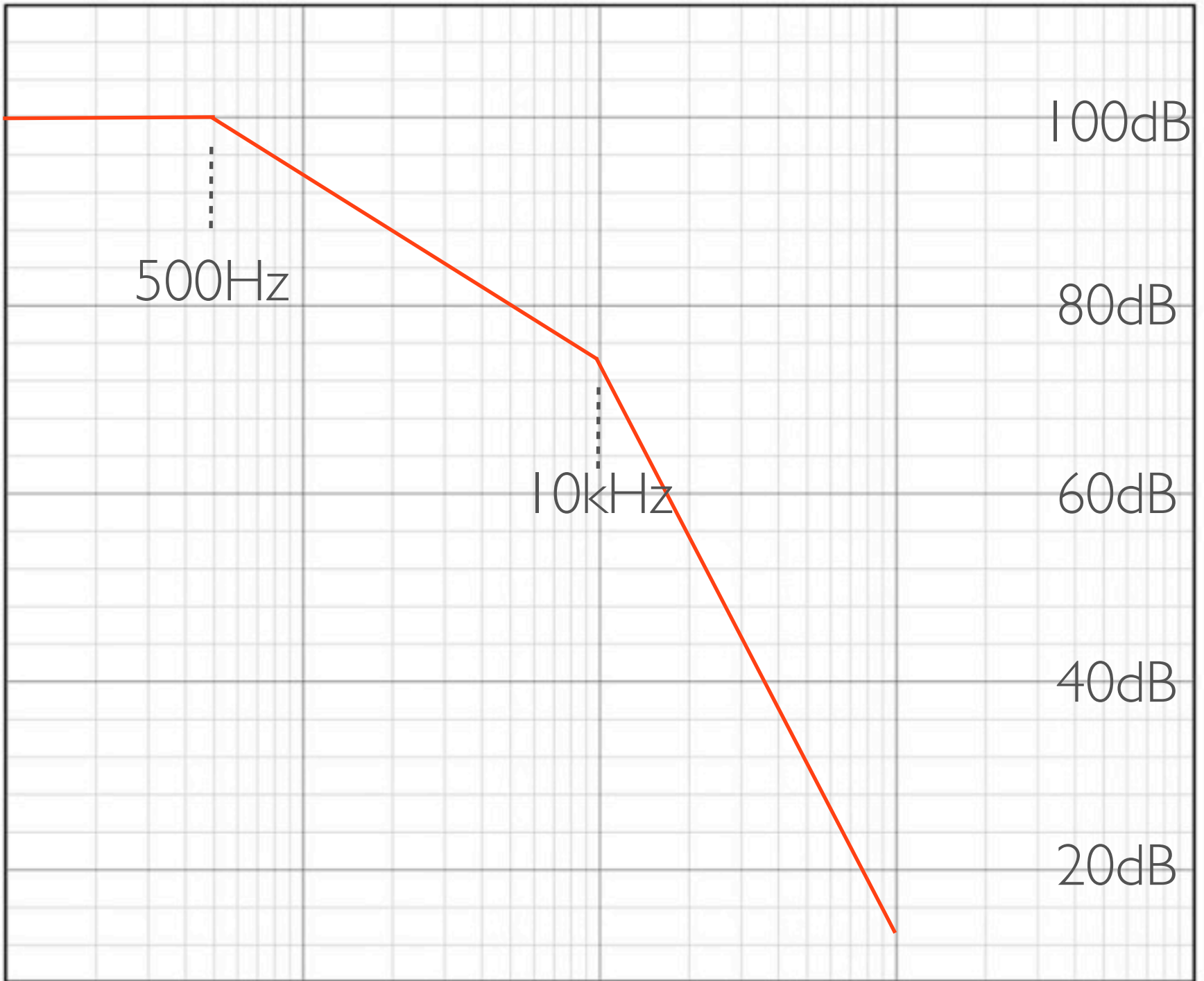Extra: c) find the the value of  $\beta$  such that the phase margin is 45 degrees; (d) repeat for a phase margin of 60 degrees; (e) sketch the magnitude and phase bode plots of the amplifier's gain.



- Geometrical reasoning:

- phase of A is about -180 degrees at the frequency of the double pole (-90 degrees from first pole plus 2 times -45 degrees from double pole), i.e. 10kHz

- at 10kHz, gain magnitude shown in approximate bode plot is about 74dB, but we know that the real magnitude is about 6dB less (3 from each pole) so use 68dB = 2512V/V and beta = 1/2512 V/V

- Exact approach: express angle as pi radians and

solve	$-\tan^{-1}\left(\frac{f}{0.5}\right) - 2 \tan^{-1}\left(\frac{f}{10}\right) = -\pi$
-------	--

to get  $f = 10488.1$  Hz. Then find gain at this frequency:

$$A = \frac{1}{\beta} = \frac{100\,000}{\left(1 + \left(\frac{10\,488.1}{10\,000}\right)^2\right) \sqrt{1 + \left(\frac{10\,488.1}{500}\right)^2}} = 2268 \text{ V/V}$$

Notice that the value of  $f$  was estimated numerically.

Example 1: An op amp with  $a_0 = 10^3$  V/V and two pole frequencies at  $f_1 = 100\text{kHz}$  and  $f_2 = 2\text{MHz}$  is connected as a unity-gain voltage follower. Find  $\phi_m$ .

ANSWER:

solve	$\frac{1000}{\sqrt{1 + \left(\frac{f}{100}\right)^2} \sqrt{1 + \left(\frac{f}{2000}\right)^2}} = 1$
-------	---

to get  $f = 14.07\text{MHz}$  and  $\text{pm} = 180 - \arctan(14.07/0.1) - \arctan(14.07/2) = 8.5$  degrees.

Example 2: An amplifier has 3 identical poles at a frequency  $f_1$  and is placed in a negative-feedback loop with a frequency independent feedback factor  $\beta$ . Find an expression for  $f_{-180^\circ}$  as well as the corresponding value of T.

ANSWER: Phase given by each identical pole is  $180/3 = 60$  so  $f_{-180} = f_p * \tan(60) = 1.732f_p$ . The magnitude of T is  $(A_0*\beta)/(1 + 1.732^2)^{3/2} = (A_0*\beta)/8$

Example 3: (a) Verify that the circuit with loop gain  $T_0 = 10^2$  and three pole frequencies  $f_1 = 100\text{kHz}$ ,  $f_2 = 1\text{MHz}$  and  $f_3 = 2\text{MHz}$  is unstable. (b) Reduce  $T_0$  so that  $\phi_m=45^\circ$ . (c) repeat for  $\phi_m=60^\circ$ .

solve	$\frac{100}{\sqrt{1 + \left(\frac{f}{0.1}\right)^2} \sqrt{1 + f^2} \sqrt{1 + \left(\frac{f}{2}\right)^2}} = 1$
-------	--

To get  $f = 2.42\text{MHz}$ , and

$$\begin{aligned} \phi &= -\arctan(2.42/0.1) - \arctan(2.42/1) - \arctan(2.42/2) \\ &= -87.6^\circ - 67.6^\circ - 50.4^\circ = -206^\circ \end{aligned}$$

For a margin = 45 degrees, phase should be -135 degrees, which happens at the freq.  $f$  obtain from

solve	$\tan^{-1}\left(\frac{f}{0.1}\right) + \tan^{-1}(f) + \tan^{-1}\left(\frac{f}{2}\right) = \pi \times \frac{135}{180}$
-------	---


or  $f = 645\text{kHz}$ . The magnitude at this frequency is


$$|T| = \frac{100}{\sqrt{1 + (6.45)^2} \sqrt{1 + (0.645)^2} \sqrt{1 + (0.645/2)^2}} = 12.25$$

so the gain must be reduced by a factor of 12.25 to have a phase margin of 45 degrees.

For a phase margin of 60 degrees, repeat the procedure but use 120 degrees to find  $f$ .

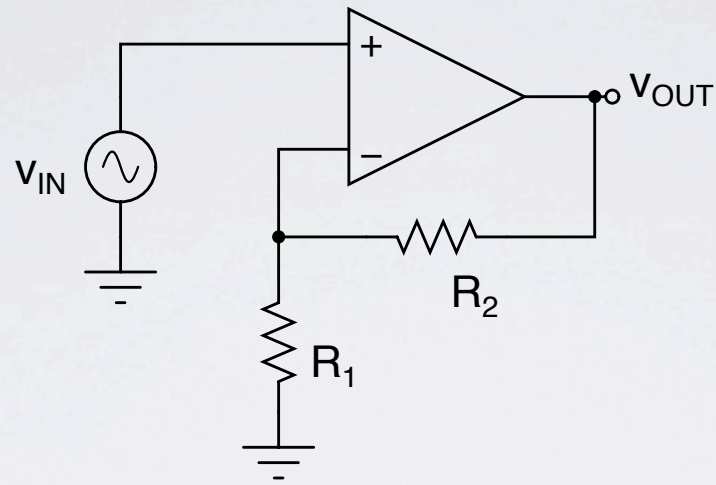III. (33 pts.) In the following amplifier, the opamp has an open-loop d.c. gain of  $10^4$  and 4 poles at 1MHz, 10MHz, 10MHz and 200MHz. Find the smallest ratio  $R_2/R_1$  for which the amplifier is stable.



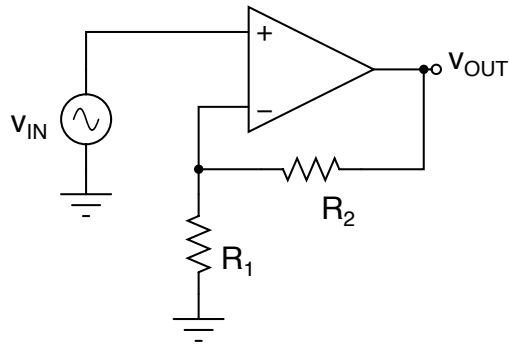

At 10MHz the phase is:

-90 deg from pole at 1MHz

-45 deg from each pole at 10MHz

-0 from pole at 200MHz

So phase at 10MHz = -180 deg. and  $1/\beta$  must be equal or larger to the gain at 10MHz for the amplifier to be stable

$$|A(10MHz)| = \frac{10^4}{\sqrt{1 + \left(\frac{10}{1}\right)^2} \times \left(1 + \left(\frac{10}{10}\right)^2\right) \times \sqrt{1 + \left(\frac{10}{200}\right)^2}}$$

$$= \frac{10^4}{\sqrt{101} \times 2 \times 1} = 498V/V$$

$$\boxed{\frac{R_2}{R_1} \geq 497V/V}$$

An amplifier has a low-frequency gain of 200 and its transfer function has three poles at  $1\text{ MHz}$ ,  $2\text{ MHz}$  and  $4\text{ MHz}$ .

(a) Sketch the bode plot.

(b) The amplifier is placed in a negative feedback loop with a feedback network with a frequency independent factor  $\beta = 0.025$ . Is the amplifier stable? Use your estimate of the phase or gain margin to justify your answer.

The response of an op amp can be approximated with a dominant pole frequency  $f_1$  and a high-frequency pole  $f_2$  to account for higher order roots. (a) Assuming  $a_0 = 10^5$  V/V,  $f_1 = 10$ Hz, and  $\beta = 1$  V/V, find the phase margin  $\phi_m$  if  $f_2 = 1$ MHz. (b) Find  $f_2$  for  $\phi_m = 45^\circ$  and for  $\phi_m = 60^\circ$ .