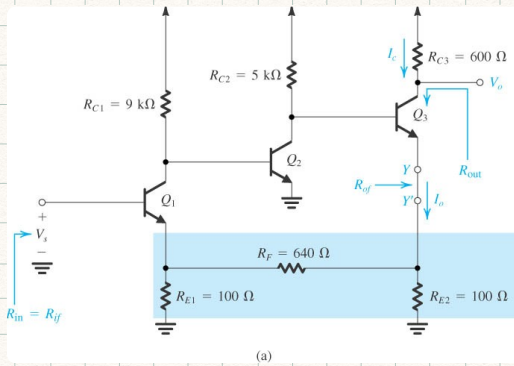


### Feedback example




$$\begin{aligned}
 gm1 &= 0.6\text{mA}/0.025\text{V} = 24\text{mA/V} \\
 gm2 &= 1\text{mA}/0.025\text{V} = 40\text{mA/V} \\
 gm3 &= 4\text{mA}/0.025\text{V} = 160\text{mA/V} \\
 r\pi1 &= 100/24\text{mA/V} = 4.1\text{k}\Omega \\
 r\pi2 &= 100/40\text{mA/V} = 2.5\text{k}\Omega \\
 r\pi3 &= 100/160\text{mA/V} = 625\Omega
 \end{aligned}$$

$$I_{C1} = 0.6\text{mA}, I_{C2} = 1\text{mA}, I_{C3} = 4\text{mA}, h_{fe} = 100, r_O = \infty$$

Type of feedback: current-sampling, voltage-mixing (series-series)

Feedback network:

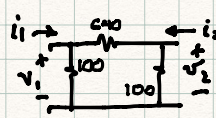


$$R_{11} = \left. \frac{v_1}{i_1} \right|_{i_2=0} = 100 \parallel 740 = 88\Omega$$

$$R_{22} = \left. \frac{v_2}{i_2} \right|_{i_1=0} = 88\Omega$$

$$\beta = \left. \frac{v_2}{i_2} \right|_{i_1=0} = (100 \parallel 740) \frac{100}{740} = 11.9\Omega$$

Non-feedback amplifier:

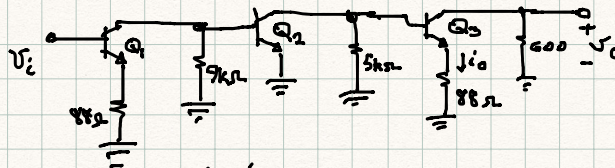

$$\text{non-feedback gain} = \text{transconductance} = i_o/v_i = G$$

$$G = \left( \frac{v_{c1}}{v_i} \right) \left( \frac{v_{c2}}{v_{c1}} \right) \left( \frac{v_o}{v_{c2}} \right) \left( \frac{i_o}{v_o} \right)$$

$$G = \frac{+g_{m1} R_{e1}}{1 + g_{m1} R_{e1}} \times \left( +g_{m2} R_{c2} \right) \frac{+g_{m3} R_{e3}}{1 + g_{m3} R_{e3}} \left( \frac{+1}{600} \right)$$

$R_{e1} = 88$        $R_{c2} = 88$        $R_{e3} = 88$

$$= \frac{(24\text{mA/V})(9\text{k}\Omega / 4.1\text{k}\Omega)}{1 + (24\text{mA/V})(88\Omega)} \left( 40\frac{\text{mA}}{\text{V}} \sqrt{3227} \right) \frac{160\text{mA/V}}{1 + (160\text{mA/V})(88\Omega)}$$

$$\approx (15.1)(131)(0.01001) \approx 21\text{A/V}$$

$$G_f = \frac{21 \text{ A/V}}{1 + (11.9)(21)} = \frac{21 \text{ A/V}}{250.76} = 83.8 \text{ mA/V} = \frac{i_o}{v_o}$$

To find the voltage gain for the feedback amplifier, observe that

$$v_o = (-600 \Omega)(i_o) \Rightarrow \frac{v_o}{v_i} = (-600 \Omega) G_f = -600 \Omega (83.8 \frac{\text{mA}}{\text{V}}) = 50 \text{ V/V}$$

Input resistance:

$$R_i = r_{\pi} + (101)88 \Omega = 13 \text{ k}\Omega \Rightarrow R_{i,f} = (250.76)(13 \text{ k}\Omega) = 3.26 \text{ M}\Omega$$

Output resistance:

$$R_o = \frac{625 + 5 \text{ k}}{101} + 88 \Omega = 144 \Omega \Rightarrow R_{o,f} = 144 \Omega \times 250.76 = 36 \text{ k}\Omega$$

$R_o$  is the resistance seen by the ideal load, a short between points Y and Y' in the original diagram.


An estimate of  $R_{out}$  can be obtained interpreting  $R_{o,f}$  as a resistance in the emitter and using the formula

$$R_{out} \approx r_o (1 + g_m R_e) = 25 \text{ k}\Omega (1 + [160 \frac{\text{mA}}{\text{V}}](36 \text{ k}\Omega)) = 144 \text{ M}\Omega$$

Note: The book uses a different formula

$$R_{out} \approx r_o (1 + g_m \{R_{o,f} \parallel r_{\pi}\}) = 25 \text{ k}\Omega (1 + [160 \frac{\text{mA}}{\text{V}}] \{625 \parallel 36 \text{ k}\}) = 2.4 \text{ M}\Omega$$

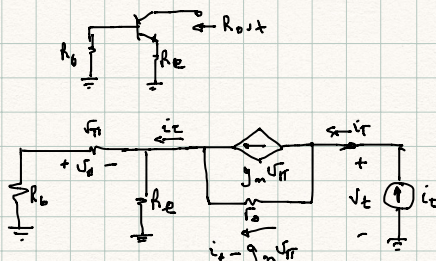The above formula for  $R_{out} = r_o(1 + g_m(R_e))$  is approximate. To obtain a more accurate estimate, consider the following analysis.



$$v_t = i_t (R_e \parallel (r_{\pi} + R_b)) + r_o (i_t - g_m v_{\pi})$$

$$v_{\pi} = - \frac{r_{\pi}}{r_{\pi} + R_b} i_t (R_e \parallel (r_{\pi} + R_b))$$

$$\text{Let } R_A = R_e \parallel (r_{\pi} + R_b)$$

$$v_t = i_t R_A + i_t r_o + i_t r_o \frac{\beta R_A}{r_{\pi} + R_b}$$

$$R_{out} = \frac{v_t}{i_t} = R_A + r_o \left(1 + \frac{\beta R_A}{r_{\pi} + R_b}\right)$$

$$\frac{\beta R_A}{r_{\pi} + R_b} = \frac{R_e (\cancel{r_{\pi} + R_b})}{R_e + r_{\pi} + R_b} \frac{1}{\cancel{r_{\pi} + R_b}}$$

$$\therefore R_{out} = R_A + r_o \left( 1 + \frac{\beta R_e}{R_e + r_{\pi} + R_b} \right) \quad (\text{eq. 1})$$

If  $r_{\pi} \gg R_e + R_b$ , and  $r_o \gg R_A$

$$R_{out} \approx r_o (1 + g_m R_e)$$

If this approximation does not hold, use the above eq. 1

Back to the feedback problem.

$$R_A = R_e \parallel (r_{\pi} + R_b) = 36k\Omega \parallel 5625\Omega = 4865\Omega$$

$$R_{out} = 4865\Omega + 25k\Omega \left( 1 + \frac{100(36k)}{36k + 625 + 5k} \right)$$

$$= 4865\Omega + 25k\Omega (86.5) \approx 2.1\text{M}\Omega$$

in good agreement with the book's estimate.