
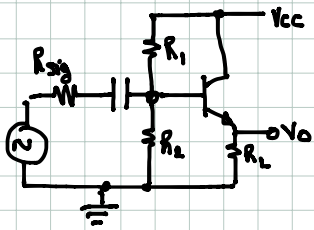


CC
SCHEMATIC

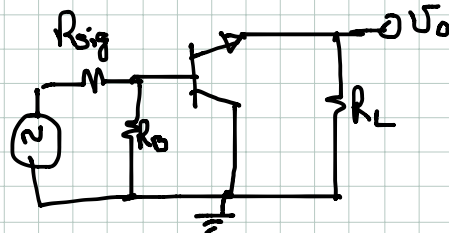




[Shows dc and ac connections

AC equivalent




$$R_B = R_1 // R_2$$

Now substitute high-frequency model

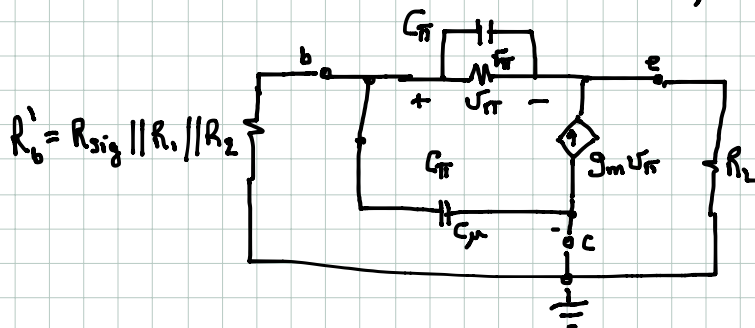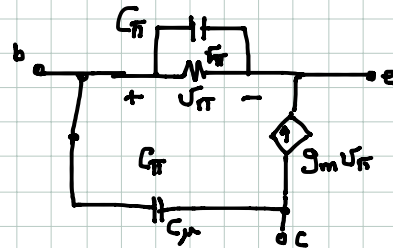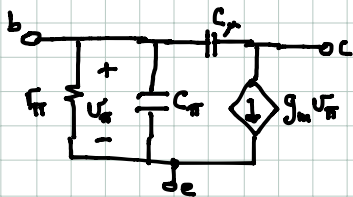


Now use open-circuit t.c. method

R_{μ} Resistance seen by C_{μ}

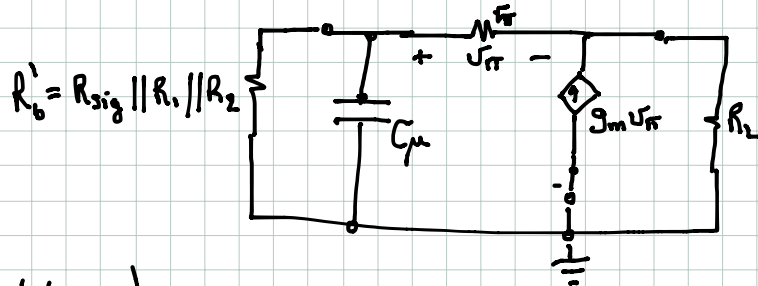

$$R_b' \parallel R_{eq}'$$

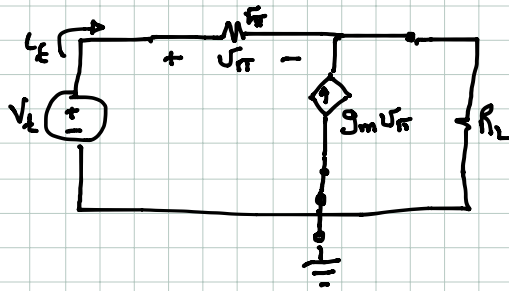

$$v_{\pi} = i_t r_{\pi}$$

$$v_t = v_{\pi} + (i_t + g_m v_{\pi}) R_L$$

$$R_{eq}' = \frac{v_t}{i_t} = r_{\pi} + (1 + g_m r_{\pi}) R_L$$

$$R_{\mu} = \left[r_{\pi} + (1 + g_m r_{\pi}) R_L \right] \parallel R_{sig} \parallel R_1 \parallel R_2$$


$$f_{p1} = \frac{1}{2\pi C_{\mu} \left[\left(r_{\pi} + (1 + g_m r_{\pi}) R_L \right) \parallel R_{sig} \parallel R_1 \parallel R_2 \right]}$$

R resistance seen by C

π

π
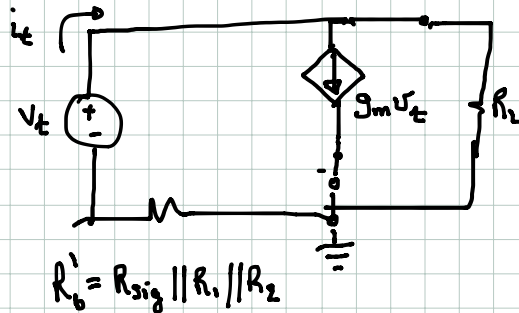
$$U_t = -U_\pi$$
$$R_\pi = r_\pi \parallel R_{eq}$$
$$R_{eq} = U_t / i_t$$



$$U_t = i_t R_b' + (i_t - g_m U_t) R_L$$

$$U_t (1 + g_m R_L) = i_t (R_b' + R_L)$$

$$R_{eq} = \frac{R_b' + R_L}{1 + g_m R_L}$$

$$f_{p2} = \frac{1}{2\pi C_\pi \left(r_\pi \parallel \frac{R_b' + R_L}{1 + g_m R_L} \right)}$$