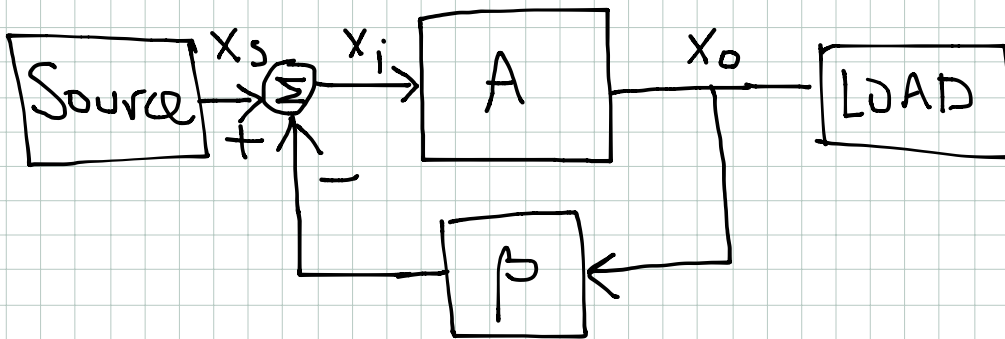


Basic feedback analysis



$$x_o = A x_i = A (x_s - \beta x_o)$$

$$A_f = \frac{x_o}{x_s} = \frac{A}{1 + \beta A}$$


A is non-feedback amplifier gain

A_f is feedback amplifier gain


To apply the above equation, the A and β blocks should be ideal.

Feedback analysis of simple non-inverting opamp circuit

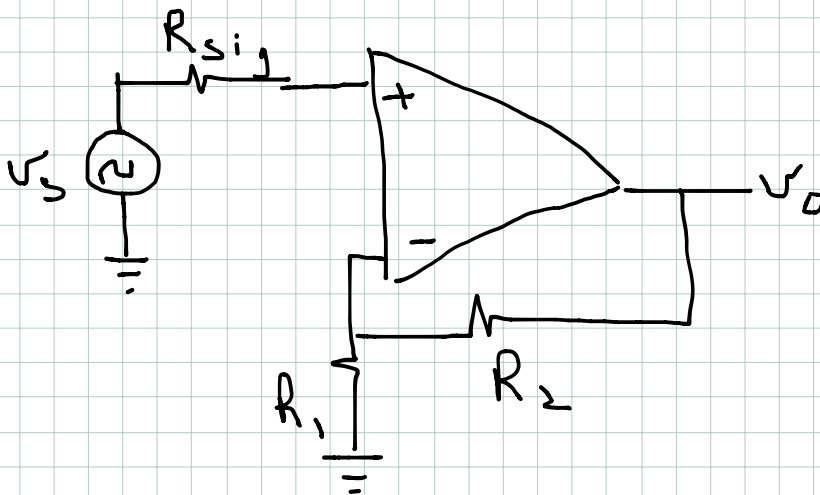Assume opamp with finite gain a but otherwise ideal



feedback network

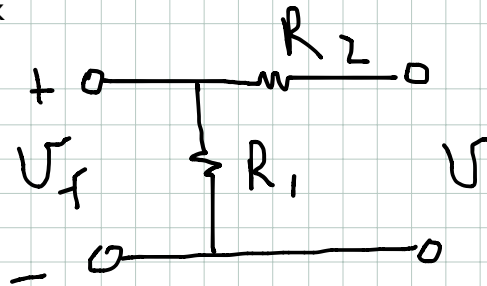

$$\beta = \frac{U_F}{U_0} = \frac{R_1}{R_1 + R_2}$$

A \rightarrow op amp gain a

$$A_f = \frac{a}{1 + \frac{a R_1}{R_1 + R_2}}$$

Example: $R_2 = 100 \cdot R_1$, $a = 10000$

$$A_f = 10000 / (1 + 10000/101) = 99.99 \text{ V/V}$$

Finite opamp gain produces a 1% error on voltage gain.

Example: For above R_1 and R_2 , find value of a required to have 0.1% error

$A_{\text{ideal}} = 1 + R_2/R_1 = 101$; $A_f = 101 \cdot 0.999 = 100.899 \text{ V/V}$ (for 0.1% error)


$$A_f = 100.899 \Rightarrow 100.899(1 + a/101) = a$$

$$100.899 + 100.899 \cdot a/101 = a$$

$$100.899 = a(1 - 100.899/101)$$

$$a = 100899 \quad \leftarrow \text{value required to have 0.1\% error in gain}$$

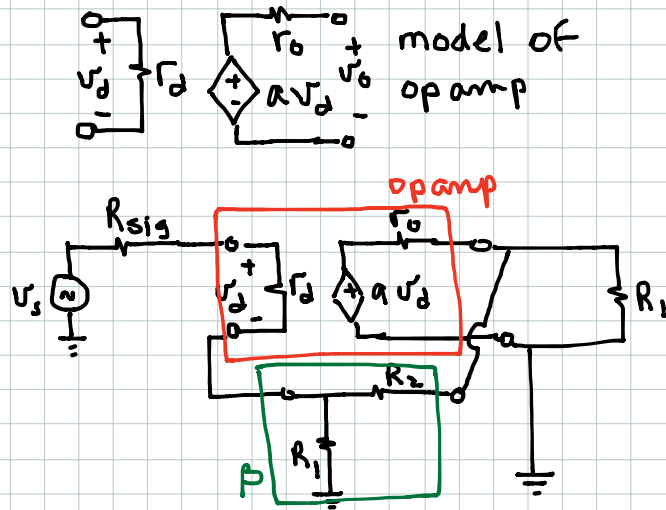Non-inverting amplifier with finite a , r_d and r_o



Feedback method: Integrate

- 1) non-ideal features of feedback network into amplifier
- 2) non-ideal characteristics of load into amplifier
- 3) non-ideal characteristics of source into amplifier
- 4) find non-feedback amplifier gain A
- 5) apply feedback gain formula



$$A_f = A / (1 + \beta A)$$

For a voltage amplifier:

- 1) ideal source is voltage source without thevenin resistor
- 2) ideal load is open circuit
- 3) feedback network resistances must be transferred to amp

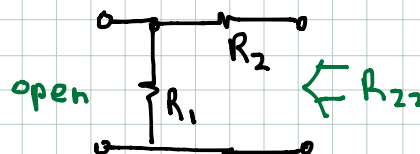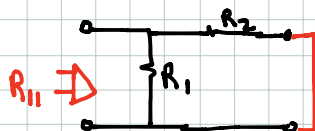
Example: Let $r_o = 100$, $r_d = 10k$, $a = 10000$, $R_{sig} = 1k$, $R_1 = 100$, $R_2 = 10000$, $R_L = 10k$

Find R_{11} and R_{22} for feedback network



$$R_{11} = R_1 \parallel R_2 = 100 \parallel 10000 = 99$$

$$R_{22} = 100 + 10,000 = 10,100$$

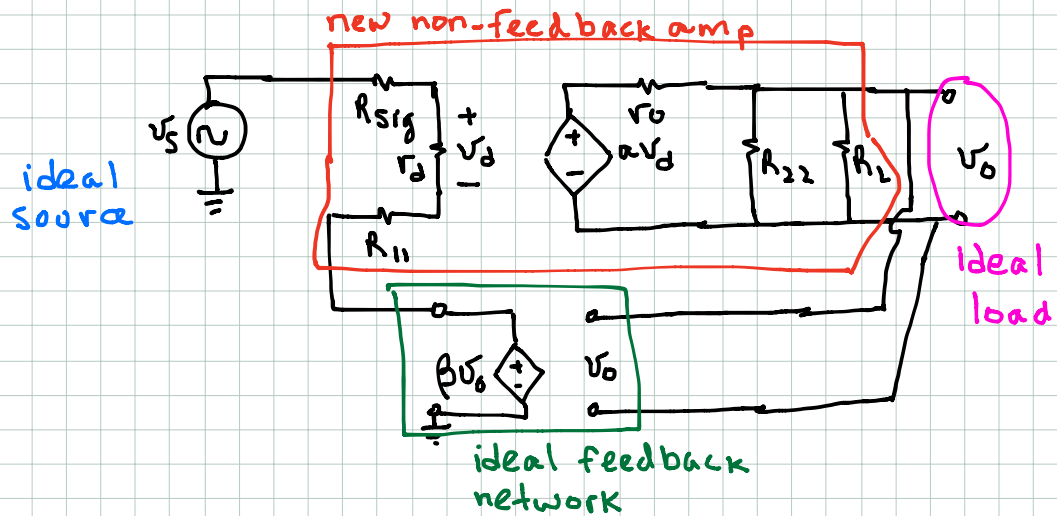

$$v_o = \frac{R_{22} \parallel R_L}{r_o + R_{22} \parallel R_L} a v_d$$

$$v_d = \frac{r_d}{r_d + R_{11} + R_{sig}} v_s$$

$$A = \frac{v_o}{v_s} = \frac{R_{22} \parallel R_L}{r_o + R_{22} \parallel R_L} a \frac{r_d}{r_d + R_{11} + R_{sig}}$$

$$R_{22} \parallel R_L = 10101 \parallel 10k \approx 5k$$

$$A = \frac{5k}{5k + 100} \cdot 10000 \cdot \frac{10k}{10k + 99 + 1k} = 8833 \frac{V}{V}$$

$$A_f = \frac{8833}{1 + 8833/101} = \boxed{99.85 \frac{V}{V}}$$

Advantage of feedback method: calculate feedback amplifier gain (closed-loop) from analysis of non-feedback amplifier (open-loop).

Direct calculation (analyzing circuit without applying the feedback method) is practical for only the simplest cases.