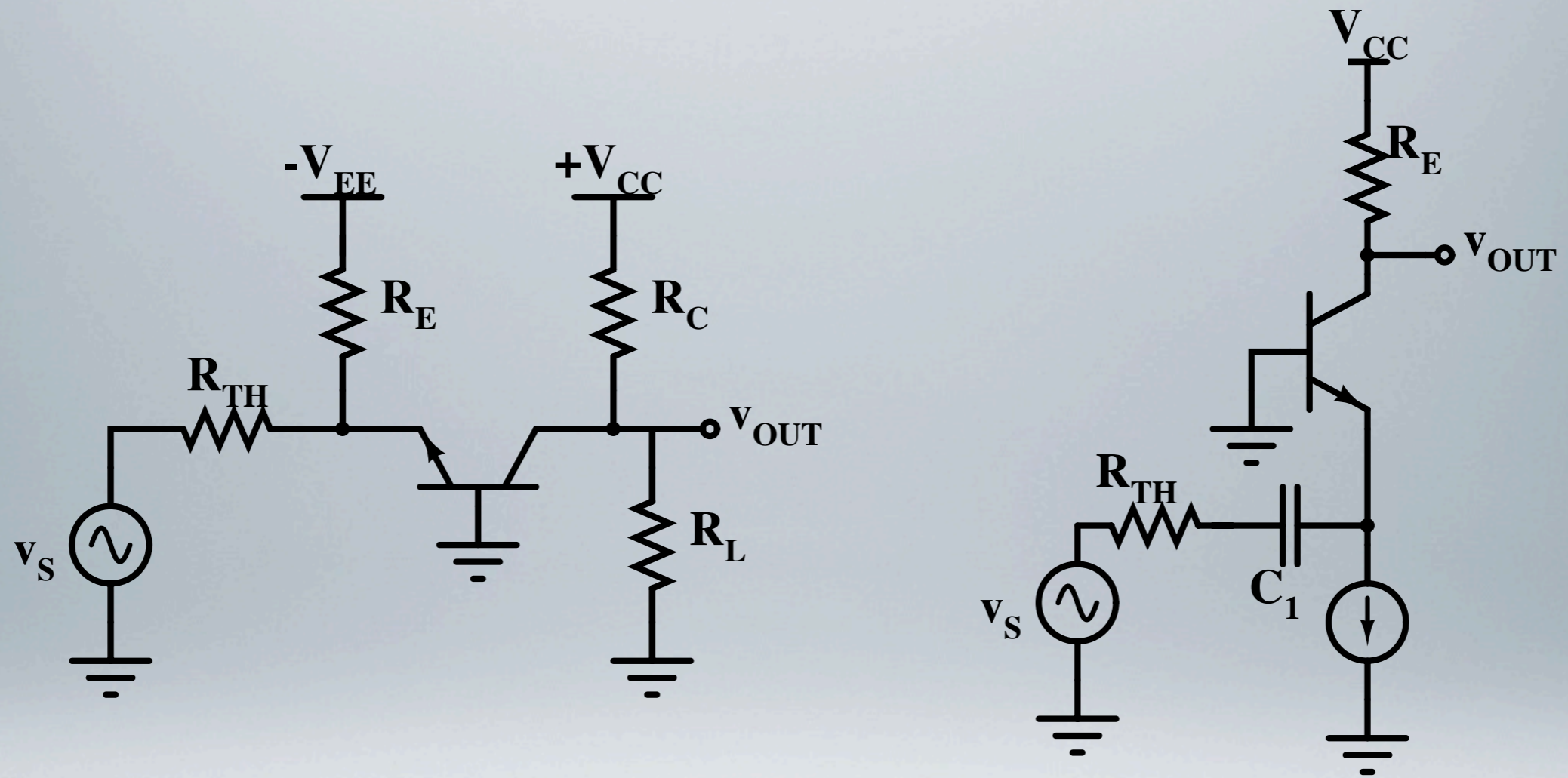



# CB/CG AMPLIFIERS

INEL 4202 - Fall 2012




Two biasing configurations

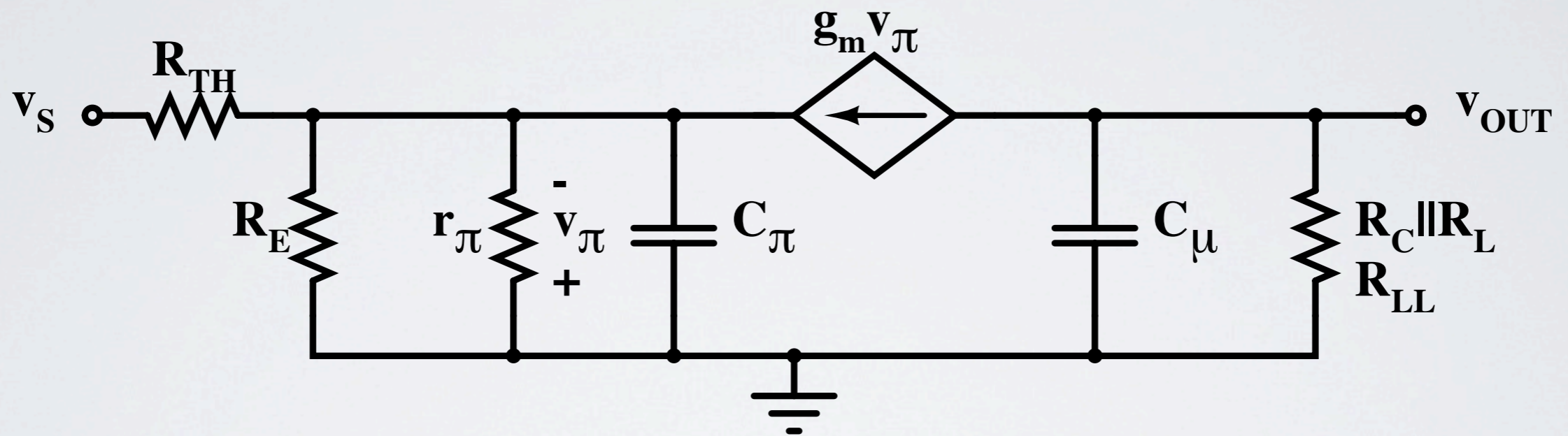High frequency equivalent circuit, left configura-  
tion:



No Miller effect!

# Dependent source transformation

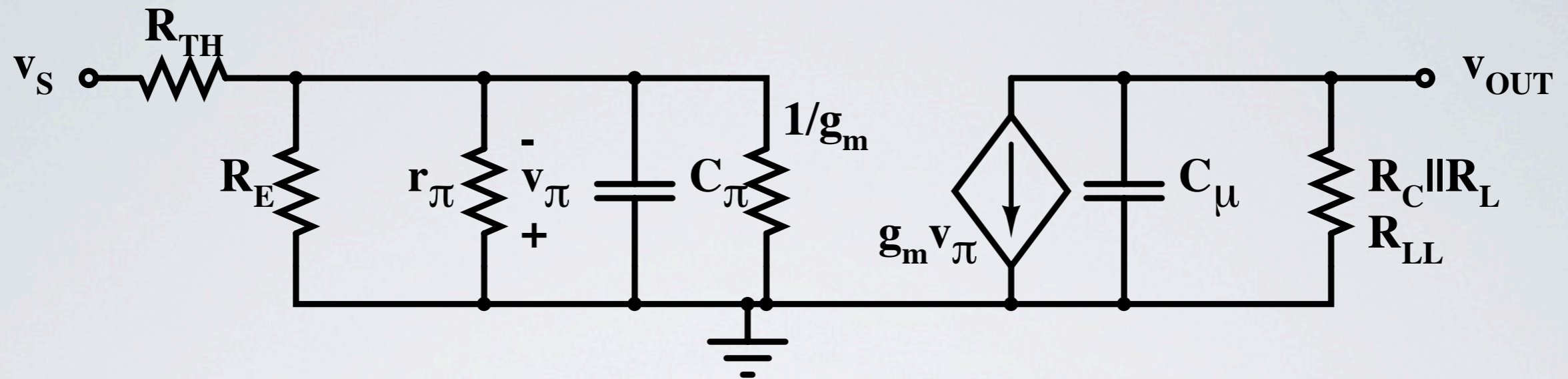

Poles at:

$$\omega_{H1} = \frac{1}{C_{\pi} R_{\pi}}$$

$$R_{\pi} = R_{TH} \parallel R_E \parallel r_{\pi} \parallel 1/g_m \approx 1/g_m$$


$$\omega_{H2} = \frac{1}{C_{\mu} R_{LL}}$$

6.86 A CG amplifier is specified to have

$$C_{gs} = 2\text{pF}, C_{gd} = 0.1\text{pF}, C_L = 2\text{pF}, \\ g_m = 5\text{mA/V}, R_{sig} = 1\text{ k}\Omega, \text{ and } R_L' = 20\text{ k}\Omega$$


Neglecting the effects of  $r_o$ , find the low-frequency gain  $v_o/v_{sig}$ , the frequencies of the poles  $f_{P1}$  and  $f_{P2}$ , and hence an estimate of the 3-dB frequency  $f_H$ .

# CE-CB cascode circuit


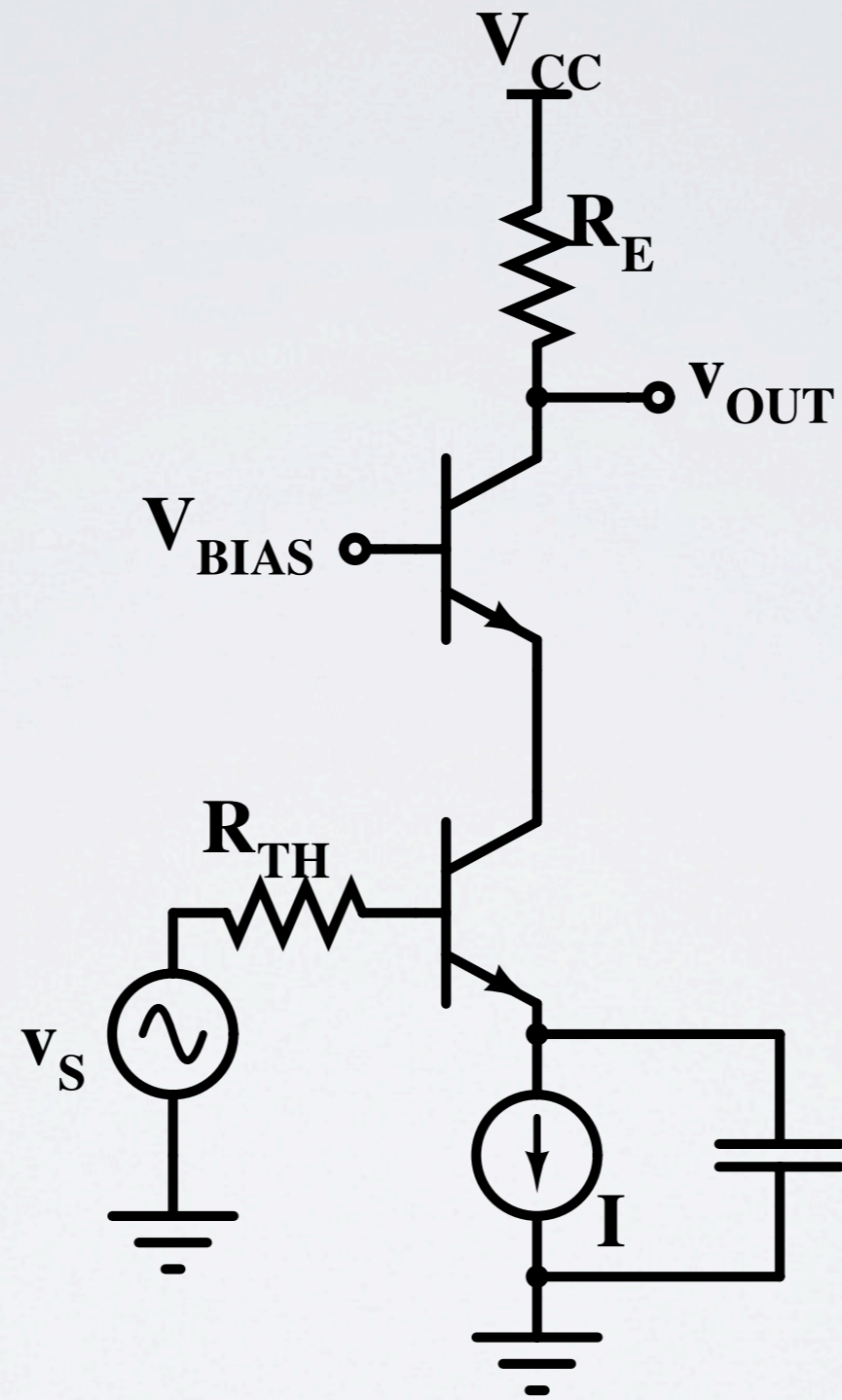



Find the dc gain and the 3-dB frequency of a MOS cascode amplifier operated at  $g_m = 1 \text{ mA/V}$  and  $r_o = 50 \text{ k}\Omega$ . The MOSFETs have  $C_{gs} = 30 \text{ fF}$ ,  $C_{gd} = 10 \text{ fF}$ , and  $C_{db} = 10 \text{ fF}$ . The amplifier is fed from a signal source with  $R_{sig} = 100 \text{ k}\Omega$  and is connected to a load resistance of  $2 \text{ M}\Omega$ . There is also a load capacitance  $C_L$  of  $40 \text{ fF}$ .

# CC/CD (Emitter/Source follower)

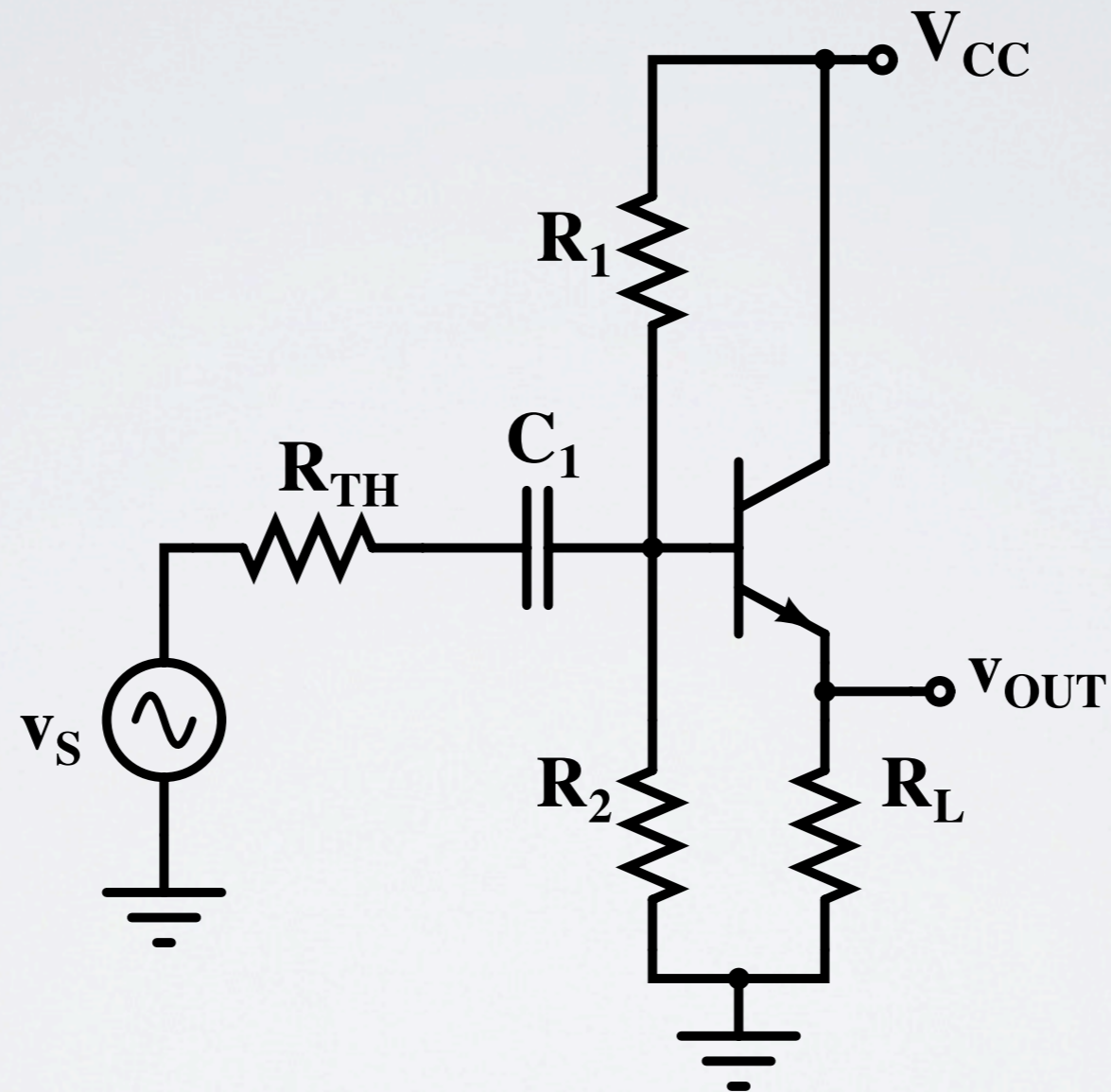

# CC/CD (Emitter/Source follower)

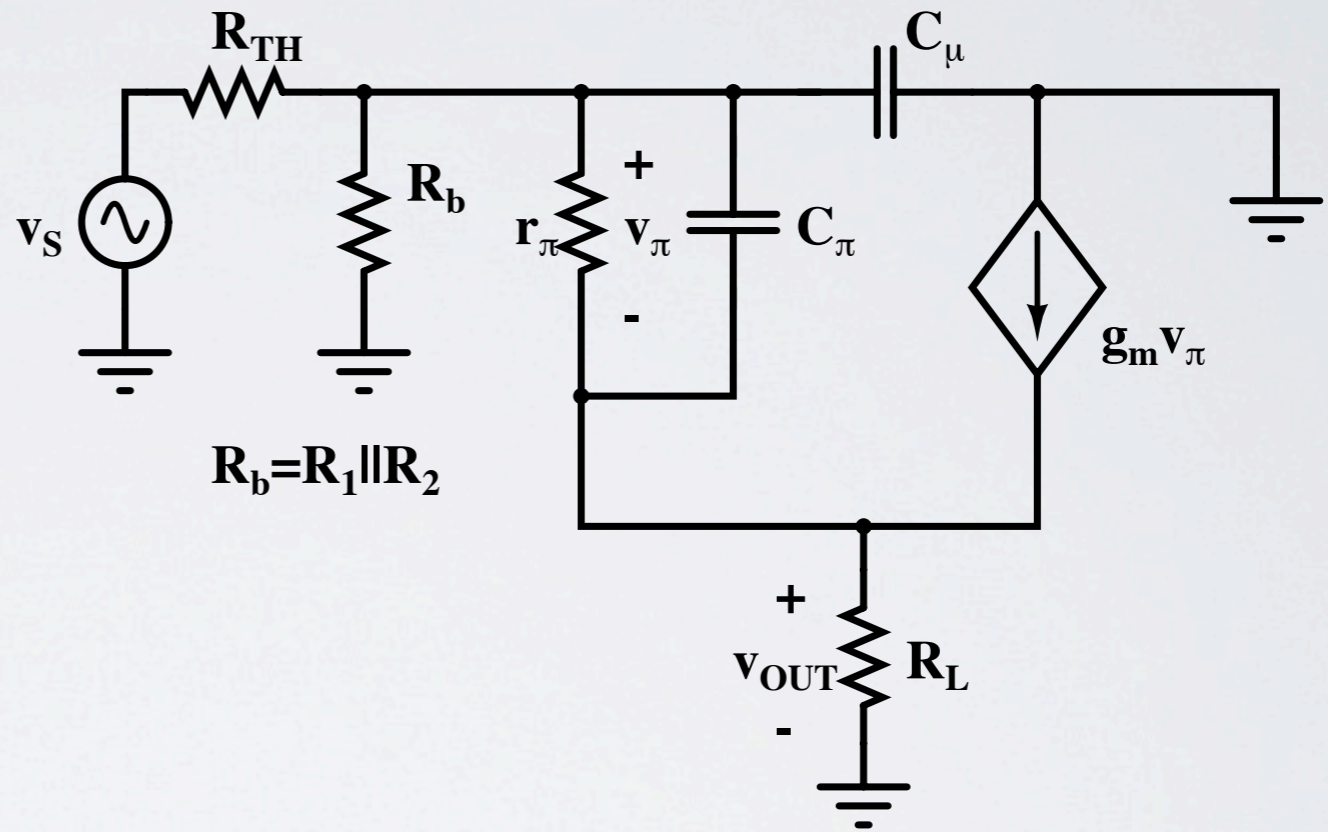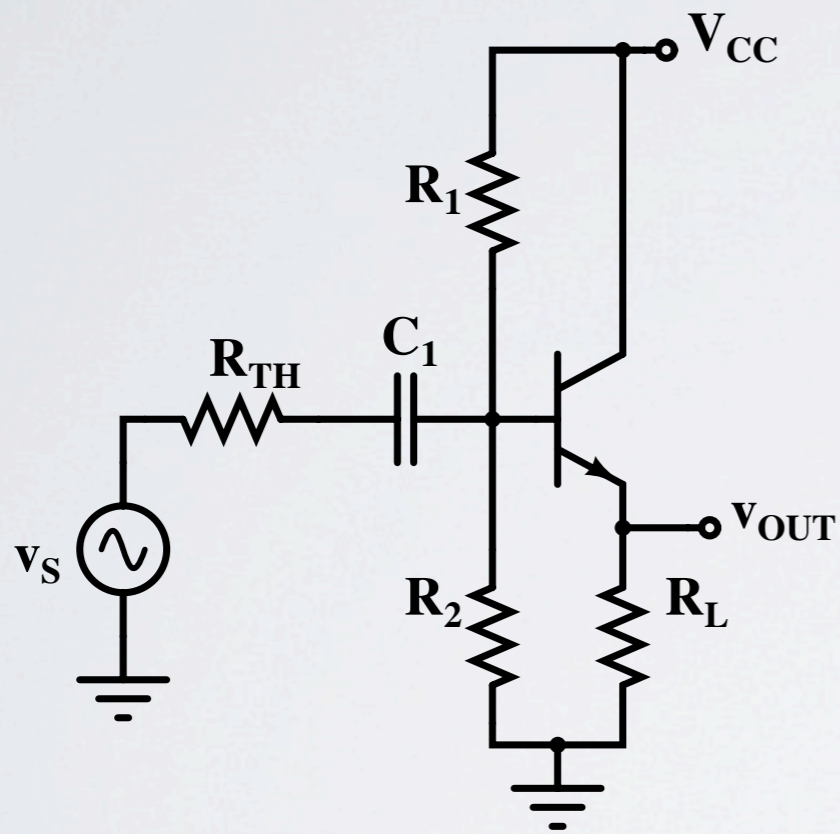


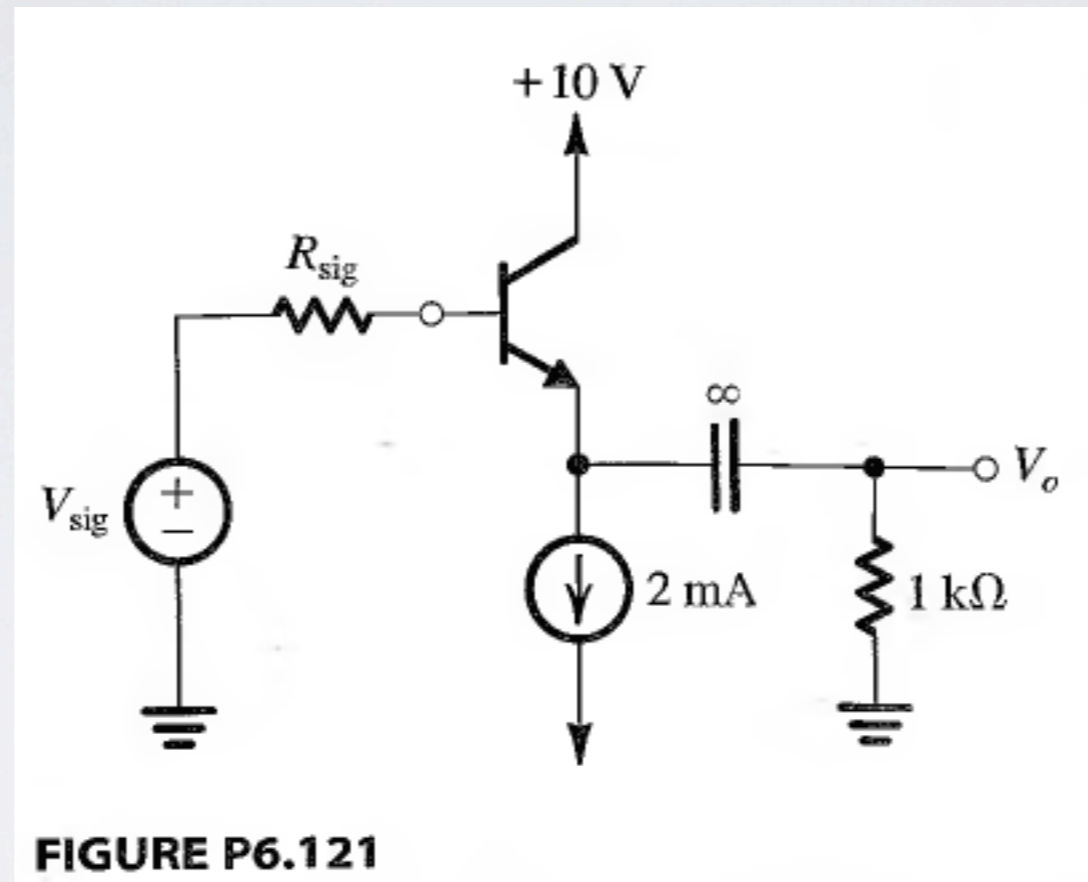

Prob. 6.121 For the emitter follower shown in Fig. P6.121, find the low-frequency gain and the 3-dB frequency  $f_H$  for the following three cases:

- (a)  $R_{sig} = 1 \text{ k}\Omega$ .
- (b)  $R_{sig} = 10 \text{ k}\Omega$ .
- (c)  $R_{sig} = 100 \text{ k}\Omega$ .

Let  $\beta = 100$ ,  $f_T = 400 \text{ MHz}$ , and  $C_\mu = 2 \text{ pF}$ .

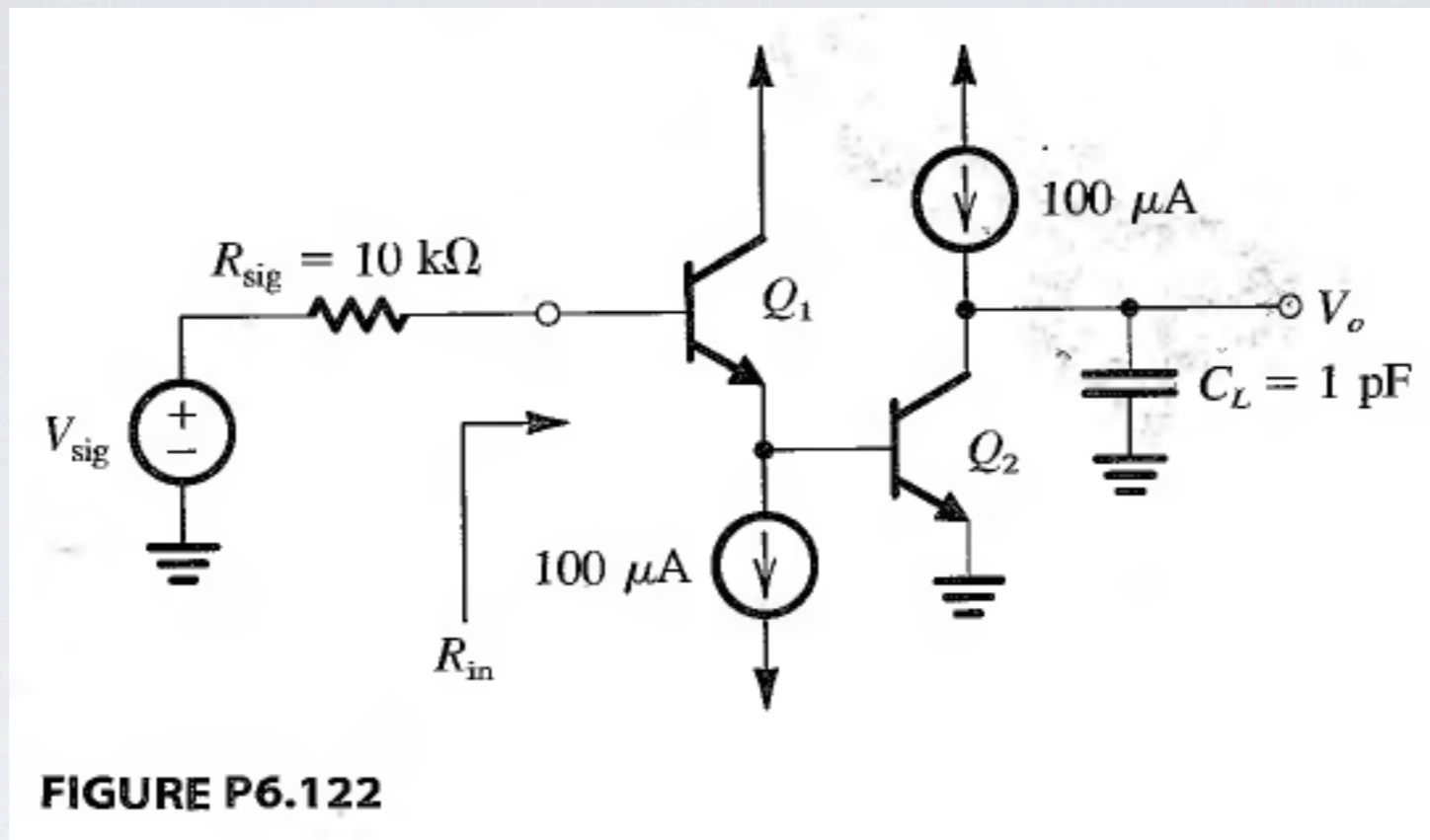

**FIGURE P6.122**

P6.122 The transistors in the circuit of Fig. P6.122 have  $\beta = 100$ ,  $V_A = 100$  V,  $C_\mu = 0.2$  pF, and  $C_{je} = 0.8$  pF. At a bias current of  $100\mu\text{A}$ ,  $f_T = 400$  MHz. (Note that the bias details are not shown.)

- Find  $R_{in}$  and the midband gain.
- Find an estimate of the upper 3-dB frequency  $f_H$ . Which capacitor dominates? Which one is the second most significant?
- What are the effects of increasing the bias currents by a factor of 10?