
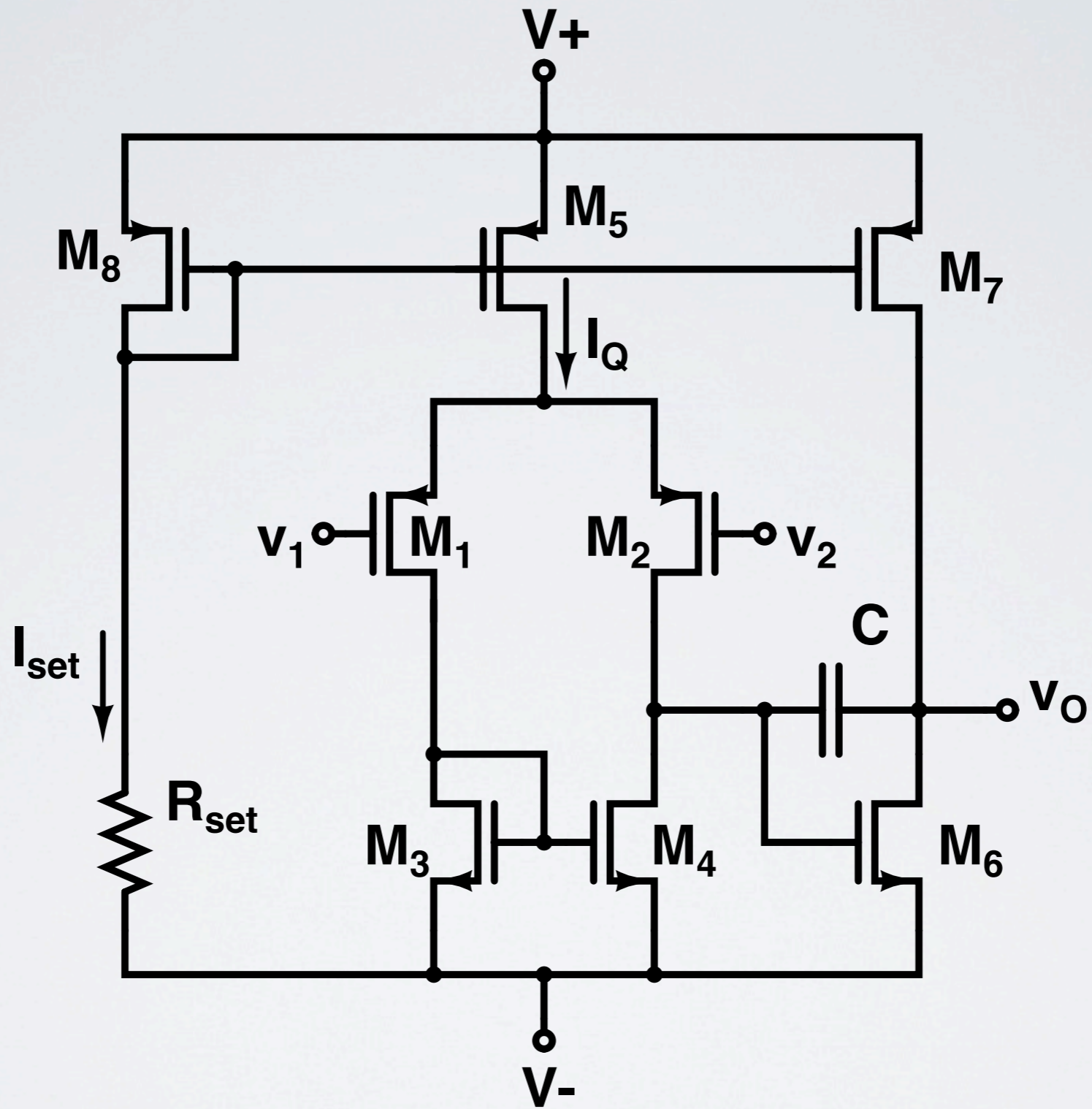


CMOS OPAMPS


INEL4202 Electronics II

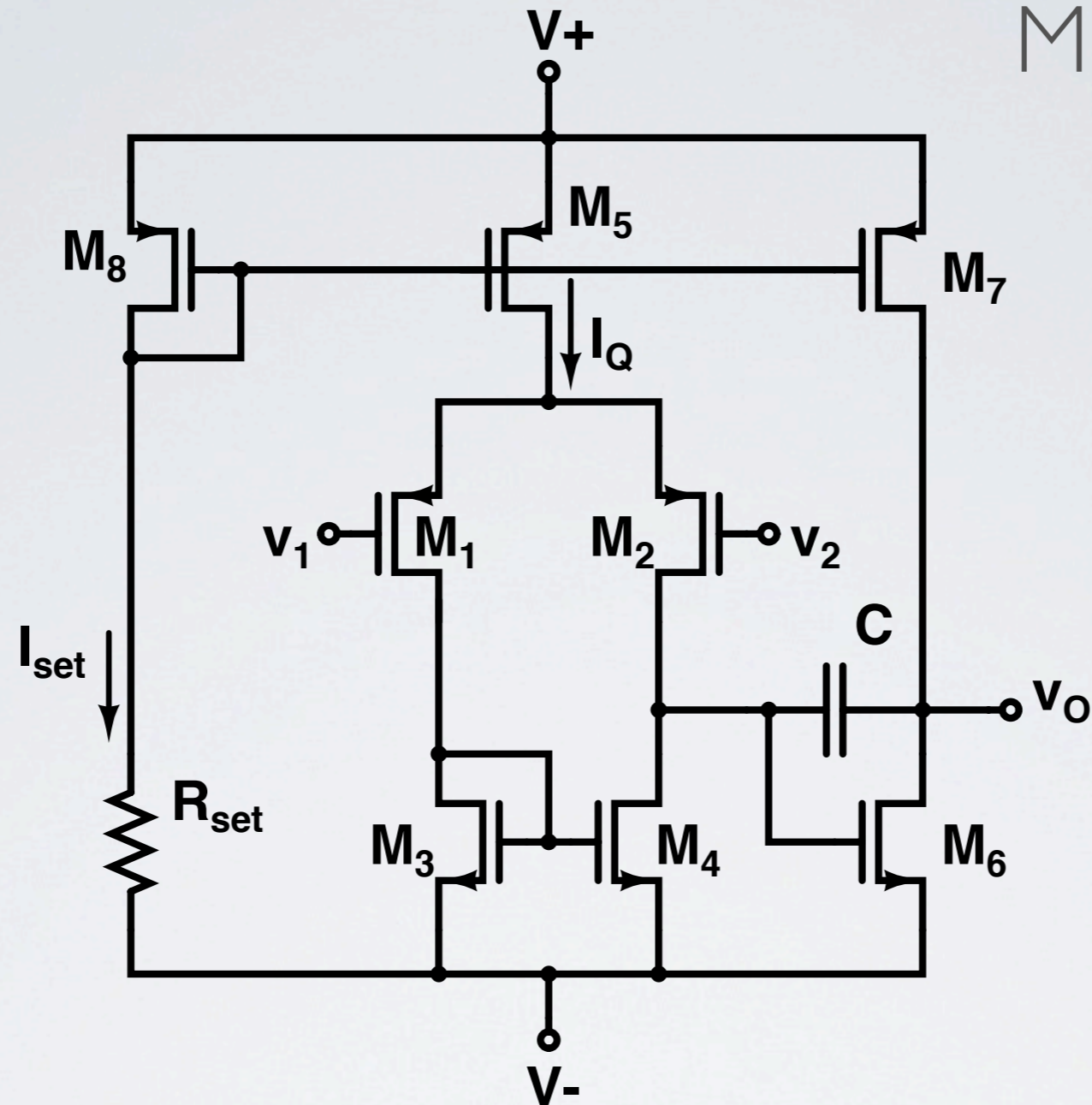



Example: Find DC bias current when $V_{TN}=0.5V$, $\frac{1}{2}\mu_n C_{ox}=20\mu A/V^2$, $\lambda_n=0.02V^{-1}$, $V_{TP}=-0.5V$, $\frac{1}{2}\mu_p C_{ox}=10\mu A/V^2$, $\lambda_p=0.02V^{-1}$, $R_{SET}=225k\Omega$, $(W/L)_3=(W/L)_4=6.25$, $(W/L)_{OTHER}=12.5$, $V_+=5V$, $V_-=-5V$.


Example: Find gain.

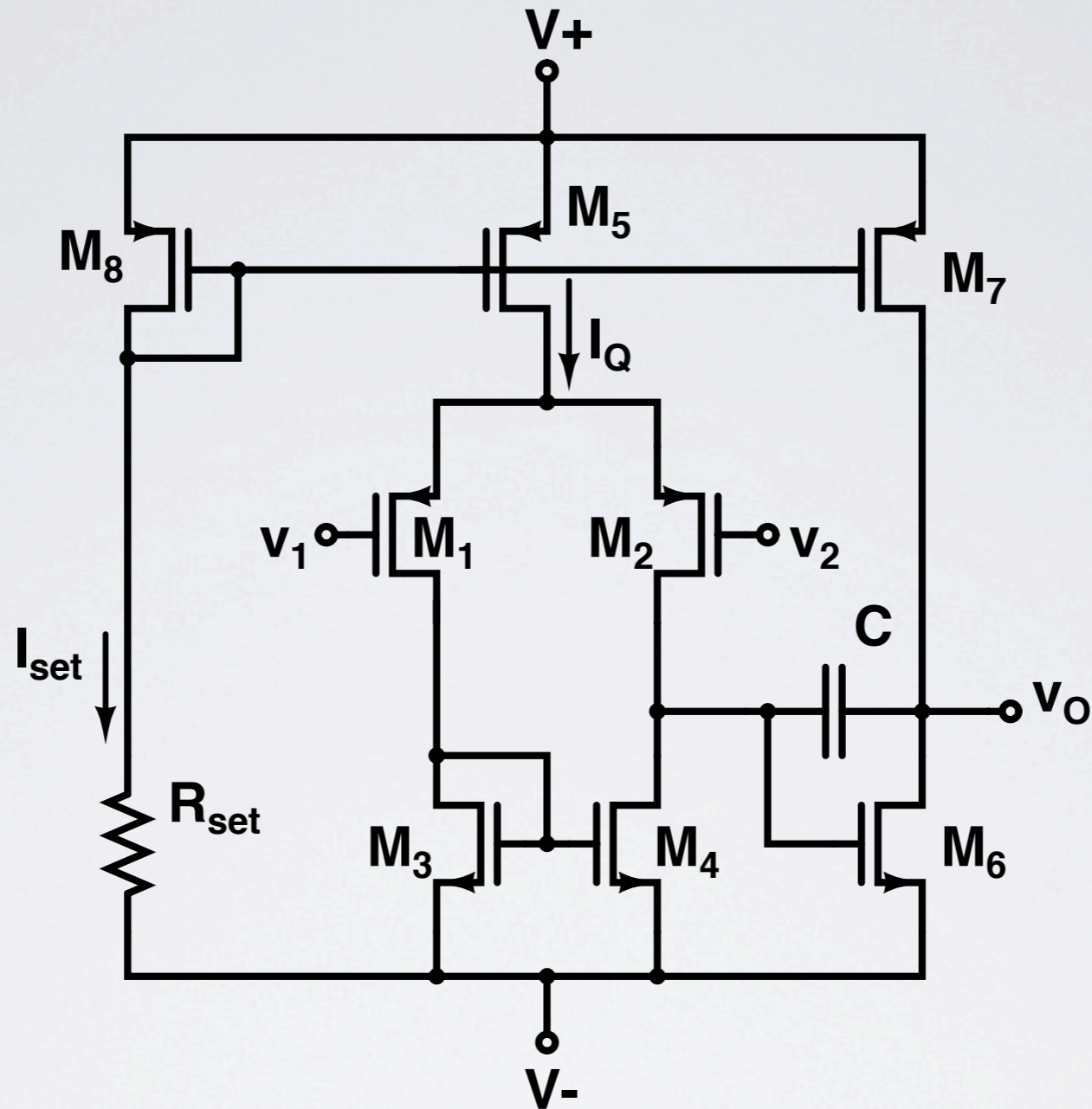

Example 13.8: Find DC bias current when $V_{TN}=0.5V$, $\frac{1}{2}\mu_n C_{ox}=20\mu A/V^2$, $\lambda_n=0.02V^{-1}$, $V_{TP}=-0.5V$, $\frac{1}{2}\mu_p C_{ox}=10\mu A/V^2$, $\lambda_p=0.02V^{-1}$, $R_{SET}=225k\Omega$, $(W/L)_3=(W/L)_4=6.25$, $(W/L)_{OTHER}=12.5$, $V_+=5V$, $V_-=-5V$. (ANSWER: $I_{REF}=39.7\mu A$)


Example 13.9: Find gain. (ANSWER: $A_v=(125)(125)=15,625$)

Three-stage cmos opamp

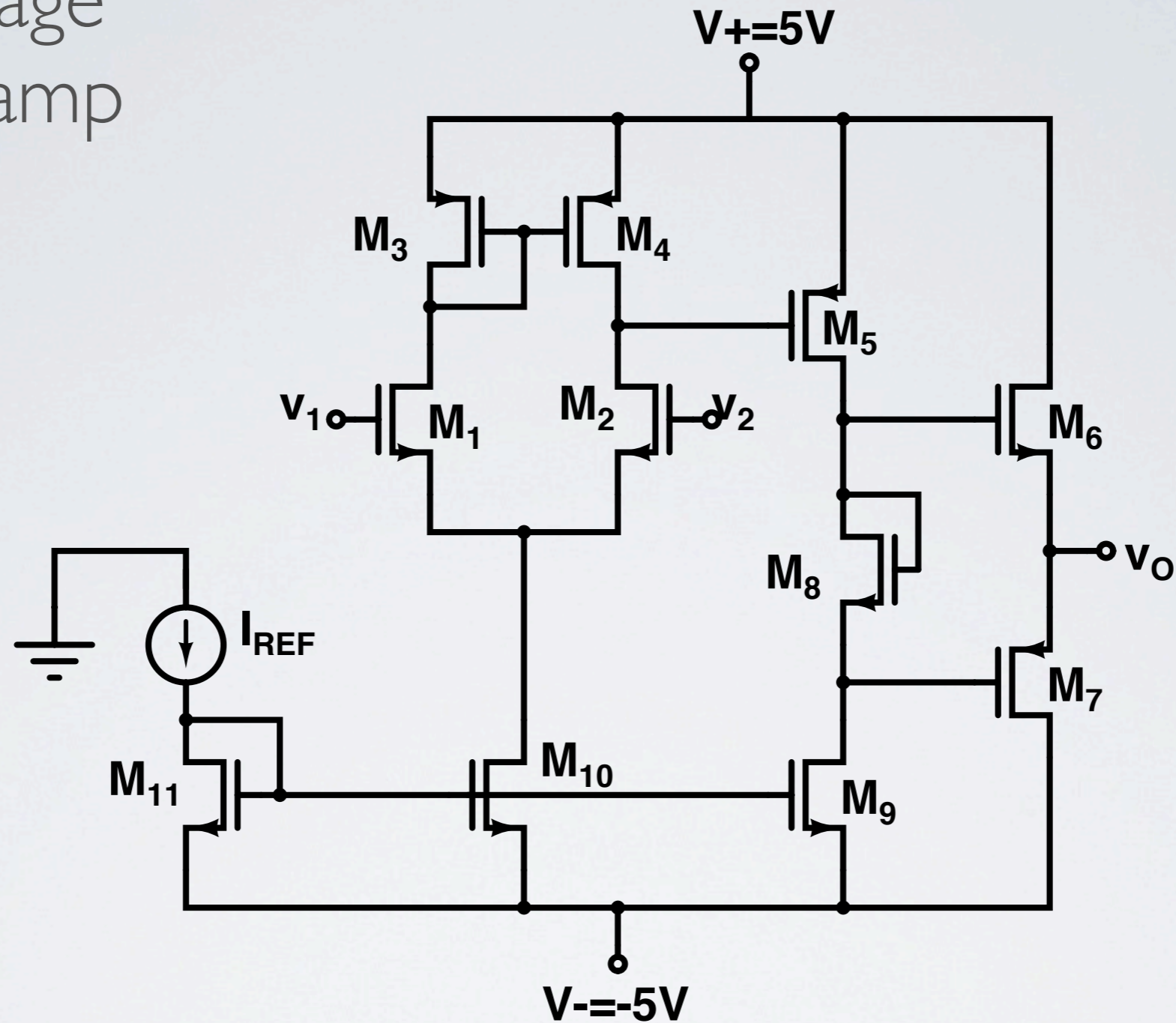


Example 13.10: Find DC and AC characteristics. $V_{TN}=0.7V$, $k_n'=80\mu A/V^2$, $\lambda_n=0.01V^{-1}$, $V_{TP}=-0.7V$, $k_p'=40\mu A/V^2$, $\lambda_p=0.015V^{-1}$, $I_{REF}=160\mu A$, $(W/L)_1=(W/L)_2=15/1$, $(W/L)_3=(W/L)_4=40/1$, $(W/L)_5=80/1$, $(W/L)_6=25/1$, $(W/L)_7=50/1$, $(W/L)_9=(W/L)_{10}=(W/L)_{11}=20/1$. Select $(W/L)_8$ so that $V_{GS6}=V_{GS7}=0.85V$.

Three-stage cmos opamp

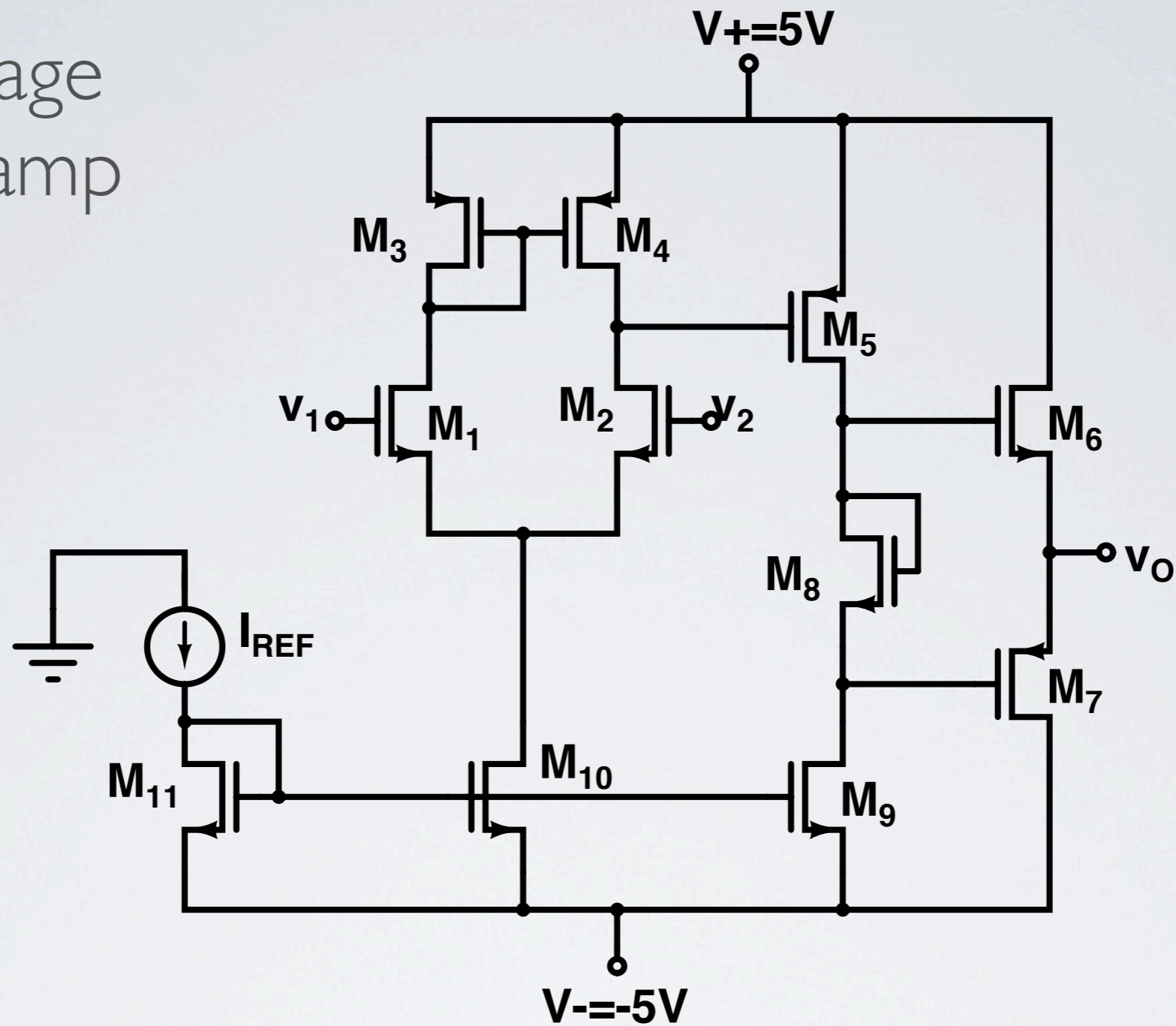

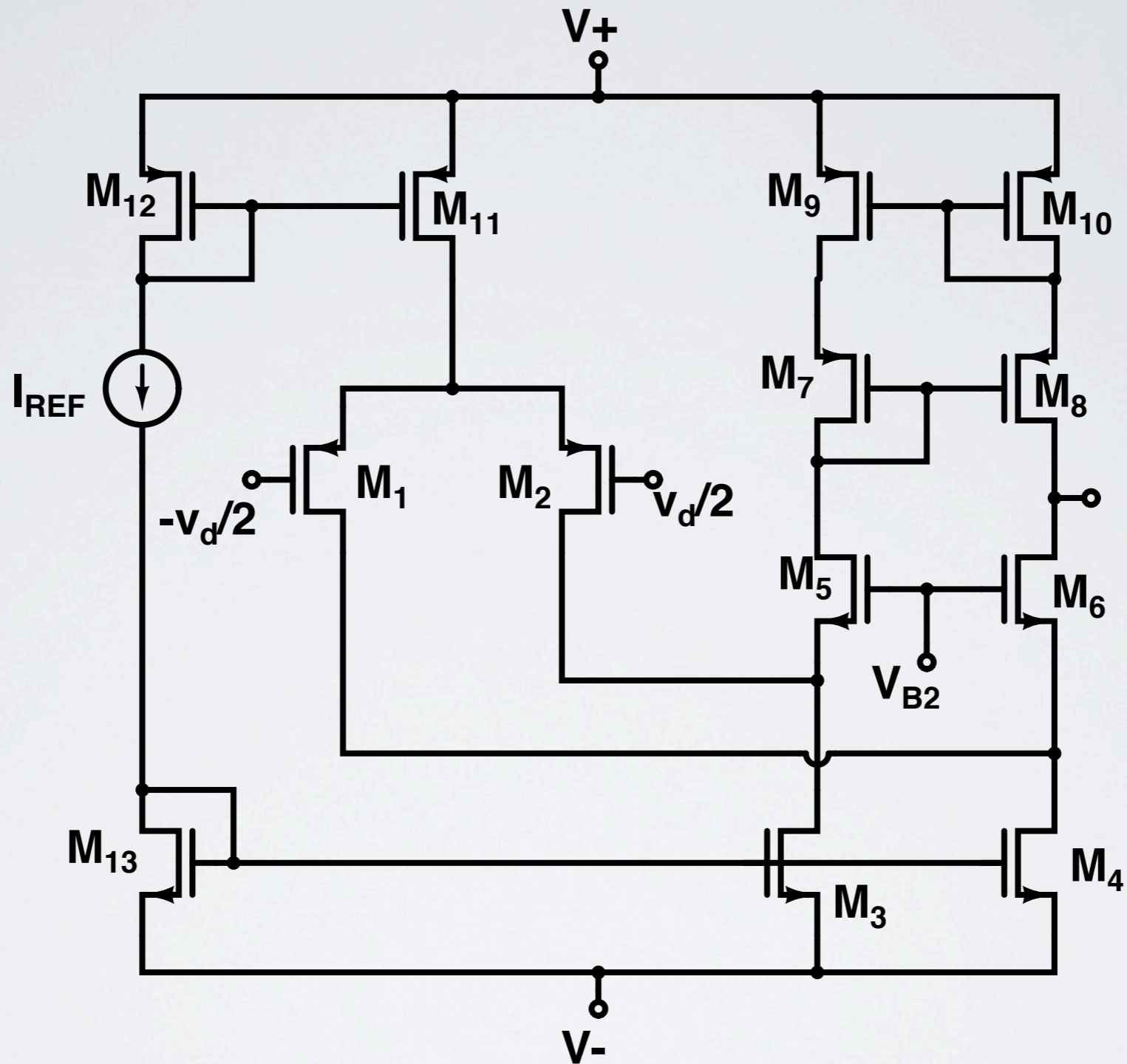Example: Find DC and AC characteristics. $V_{TN}=0.7V$, $k_n'=80\mu A/V^2$, $\lambda_n=0.01V^{-1}$, $V_{TP}=-0.7V$, $k_p'=40\mu A/V^2$, $\lambda_p=0.015V^{-1}$, $I_{REF}=160\mu A$, $(W/L)_1=(W/L)_2=15/1$, $(W/L)_3=(W/L)_4=40/1$, $(W/L)_5=80/1$, $(W/L)_6=25/1$, $(W/L)_7=50/1$, $(W/L)_9=(W/L)_{10}=(W/L)_{11}=20/1$. Select $(W/L)_8$ so that $V_{GS6}=V_{GS7}=0.85V$.
ANSWER: $(W/L)_8 = 4$; $I_{D6}=I_{D7}=22.5\mu A$; $A_v=(219)(-253)=-55407 V/V$.




Example: $I_{REF} = 100\mu\text{A}$, $k_n' = 80\mu\text{A}/\text{V}^2$, $K_p' = 40\mu\text{A}/\text{V}^2$, $(W/L) = 25$, γ , $\lambda_n = \lambda_p = 0.02\text{V}^{-1}$.
Find voltage gain.

For the following CMOS amplifier, where V_{b1} and V_{b2} are DC voltages for proper operation of the circuit:

- identify the negative and the positive terminals
- find the expression for the differential gain $A_{id} = V_{out}/V_{id}$
- find the expression for the differential input resistance R_{ind}
- find the expression for the output resistance R_{out}

Assume: I_{ss} = ideal current source

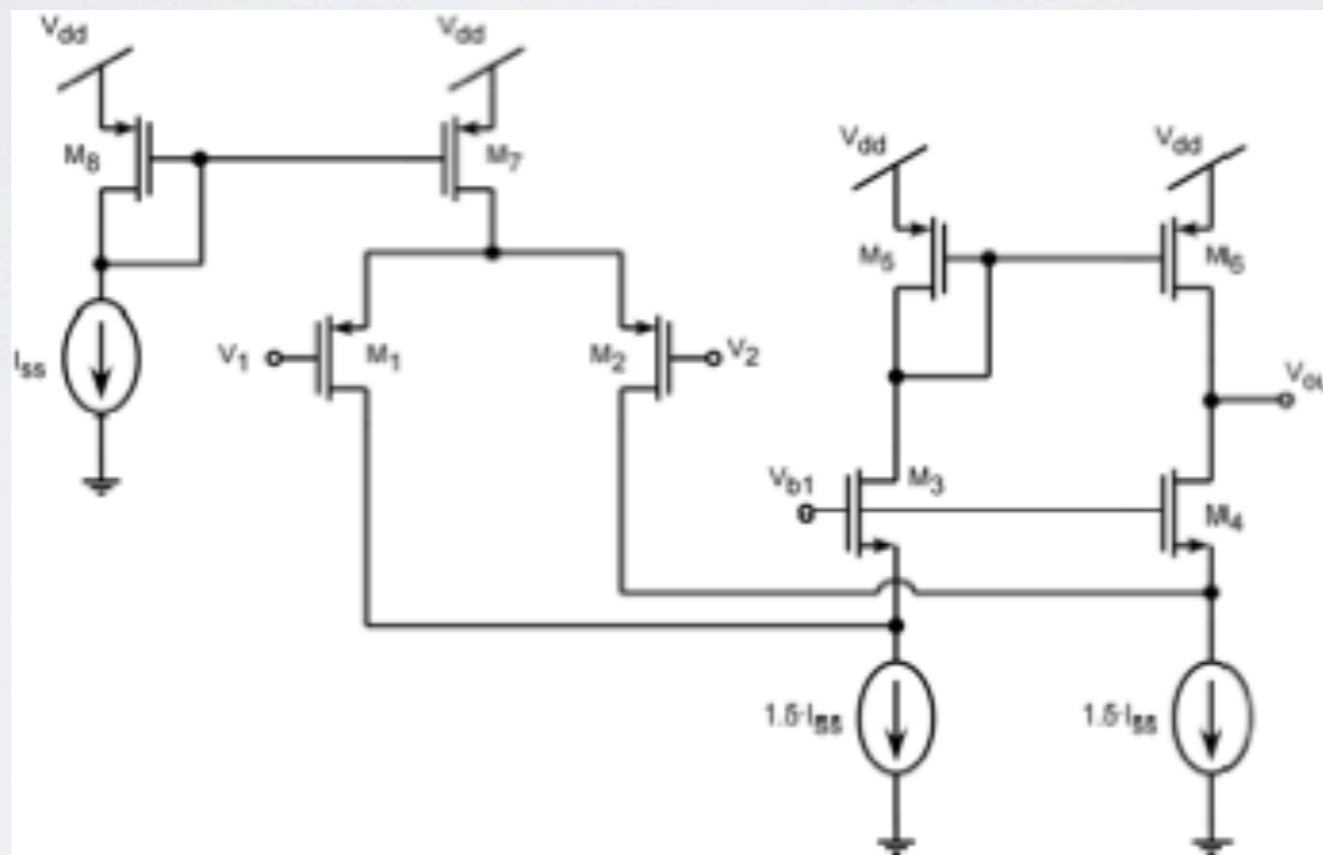


III. For the following CMOS amplifier, where V_{b1} and V_{b2} are DC voltages for proper operation of the circuit:

- identify the negative and the positive terminals
- find the expression for the differential gain $A_{id} = V_{out}/V_{id}$
- find the expression for the differential input resistance R_{ind}
- find the expression for the output resistance R_{out}

Assume: I_{ss} = ideal current source

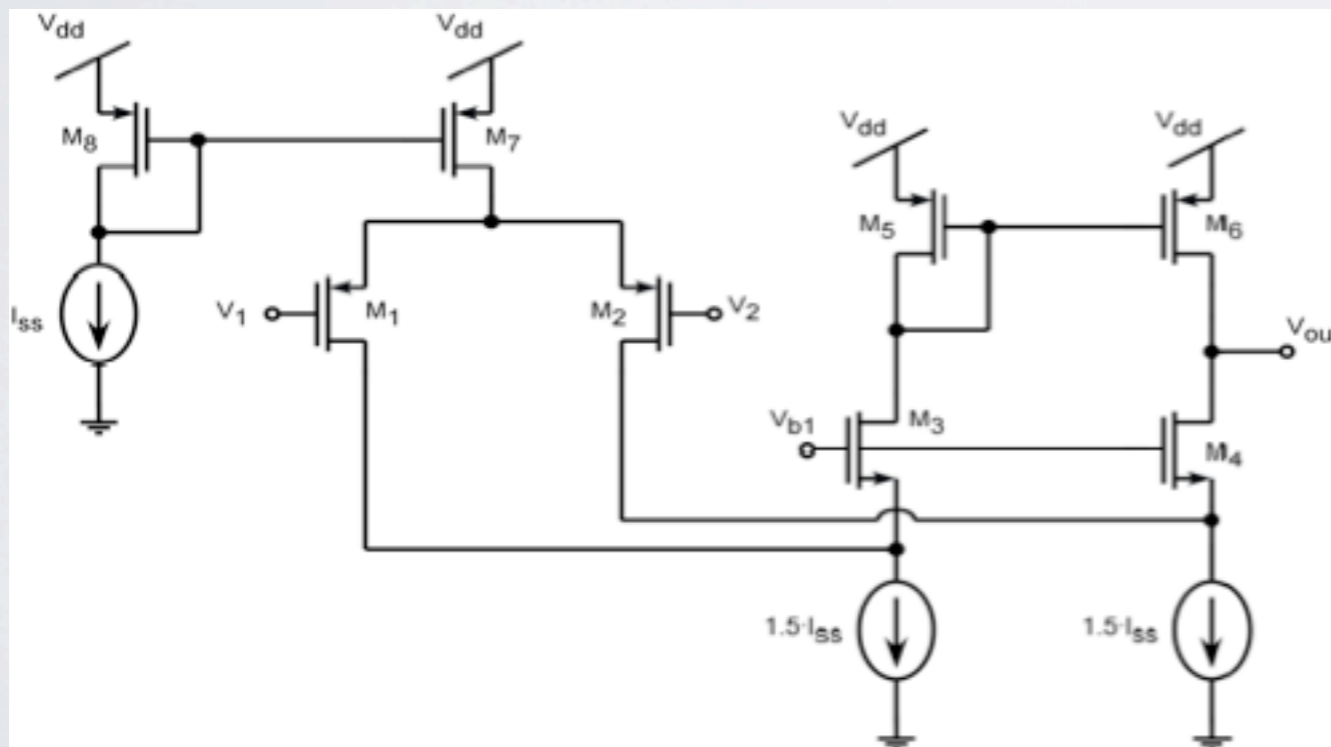a)
 $v_1 \uparrow \Rightarrow i_{d1} \uparrow \Rightarrow i_{d5} \downarrow \Rightarrow i_{d6} \downarrow$
 $\therefore v_1$ is + ; v_2 is -



$$\begin{aligned}
 \text{b) } A_{id} &= \frac{v_{OUT}}{v_{id}} = g_{m1} R_O \\
 R_O &= r_{O6} \parallel r_{O4} (1 + g_{m4} r_{O2}) \\
 g_{m1} &= 2\sqrt{K_P I_{SS}/2} & g_{m4} &= 2\sqrt{K_N I_{SS}} \\
 r_{O6} &= \frac{1}{\lambda_{P6} I_{SS}} & r_{O2} &= \frac{2}{\lambda_{P2} I_{SS}} \\
 r_{O4} &= \frac{1}{\lambda_{N4} I_{SS}}
 \end{aligned}$$

$$\text{c) } R_{ind} = \infty$$

$$\begin{aligned}
 \text{d) } R_O &= r_{O6} \parallel r_{O4} (1 + g_{m4} r_{O2}) \\
 g_{m1} &= 2\sqrt{K_P I_{SS}/2} & g_{m4} &= 2\sqrt{K_N I_{SS}} \\
 r_{O6} &= \frac{1}{\lambda_{P6} I_{SS}} & r_{O2} &= \frac{2}{\lambda_{P2} I_{SS}} \\
 r_{O4} &= \frac{1}{\lambda_{N4} I_{SS}}
 \end{aligned}$$