


INEL4202 Electrónica II

Introducción al Curso

- Libro de Texto: Sedra, Adel S.; Smith, Kenneth C.; *Microelectronic Circuits, 5th Edition*, Oxford University Press, New York, 2004.
- Tres exámenes parciales y un examen final
- Fechas: Lunes 10 de sept., Martes 9 de octubre y miércoles 21 de noviembre; de 8pm a 10pm.
- De necesitar acomodo razonable, favor de consultar al profesor durante la primera semana del semestre. para obtener acomodo razonable debe dirigirse a la Oficina de Calidad de Vida, a la extensión 5467, 3107 y 3894 o visitar el Decanato de Estudiantes, Primer Piso, Oficina de Calidad de Vida.

Microelectronic CIRCUITS

Sedra/Smith

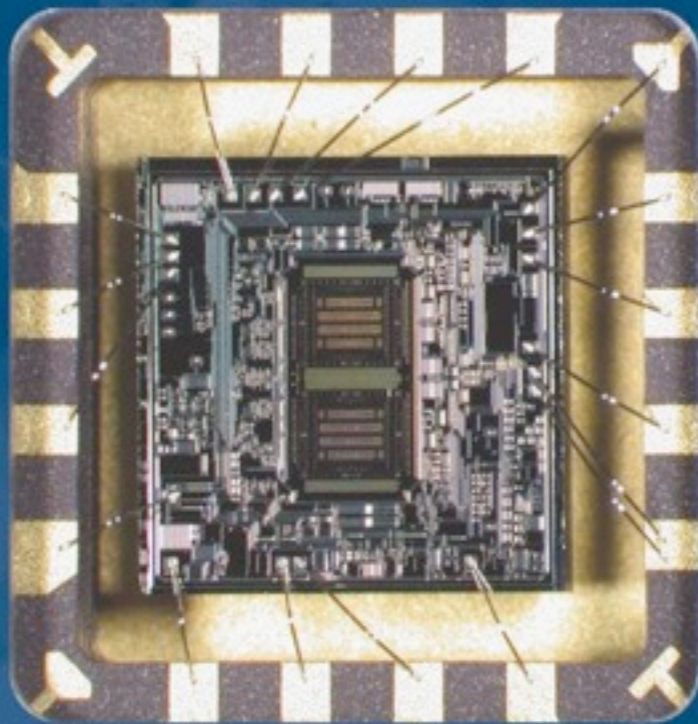

FIFTH EDITION



CD-ROM ENCLOSED
NOW WITH PSPICE 9.2
LITE EDITION

Textbook

Sedra/Smith


Microelectronic Circuits 5/e

©2004 Oxford University Press.


Info del Prof

- Nombre: Manuel Toledo
- Email: mtoledo@ece.uprm.edu
- Oficina: Stefani 703
- horas de oficina: vea <http://ece.uprm.edu/~mtoledo>
- Página del curso: <http://ece.uprm.edu/~mtoledo/4202>

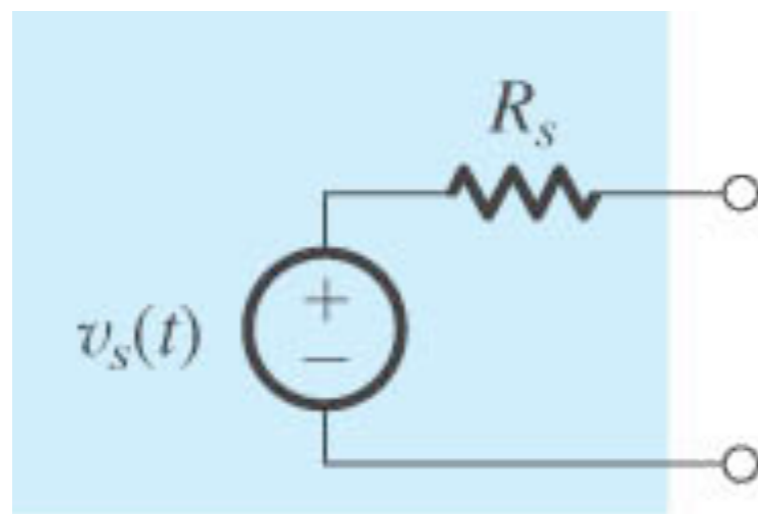- Temas
 - Ex. 1: Respuesta de frecuencia
 - Ex. 2: Retro-alimentación, estabilidad y osciladores
 - Ex. 3: Opamps
 - Amplificadores de potencia



(a)

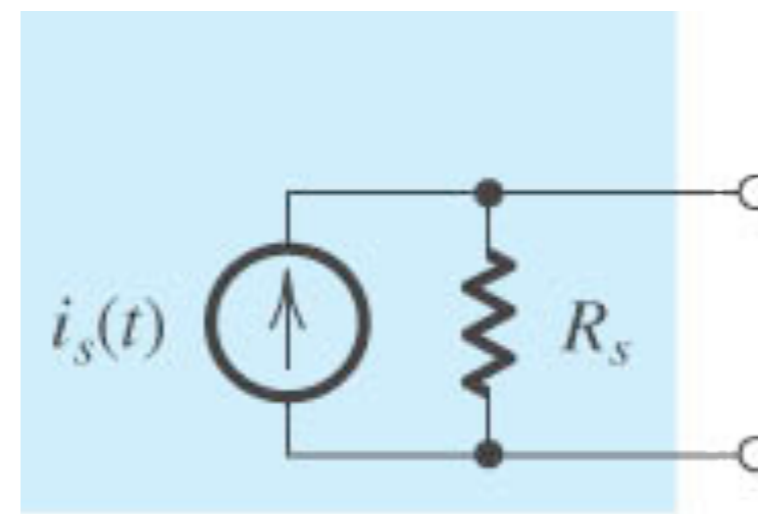

(b)

Figure 1.1 Two alternative representations of a signal source: (a) the Thévenin form, and (b) the Norton form.

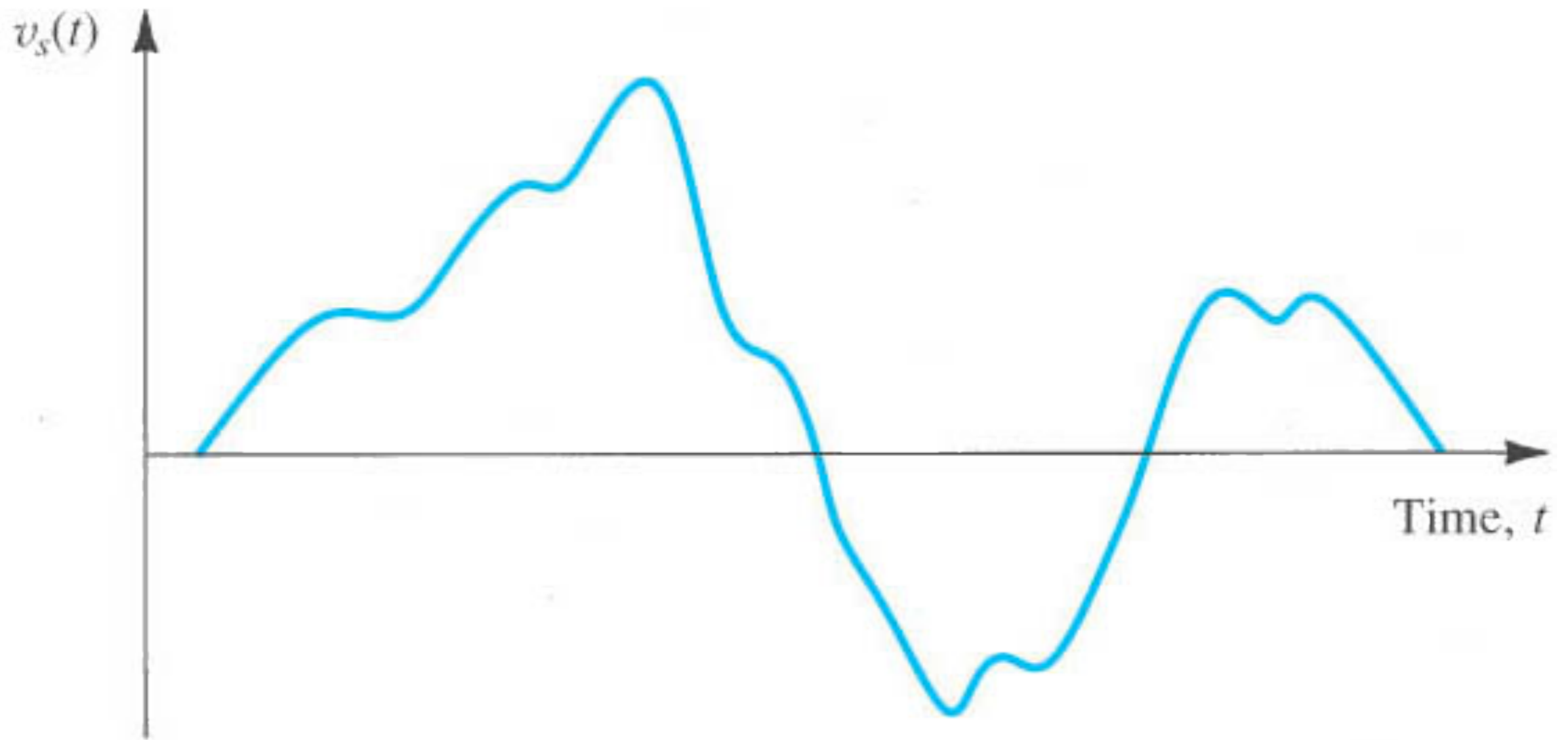


Figure 1.2 An arbitrary voltage signal $v_s(t)$.

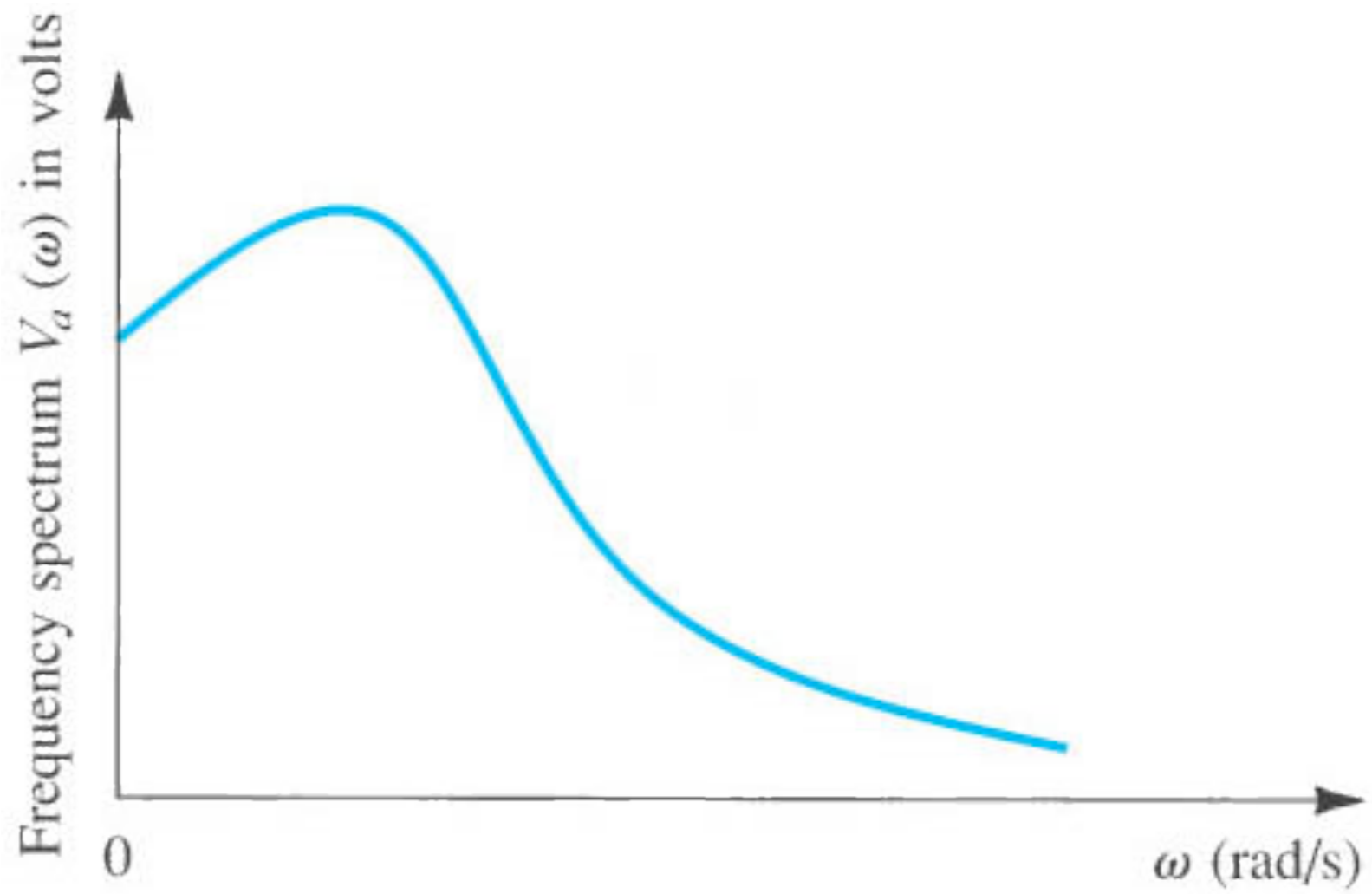


Figure 1.6 The frequency spectrum of an arbitrary waveform such as that in Fig. 1.2.

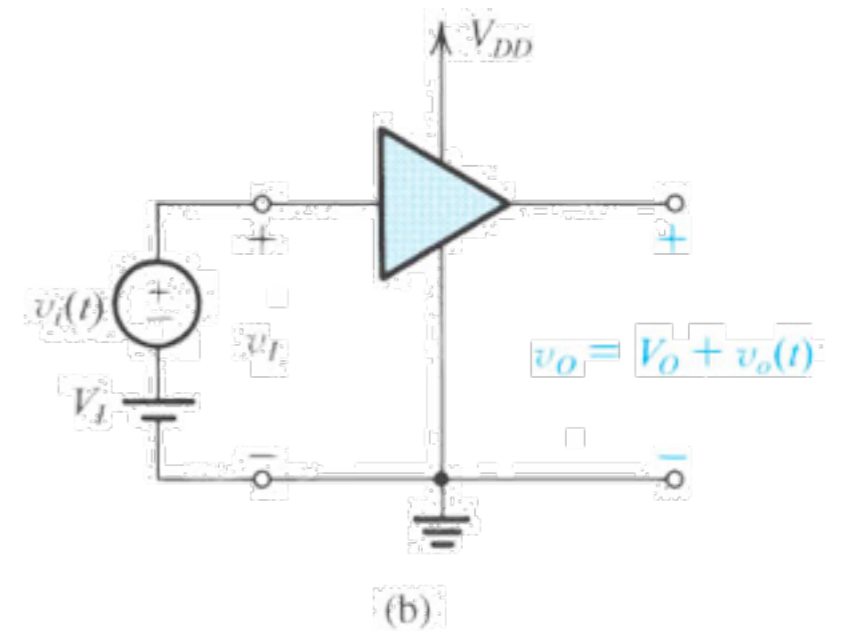
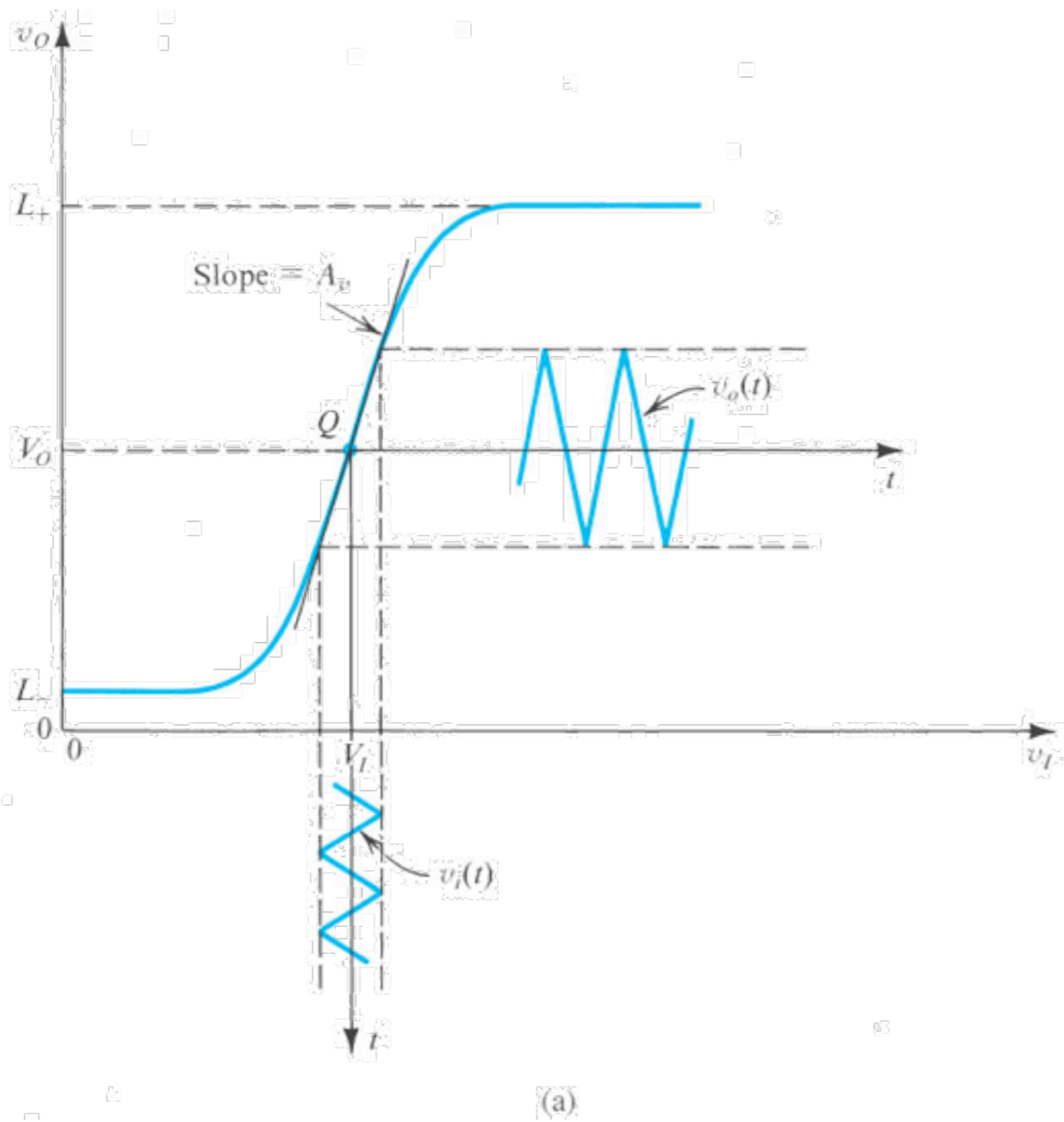


Figure 1.14 (a) An amplifier transfer characteristic that shows considerable nonlinearity. (b) To obtain linear operation the amplifier is biased as shown, and the signal amplitude is kept small. Observe that this amplifier is operated from a single power supply, V_{DD} .

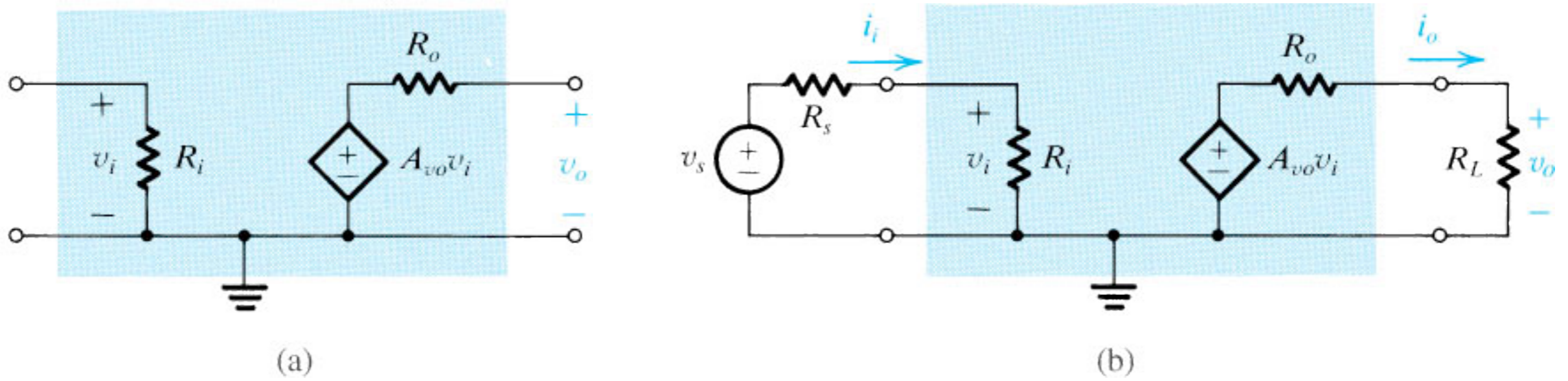


Figure 1.17 (a) Circuit model for the voltage amplifier. (b) The voltage amplifier with input signal source and load.

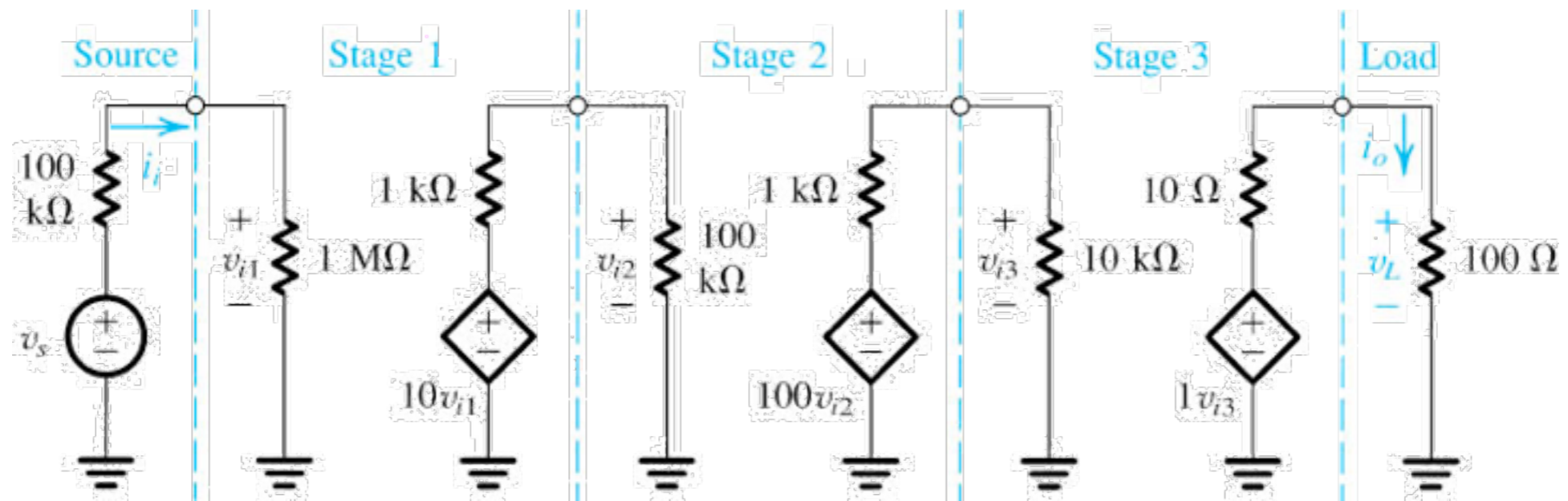


Figure 1.18 Three-stage amplifier for Example 1.3.

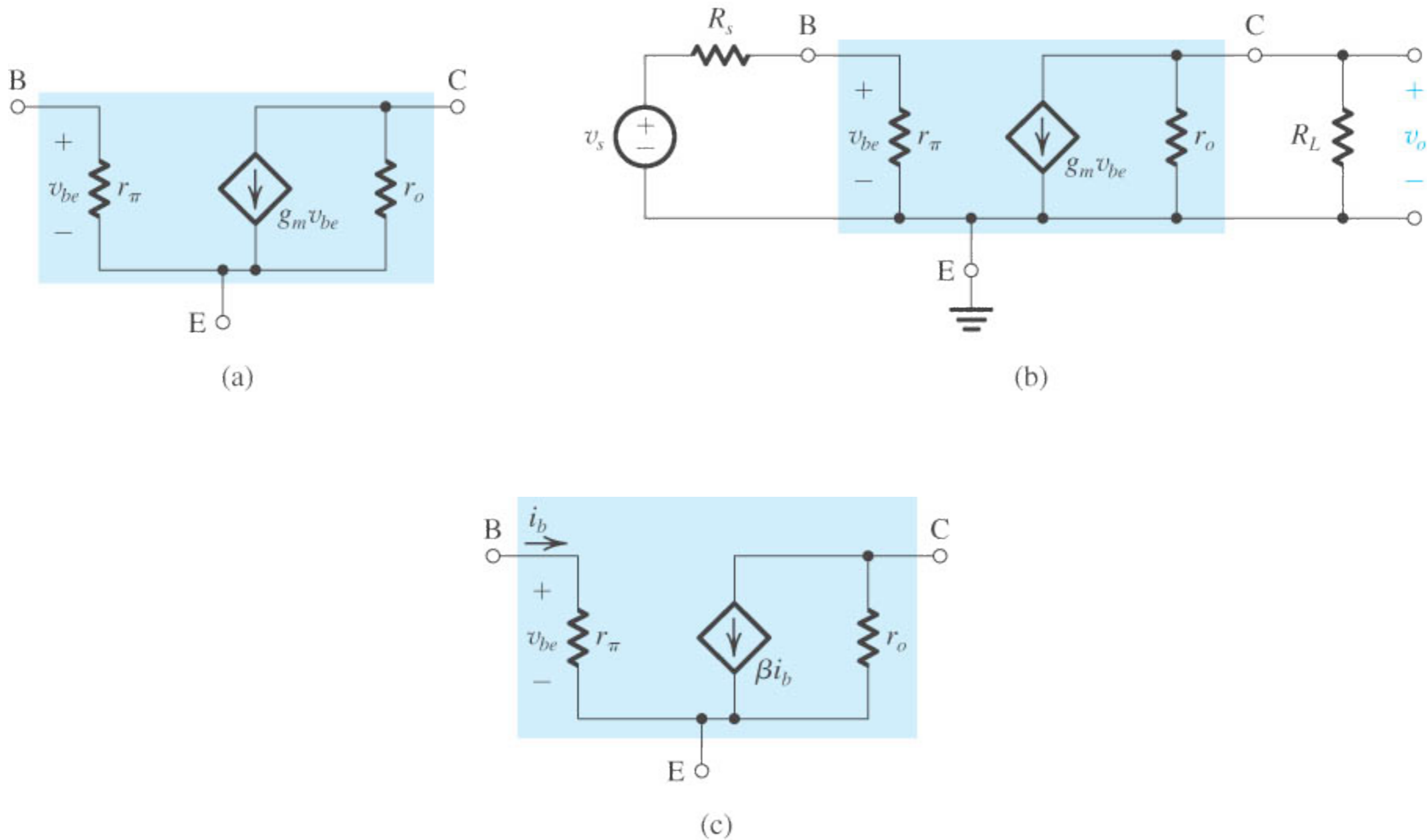


Figure 1.19 (a) Small-signal circuit model for a bipolar junction transistor (BJT). (b) The BJT connected as an amplifier with the emitter as a common terminal between input and output (called a common-emitter amplifier). (c) An alternative small-signal circuit model for the BJT.

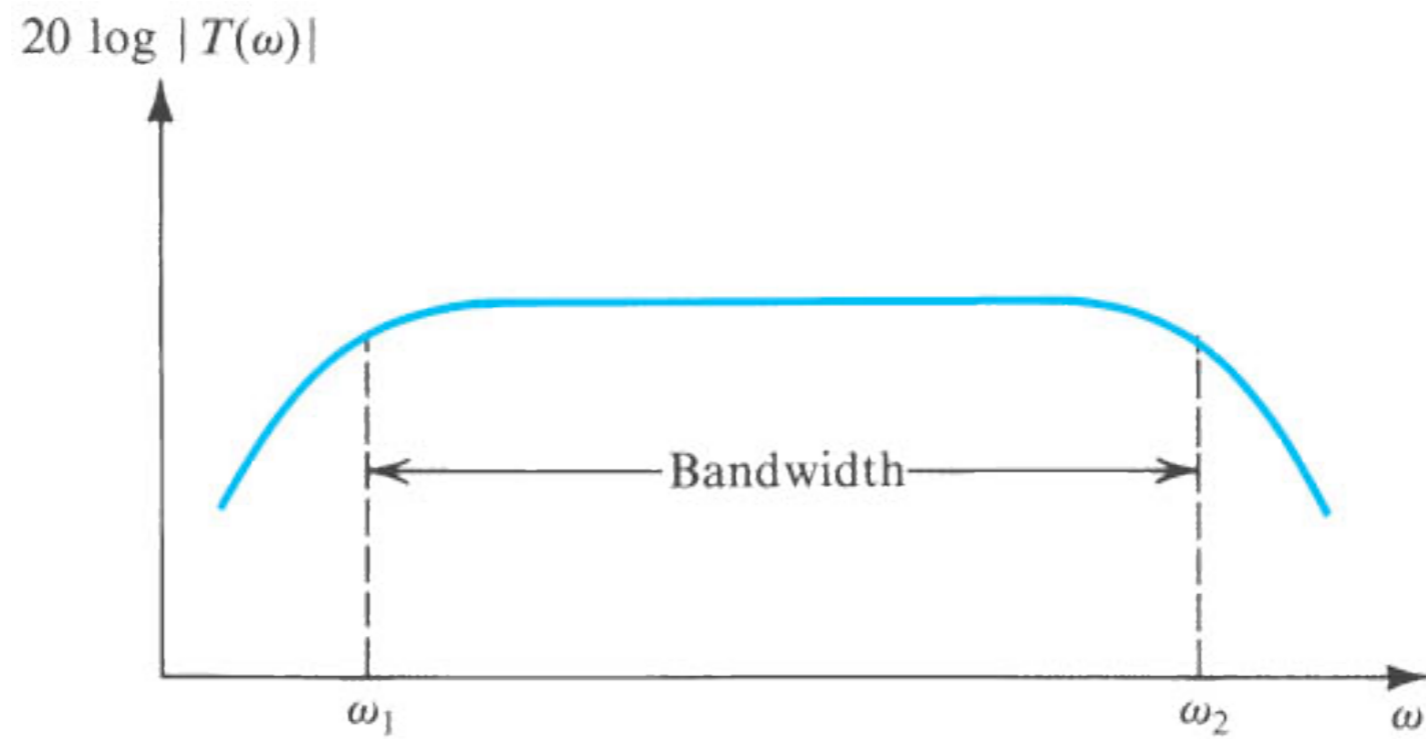


Figure 1.21 Typical magnitude response of an amplifier. $|T(\nu)|$ is the magnitude of the amplifier transfer function—that is, the ratio of the output $V_o(\nu)$ to the input $V_i(\nu)$.



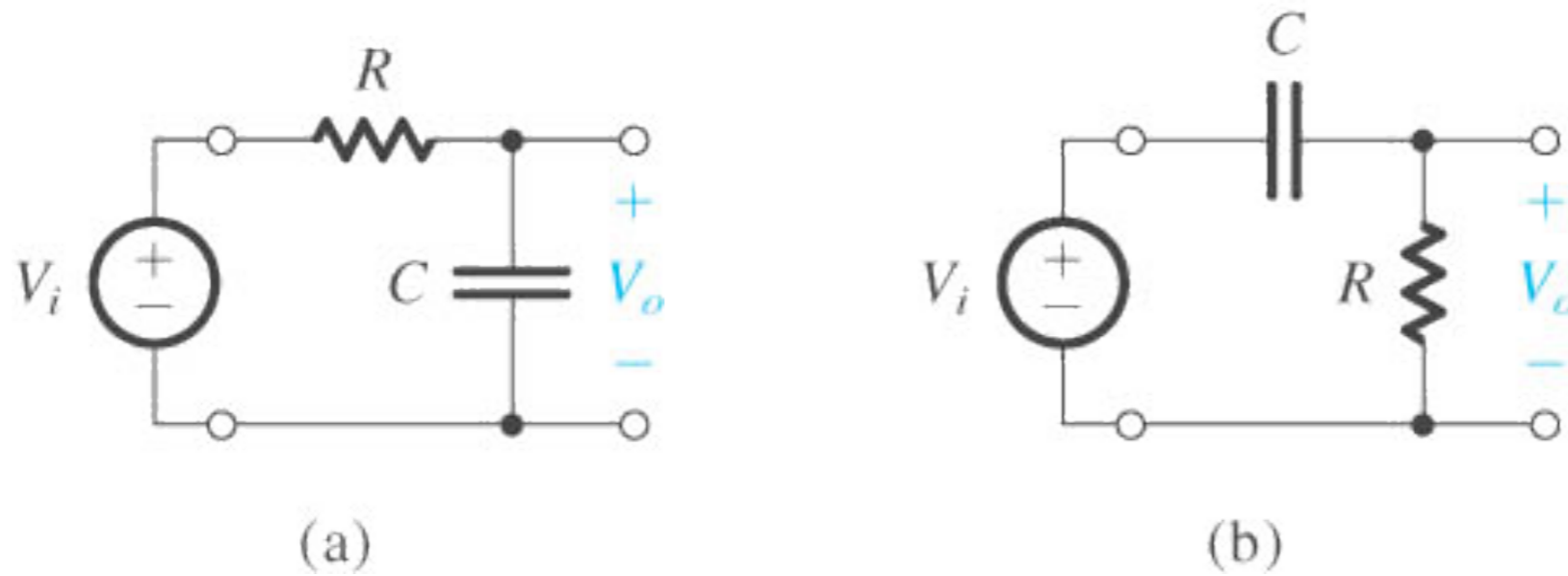


Figure 1.22 Two examples of STC networks: (a) a low-pass network and (b) a high-pass network.

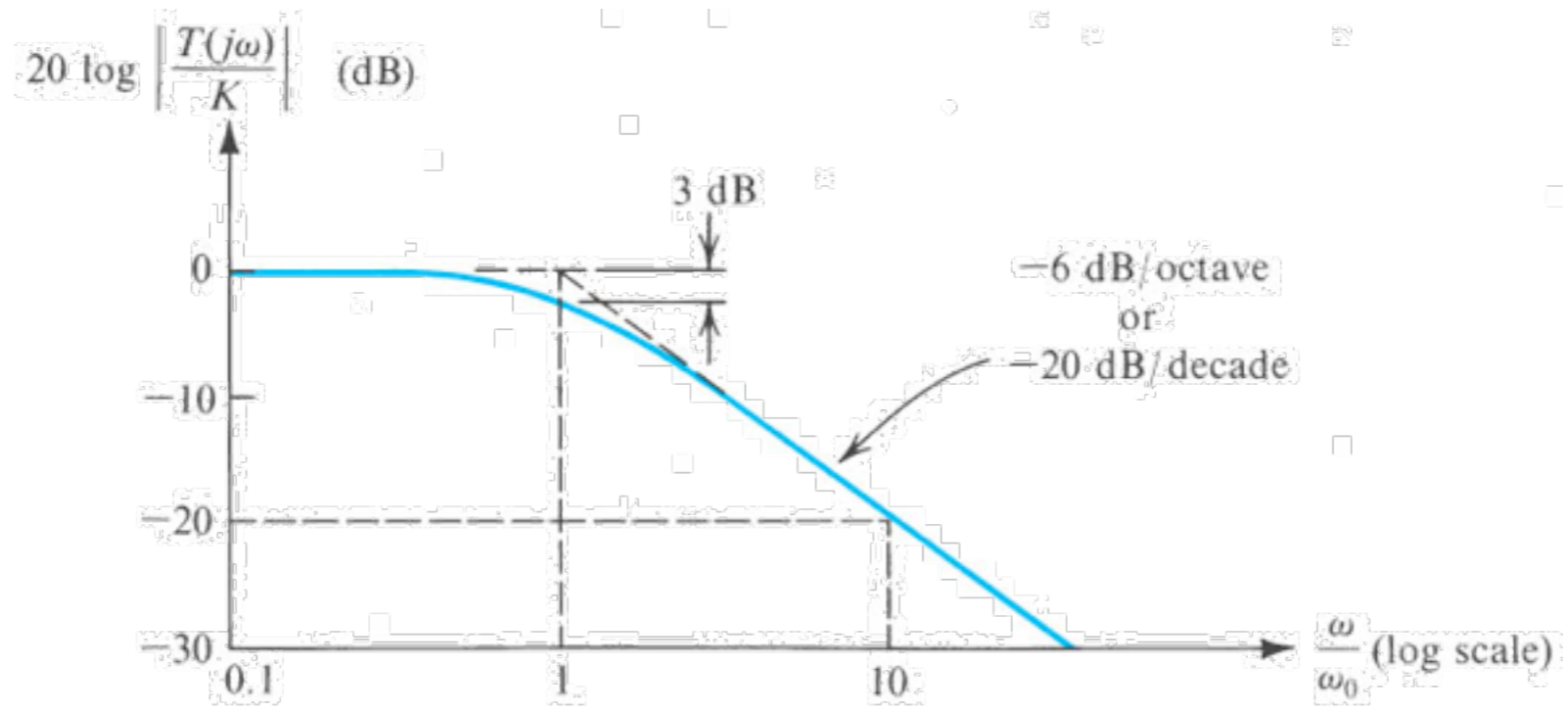

(a)

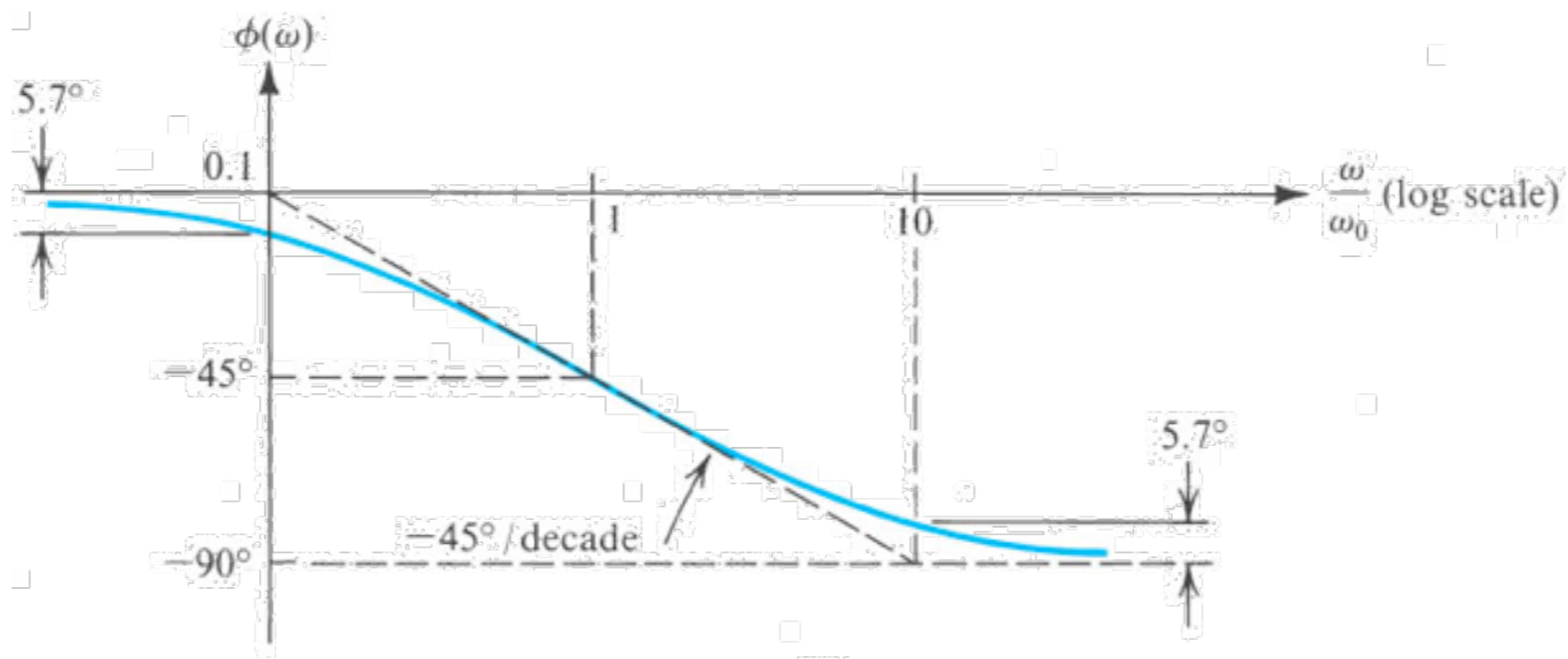

(b)

Figure 1.23 (a) Magnitude and (b) phase response of STC networks of the low-pass type.

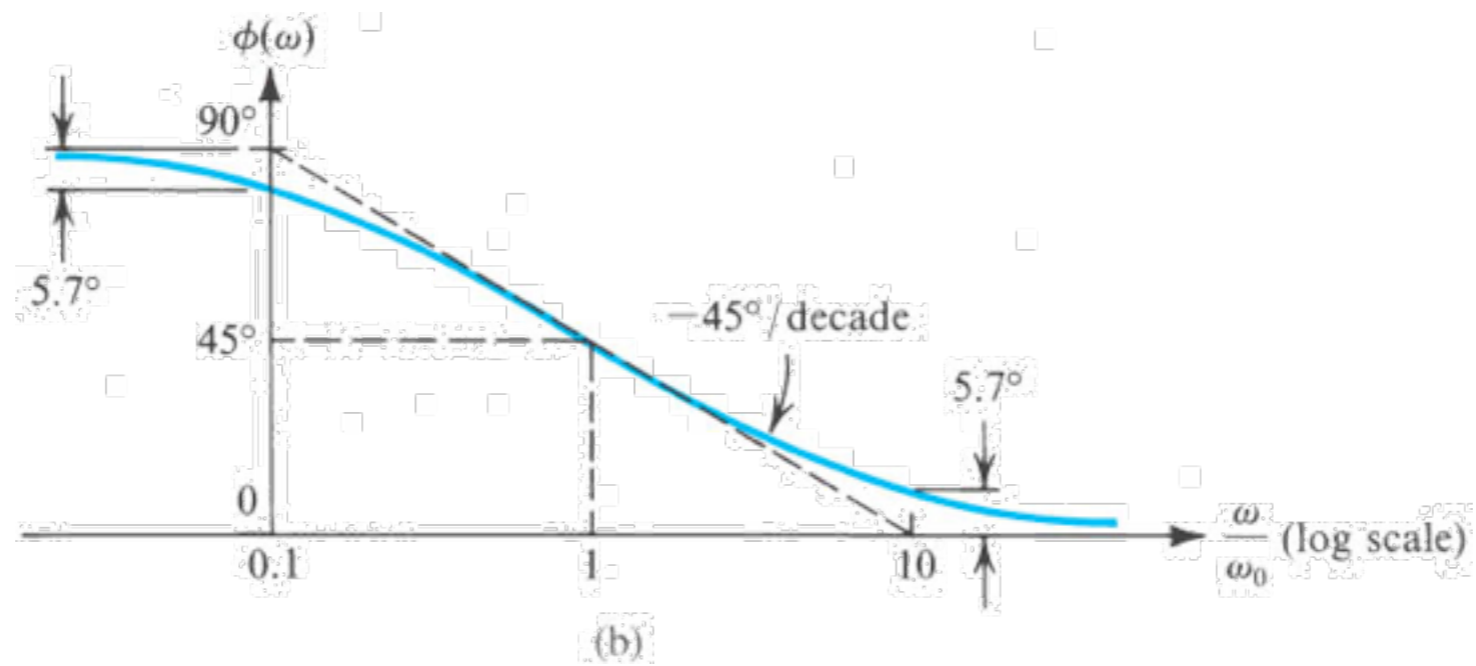
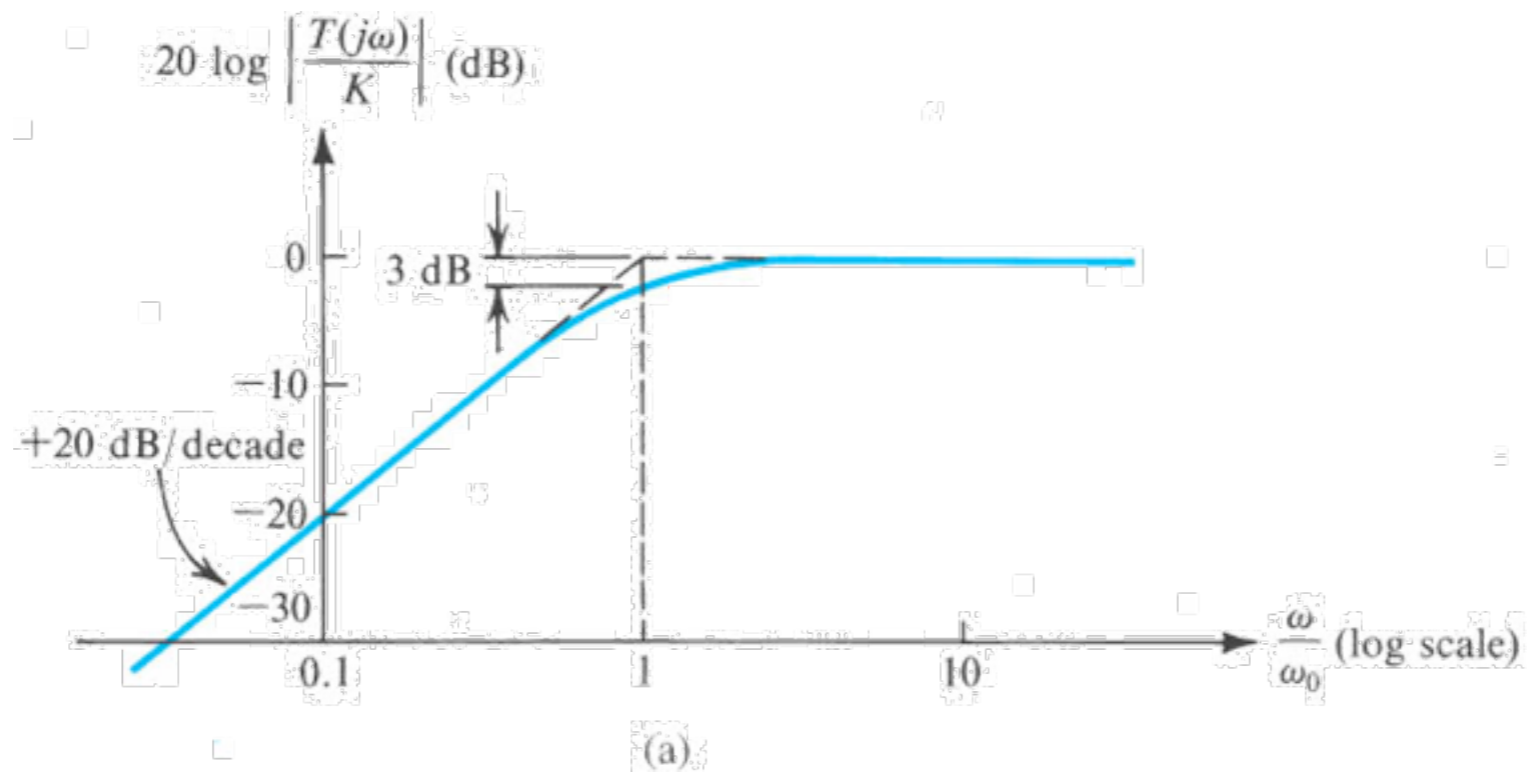


Figure 1.24 (a) Magnitude and (b) phase response of STC networks of the high-pass type.


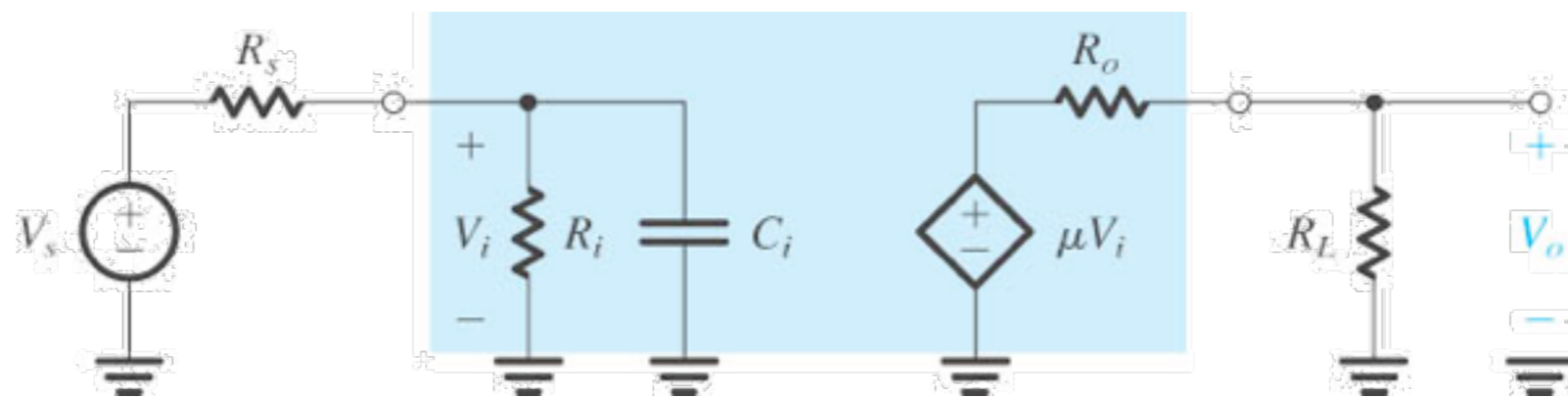



Figure 1.25 Circuit for Example 1.5.

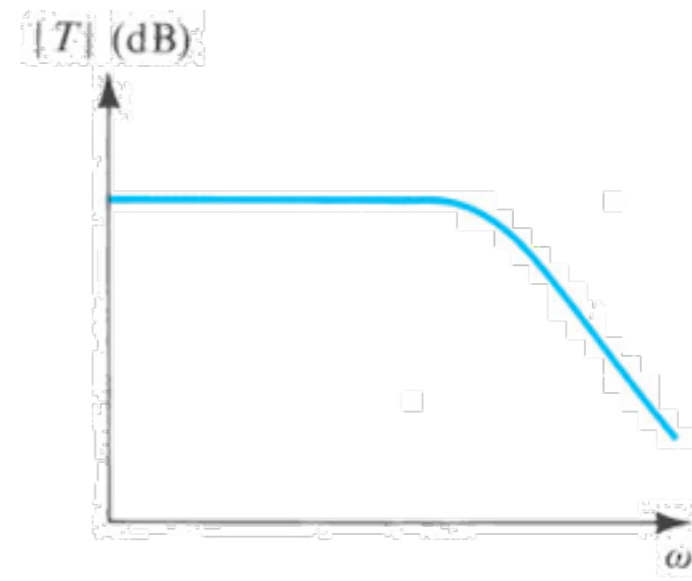

(a)



(b)

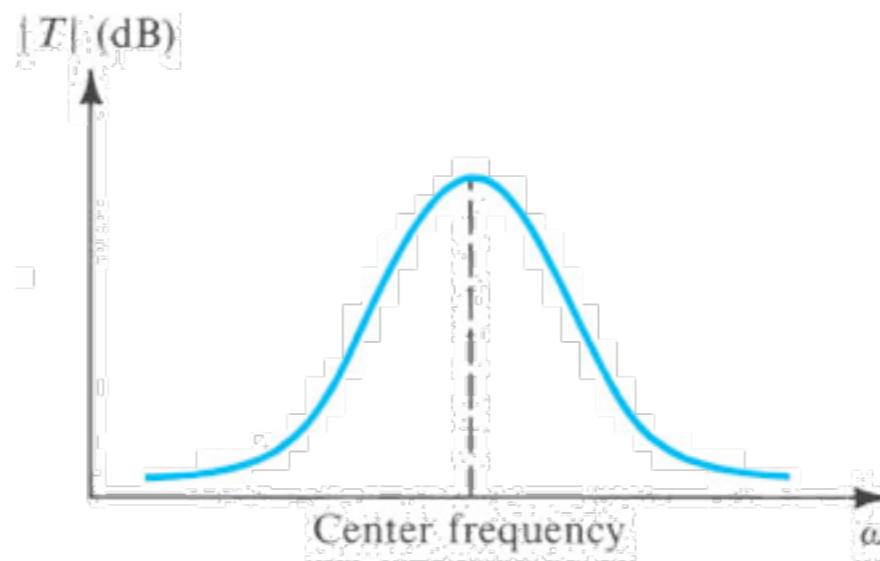

(c)

Figure 1.26 Frequency response for (a) a capacitively coupled amplifier, (b) a direct-coupled amplifier, and (c) a tuned or bandpass amplifier.

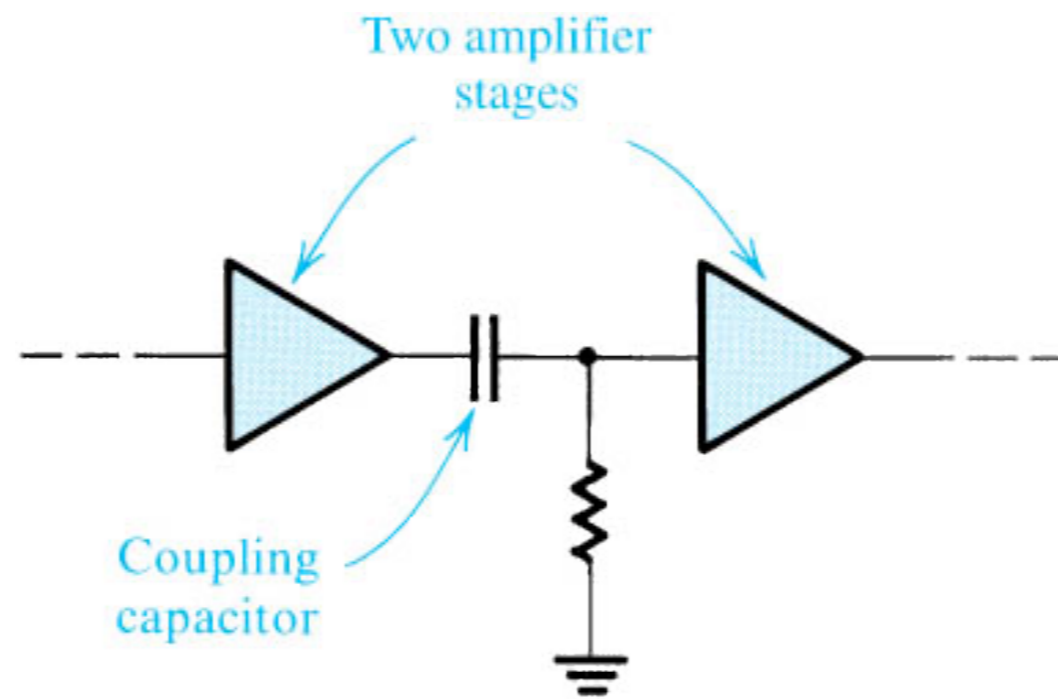


Figure 1.27 Use of a capacitor to couple amplifier stages.

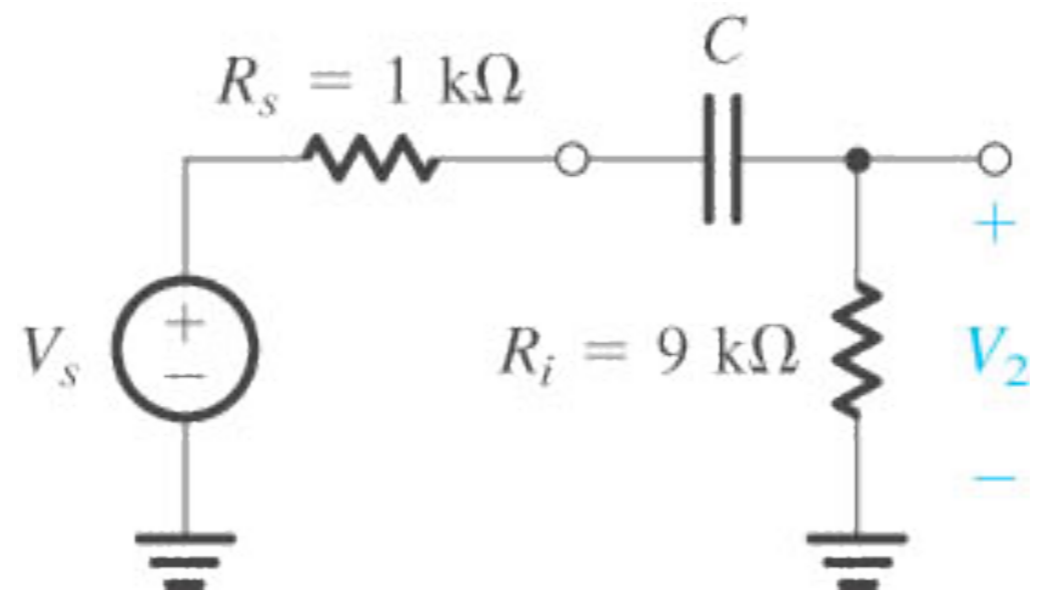


Figure E1.23

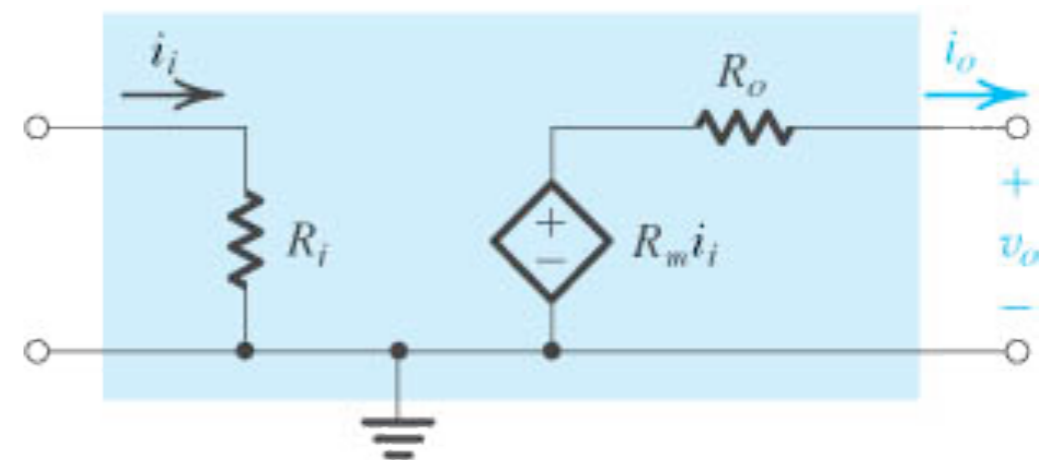
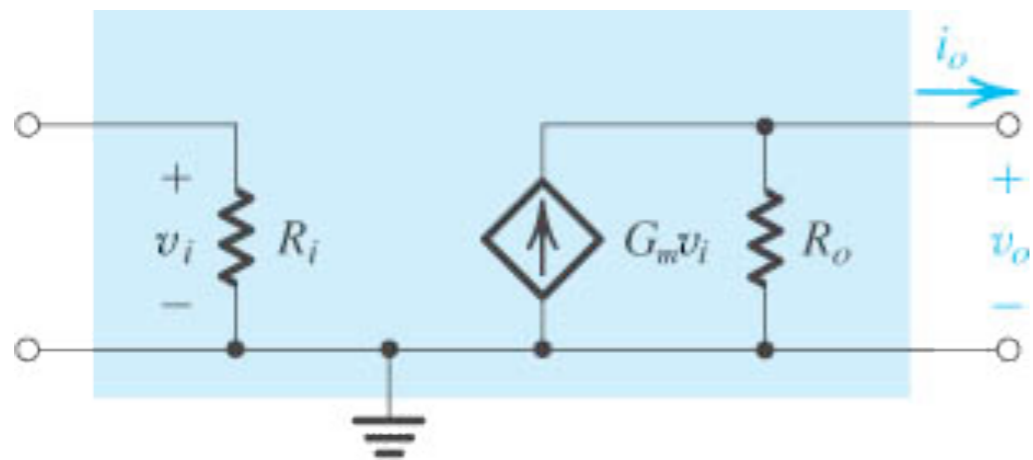
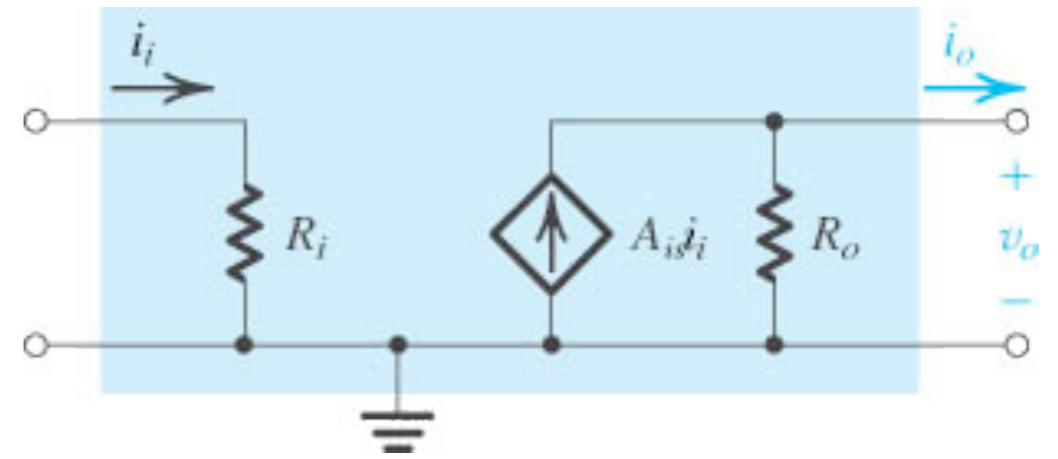
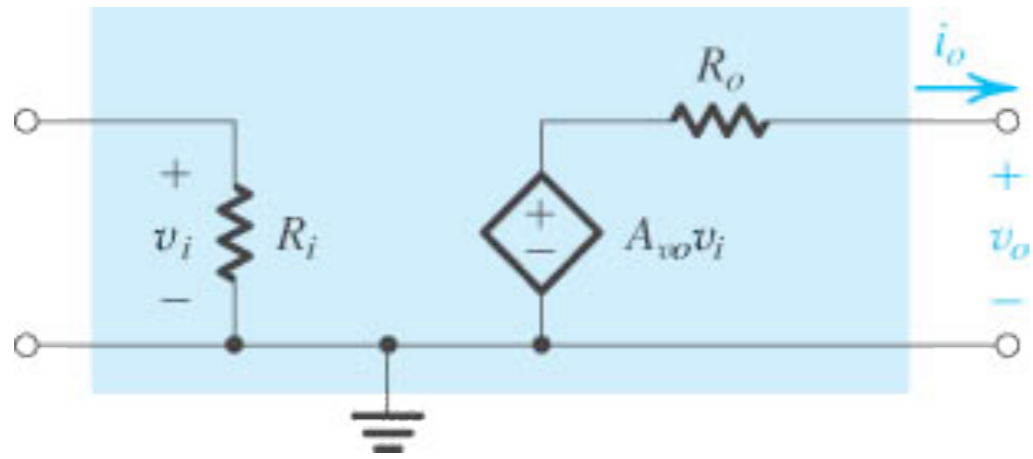


Table 1.1 The Four Amplifier Types