
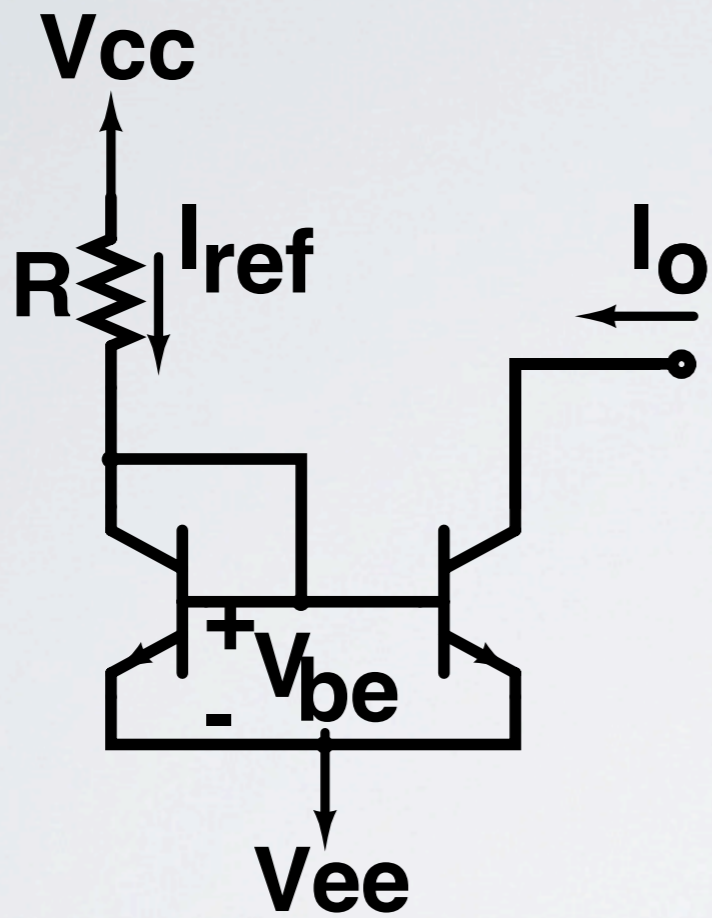


CURRENT SOURCES & ACTIVE LOADS


INEL 4202 - Electronics II - Fall 2012

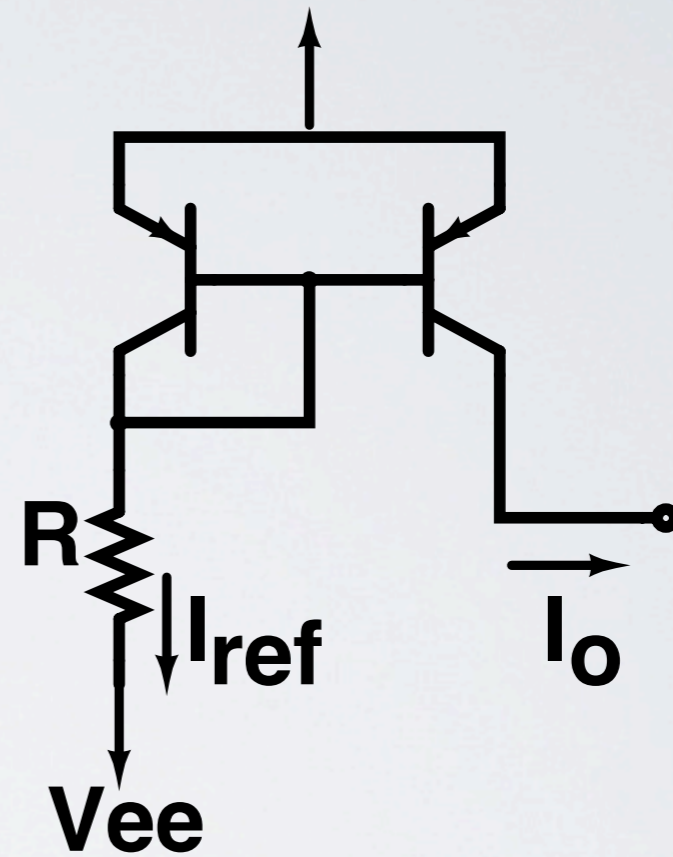


Basic C.S.



Basic C.S. with PNP BJTs

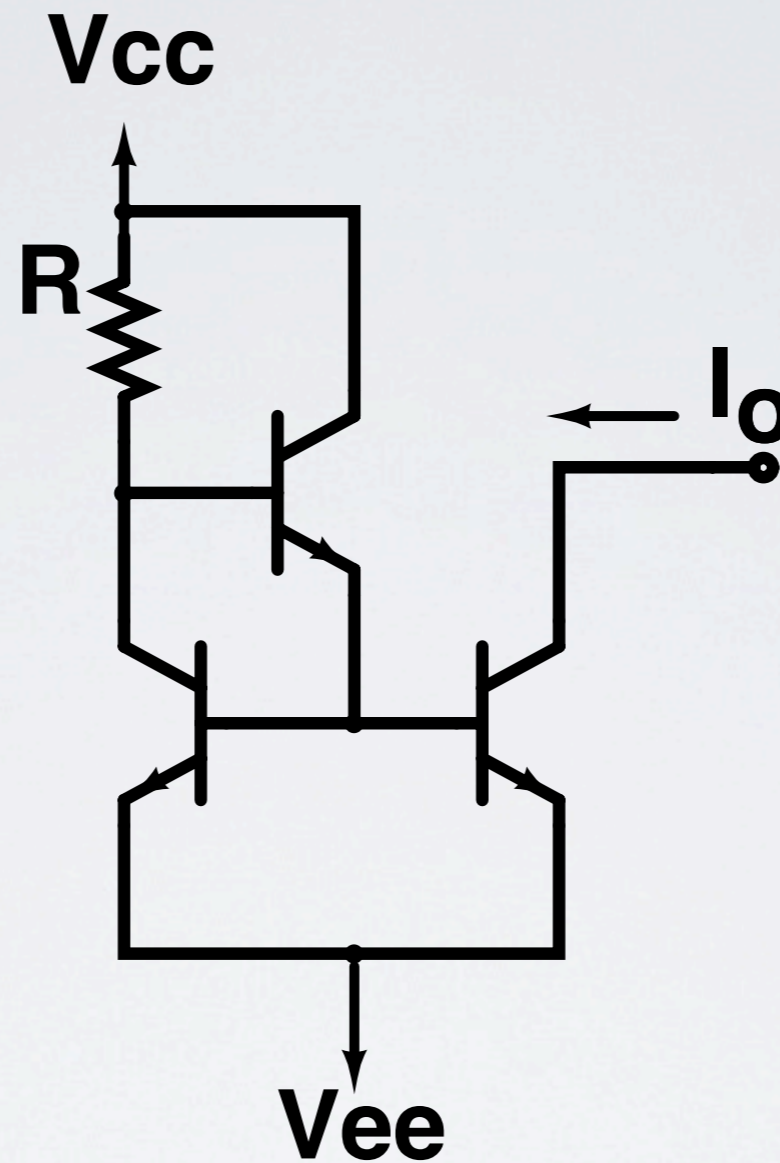


Mirror with base-current compensation

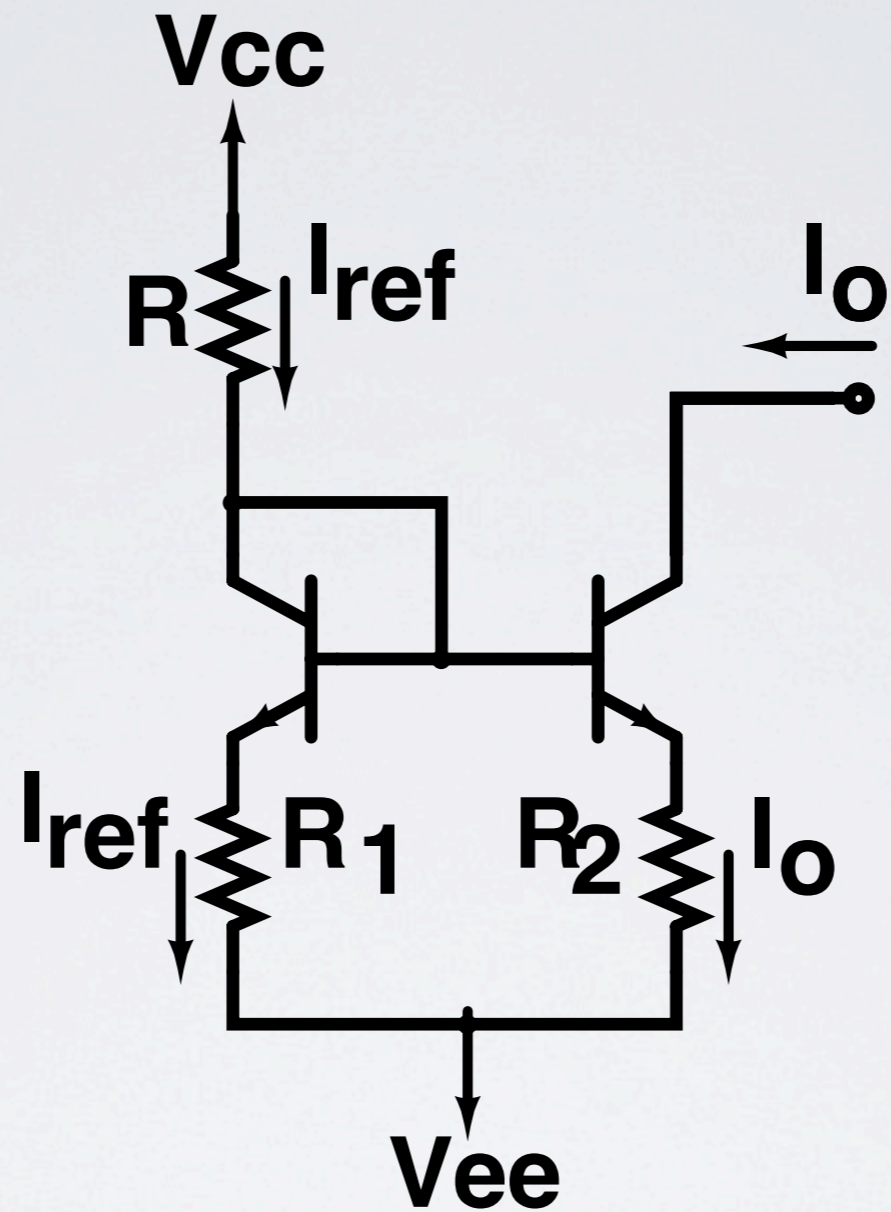


**Basic Source with
Emitter Resistors**

Output Resistance

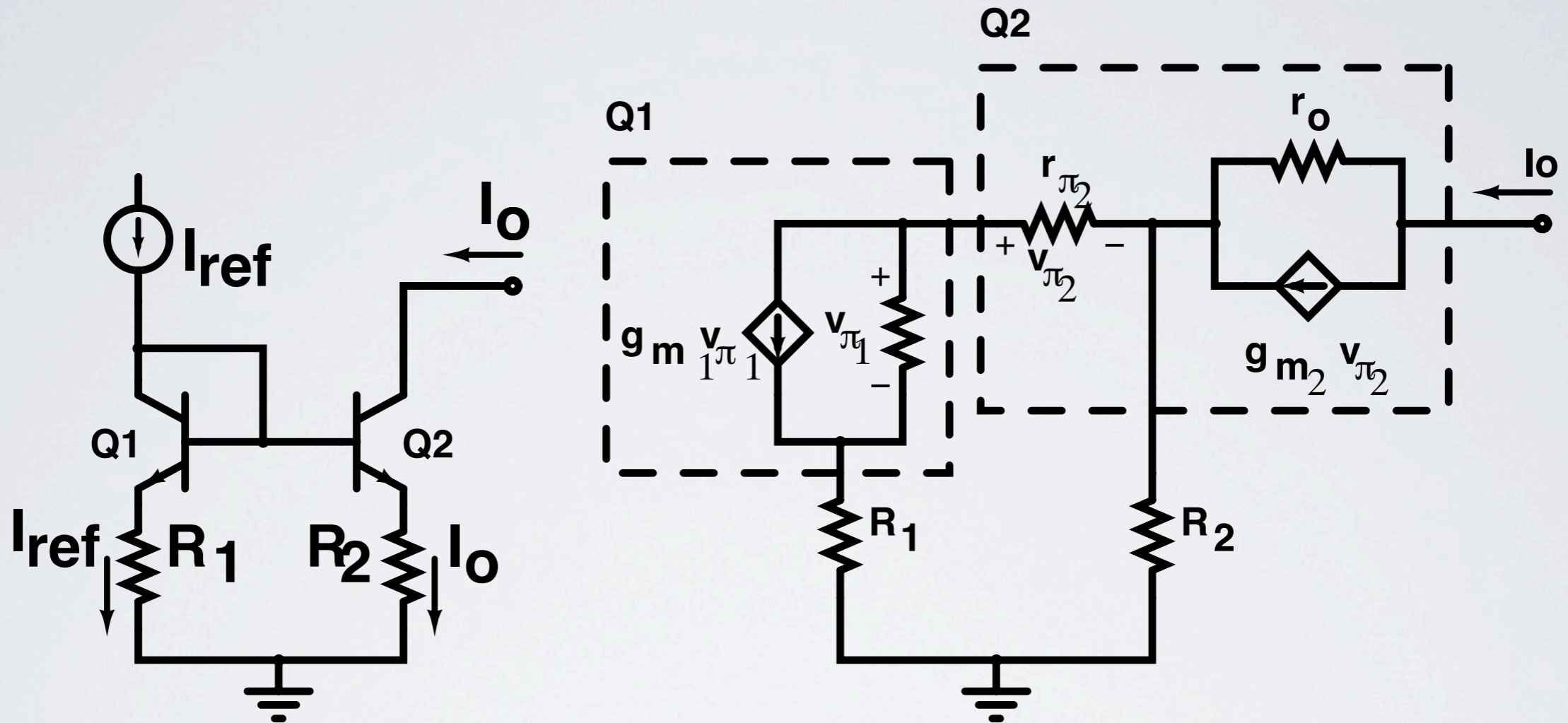



Mirror with emitter resistors


small-signal equivalent circuit

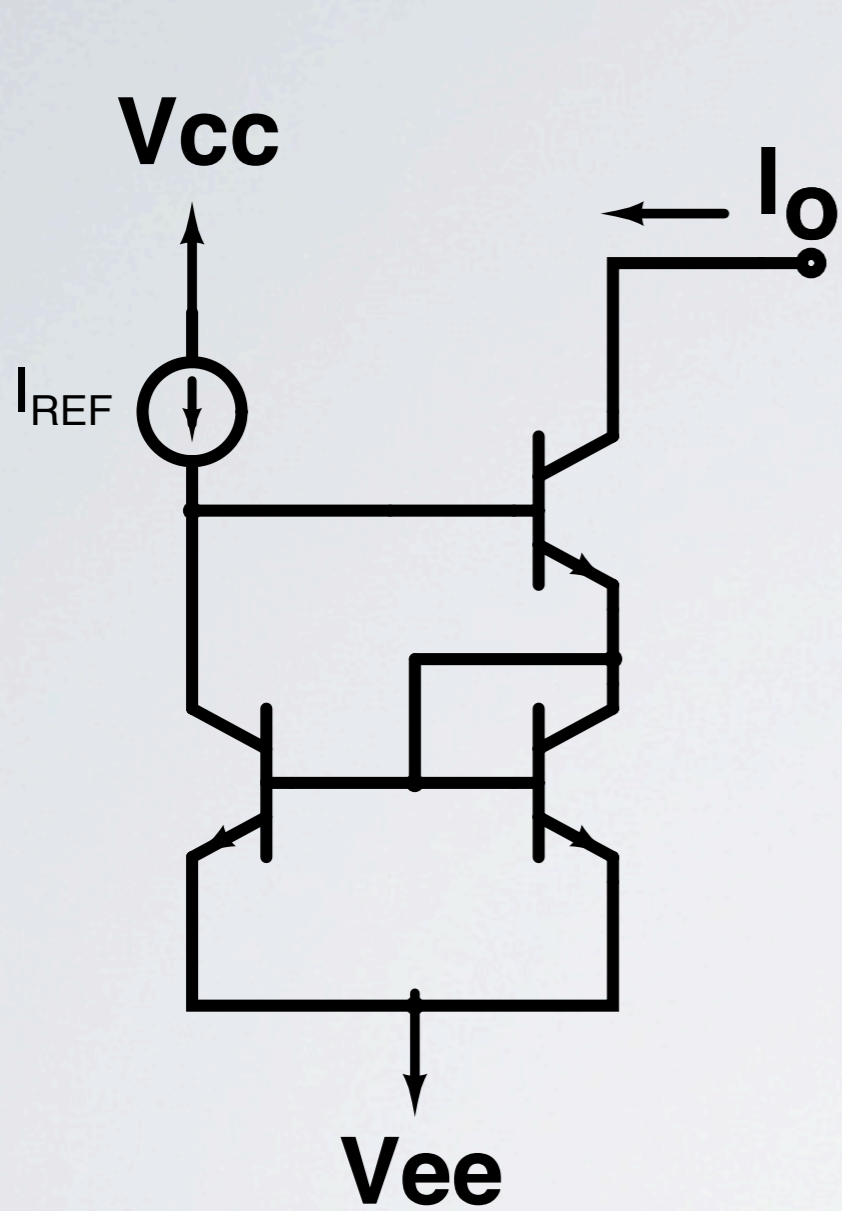

Wilson C.S.

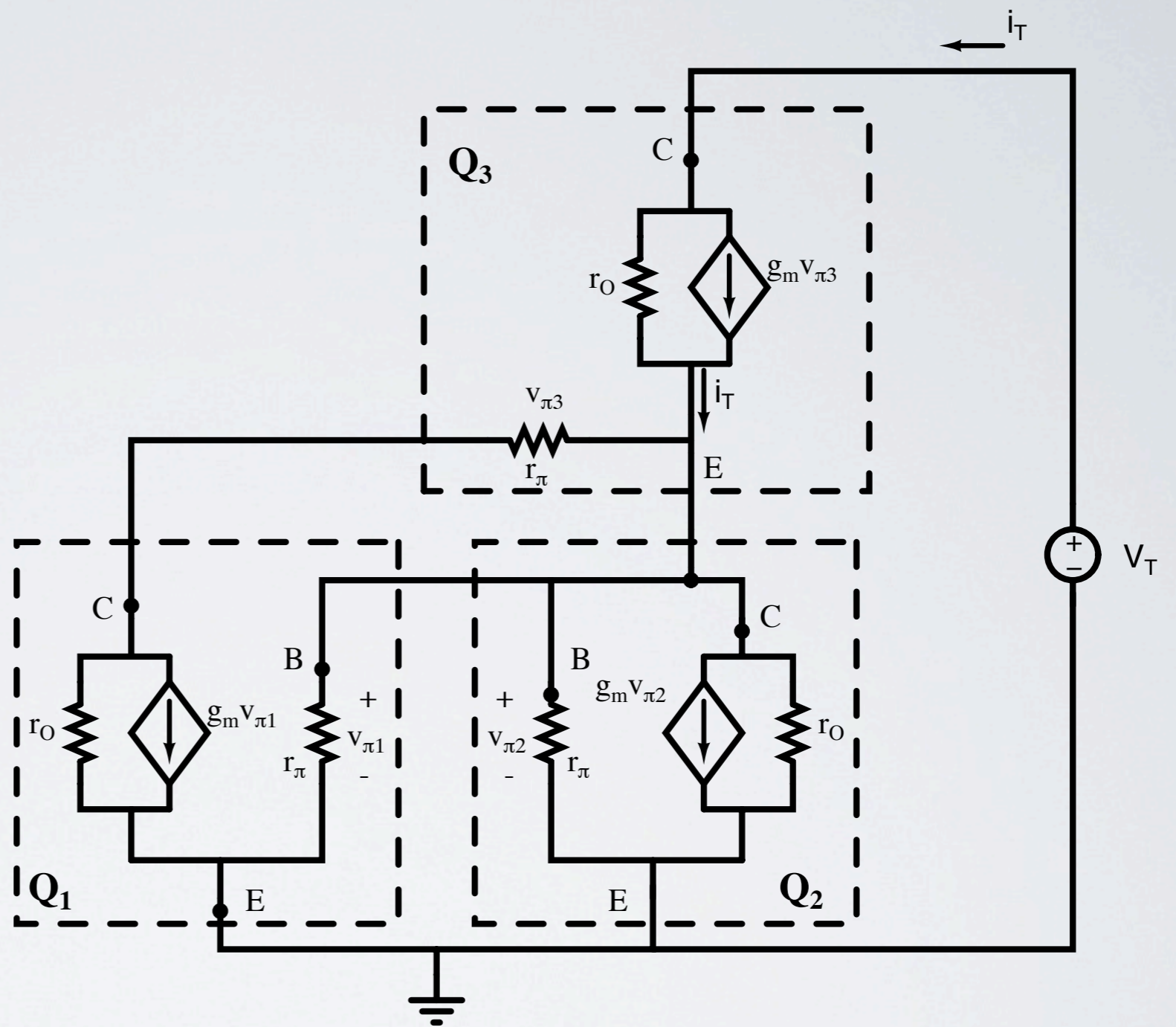

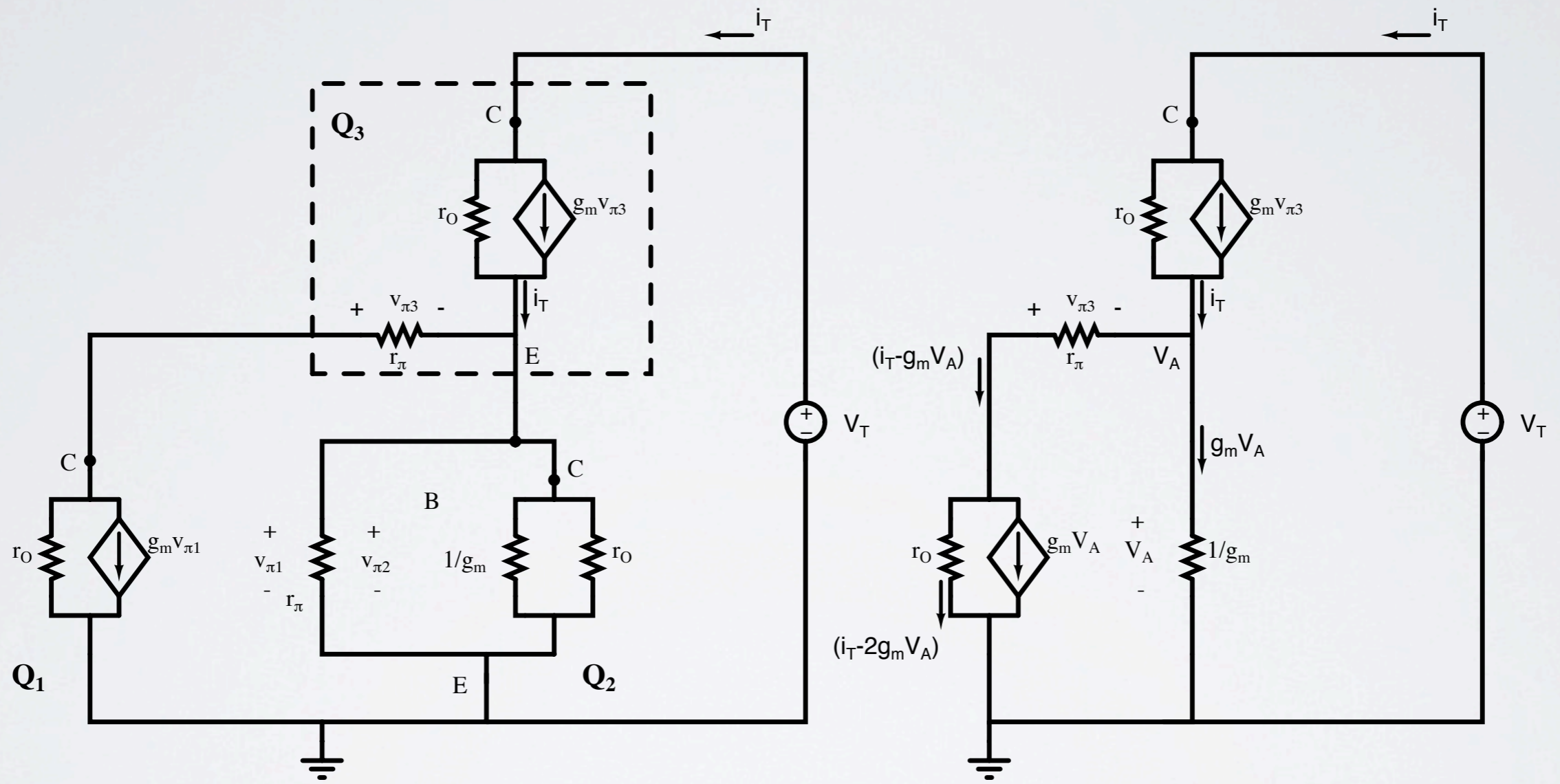

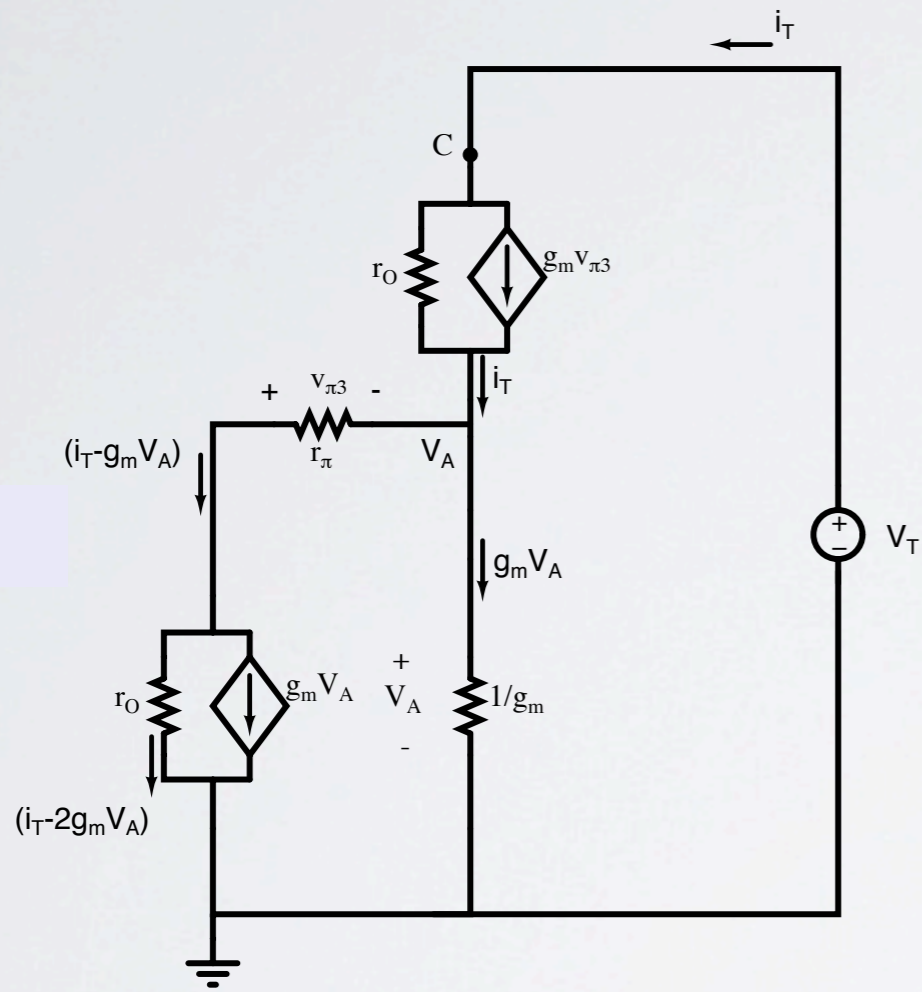

$$V_T = (i_T - g_m v_{\pi 3}) r_O + v_A$$

$$V_A = (i_T - g_m v_A) r_{\pi} + (i_T - 2g_m v_A) r_O$$

$$= \frac{r_{\pi} + r_O}{1 + \beta + 2g_m r_O} i_T \simeq \frac{1}{2g_m} i_T$$


$$v_{\pi,3} = -(i_T - g_m v_A) r_{\pi} = -i_T r_{\pi} + \beta v_A$$

$$= -i_T r_{\pi} + \beta \frac{1}{2g_m} i_T = i_T \frac{\beta - 2\beta}{2g_m} = -i_T \frac{\beta}{2g_m}$$

$$V_T = i_T r_O + i_T \frac{\beta g_m}{2g_m} r_O + \frac{1}{2g_m} i_T$$

$$R_{OUT} = \frac{V_T}{i_T} = r_O + \frac{\beta r_O}{2} + \frac{1}{2g_m} \simeq \boxed{\frac{\beta r_O}{2}}$$

Textbook approach

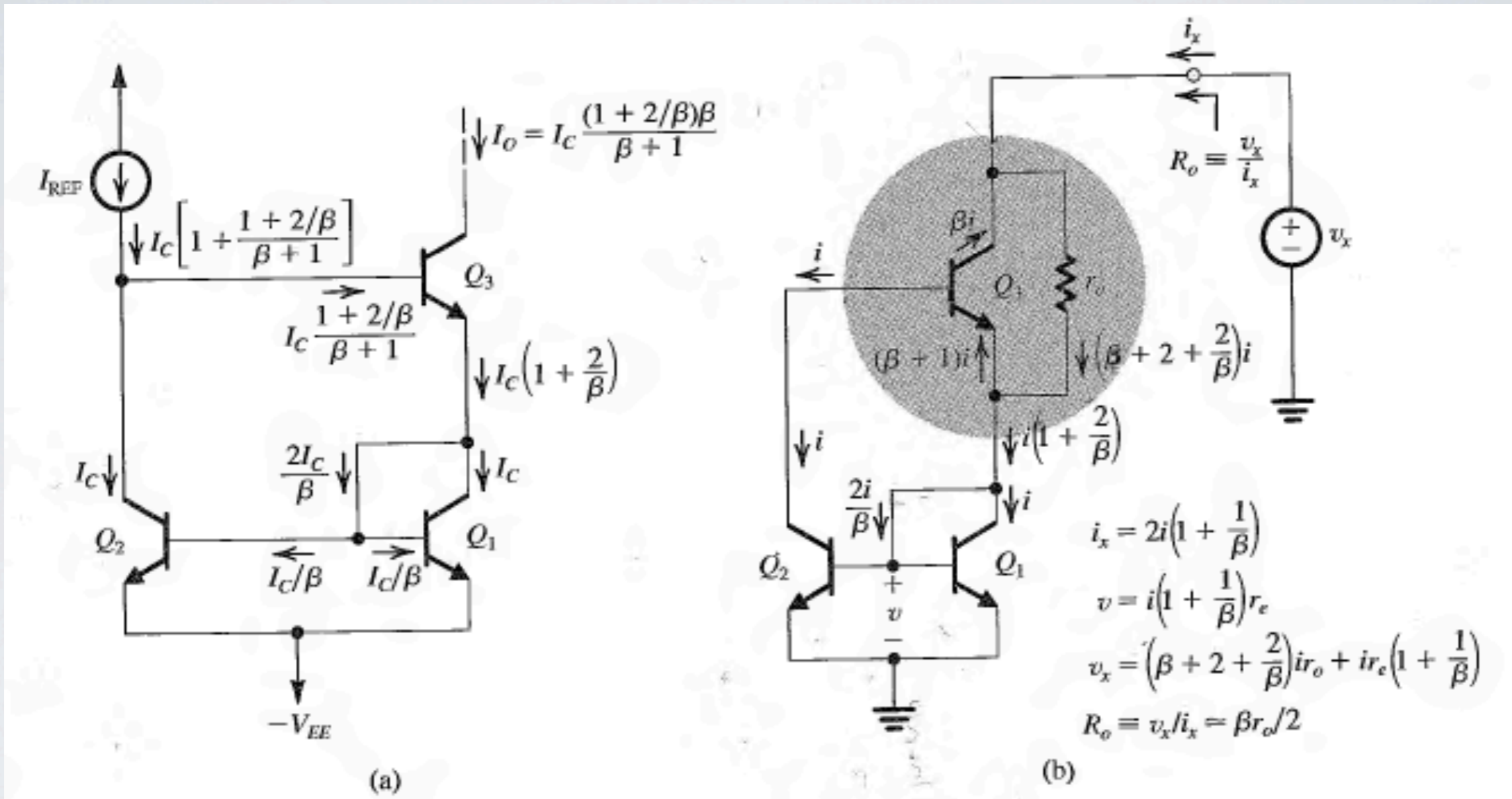

$$I_o = I_c \frac{(1 + 2/\beta)\beta}{\beta + 1}$$

$$I_{REF} \downarrow I_c \left[1 + \frac{1 + 2/\beta}{\beta + 1} \right]$$

$$I_c \frac{1 + 2/\beta}{\beta + 1}$$

$$\downarrow I_c \left(1 + \frac{2}{\beta} \right)$$

$$I_c \downarrow$$

$$\frac{2I_c}{\beta} \downarrow$$

$$\downarrow I_c$$

$$-V_{EE}$$

$$i_x$$

$$R_o \equiv \frac{v_x}{i_x}$$

$$v_x$$

$$i$$

$$\beta i$$

$$(\beta + 1)i \uparrow$$

$$\downarrow (\beta + 2 + \frac{2}{\beta})i$$

$$\downarrow i \left(1 + \frac{2}{\beta} \right)$$

$$\downarrow i$$

$$\frac{2i}{\beta} \downarrow$$

$$\downarrow i$$

$$v$$


$$i_x = 2i \left(1 + \frac{1}{\beta} \right)$$


$$v = i \left(1 + \frac{1}{\beta} \right) r_e$$

$$v_x = \left(\beta + 2 + \frac{2}{\beta} \right) i r_o + i r_e \left(1 + \frac{1}{\beta} \right)$$

$$R_o \equiv v_x / i_x = \beta r_o / 2$$



Cascode C.S.

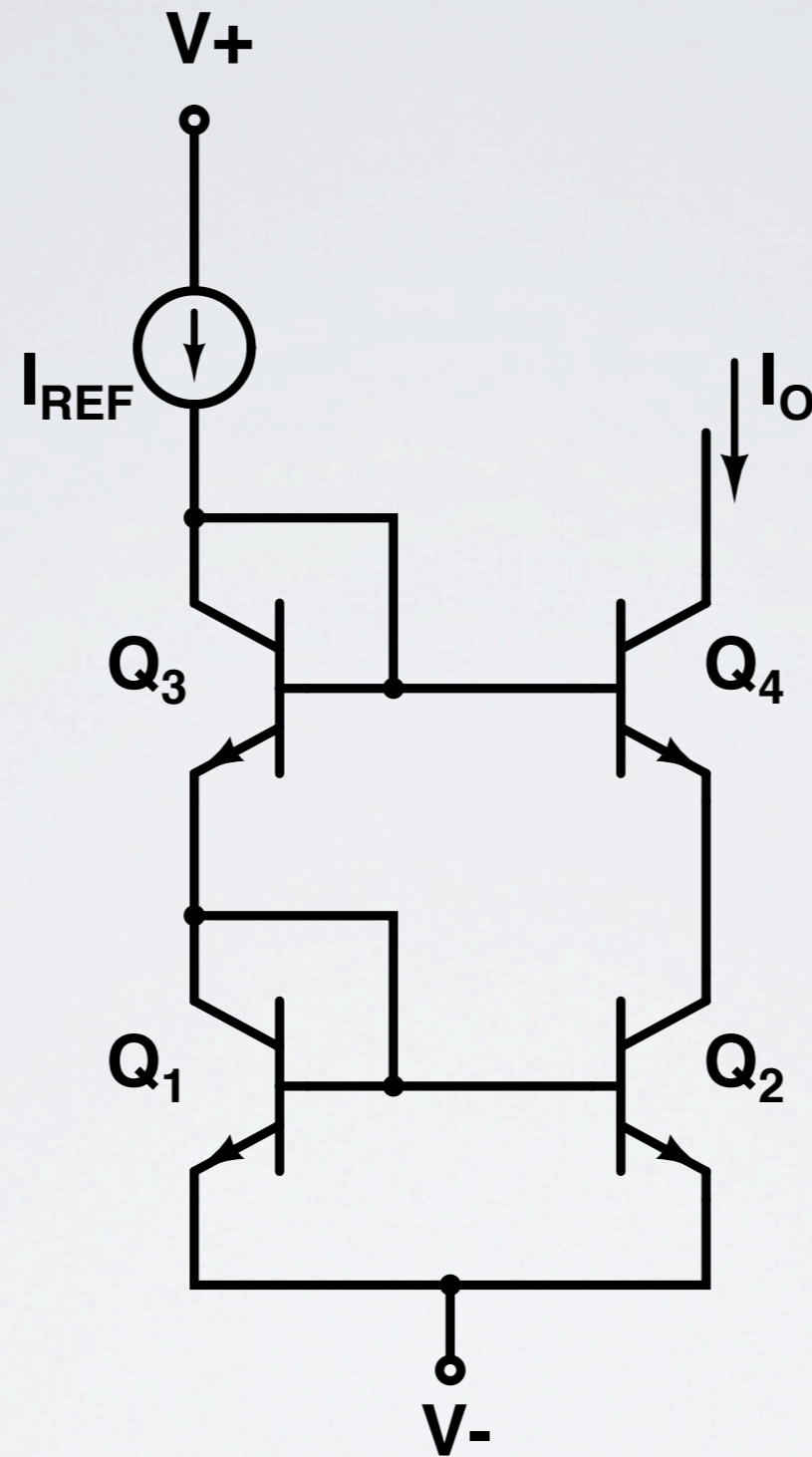

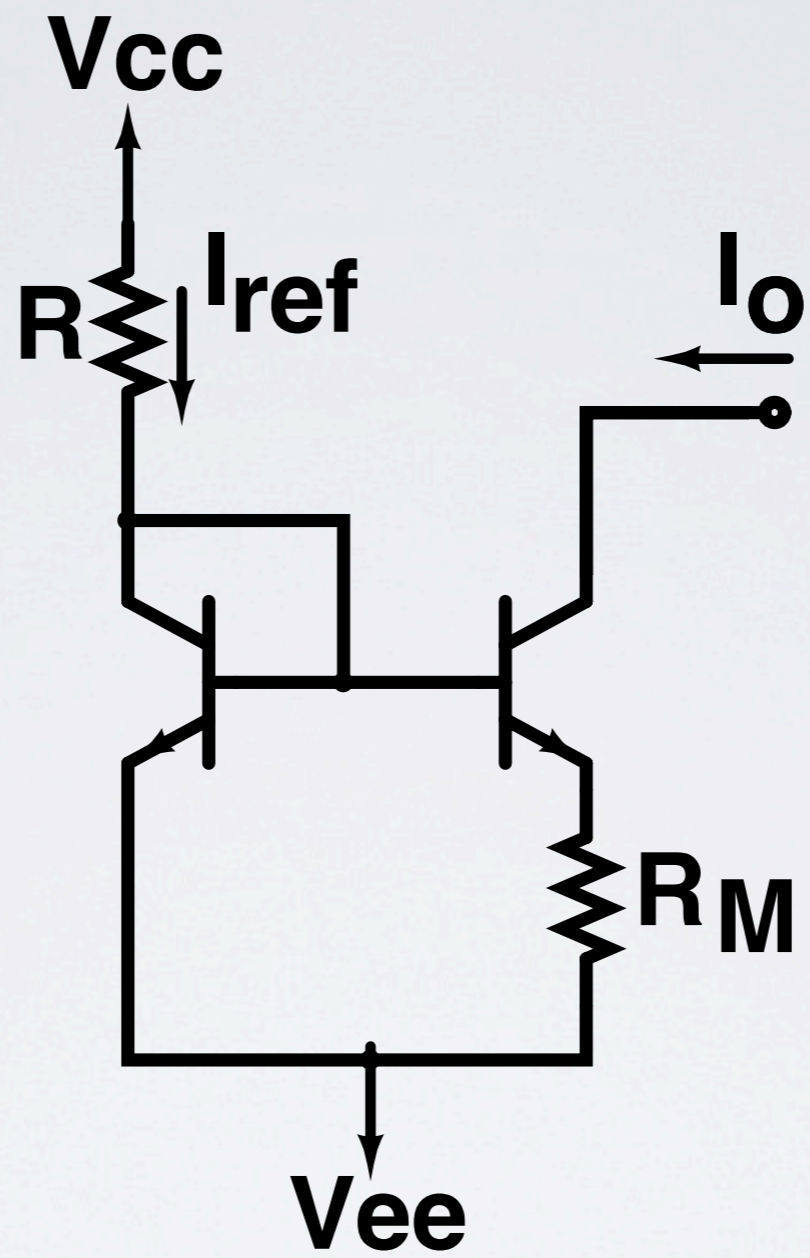


Widlar C.S.

MOSFET CSs

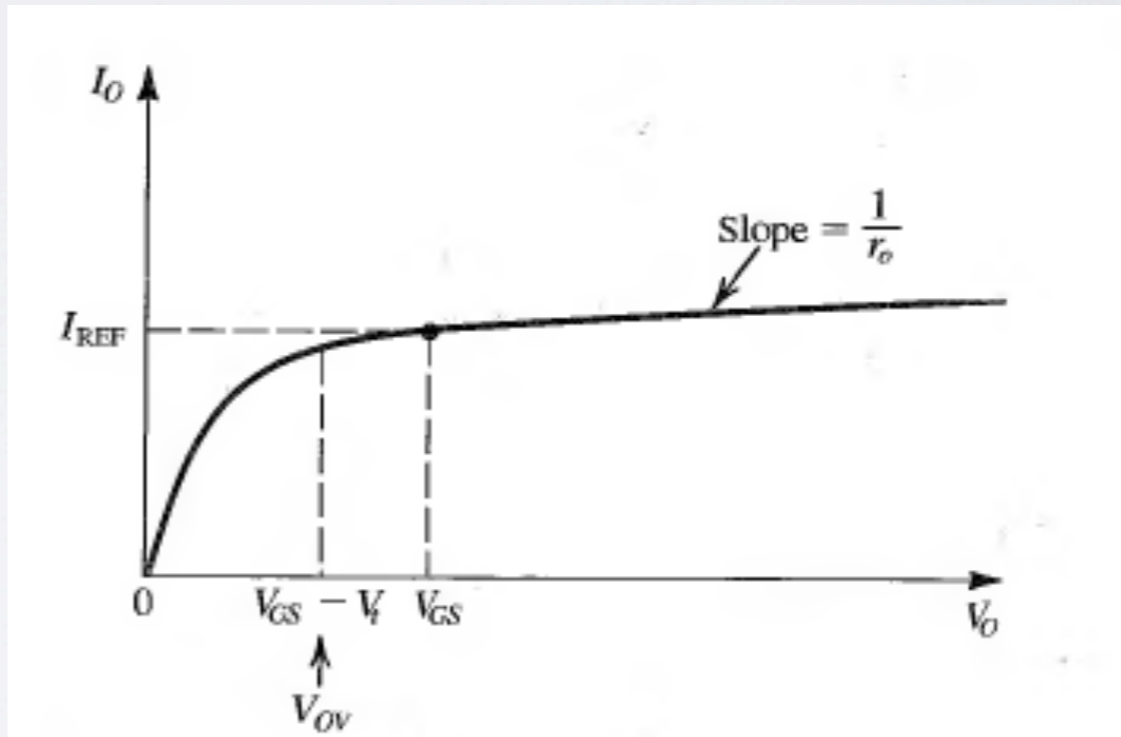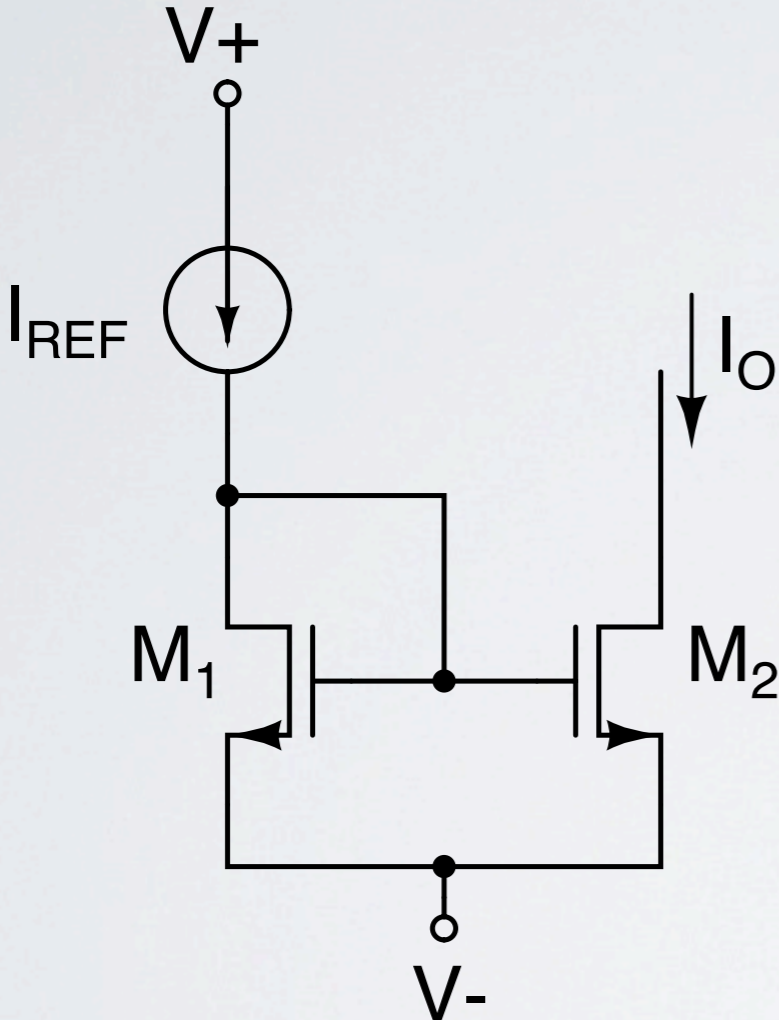

MOSFET CSs

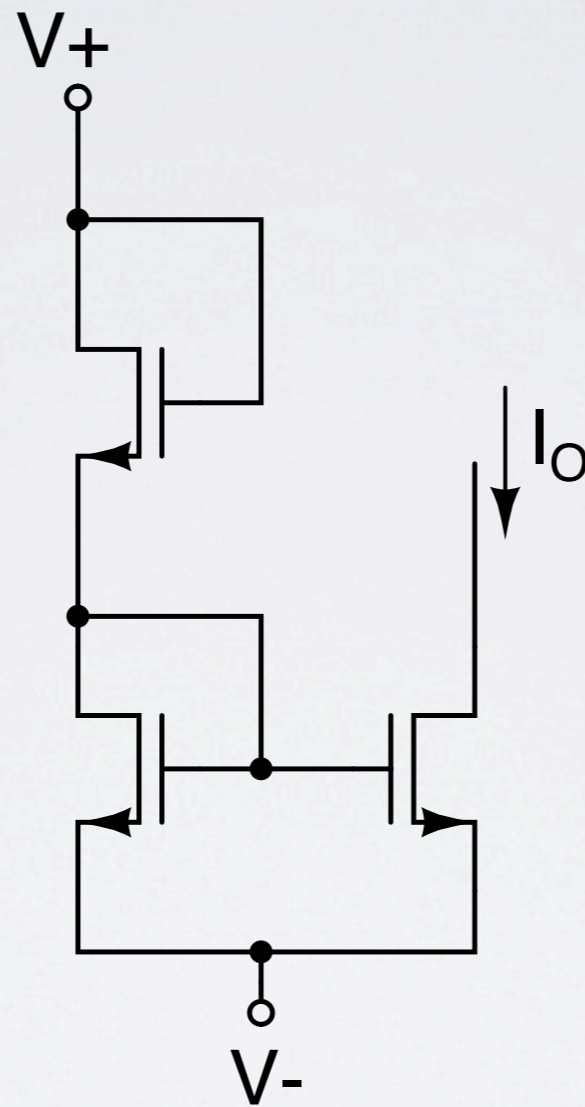

Active Loads

