

# OSCILLATORS

INEL 4202

# REVIEW

- Feedback method: Find  $\beta$ ,  $R_{11}$  and  $R_{22}$  and then use feedback formula  $A_f = A/(1 + A\beta)$  to find feedback gain.
- Stability: Loop gain  $A\beta$  determines stability of feedback amp.
  - $\Phi_M = 180^\circ - \sum \arctan(f_{0dB}/f_{p,i})$  :  $f_{0dB} = f$  at which  $|T|=1$  V/V
  - gain margin =  $-|T(f_{-180^\circ})|_{dB}$  :  $f_{-180^\circ} = f$  at which  $\Phi = -180^\circ$
  - $|T|_{dB} = |A\beta|_{dB} = |A|_{dB} - |1/\beta|_{dB}$  : can be subtracted graphically
  - graphical/approximate method using magnitude bode plot and phase equation
  - exact method using magnitude and phase equations
  - Phase equation: phase (at freq.  $f$ ) =  $\Phi = - \sum \arctan(f/f_{p,i})$  ; sum is over all poles at freqs  $f_{p,i}$ .



$$A_{dB} = 20 \log A$$

$$\frac{A_0}{1 + j \frac{f}{f_p}}$$

| $f/f_p$ | $\phi$       |
|---------|--------------|
| 0.1     | $5.7^\circ$  |
| 1       | $45^\circ$   |
| 10      | $84.3^\circ$ |

1 decada =  $10 \cdot \text{frec.}$

1 octava =  $2 \cdot \text{frec}$

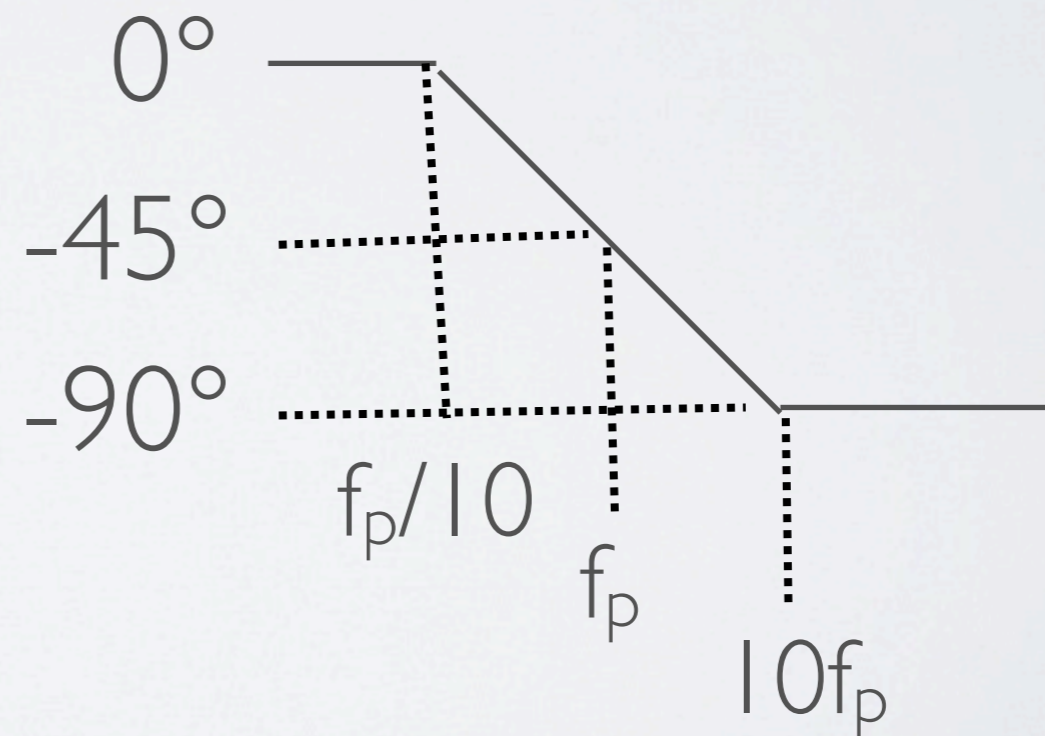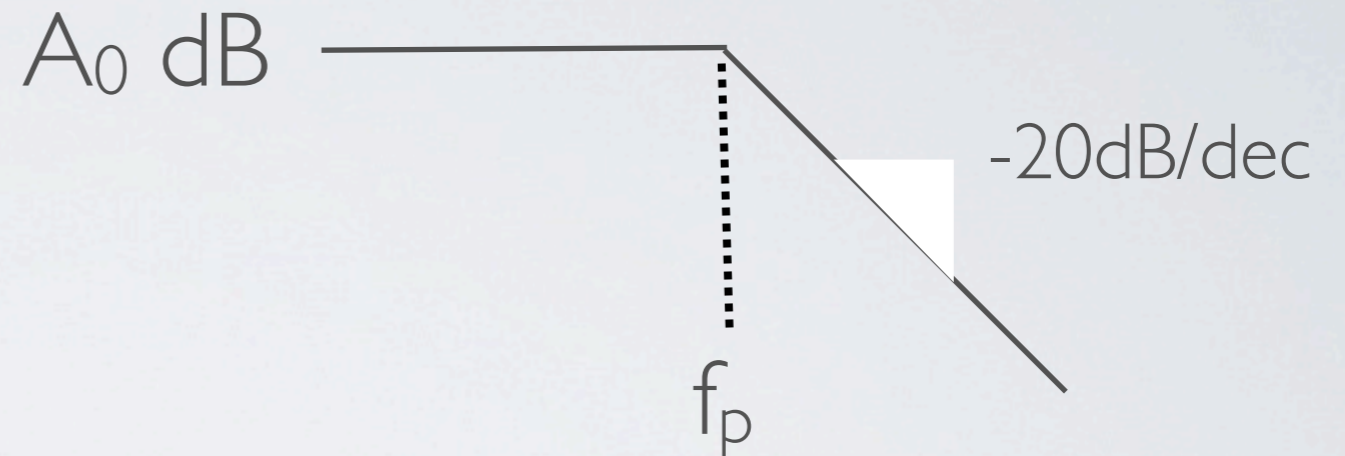

## Algebraic or exact method


$$|A(f)| = \frac{A_0}{\prod_{\forall i} \sqrt{1 + \left(\frac{f}{f_{p,i}}\right)^2}}$$

$$\phi(f) = - \sum_{\forall i} \tan^{-1} \left( \frac{f}{f_{p,i}} \right)$$


The response of an op amp can be approximated with a dominant pole frequency  $f_1$  and a high-frequency pole  $f_2$  to account for higher order roots. (a) Assuming  $a_0 = 10^5$  V/V,  $f_1 = 10$ Hz, and  $\beta = 1$  V/V, find the phase margin  $\phi_m$  if  $f_2 = 1$ MHz. (b) Find  $f_2$  for  $\phi_m = 45^\circ$  and for  $\phi_m = 60^\circ$ .
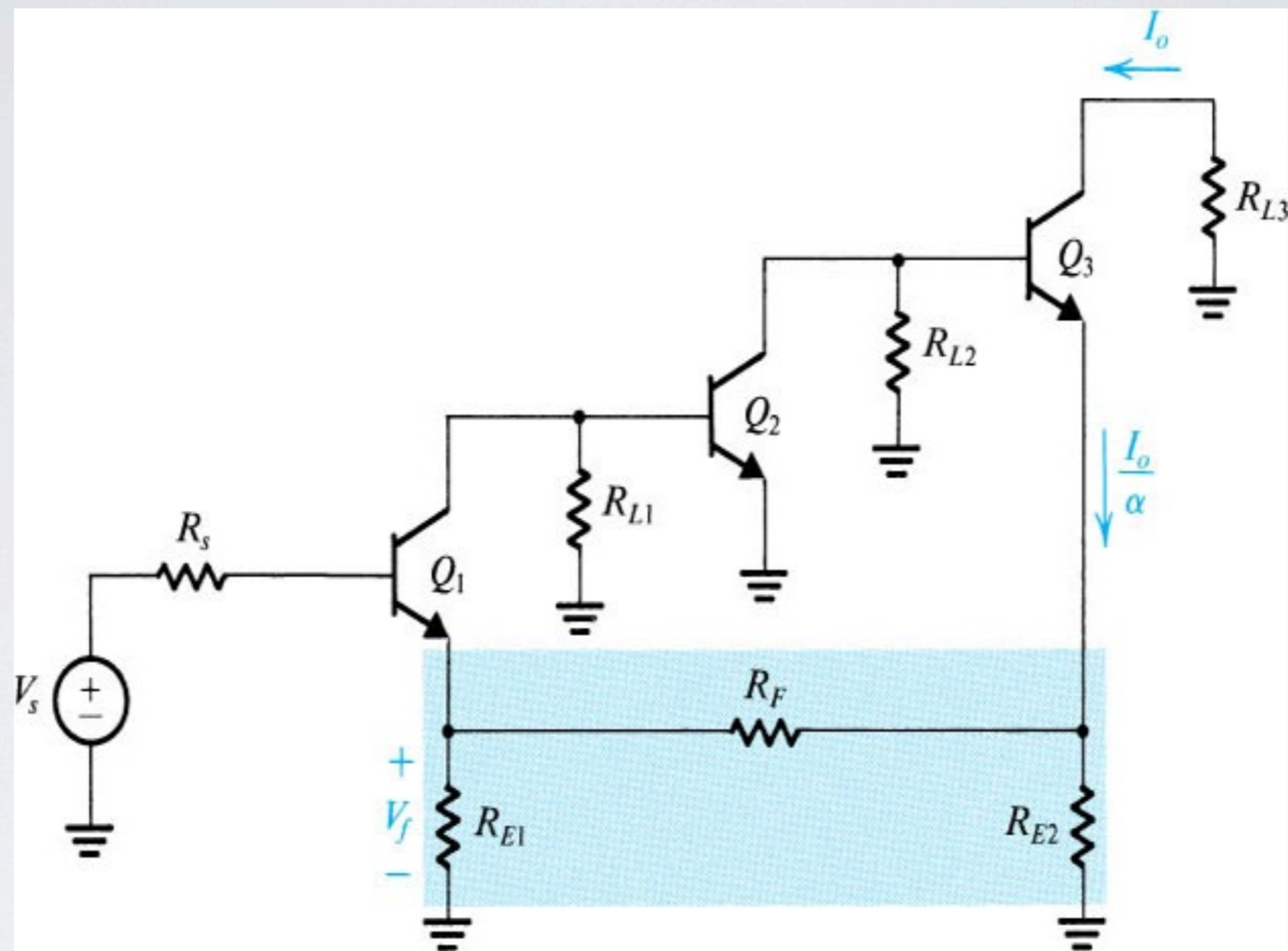
## Finding $A\beta$ by opening the loop

- Given a circuit with feedback, you can calculate the loop gain  $T=A\beta(s)$  by
  - finding  $A$  and  $\beta$  and multiplying, or
  - opening the loop at a convenient point, and
    - take care of including loading effects, and
    - apply a test source  $V_t$ , calculate the return's output voltage  $V_r$  and find  $T = -V_r/V_t$
    - Alternatively, a current test source  $I_t$  may be applied, a return output current calculated to find  $T = -I_r/I_t$



# 1 Barkhausen Criterion

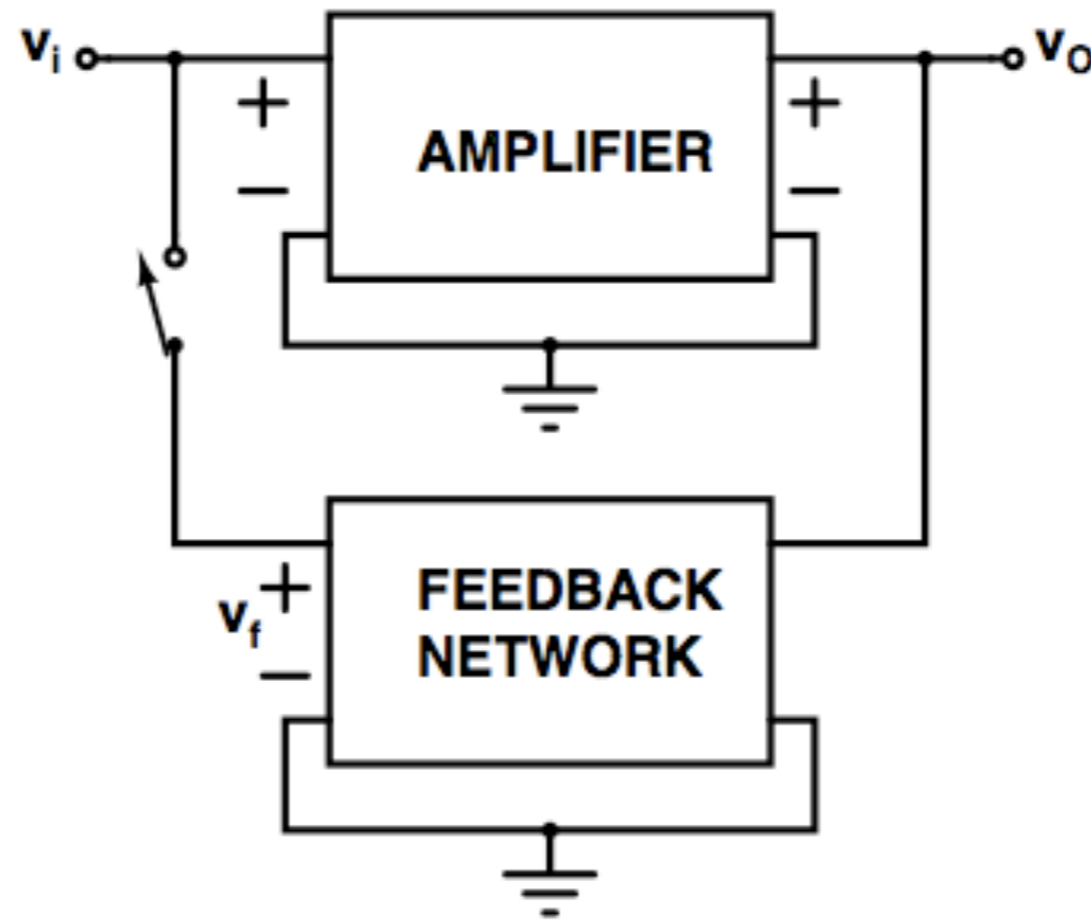

If the loop gain  $L = A(\omega)\beta(\omega)$  is real and larger than one at a frequency  $\omega_0$ , the circuit will produce a sinusoidal output voltage with frequency  $\omega_0$ .


$$\frac{v_f}{v_i} = A(\omega_0)\beta(\omega_0) = M(\omega_0)\angle\phi(\omega_0) = +1$$

This means that the magnitude  $M(\omega_0)$  must be unity and the phase angle  $\angle\phi(\omega_0) = 0^\circ$ .


Strategy:

- find loop gain  $L = A(\omega)\beta(\omega)$
- find frequency  $\omega_0$  at which the loop gain is real; the imaginary part is zero
- determine the amplifier gain required to make the loop gain larger than 1
- the criterion must be satisfied at a single, well defined  $\omega_0$
- the amplifier gain  $A$  will depend on the input impedance of the feedback network, unless the amplifier's output impedance is zero (i.e. op amps)


# Phase-shift oscillator

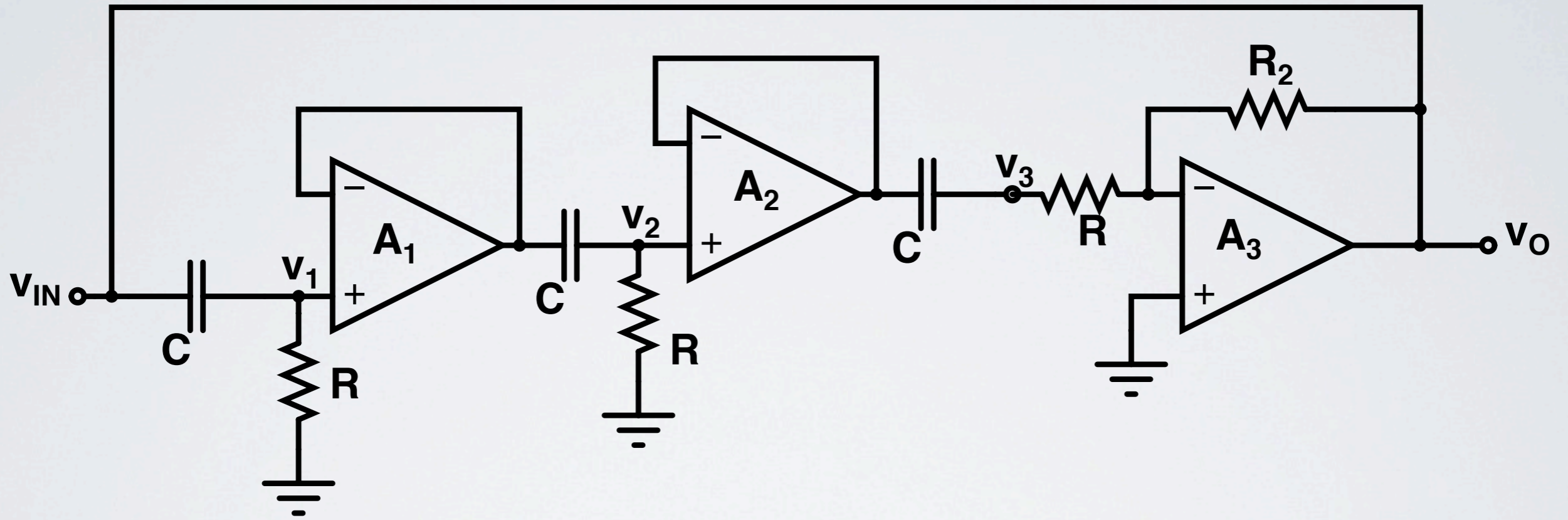


# Wein-Bridge Oscillator

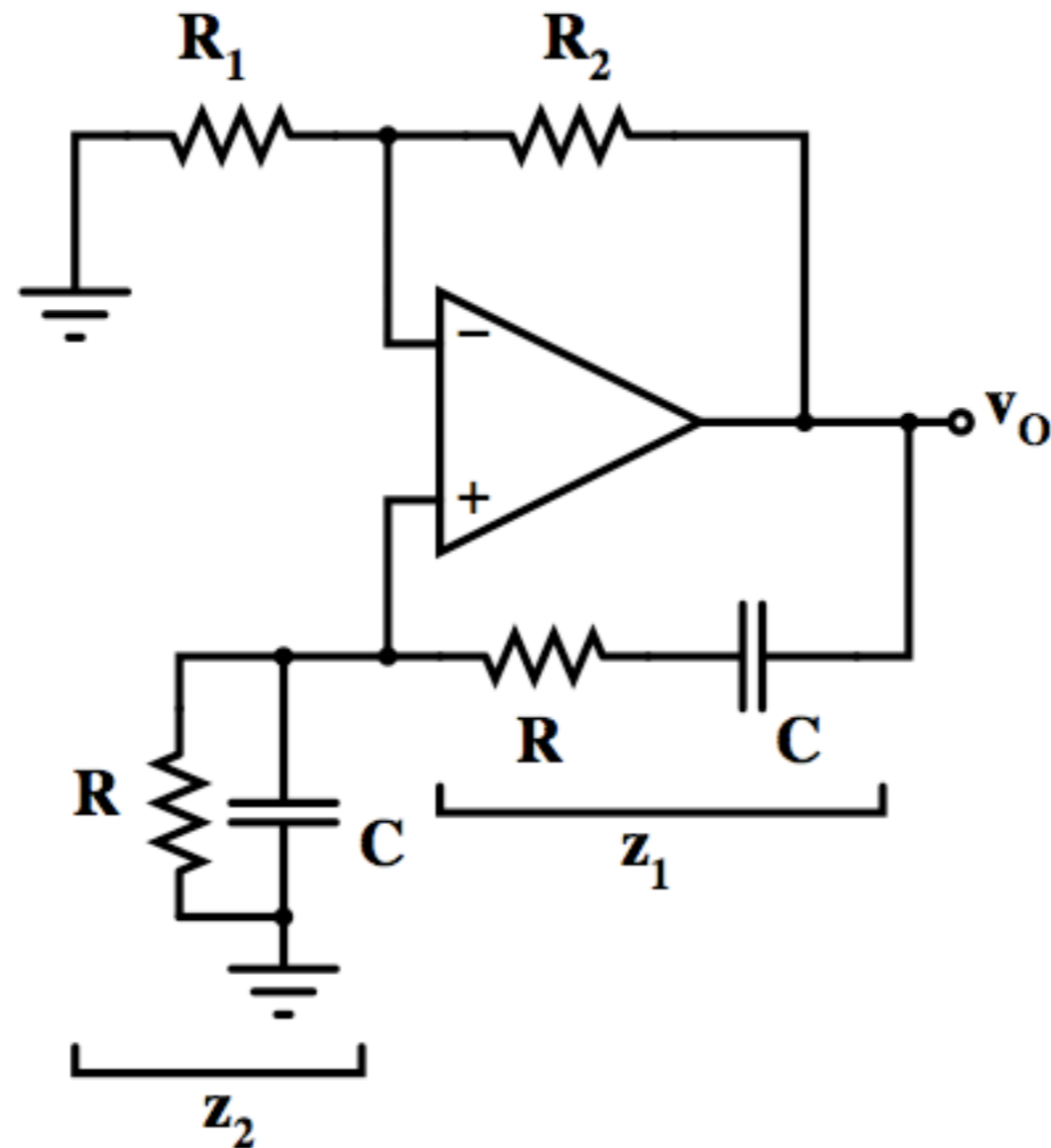

# LC Oscillators: Colpitts Oscillator

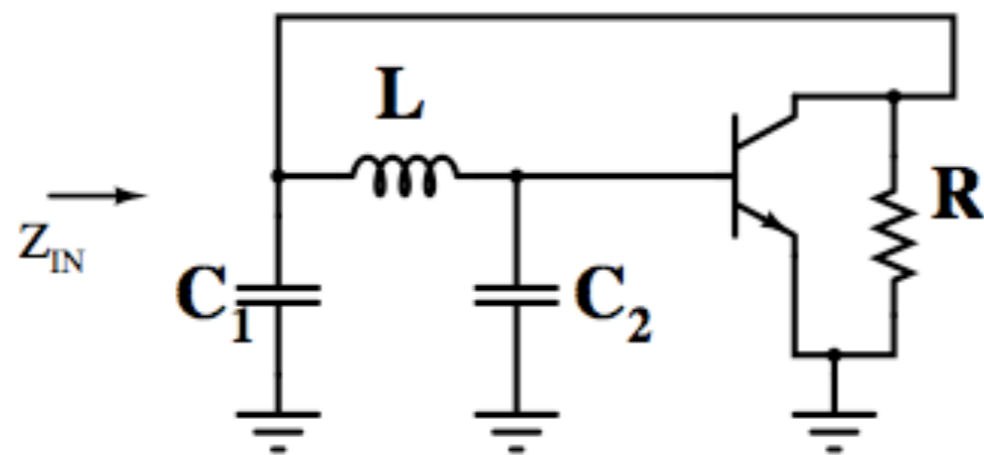


**Colpitts Oscillator**

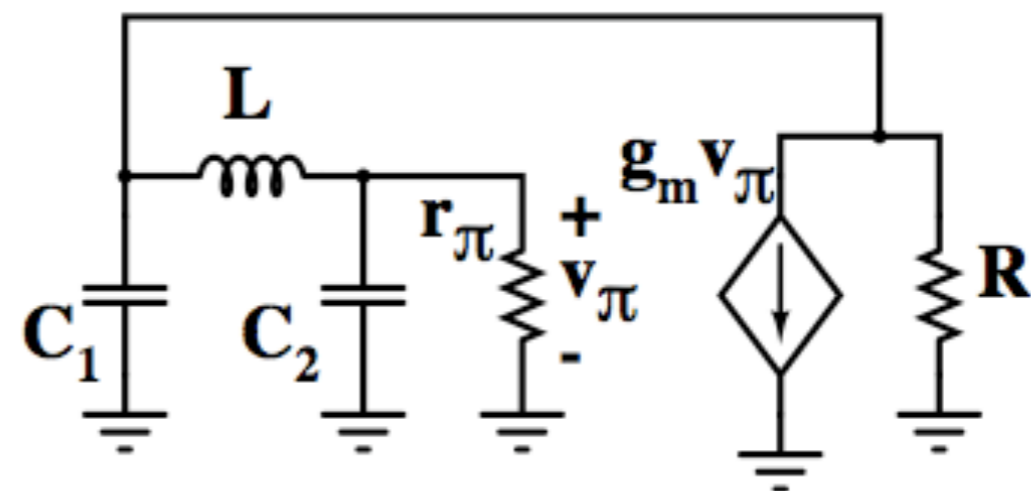



**Equivalent Circuit**

# Hartley Oscillator

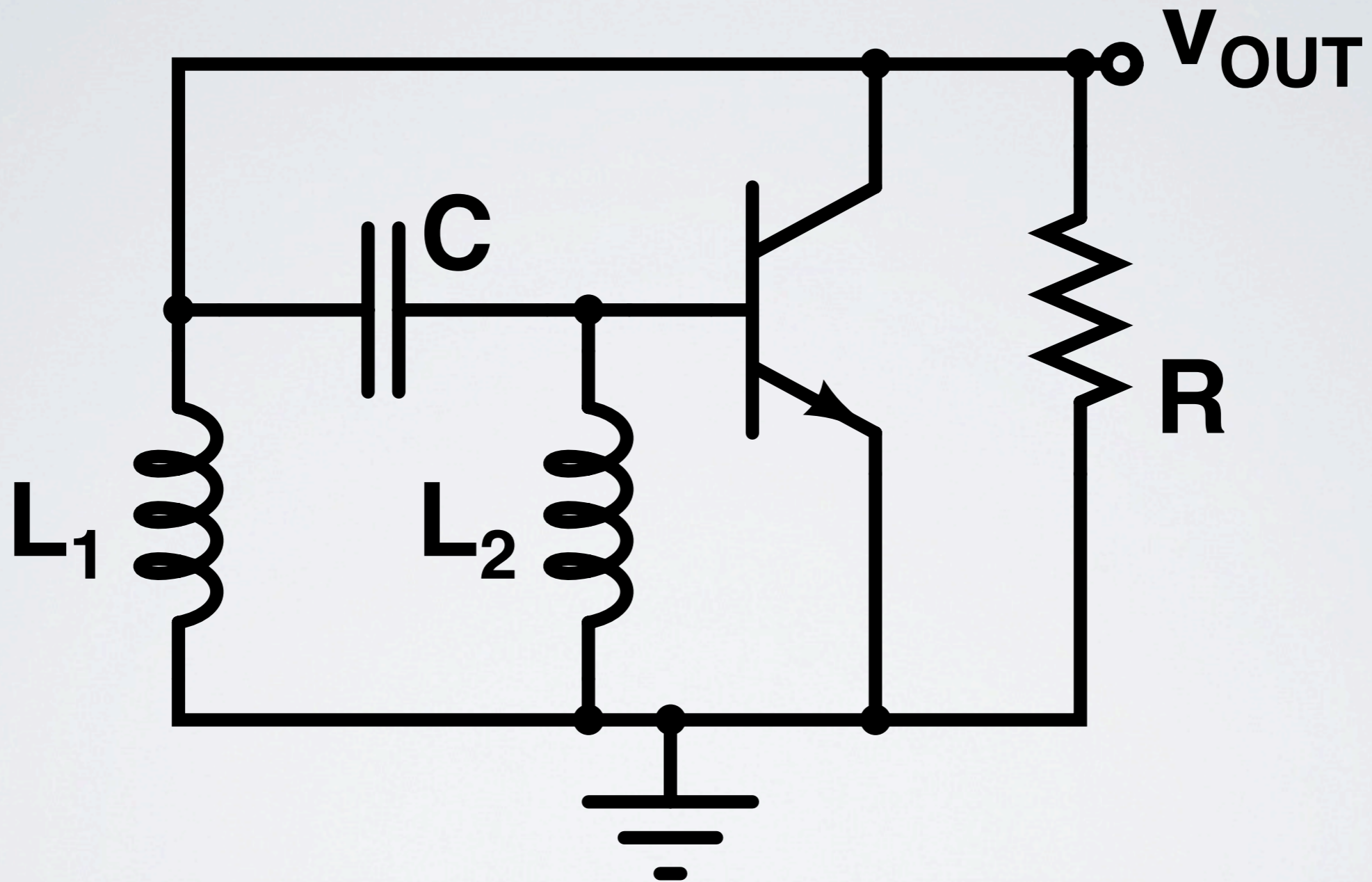


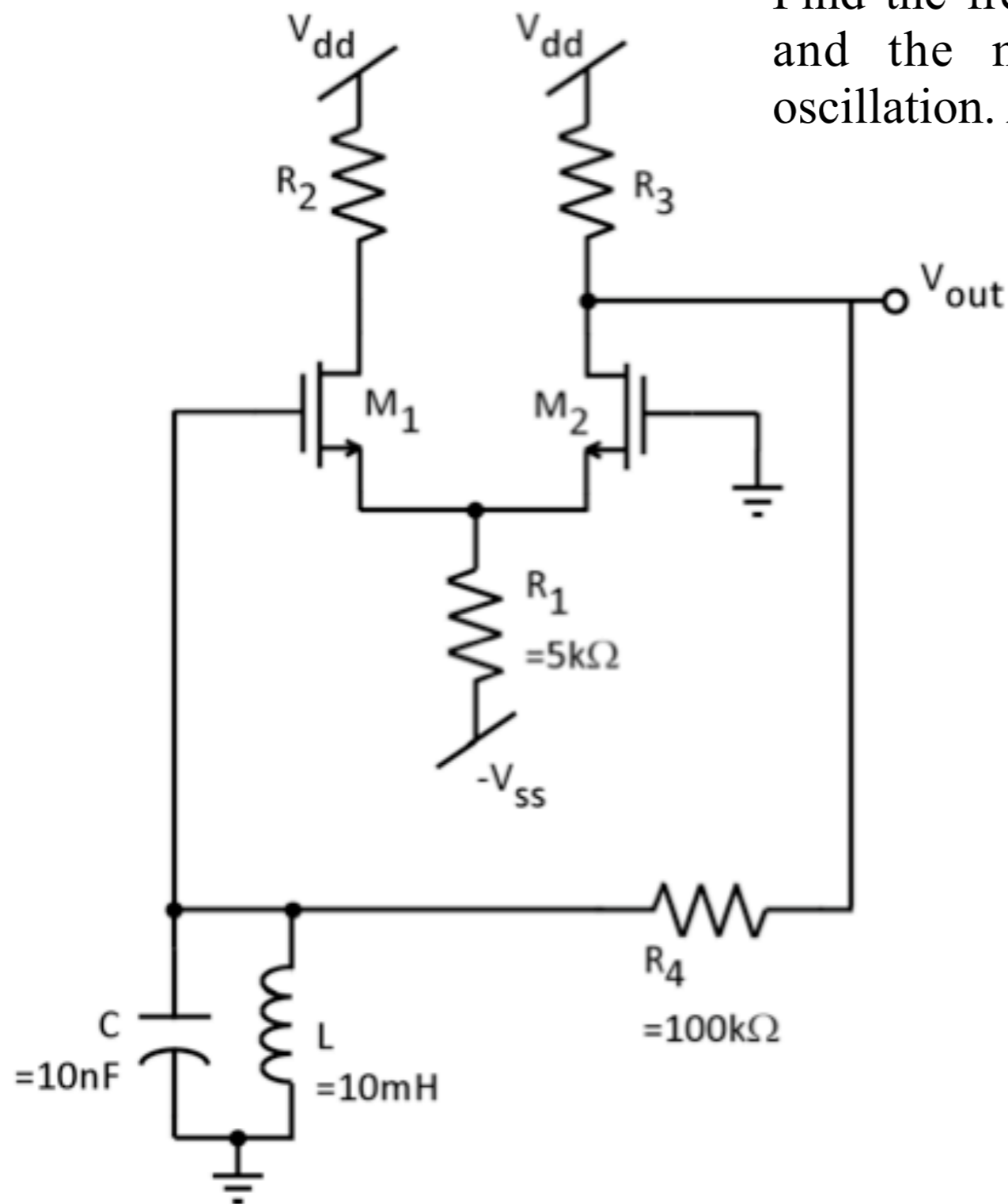Find the frequency of oscillation  $\omega_0$  of this circuit, and the minimum value of  $R_3$  required for oscillation. Assume transistor  $g_m=45\text{mS}$  and  $r_{ds} = \infty$ .




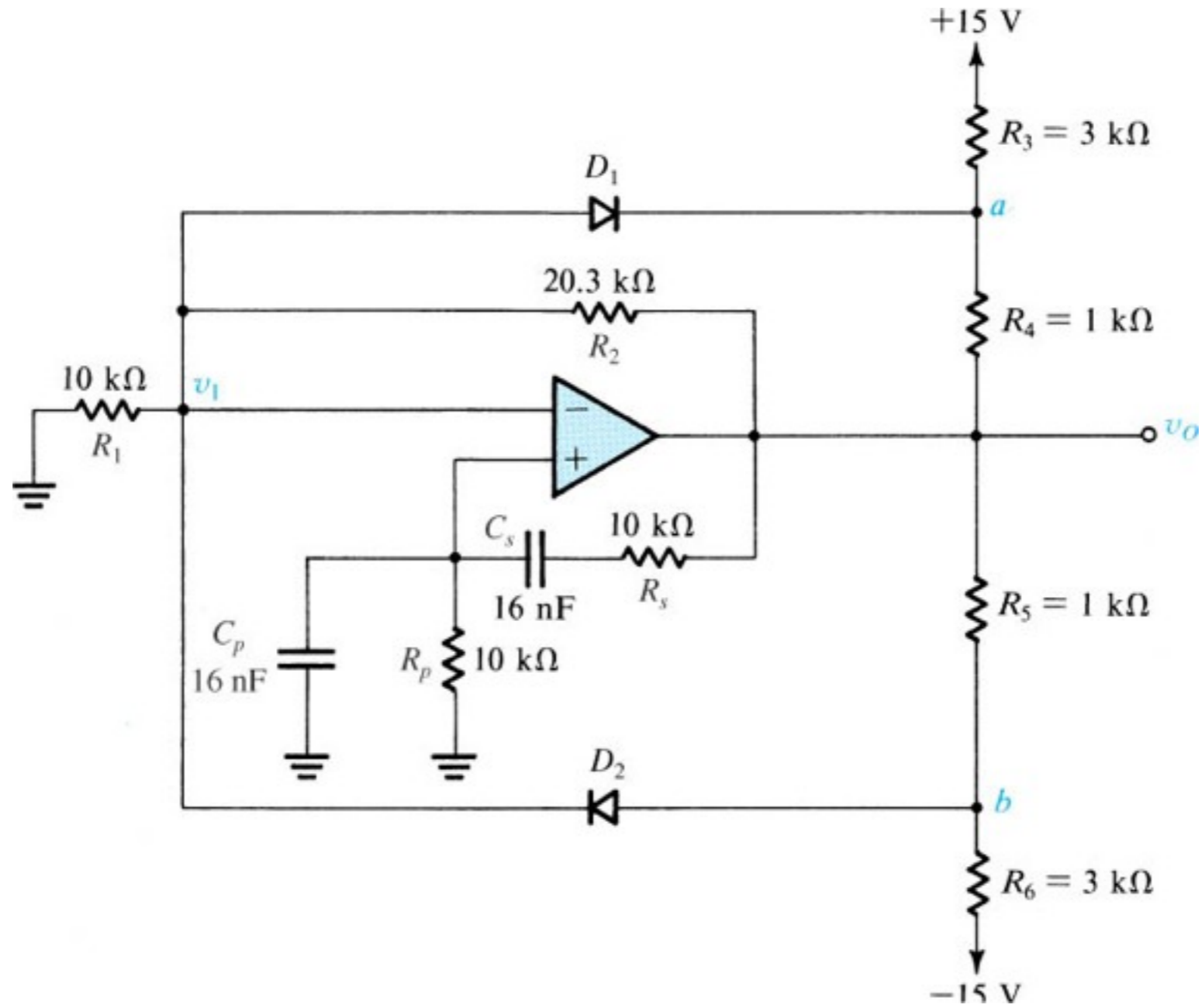

**Figure 13.5** A Wien-bridge oscillator with a limiter used for amplitude control.

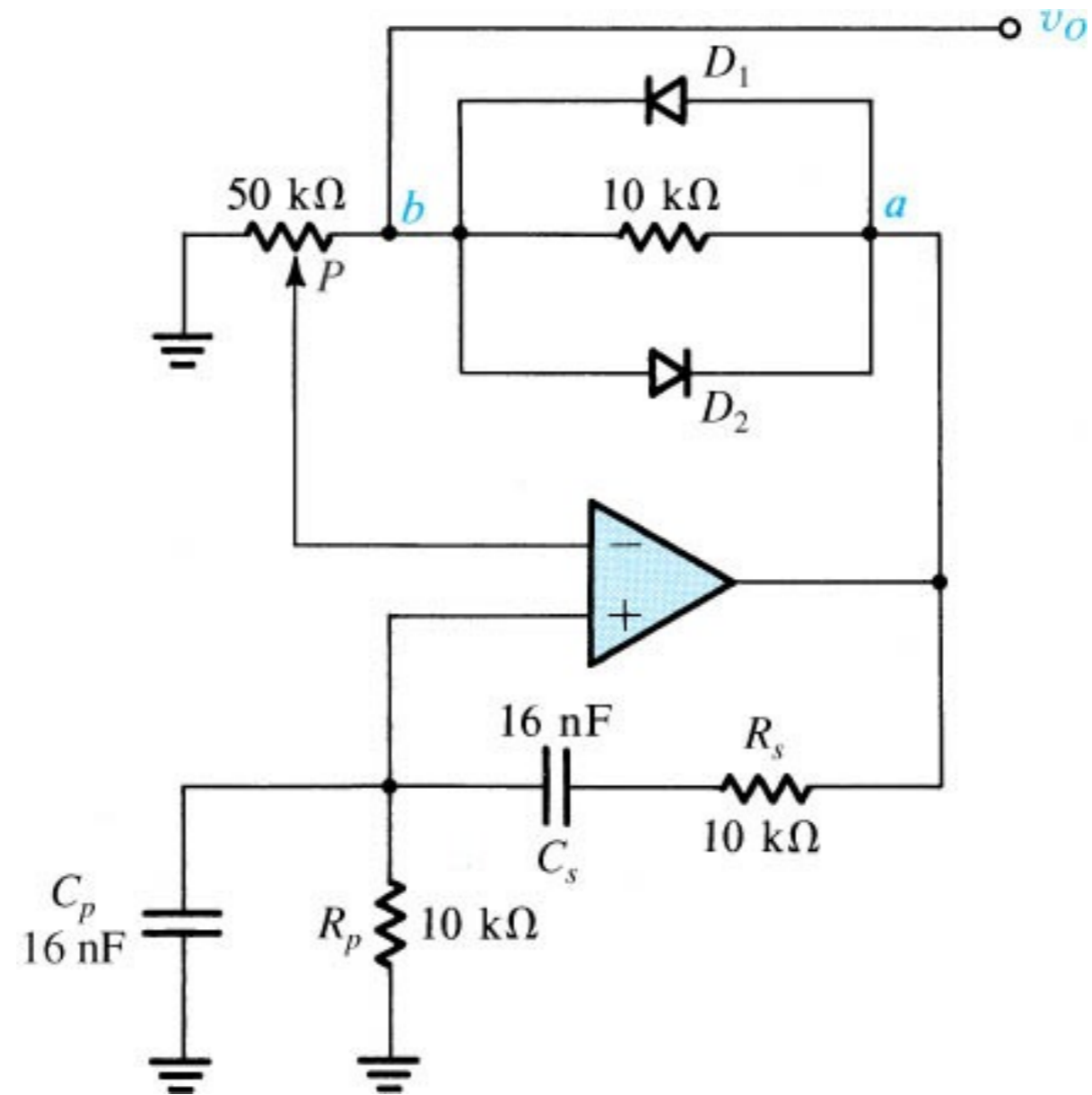

**Figure 13.6** A Wien-bridge oscillator with an alternative method for amplitude stabilization.

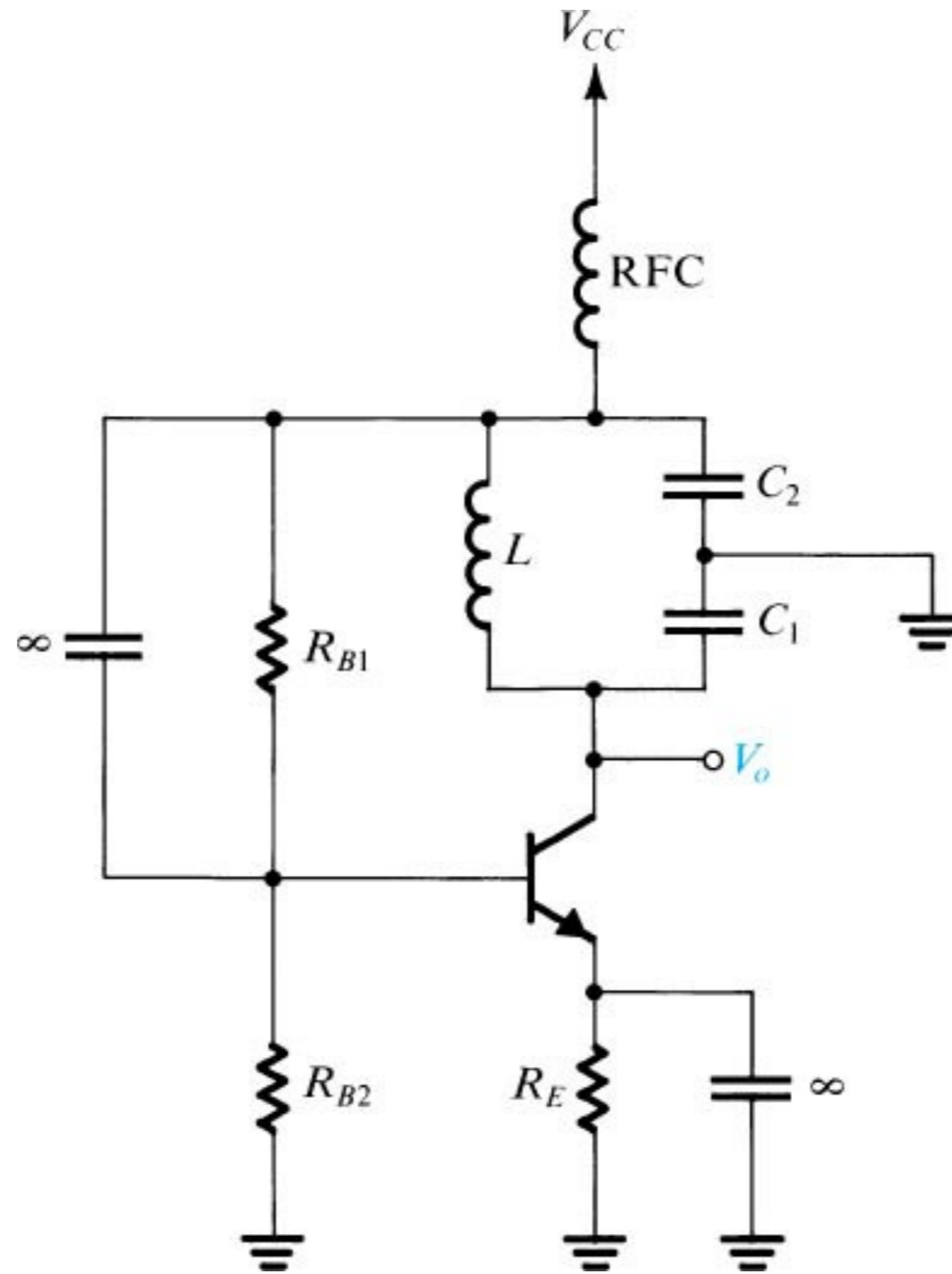

**Figure 13.14** Complete circuit for a Colpitts oscillator.

**13.13** For the circuit in Fig. P13.13 find  $L(s)$ ,  $L(j\omega)$ , the frequency for zero loop phase, and  $R_2/R_1$  for oscillation.

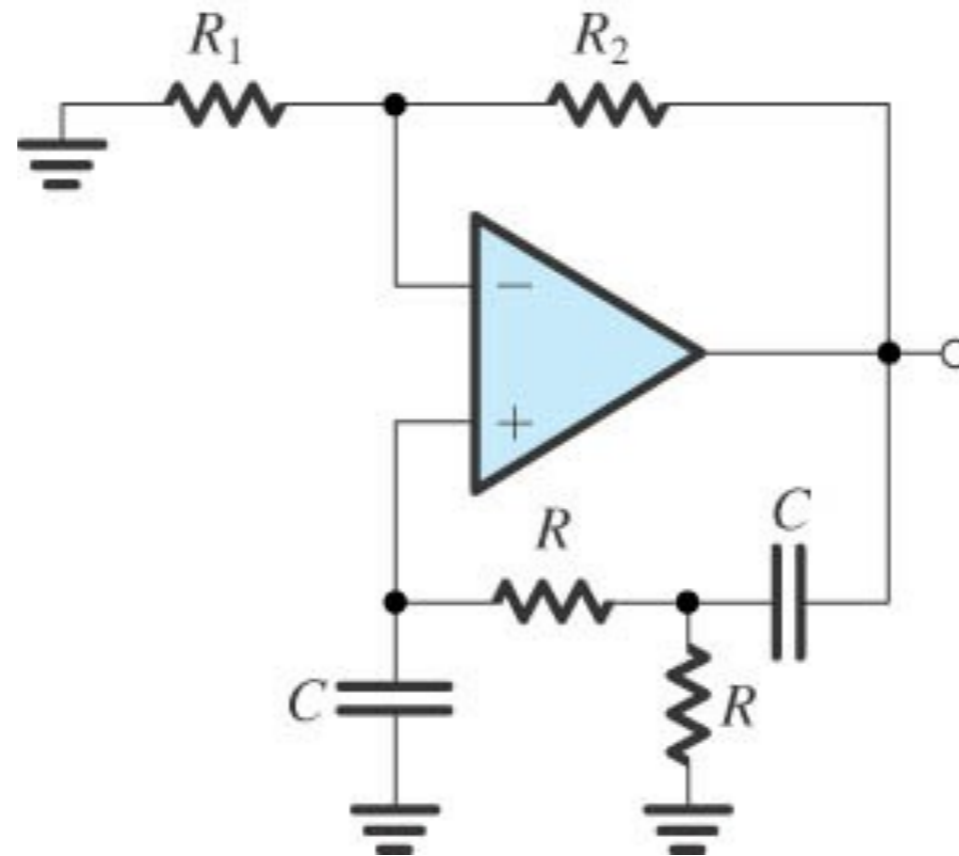


Figure P13.13

**\*\*13.21** Figure P13.21 shows four oscillator circuits of the Colpitts type, complete with bias detail. For each circuit, derive an equation governing circuit operation, and find the frequency of oscillation and the gain condition that ensures that oscillations start.

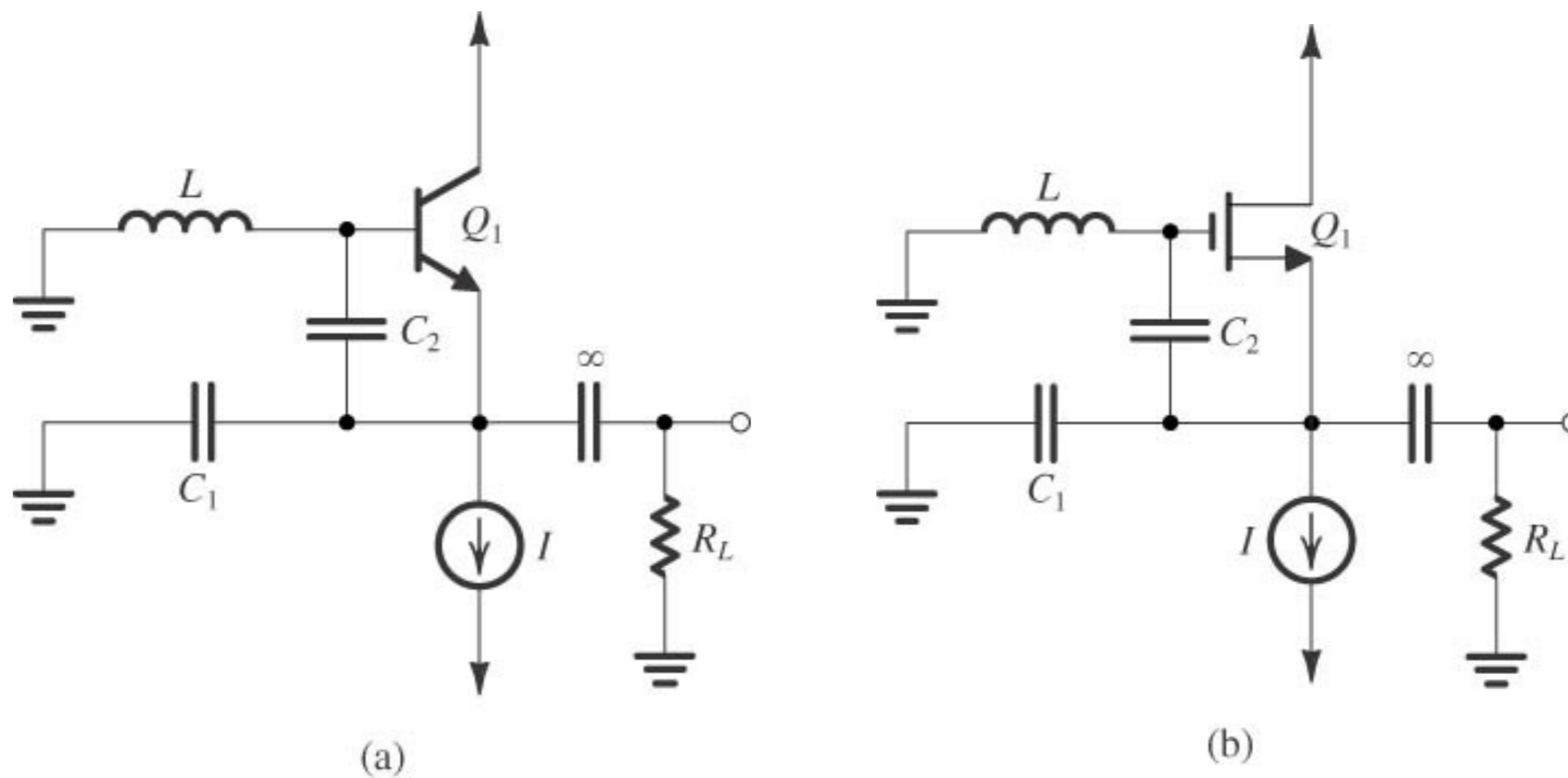


Figure P13.21

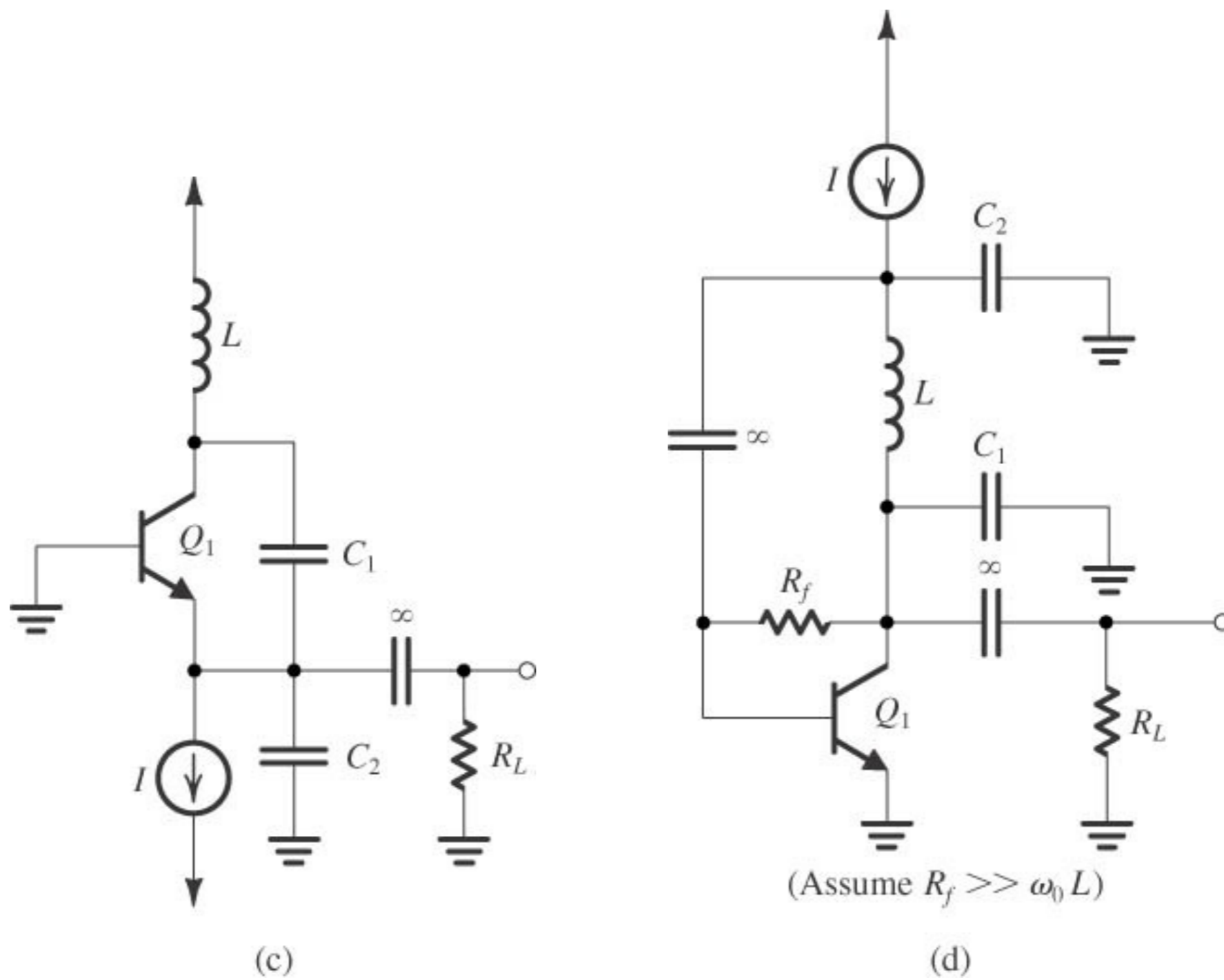


Figure P13.21 (Continued)

**\*\*13.22** Consider the oscillator circuit in Fig. P13.22, and assume for simplicity that  $\beta = \infty$ .

(a) Find the frequency of oscillation and the minimum value of  $R_C$  (in terms of the bias current  $I$ ) for oscillation to start.

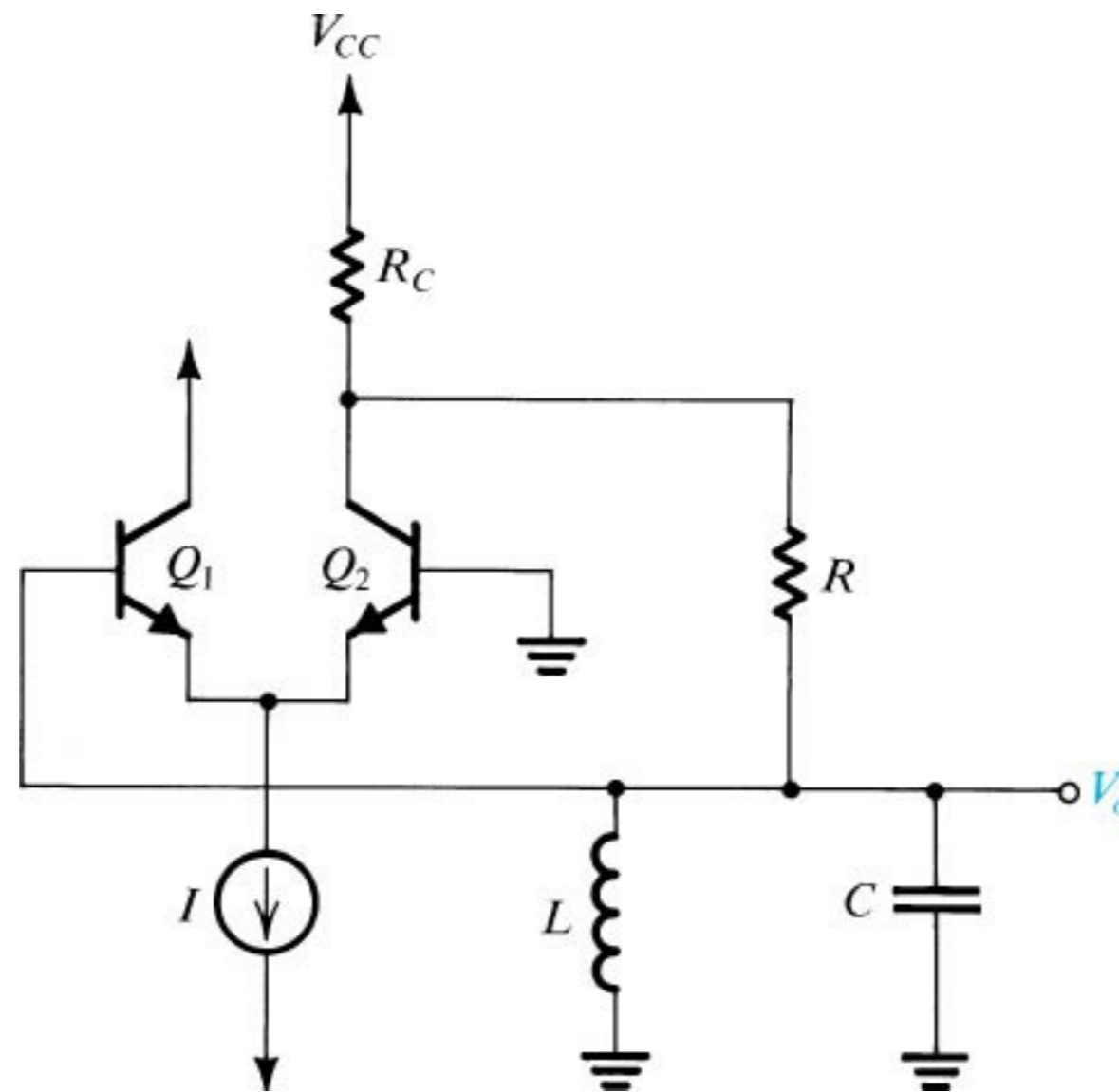


Figure P13.22