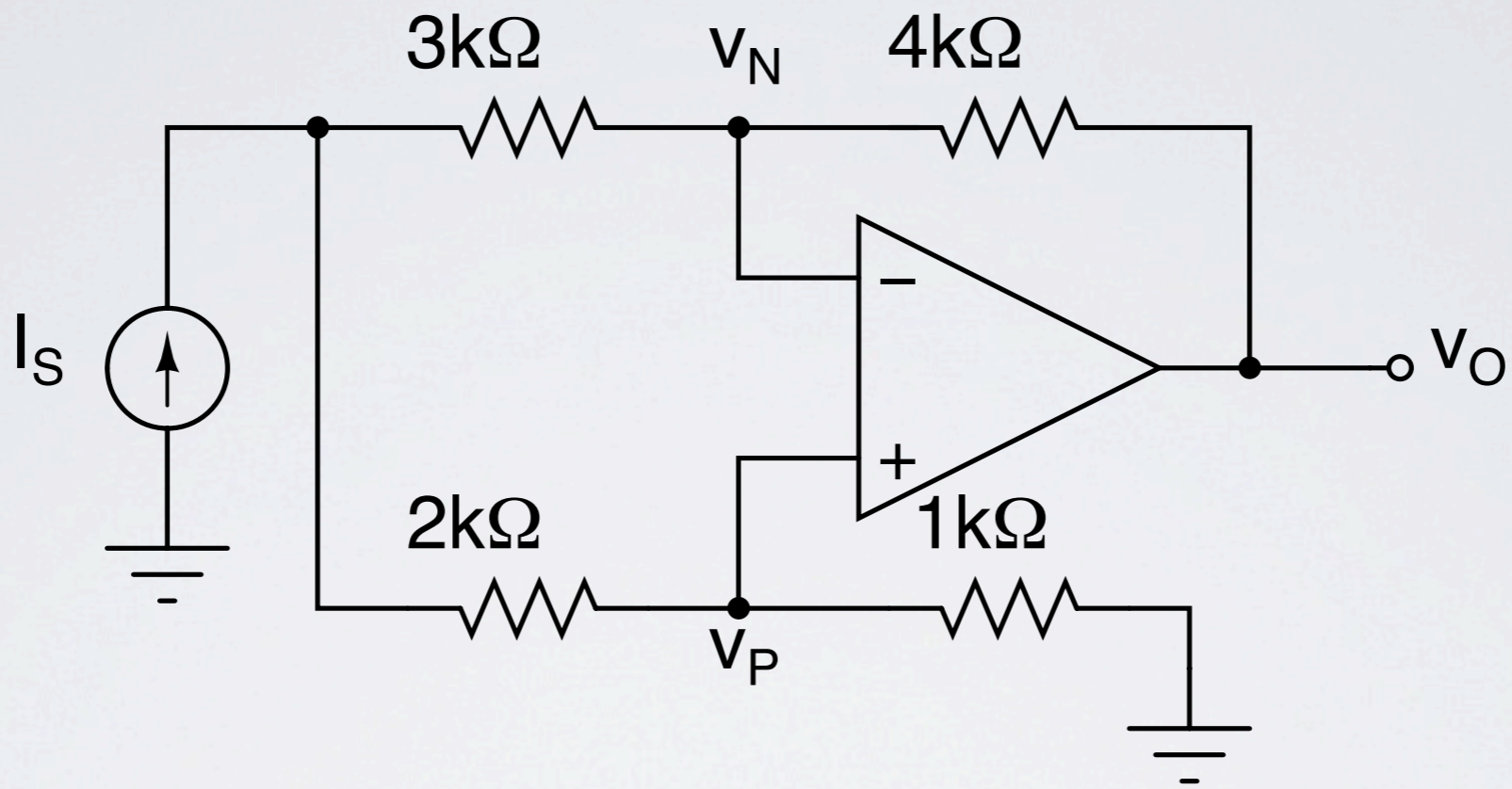


REVIEW PARTIAL EXAM 3


INEL 4202 Electronics II
Fall 2012

TOPICS

Topic	Section	Practice problems
Operational amplifiers, Summers, integrators, inverting and non-inverting amplifiers	2.1- 2.4	2(1, 2, 8, 9, 11, 12, 16, 20, 22, 30, 44, 46, 49, 60, 62, 72, 74)
Integrators and differentiators, Applications	2.8	2.112, 2.113
Current sources	6.3, 6.12	6.21, 6.22, 6.23, 6.30, 6.31, 6.33, 6.131, 6.140, 6.141, 6.142, 6.143
The differential amplifier	7.1-3, 7.5	7.1, 7.2, 7.11, 7.14, 7.15, 7.17, 7.20, 7.21, 7.37, 7.38, 7.39, 7.40, 7.41, 7.42, 7.62, 7.67, 7.68, 7.74
DC analysis of the 741 opamp	9.3, 9.4...	9.20, 9.21, 9.22, 9.25, 9.27, 9.35, 9.37
AC analysis of the 741 op-amp	9.5	9.40, 9.41, 9.46, 9.47, 9.48
Frequency response and slew rate	9.6	9.57, 9.60, 9.61
CMOS opamp DC and AC analysis	9.1	9.2, 9.3, 9.5
Freq. resp. and slew rate of CMOS opamp	9.2	9.7, 9.8, 9.9



$$\beta = 100$$

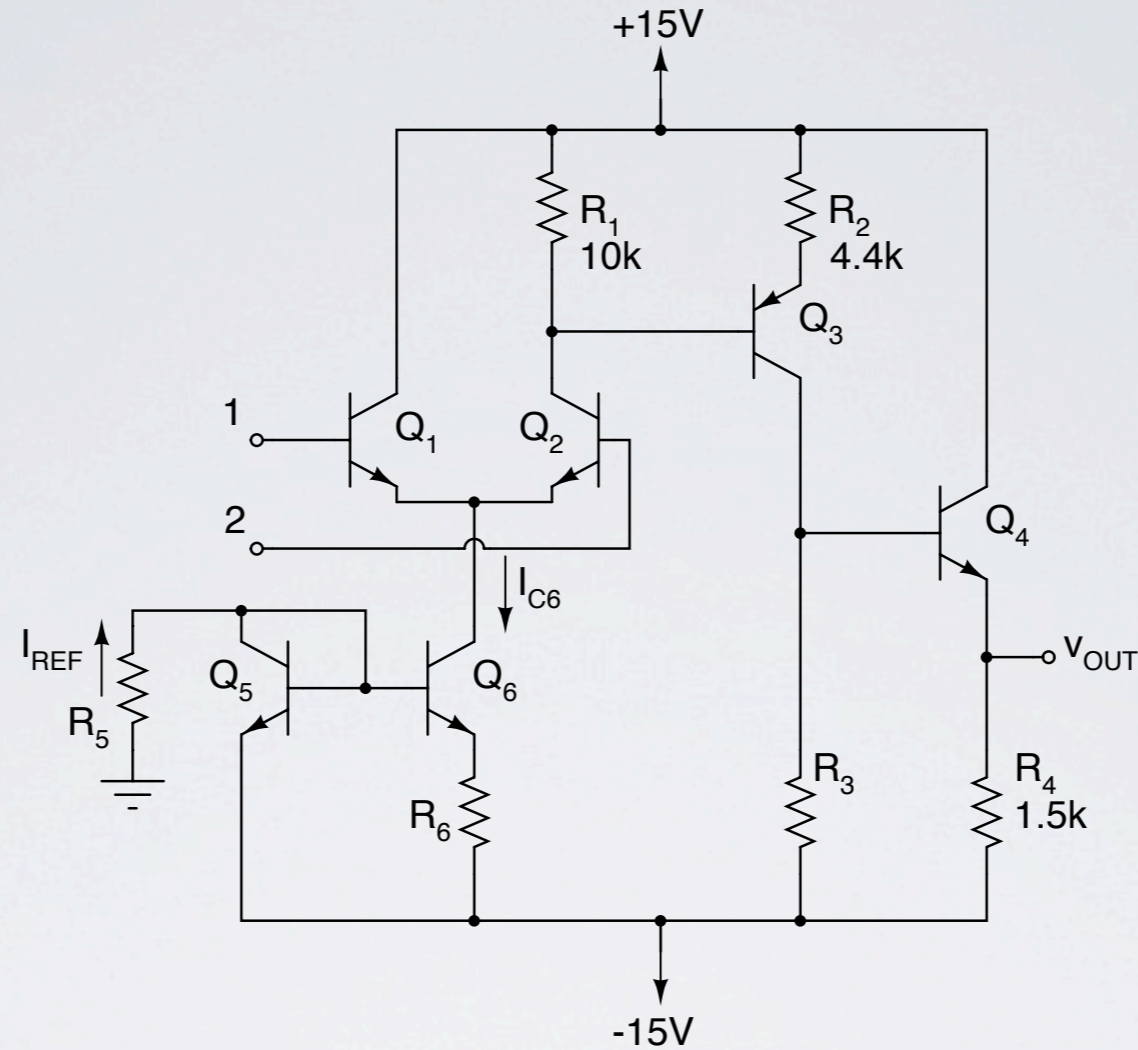

- Assuming $R_5 = 50k\Omega$, $R_3 = 10k\Omega$, $R_6 = 0$, and that the area of Q_6 equals 5 times the area of Q_5 , find:
 - the differential gain $A_d = \frac{v_{OUT}}{v_1 - v_2}$ (40 points)
 - the input resistance R_{in} seen by differential signals between terminals 1 and 2. (15 points)
 - the output resistance R_{out} at the output terminal. (15 points)
- Assuming $I_{C6} = 1mA$, select R_3 so that $v_{OUT} \approx 0V$ when $v_1 = v_2 = 0V$. (15 points)
- Select R_5 and $R_6 \neq 0$ such that $I_{C6} = 5 \times I_{REF}$ and $I_{C6} = 1mA$. (15 points)
- Find the Common-mode rejection ratio (CMRR) for your selection of R_6 in the previous problem. Assume $V_A = 100V$. (15 points)

1. (a) To find the gain, we need to determine the bias currents.

$$I_{REF} = \frac{15 - 0.7}{R_5} = \frac{14.3V}{50K} = 286 \mu A$$

$$I_{C6} = 5 \times I_{REF} = 1.43 \text{ mA}$$

$$I_{C2} = \frac{1}{2} I_{C6} = 0.715 \text{ mA}$$

$$V_{C2} = 15 - 10K (0.715 \text{ mA}) = 7.85V$$

$$I_{C3} = \frac{15V - (V_{C2} + 0.7)}{4.4K\Omega} = \frac{15 - (7.85 + 0.7)}{4.4K} = 1.47 \text{ mA}$$

$$V_{B4} = -15 + (1.47 \text{ mA})(R_3) = -15 + (1.47 \text{ mA})(10K) = -0.37V$$

$$I_{E4} = \frac{V_{B4} - 0.7 + 15}{1.5K} = 9.3 \text{ mA}$$

From this we can find the g_m 's

$$g_{m2} = \frac{0.715 \text{ mA}}{25 \text{ mV}} = 0.0286 \text{ A/V}$$

$$g_{m3} = \frac{1.47 \text{ mA}}{25 \text{ mV}} = 0.0588 \text{ A/V}$$

$$g_{m4} = \frac{9.3 \text{ mA}}{25 \text{ mV}} = 0.372 \text{ A/V}$$

The load at the collector of C_2 is

$$R_{C2} = R_C \parallel (R_{E3} + (\beta + 1) 4.4K) \\ = 10K \parallel \left[\frac{100(25)}{1.47} + 101 \times 4.4K \right] = 9.78K\Omega$$

$$\therefore \frac{V_{C2}}{V_1 - V_2} = + \frac{1}{2} g_{m2} R_{C2} = \frac{1}{2} (0.0286 \text{ A/V})(9.78K\Omega) = 140 \text{ V/V}$$

$$\frac{v_{c3}}{v_{c2}} = \frac{-g_{m3} R_{c3}}{1 + g_{m3} R_2}$$

$$R_{c3} = R_3 // (r_{\pi 4} + 101 \times 1.5k\Omega) = 10k // \left(\frac{100}{0.372} + 151.5k \right)$$

$$= 10k // (151.8k\Omega) = 9.38k\Omega \quad \leftarrow$$

$$\frac{v_{c3}}{v_{c2}} = \frac{-0.0588 \times 9.38k\Omega}{1 + 0.0588 \times 4.4k} = -2.12 v/v \quad \leftarrow$$

$$\frac{v_{e4}}{v_{c3}} = \frac{+g_{m4} R_4}{1 + g_{m4} R_4} = \frac{0.372(1500)}{1 + 0.372 \times 1500} = 0.998 \quad \leftarrow$$

$$A_d = (+140 v/v)(-2.12 v/v)(0.998 v/v) = \boxed{-296.3 v/v} \quad \leftarrow$$

$$(b) R_{in} = 2r_{\pi} = 2 \times \frac{100}{g_{m2}} = 2 \times \frac{100}{0.0286 A/V} = \boxed{7k\Omega}$$

$$(c) R_{out} = 1.5k // \frac{r_{\pi 4} + R_3}{101} = 1.5k // \frac{\frac{100}{0.372} + 10k\Omega}{101} = \boxed{95.2\Omega}$$

$$(2) \text{ if } I_{C6} = 1mA, I_{C2} = 0.5mA, v_{c2} = 10V; I_{C3} = \frac{15 - 10.7}{4.4k} = 0.98mA$$

$$\text{For } v_{out} = 0, v_{c3} = +0.7V; \therefore R_3 = \frac{15.7V}{0.98mA} = \boxed{16k\Omega}$$

(3) Widlar Current Source

$$I_0 R_M = V_T \ln\left(\frac{I_{REF}}{I_0}\right); I_{REF} = 0.2mA \Rightarrow R_5 = \frac{14.3V}{0.2mA} = \boxed{71.5k\Omega}$$

$$R_6 = \frac{25mV}{1mA} \ln(2) = 17.3\Omega$$

$$= \frac{14.3V}{0.2mA} = 71.5k\Omega$$

