

TABLE 8.1 Summary of Relationships for the Four Feedback Amplifier Topologies

Feedback Amplifier	x_i	x_o	x_f	x_s	A	β	A_f	Source Form	Loading of Feedback Network Is Obtained		To Find β , Apply to Port 2 of Feedback Network	Z_{if}	Z_{of}	Refer to Figs.
									At Input	At Output				
Series-shunt (voltage amplifier)	V_i	V_o	V_f	V_s	$\frac{V_o}{V_i}$	$\frac{V_f}{V_o}$	$\frac{V_o}{V_s}$	Thévenin	By short-circuiting port 2 of feedback network	By open-circuiting port 1 of feedback network	a voltage, and find the open-circuit voltage at port 1	$Z_i(1 + A\beta)$	$\frac{Z_o}{1 + A\beta}$	8.4(a) 8.8 8.10 8.11
Shunt-series (current amplifier)	I_i	I_o	I_f	I_s	$\frac{I_o}{I_i}$	$\frac{I_f}{I_o}$	$\frac{I_o}{I_s}$	Norton	By open-circuiting port 2 of feedback network	By short-circuiting port 1 of feedback network	a current, and find the short-circuit current at port 1	$\frac{Z_i}{1 + A\beta}$	$Z_o(1 + A\beta)$	8.4(b) 8.22 8.23 8.24
Series-series (transconductance amplifier)	V_i	I_o	V_f	V_s	$\frac{I_o}{V_i}$	$\frac{V_f}{I_o}$	$\frac{I_o}{V_s}$	Thévenin	By open-circuiting port 2 of feedback network	By open-circuiting port 1 of feedback network	a current, and find the open-circuit voltage at port 1	$Z_i(1 + A\beta)$	$Z_o(1 + A\beta)$	8.4(c) 8.13 8.15 8.16
Shunt-shunt (transresistance amplifier)	I_i	V_o	I_f	I_s	$\frac{V_o}{I_i}$	$\frac{I_f}{V_o}$	$\frac{V_o}{I_s}$	Norton	By short-circuiting port 2 of feedback network	By short-circuiting port 1 of feedback network	a voltage, and find the short-circuit current at port 1	$\frac{Z_i}{1 + A\beta}$	$\frac{Z_o}{1 + A\beta}$	8.4(d) 8.18 8.19 8.20