
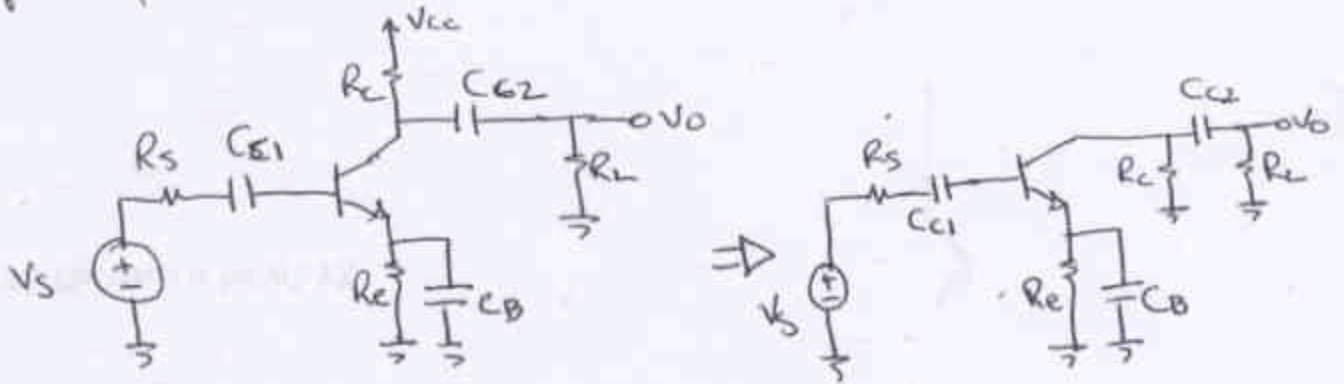


Amp. Freq. Resp. - low freq.

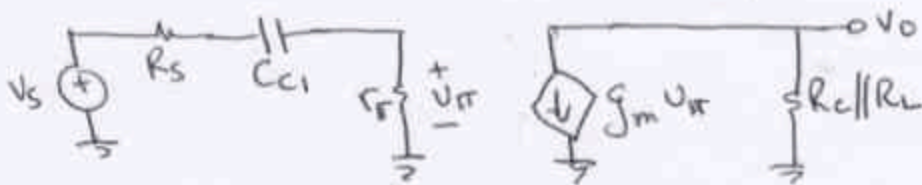

If  $C_{c2}$  &  $C_e$  are shorts, and  $r_d = \infty$




$$V_o = -g_m (R_c || R_L) V_{\pi} ; \quad V_{\pi} = \frac{r_{\pi}}{R_s + r_{\pi}} \frac{\partial \mathcal{L}_1}{\partial \mathcal{L}_1 + 1} V_s$$

$$\mathcal{L}_1 = C_{c1} (R_s + r_{\pi}) \leftarrow \text{from Lect. 1}$$

$$\frac{V_o}{V_s} = A = - \frac{r_{\pi}}{R_s + r_{\pi}} g_m (R_c || R_L) \frac{\partial \mathcal{L}_1}{\partial \mathcal{L}_1 + 1}$$

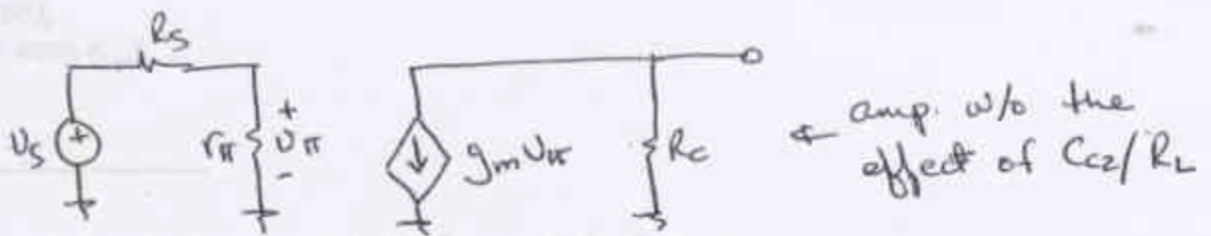
To find the effect of  $C_{c2}$  (when  $C_{c1}$  and  $C_e$  are shorts)



$$\frac{V_o}{V_s} = \underbrace{- \frac{r_{\pi}}{R_s + r_{\pi}} g_m R_c}_{A_{amp}} ; \quad R_o = R_c$$

$$R_i = R_s + r_{\pi}$$

So we can represent the amp by a model

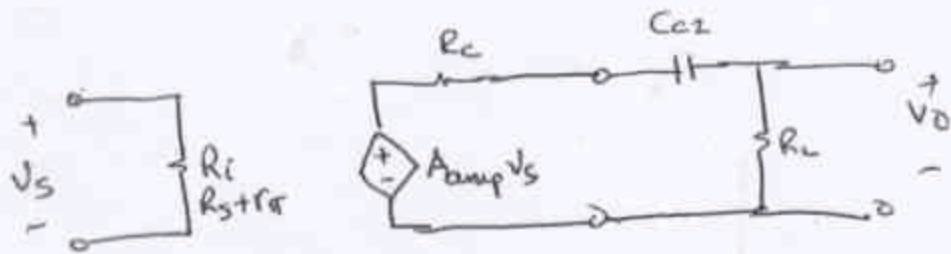

$$A_{amp} = - \frac{r_{\pi}}{R_s + r_{\pi}} g_m R_c = \frac{V_o}{V_s} |_{low}$$


taking into account  $C_{c2}$  &  $R_L$

$$A = A_{amp} V_s \frac{R_L}{R_L + R_c} \frac{1}{s\tau_{L2} + 1}$$

$$\tau_{L2} = C_{c2} (R_L + R_c) \quad \leftarrow \text{from lect. 1}$$

$$A = \frac{V_o}{V_s} = \underbrace{- \frac{r_{\pi}}{R_s + r_{\pi}} g_m \frac{R_c R_L}{R_L + R_c}}_{\text{midband gain}} \frac{1}{s\tau_{L2} + 1}$$

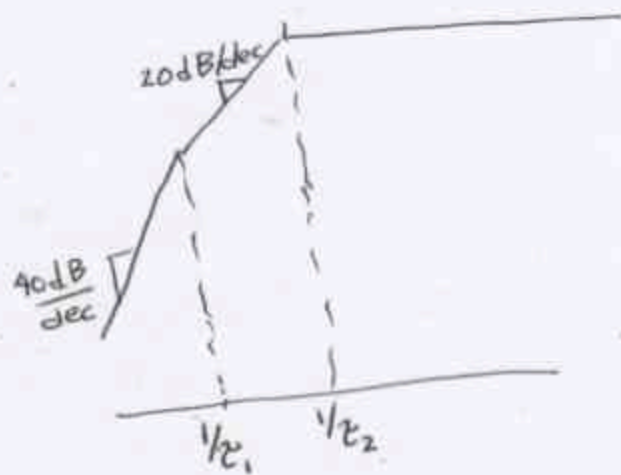For  $C_{c1}$  &  $C_{c2}$  present,  $C_B \rightarrow$  short, we have 2 poles



$\tau_1$  can be  $\tau_{c1}$  or  $\tau_{c2} \leftarrow$  largest of either

$$\omega = \frac{1}{\tau}$$

The smallest  $\epsilon$  produces the largest  $\omega$ .  $\therefore$  if  $\tau_{L2} \gg \tau_{L1}$ ,

$\omega_{L1} \gg \omega_{L2}$  and  $\omega_{L1}$  determines the BW.

Rule of thumb:



$\omega_{L1}, \omega_{L2}, \omega_{L3}, \omega_{L4}, \dots, \omega_{Ln} \Rightarrow$  low-freq. poles

$\rightarrow$  if  $\omega_i \gg$  all other  $\omega$ 's by at least a decade, then  $\omega_{BW} \approx \omega_i$

else  $\omega_{BW} \approx \sum_{j=1}^n \omega_j$   $\leftarrow$  add all of them to find an approx. bandwidth.

$\rightarrow \omega_i$  is the "dominant" low freq. pole

### Bypass cap.

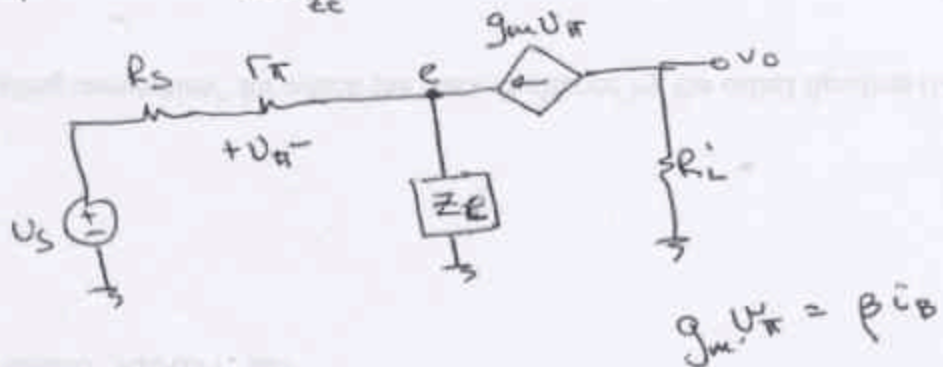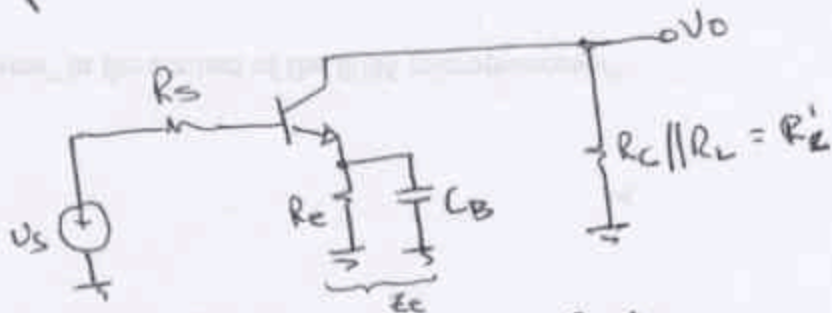

$$V_o = -\beta R'_L i_B$$

$$V_s = i_B (R_s + r_{\pi}) + \underbrace{(\beta + 1) Z_E i_B}_{\text{KCL at } e} \leftarrow \text{KVL on input loop}$$

$$i_B = \frac{v_S}{R_S + r_{\pi} + (\beta + 1) Z_e}$$

$$v_O = - \frac{\beta R_L'}{R_S + r_{\pi} + (\beta + 1) Z_e} v_S$$

$$Z_e = \frac{R_e \parallel \frac{1}{sC_B}}{R_e + \frac{1}{sC_B}} = \frac{R_e}{sC_B R_e + 1}$$

$$\frac{v_O}{v_S} = - \frac{\beta R_L'}{R_S + r_{\pi} + \frac{(\beta + 1) R_e}{sC_B R_e + 1}}$$

$$= - \frac{\beta R_L' (sC_B R_e + 1)}{sC_B R_e (R_S + r_{\pi}) + R_S + r_{\pi} + (\beta + 1) R_e}$$

$$= - \frac{\beta R_L'}{R_S + r_{\pi} + (\beta + 1) R_e} \cdot \frac{sC_B R_e + 1}{1 + sC_B \frac{R_e (R_S + r_{\pi})}{R_S + r_{\pi} + (\beta + 1) R_e}}$$

midband gain

$$C_B \frac{R_e (R_S + r_{\pi})}{R_S + r_{\pi} + (\beta + 1) R_e} = C_B \frac{R_e \frac{R_S + r_{\pi}}{\beta + 1}}{R_e + \frac{R_S + r_{\pi}}{\beta + 1}}$$

$\frac{R_S + r_{\pi}}{\beta + 1}$  ← equivalent resistance "looking" into emitter

$$\frac{v_O}{v_S} = A_{dc} \frac{s\tau_z + 1}{s\tau_p + 1}$$


← zero at  $\omega_z = \frac{1}{C_B R_e}$   
pole at  $C_B R_{eq}$ .

$$R_{eq} = R_e \parallel \frac{R_S + r_{\pi}}{\beta + 1}$$

Notice that  $\omega_p$  is always larger than  $\omega_z$ .

$\omega_p \rightarrow$  can be found from  $C_B$  & the equivalent resistance "seen" by  $C_B \rightarrow$  "open-circuit t.c."  
 $A_{dc} \rightarrow$  gain when  $C_B$  is an open circuit.

Ejemplo

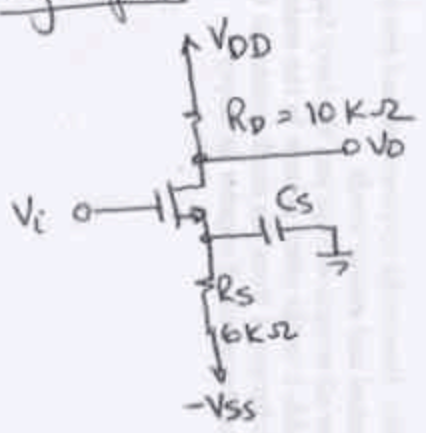


$I_D = 1\text{mA}$  ;  $g_m = 1\text{mA/V}$  ,  $r_o = \infty$

- Find:
- a) midband gain  $A_{MB}$
  - b) value of  $C_S$  that places the low-freq. pole at 10Hz
  - c) freq. of zero due to bypass for this value of  $C_S$
  - d)  $A_v(s)$

(a)  $A_{MB} = -g_m R_D = -(1\text{mA/V})(10\text{k}\Omega) = \boxed{-10\text{V/V}}$

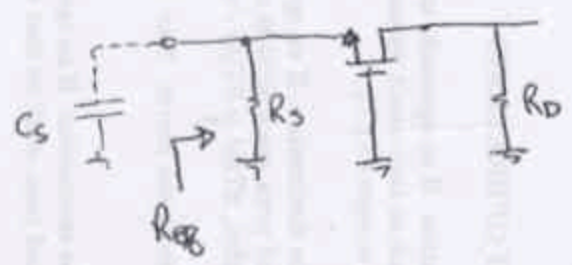(b) find the "Req" from terminals of  $C_S$ .  
 For A.C.



$R_{eq} = R_S \parallel 1/g_m$   
 $= 6\text{k}\Omega \parallel 1\text{k}\Omega$   
 $= 6/7 \text{ k}\Omega = 0.857\text{k}\Omega$

$C_S \frac{6000}{7} = \frac{1}{\omega_L} = \frac{1}{2\pi(10\text{Hz})} = \frac{1}{20\pi}$   
 $C_S = \frac{7}{12.9000\pi} = \frac{7}{1.2 \times 10^5 \pi} = \frac{7}{.12\pi} \mu\text{F}$

$C_S = 18.6 \mu\text{F}$

(c)  $\omega_z = \frac{1}{18.6\mu\text{F} \times 6\text{k}\Omega} = 8.97 \text{ rps} \Rightarrow \omega_z = \frac{\omega_z}{2\pi} = \boxed{1.4 \text{ Hz}}$

$$(d) A_v(s) = \frac{V_o}{V_i} = A_{dc} \frac{s/9 + 1}{s/20\pi + 1}$$

$$A_{dc} = \frac{-g_m R_d}{1 + g_m R_s} = \frac{-(1 \text{ mA/V})(10 \text{ k}\Omega)}{1 + (1 \text{ mA/V})(6 \text{ k}\Omega)}$$


$$= -\frac{10}{7} \text{ V/V} \Rightarrow \sim 1.6 \text{ dB}$$

$$A_v(s) = -\frac{10}{7} \frac{s/9 + 1}{s/20\pi + 1}$$

→ to find  $A_{MB}$   
let  $s \rightarrow \infty$

$$A_{MB} = -\frac{10}{7} \frac{20\pi}{9} = -9.97 \text{ V/V}$$

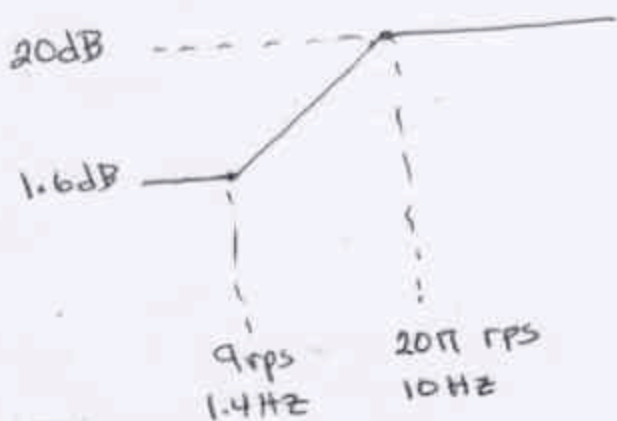
this is the gain  
when  $C_B$  is a short



← bode plot of gain (mag.)

$$\phi = -180^\circ + \tan^{-1}(\omega/9) - \tan^{-1}(\omega/20\pi)$$

Ejemplo:

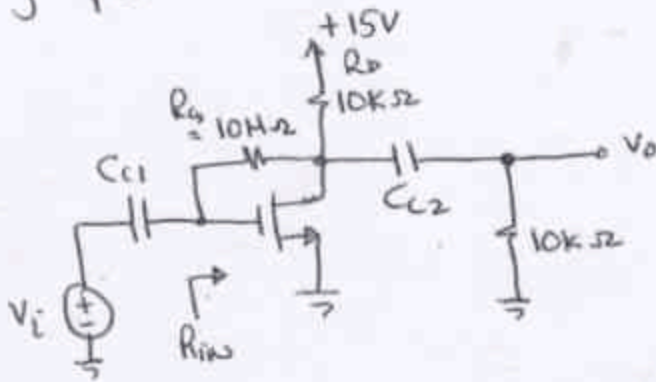

Given  $I_D = 1.06 \text{ mA}$   
 $g_m = 0.725 \text{ mA/V}$   
 $r_o = 47 \text{ k}\Omega$   
 $A_{MB} = -3.3 \text{ V/V}$   
 $R_{in} = 2.33 \text{ M}\Omega$

Select values for  $C_{c1}$  and  $C_{c2}$  so that the low-freq. response is dominated by a pole at 10 Hz with the other pole at least a decade lower.

Ans. using the S.C.T.C. method.

For  $C_{c1}$ ,  $R_{eq} \approx R_{in} = 2.33 \text{ M}\Omega$


For  $C_{c2}$ ,  $R_{eq} = 10 \text{ k}\Omega + 10 \text{ k}\Omega \parallel 10 \text{ M}\Omega \parallel 47 \text{ k}\Omega$   
 $= 10 \text{ k}\Omega + 8.24 \text{ k}\Omega$   
 $= 18.24 \text{ k}\Omega \approx 18.2 \text{ k}\Omega$

Let  $\tau_2 = \frac{1}{20\pi} = C_{c2} (18 \text{ k}\Omega) \Rightarrow \boxed{C_{c2} = 0.87 \mu\text{F}}$

$\tau_1 = \frac{1}{2\pi} = C_{c1} (2.33 \text{ M}\Omega)$   
 $\Rightarrow \boxed{C_{c1} = 68 \text{ nF}}$

Notice that if  $\tau_2 = 1/2\pi$  and  $\tau_1 = 1/20\pi$   
 $C_{c2} = 8.7 \mu\text{F}$  &  $C_{c1} = 6.80 \text{ nF} \Rightarrow$  bigger  $C_{c2}$   
 caps. so less convenient.

# Ejemplo

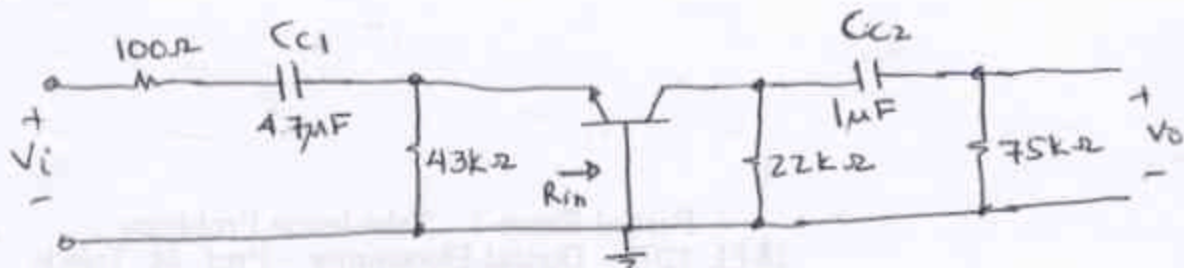

Given:  $I_C = 0.1 \text{ mA}$  ;  $\beta_0 = 100$  ;  $r_0 = \infty$

Find: midband gain and low-freq. poles

midband gain

$$A_{MB} = \frac{V_o}{V_e} \frac{V_e}{V_i}$$

$$\frac{V_o}{V_e} = +g_m R'_L = \left( \frac{I_C}{V_T} \right) (22 \text{ k}\Omega \parallel 75 \text{ k}\Omega)$$

$$= \frac{.1 \text{ mA}}{.025 \text{ V}} (22 \parallel 75) \cdot 1000 = 68 \text{ V/V}$$

$$\frac{V_e}{V_i} = \frac{43 \text{ k}\Omega \parallel R_{in}}{100 + 43 \text{ k}\Omega \parallel R_{in}} ; R_{in} = \frac{r_{\pi}}{\beta + 1} = \frac{100}{101} \frac{25 \text{ mV}}{.1 \text{ mA}} \approx 250 \Omega$$

$$43 \text{ k}\Omega \parallel R_{in} \approx 250 \Omega$$

$$\frac{V_e}{V_i} = \frac{25}{35}$$

$$A_{MB} = \frac{25}{35} 68 \text{ V/V} \approx \boxed{49 \text{ V/V}}$$


due to  $C_{c1}$   $\omega_1 \rightarrow \tau_1 = (4.7 \mu\text{F})(350 \Omega) = 1645 \times 10^{-6} \text{ s} \leftarrow \text{dominant}$

due to  $C_{c2}$   $\omega_2 \rightarrow \tau_2 = (1 \mu\text{F})(97 \text{ k}\Omega) = 97 \times 10^{-3} \text{ s}$

$$\omega_1 = \frac{1}{1645} \times 10^6 \text{ rps} = 607.9 \text{ rps} \approx \underline{98 \text{ Hz}}$$

$$\omega_2 = \frac{1000}{97} \text{ rps} = 10.3 \text{ rps} \approx 1.64 \text{ Hz}$$

Ejemplo

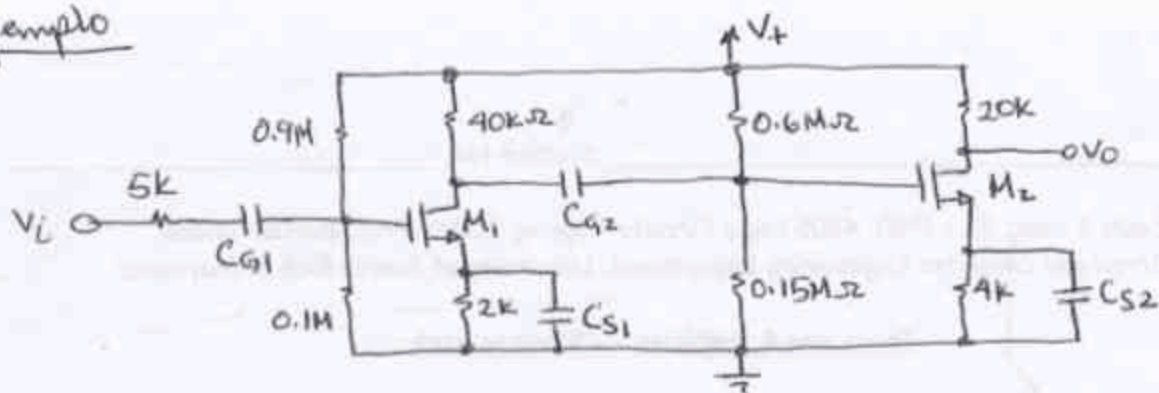

$$g_{m1} = g_{m2} = 2 \text{ mA/V}, \quad r_{d1} = r_{d2} = 40 \text{ k}\Omega$$

$$C_{G1} = C_{G2} = 1 \mu\text{F}, \quad C_{S1} = C_{S2} = 100 \mu\text{F}$$

Find: midband gain; low-freq. poles and zeroes

$$A_{MB} = \frac{V_o}{V_i} = \frac{V_o}{V_{G2}} \cdot \frac{V_{G2}}{V_{D1}} \cdot \frac{V_{D1}}{V_{G1}} \cdot \frac{V_{G1}}{V_i}$$

$$\frac{V_o}{V_{G2}} = -(g_{m2})(20\text{k}) = -2 \frac{\text{mA}}{\text{V}} \times 20\text{k}\Omega = \underline{-40 \text{ V/V}}$$

$$\frac{V_{D1}}{V_{G1}} = -g_{m1} R_{D1}' ; \quad R_{D1}' = 40\text{k} \parallel 150\text{k} \parallel 600\text{k} \parallel 40\text{k} = 17\text{k}\Omega$$

$$\frac{V_{D1}}{V_{G1}} = -2 \frac{\text{mA}}{\text{V}} (17\text{k}\Omega) = \underline{-34 \text{ V/V}}$$

$$\frac{V_{G2}}{V_{D1}} = 1 \quad \text{since we account for loading when finding } V_{D1}/V_{G1}$$

$$\frac{V_{G1}}{V_i} = \frac{900 \parallel 100}{5 + 900 \parallel 100} = \frac{90}{95}$$

$$A_{MB} = -40 \times (-34) \times \frac{90}{95} = \boxed{+1288 \text{ V/V}} \Rightarrow \underline{62.2 \text{ dB}}$$

$$\tau_{CG1} = (1\mu F)(5K + 100K \parallel 900K) = (1\mu F)(90K) = 90ms$$

$$\begin{aligned}\tau_{CG2} &= (1\mu F)(600K \parallel 150K + 40K \parallel 40K) \\ &= (1\mu F)(120K + 20K) = 140ms\end{aligned}$$

$$\tau_{CS1} = (100\mu F)(2K \parallel \frac{1}{g_{S1}}) = 100\mu F(2K \parallel 500\Omega) = \underline{40ms}$$

pole due to CS1

$$\tau_{CS2} = (100\mu F)(4K \parallel \frac{1}{g_{S2}}) = 100\mu F(4K \parallel 500\Omega) = \underline{44.4ms}$$

pole due to CS2

zeros @  $\tau_{CS1z} = (100\mu F)(2K) = 200ms$

$$\tau_{CS2z} = (100\mu F)(4K) = 400ms$$

### Frequencies

poles at 25 rps, 22.5 rps, 11 rps, 7.1 rps

zeros at 5 rps, 2.5 rps

Approximate low freq. -3dB point is

$$f_L = \sum \text{poles} - \sum \text{zeros}$$

$$\approx \frac{50 \text{ rps}}{2\pi} = \boxed{9.3 \text{ Hz}}$$