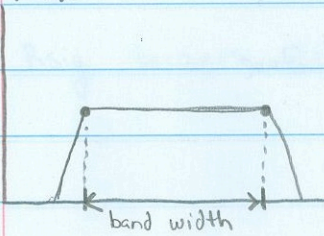


$|A|_{dB}$ Magnitude Bode Plot



$$A_{dB} = 20 \log A$$

funcion de transf

$$A(s) = A_0 \frac{\prod_{i=1}^n (s + \omega_{zi})}{\prod_{j=1}^m (s + \omega_{pj})}$$

ganancia calc.
electronica I

$\omega_{pj} \rightarrow$ poles

$\omega_{zi} \rightarrow$ zeroes

$$A_{dB}(s) = A_{0dB} + \sum_{i=1}^n |s + \omega_{zi}| - \sum_{j=1}^m |s + \omega_{pj}|$$

$|s + \omega_{pj}| =$ magnitude of $s + \omega_{pj}$


$$s = j\omega$$

$$|s + \omega_{pj}| = \sqrt{\omega^2 + \omega_{pj}^2}$$

poles $\rightarrow -20 \text{ dB/dec} = -6 \text{ dB/octave}$

zeroes $\rightarrow +20 \text{ dB/dec} = +6 \text{ dB/octave}$

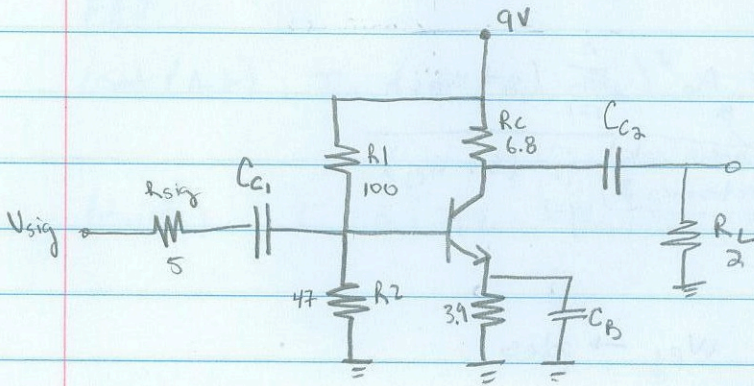Example - amp from class 1 but single stage



all R 's are
expressed in $k\Omega$

$$A_v = \frac{V_o}{V_s} = \frac{-g_m R_c \parallel R_L}{1 + g_m R_e} \frac{R'_b}{R_{sig} + R'_b}$$

$$R'_b = 100 \parallel 47 \parallel [r_{\pi} + (\beta + 1) R_e]$$

4201
w/o C_B

Simplified proc: consider 1 cap at a time; others are shorts

- Take C_{c1} into account and let the other external caps be shorts.

$$R_{sig} \text{ becomes } Z_{sig} = R_{sig} + \frac{1}{sC_{c1}} = \frac{sC_{c1}R_{sig} + 1}{sC_{c1}}$$

$$= R_{sig} \frac{s + 1/R_{sig}C_{c1}}{s}$$

$$A(s) = -g_m (R_C \parallel R_L) \frac{R'_b}{Z_{sig} + R'_b} ; R'_b = 100 \parallel 47 \parallel r_{\pi}$$

short in C_B
makes $R_e \rightarrow 0$

Sustituyendo:
$$A(s) = -g_m (R_C \parallel R_L) \frac{R'_b}{R_{sig} \frac{s + 1/R_{sig}C_{c1}}{s} + R'_b}$$

$$A(s) = -g_m (R_C \parallel R_L) \frac{sR'_b}{s[R_{sig} + R'_b] + \frac{1}{C_{c1}}}$$

// Aislando la parte q tiene que ver con freq.

$$A(s) = \underbrace{-g_m (R_C \parallel R_L) \frac{R'_b}{R_{sig} + R'_b}}_{\text{midband gain}}$$

$$\frac{s}{s + \underbrace{\frac{1}{C_{c1}(R_{sig} + R'_b)}}_{\omega_p}}$$

Zero at origin \leftarrow


$\leftarrow \omega_p$

midband
gain

Otra forma con resistencias equivalente:

ro = infinity

Q is an open circuit

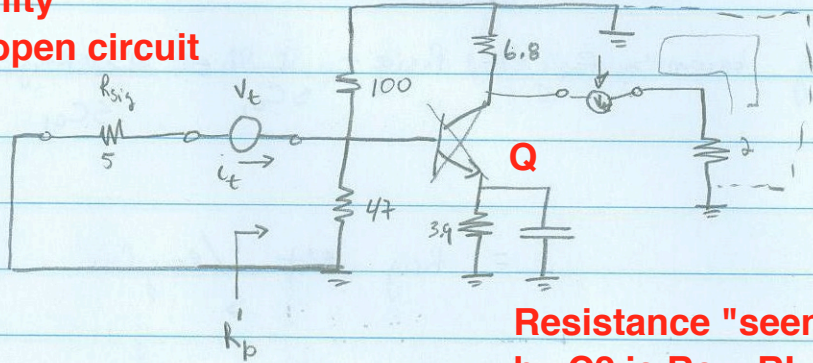

Resistance "seen" by C2 is Rc + RL

// El condensador de bypass es un poco más complicado:


Resultado es:

Electronica I

$$A_{MB} = \frac{s + \omega_z}{s + \omega_p} ; \quad \omega_z = \frac{1}{C_B R_e} ; \quad \omega_p = \frac{1}{C_B R_{eq}}$$


Amb = midband gain = gain calc. in 4201

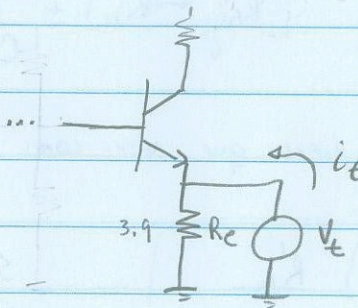R_{eq} = equivalent resistant seen from the terminals where C_B is connected.



$$R_{eq} = R_e \parallel \frac{r_{\pi} + R_{B_{eq}}}{\beta + 1}$$
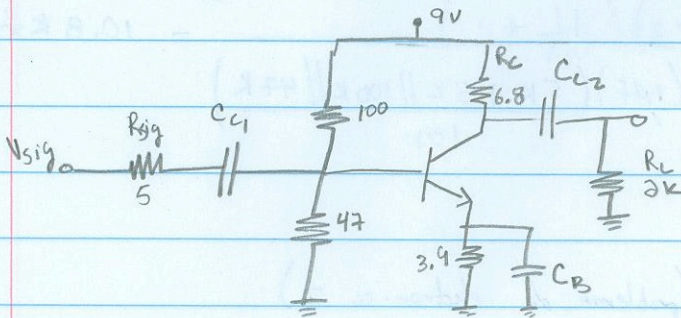
$$= R_e \parallel \left[\frac{1}{g_m} + \frac{R_{B_{eq}}}{\beta + 1} \right]$$



All R's are in kΩ

1) Find low-freq poles and zeroes if $C_{c1} = C_{c2} = C_B = 1\mu F$

C_{c1}

Zero at origin

$$\omega_{p1} = \frac{1}{(1\mu F)(5 + 100 \parallel 47 \parallel 5 \text{ k}\Omega)} \approx 100 \text{ rps}$$

C_{c2}

zero at origin

$$\omega_{p2} = \frac{1}{(1\mu F)(6.8 \text{ k}\Omega + 2 \text{ k}\Omega)} = 11.4 \text{ rps}$$

C_B

$$\text{Zero at } \omega_z = \frac{1}{(1\mu\text{F})(3.9\text{k}\Omega)} = 256 \text{ rps}$$

$$\text{pole at } \omega_{p3} = \frac{1}{(1\mu\text{F})\left(\frac{5\text{k} + 5\text{k} \parallel 100\text{k} \parallel 47\text{k}}{101}\right)} = 10.8 \text{ k rps}$$

(2) Find $A_{\text{mid Band}}$ (problema de electronica I)

(3) Write an expression for $A(s)$

$$\textcircled{2} A_{\text{mid}} = -g_m R_c' \frac{R_b'}{r_{\pi} + R_b'}$$

$$R_c' = R_c \parallel R_L = 6.8\text{k} \parallel 2\text{k} = 1.55\text{k}$$

$$R_b' = 5\text{k} \parallel 47\text{k} \parallel 100\text{k} = 4.3\text{k}$$

$$g_m = 20 \frac{\text{mA}}{\text{V}} \text{ (resultado anterior)}$$

$$A_{mid} = -20 \frac{\mu A}{V} (1.55 K) \left(\frac{4.3 K}{9.3 K} \right) = -14.3 \frac{V}{V}$$

③


$$A(s) = \left(-14.3 \frac{V}{V} \right) \frac{s^2 \left(s + \frac{1}{256} \right)}{\left(s + \frac{1}{100} \right) \left(s + \frac{1}{114} \right) \left(s + \frac{1}{10.8 K} \right)}$$

L $\frac{1}{s} (11K)$
 Este es el dominante porque esta a freq más baja.

Rule of thumb: if a pole is a decade or more above other low freq poles it is dominant. The -3dB freq. is approx. equal to the pole freq.

It's more that a decade above other poles

④ sketch the Magnitude Bode plot

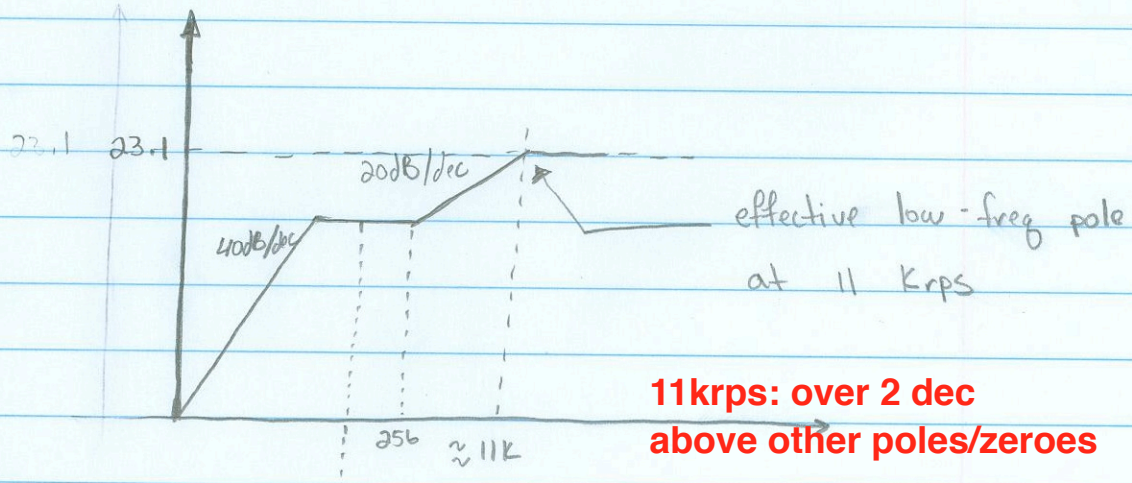

If no pole is dominant: effective pole = $f_{eff} = \sum \text{poles} - \sum \text{zeros}$ (this is one way to estimate f_{eff} ; there are other ways)

(5) Select the caps so that $W_{eff} \approx 1/k_{rps}$

Do for homework:

Hint: make bypass cap pole dominant; select other poles so that they are 1-2 decades below