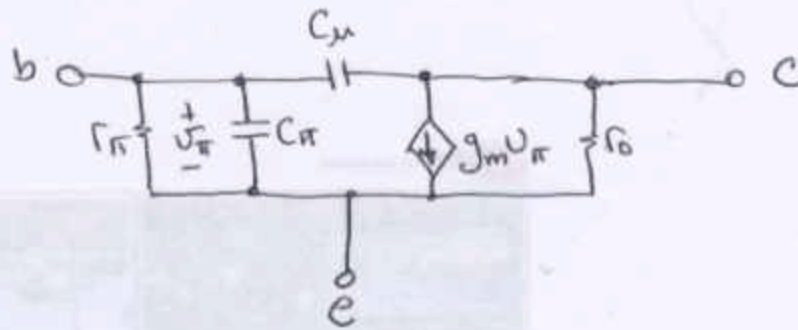




High-frequency response

BJT \rightarrow hybrid- π equivalent circuit is expanded to include capacitive effects on the transistor's junctions.



C_{π} & C_{μ} reduce the gain at higher frequencies

Short-circuit current gain

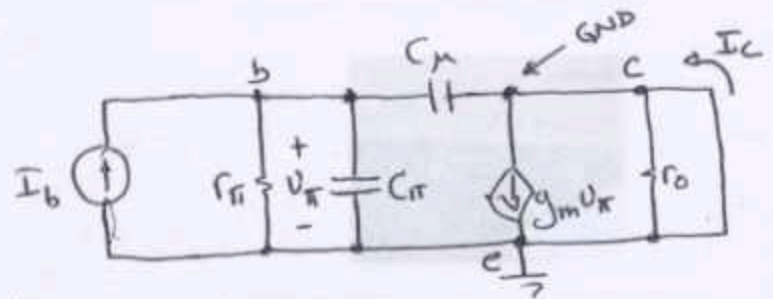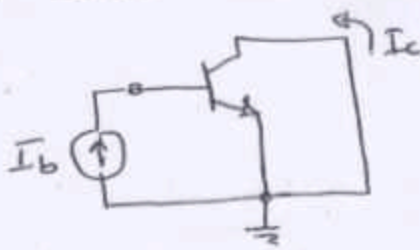

$$V_{C\mu} = V_{\pi}$$

KCL at b

$$I_b = \frac{V_{\pi}}{r_{\pi}} + \frac{V_{\pi}}{1/sC_{\pi}} + \frac{V_{\pi}}{1/sC_{\mu}}$$

$$I_b = V_{\pi} \left(\frac{1}{r_{\pi}} + sC_{\pi} + sC_{\mu} \right)$$

$$V_{\pi} = \frac{r_{\pi} I_b}{1 + s r_{\pi} (C_{\pi} + C_{\mu})}$$

KCL at c

$$I_c = g_m V_{\pi} - \frac{V_{\pi}}{1/sC_{\mu}} = (g_m - sC_{\mu}) V_{\pi}$$

For all frequencies of interest, $g_m \gg sC_{\mu}$


$$\therefore I_c \approx g_m V_{\pi} = \frac{g_m r_{\pi}}{1 + s r_{\pi} (C_{\pi} + C_{\mu})} I_b$$

This provides an expression for $I_c/I_b = \beta$ as a function of s ,

$$\beta(s) = \frac{I_c}{I_b} = \frac{\beta_0}{1 + s r_{\pi} (C_{\pi} + C_{\mu})}$$

$\beta_0 = g_m r_{\pi}$ = low-frequency I_c/I_b

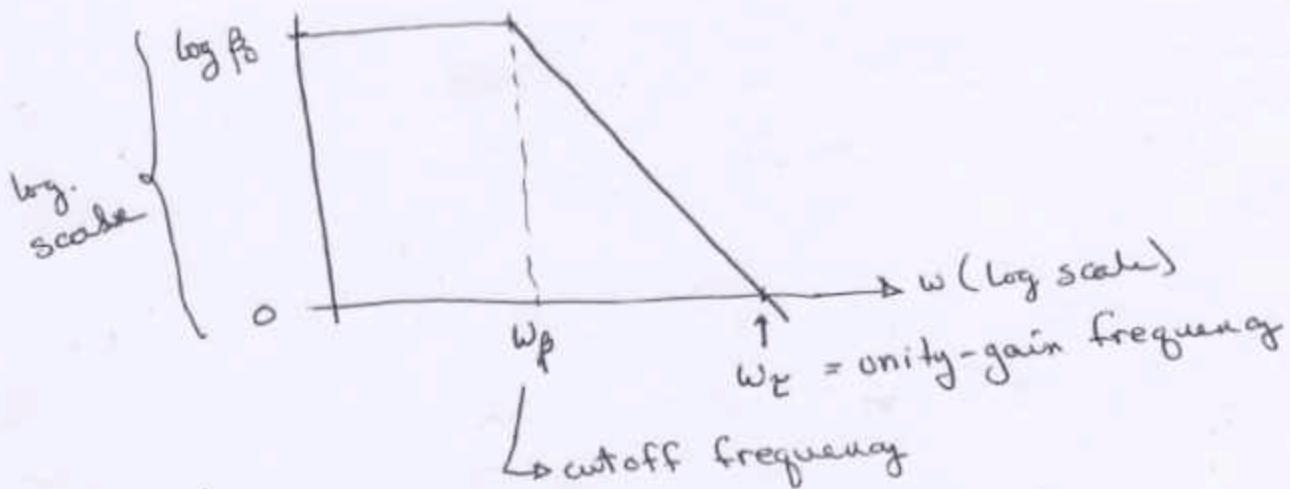pole at $\omega_p = \frac{1}{r_{\pi} (C_{\pi} + C_{\mu})}$



At ω_c , $\beta(s) = 1$ by definition

$$\left| \frac{\beta_0}{1 + j\omega_c r_{\pi} (C_{\pi} + C_{\mu})} \right| = \frac{\beta_0}{\sqrt{1 + \omega_c^2 r_{\pi}^2 (C_{\pi} + C_{\mu})^2}} = 1$$

$$\omega_c = \frac{\sqrt{\beta_0^2 - 1}}{r_{\pi} (C_{\pi} + C_{\mu})} \approx \frac{\beta_0}{r_{\pi} (C_{\pi} + C_{\mu})} = \omega_c$$

$\beta_0 \rightarrow$ also called h_{fe}

$\beta(s) \rightarrow$ " " $h_{fe}(s)$

$$\omega_T \equiv \frac{\beta_0}{r_{\pi}(C_{\pi} + C_{\mu})} = \frac{g_m r_{\pi}}{r_{\pi}(C_{\pi} + C_{\mu})} = \frac{g_m}{C_{\pi} + C_{\mu}}$$

Note: book uses ω_T (f_T) for ω_E (f_E).

For transistor 2N2222A $\rightarrow f_T \equiv 300 \text{ MHz}$.

* _____ *

P. 7.39 $I_{CQ} = 0.5 \text{ mA}$, $C_{\mu} = 0.15 \text{ pF}$, $f_T = 5 \text{ GHz}$, $\beta_0 = 150$
Find C_{π} , f_{β}

$$2\pi(5)10^9 = \frac{g_m}{C_{\pi} + 0.15 \text{ pF}}$$


$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.5 \text{ mA}}{25 \text{ mV}} = 20 \text{ mA/V}$$

$$C_{\pi} = \frac{20 \text{ mA/V}}{2\pi(5)10^9} - 0.15 \text{ pF} = \boxed{0.168 \text{ pF} = C_{\pi}}$$

$$f_{\beta} \equiv f_E / \beta_0 = \frac{5000 \text{ MHz}}{150} = \boxed{33.3 \text{ MHz} = f_{\beta}}$$

Miller's effect

Consider:

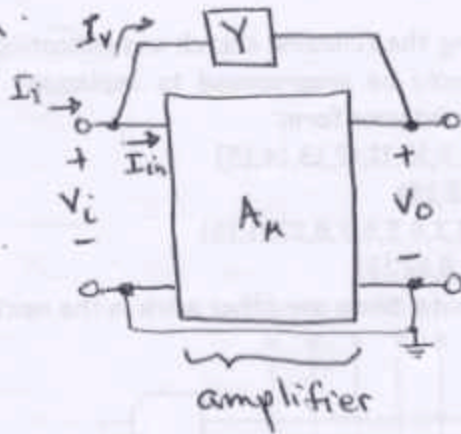

$Y = \text{admittance}$
if component is a cap
 $Y = sC$


$A_{\mu} = \text{amplifier's gain}$

Approx. \rightarrow assume A_{μ} does not depend on Y

Then
$$I_i = I_{in} + I_Y$$

$$I_Y \approx Y(V_i - V_o) = Y(1 - A_{\mu})V_i$$
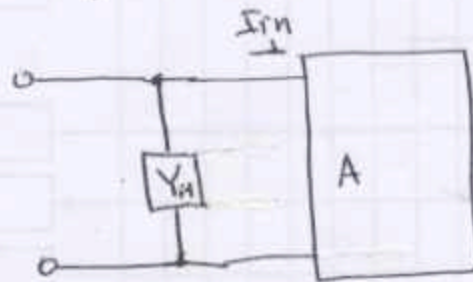
$$I_i = I_{in} + Y(1 - A_{\mu})V_i = I_{in} + Y_M V_i$$



$$Y_M = (1 - A)Y$$

If $Y = sC_{\mu}$


$$Y_M = (1 - A_{\mu})C_{\mu} s$$

$C_{\mu} \rightarrow$ augmented C_{μ} ;
if $A_{\mu} \ll -1$ (large & neg)
like in the CE

For $A_{\mu} \ll -1$

$C_{\mu} \rightarrow$ looks like a much larger capacitor from the input port.

Output port

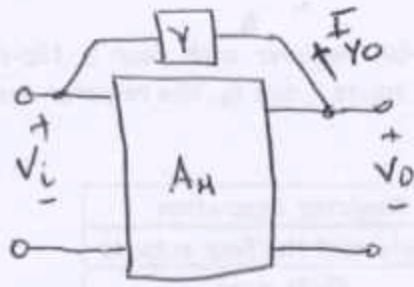

$$I_{Y0} = Y(V_o - V_i)$$

$$= Y\left(V_o - \frac{V_o}{A_M}\right)$$


$$= Y\left(1 - \frac{1}{A_M}\right)V_o$$

$$Y_o = \frac{I_{Y0}}{V_o} = Y\left(1 - \frac{1}{A_M}\right)$$

if $A_M \ll -1$

$$Y_o \approx Y$$


Common-emitter

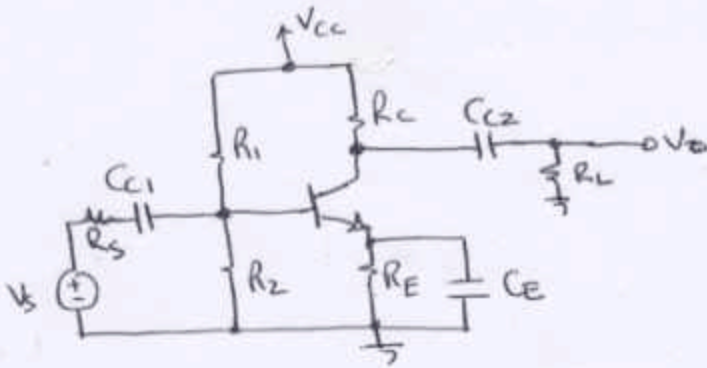


At high-freqs.

C_{c1}, C_{c2} & C_E are shorts

$V_{CC} \rightarrow$ ground

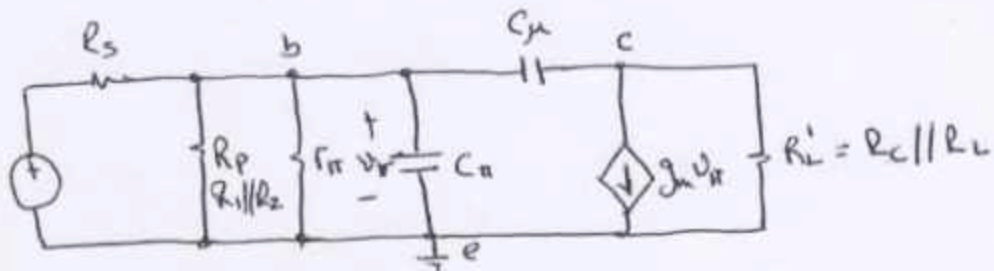
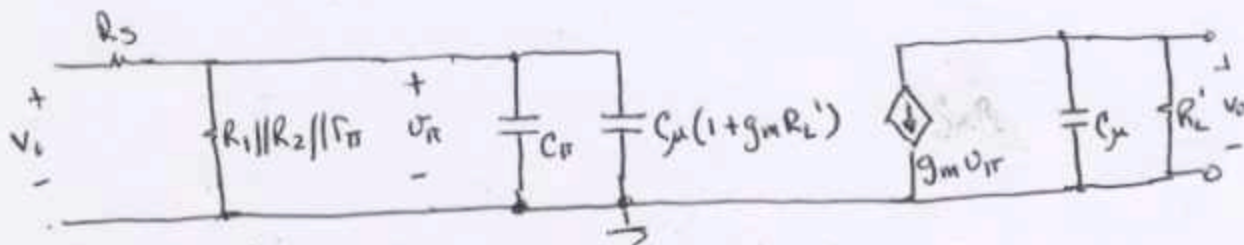
$$A_M = \frac{V_c}{V_b} \text{ (ignoring } C_{\mu}) = -g_m R_i'$$



In the input part of the circuit, we see an equivalent capacitance

$$C_{eq} = (r_{\pi} + C_{\mu}(1 + g_m R_L'))$$

Notice that, according our analysis of the RC circuits in lecture 1, this capacitance produces a pole at

$$\omega_{H1} = \frac{1}{(R_S \parallel r_{\pi} \parallel R_1 \parallel R_2) C_{eq}}$$

The output segment also exhibits a pole at

$$\omega_{H2} = \frac{1}{C_{\mu} R_L'}$$

Because typically R_S is smaller than R_L' , and also $C_{eq} \gg C_{\mu}$, $\omega_{H1} \ll \omega_{H2}$ and ω_{H1} dominates the high-frequency response of the CE.

Example

$$R_1 \parallel R_2 = 200 \text{ k}\Omega, \quad R_S = 5 \text{ k}\Omega, \quad r_{\pi} = 2.6 \text{ k}\Omega$$

$$R_C \parallel R_L = R_L' = 2 \text{ k}\Omega, \quad C_{\pi} = 4 \text{ pF}, \quad C_{\mu} = 0.2 \text{ pF}$$

and $g_m = 38.5 \text{ mA/V}$.

$$C_M = (1 + g_m R_L') C_{\mu} = 78 C_{\mu} = 15.4 \text{ pF}$$

equivalent cap. at base = $C_{eq} = 19.4 \text{ pF}$

$$\omega_{H1} = \frac{1}{(5 \text{ k}\Omega \parallel 2.5 \text{ k}\Omega \parallel 200 \text{ k}\Omega) (19.4 \text{ pF})} = \frac{1}{(1.65 \text{ k}\Omega) (19.4 \text{ pF})}$$

$$= \boxed{31.2 \text{ MHz}} \quad \text{Mrps}$$

$$\omega_{H2} = \frac{1}{(2 \text{ k}\Omega) (0.2 \text{ pF})} = \underline{2.5 \text{ MHz}} \quad \text{Grps}$$

Since ω_{H2} is larger than ω_{H1} , by more than a decade, ω_{H1} dominates the high-freq. response; it is the dominant high-freq. pole.

If there is no dominant high-frequency pole because two or more poles are closer than one decade, we can estimate the high-frequency pole using

$$f_{n, \text{eff}} \approx \frac{1}{\sum_{i=1}^n \frac{1}{f_i}}$$


example: 3 poles at 10MHz, 20MHz and 30MHz produce an "effective" h-f. pole at

$$f_n = \frac{1}{\frac{1}{10} + \frac{1}{20} + \frac{1}{30}} \approx 5.5 \text{ MHz}$$

* _____ *

Field-effect Transistors.


HF model:

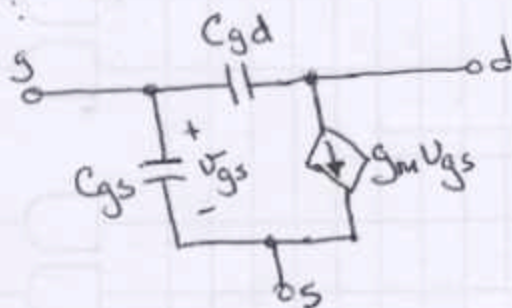

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

Miller's theorem applies to MOSFET circuits in the same way than it applies to BJT circuits.

Example: Problem 7.58

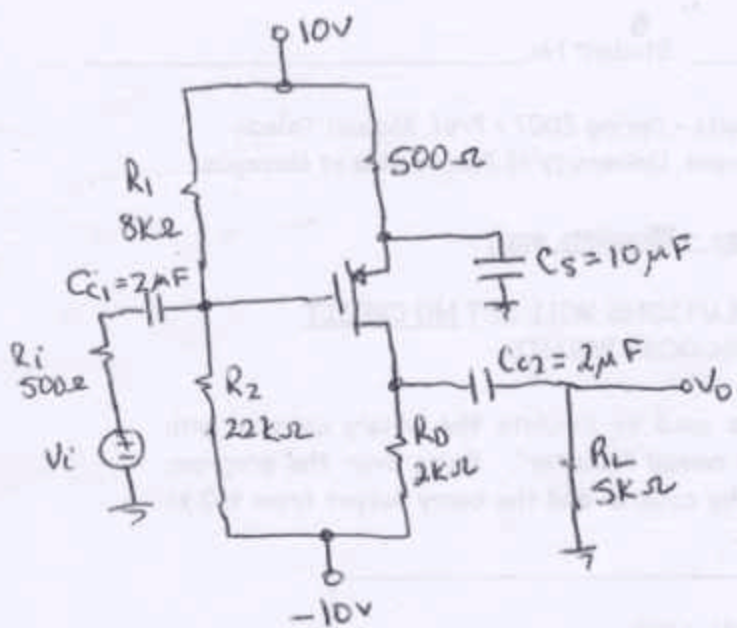

$$V_{TP} = -2V$$


$$K_P = 1\text{mA}/V^2$$

$$\lambda = 0$$

$$C_{GS} = 15\text{pF}$$

$$C_{GD} = 3\text{pF}$$

D.C. analysis

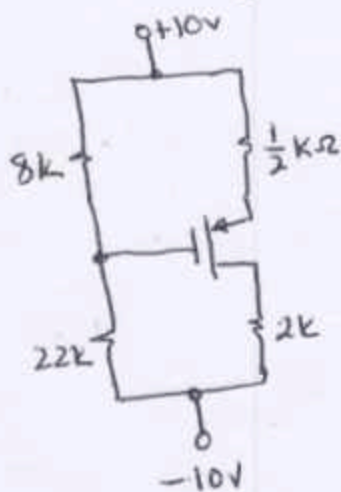

$$V_G = -10 + \frac{22}{30} 20 = 4.67V$$

$$I_D = K_P (V_{SG} + V_{TP})^2 = \frac{10 - V_{SG} - 4.67}{\frac{1}{2}k\Omega}$$

$$\left(\frac{1}{2}V^{-1}\right) (V_{SG}^2 - 4V_{SG} + 4) = 5.33 - V_{SG}$$

$$V_{SG}^2 - 2V_{SG} - 6.67 = 0$$

$$V_{SG} = \underline{3.77V}, -1.77V$$

$$g_m = 2K_P (V_{SG} - 2V) = 2\text{mA}/V^2 (3.77 - 2)$$

$$g_m = 3.54\text{mA}/V$$


midband gain

$$A_{MB} = - \frac{22 \parallel 8}{22 \parallel 8 + .5} \left(3.54 \frac{\text{mA}}{\text{V}} \right) (2\text{k} \parallel 5\text{k})$$

$$= - \frac{5.87}{6.37} (5) = \boxed{-4.6 \text{ V/V} = A_{MB}}$$

Miller gain = $A_M = -g_m R_L' = -5 \text{ V/V}$
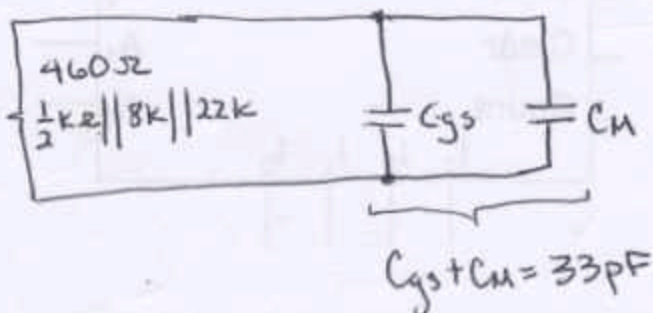
$$C_M = C_{gd} (1 + 5) = 3 \text{ pF} (6) = \boxed{18 \text{ pF} = \text{Miller's cap.}}$$



$$\omega_{H1} = \frac{1}{33 \text{ pF} \times 460 \Omega}$$

$$\boxed{\omega_{H1} = 65.8 \text{ Mrps}} \\ 10.5 \text{ MHz}$$

The other pole is at

$$\omega_{H2} = \frac{1}{(5\text{k} \parallel 2\text{k}) 3 \text{ pF}} = 233 \text{ Mrps} = 37 \text{ MHz}$$

No dominant pole. Effective pole at $\omega_H \approx \underline{8.2 \text{ MHz}}$

We can also calculate the low-freq. poles.

$$R_{eqC1} = \frac{1}{2} \text{ k}\Omega + 8\text{k} \parallel 22\text{k} = 6.37 \text{ k}\Omega \Rightarrow \omega_{LP1} = \frac{1}{2\mu\text{F} \times 6.37 \text{ k}\Omega} \\ = 78.5 \text{ rps} = 12.5 \text{ Hz}$$

$$R_{eqC2} = 7 \text{ k}\Omega ; \omega_{LP2} = \frac{1}{2\mu\text{F} \times 7 \text{ k}\Omega} = 71.4 \text{ rps} = 11.4 \text{ Hz}$$

$$R_{eqC3} = 500 \Omega \parallel \frac{1}{g_m} = 500 \parallel 282 \Omega = 180.3 \Omega ; \omega_{LP3} = \frac{1}{(10\mu\text{F})(180.3 \Omega)} \\ = 555 \text{ rps} = 88.3 \text{ Hz}$$

The zero due to the bypass cap. is located at

$$\omega_z = \frac{1}{10\mu F \times 500\Omega} = 200 \text{ rps} = 31.8 \text{ Hz}$$

We get an effective low-freq. pole at

$$\omega_L \sim \sum \omega_i = 12.5 + 11.4 + 88.3 - 31.8 \text{ Hz} \\ \approx 80.4 \text{ Hz}$$

