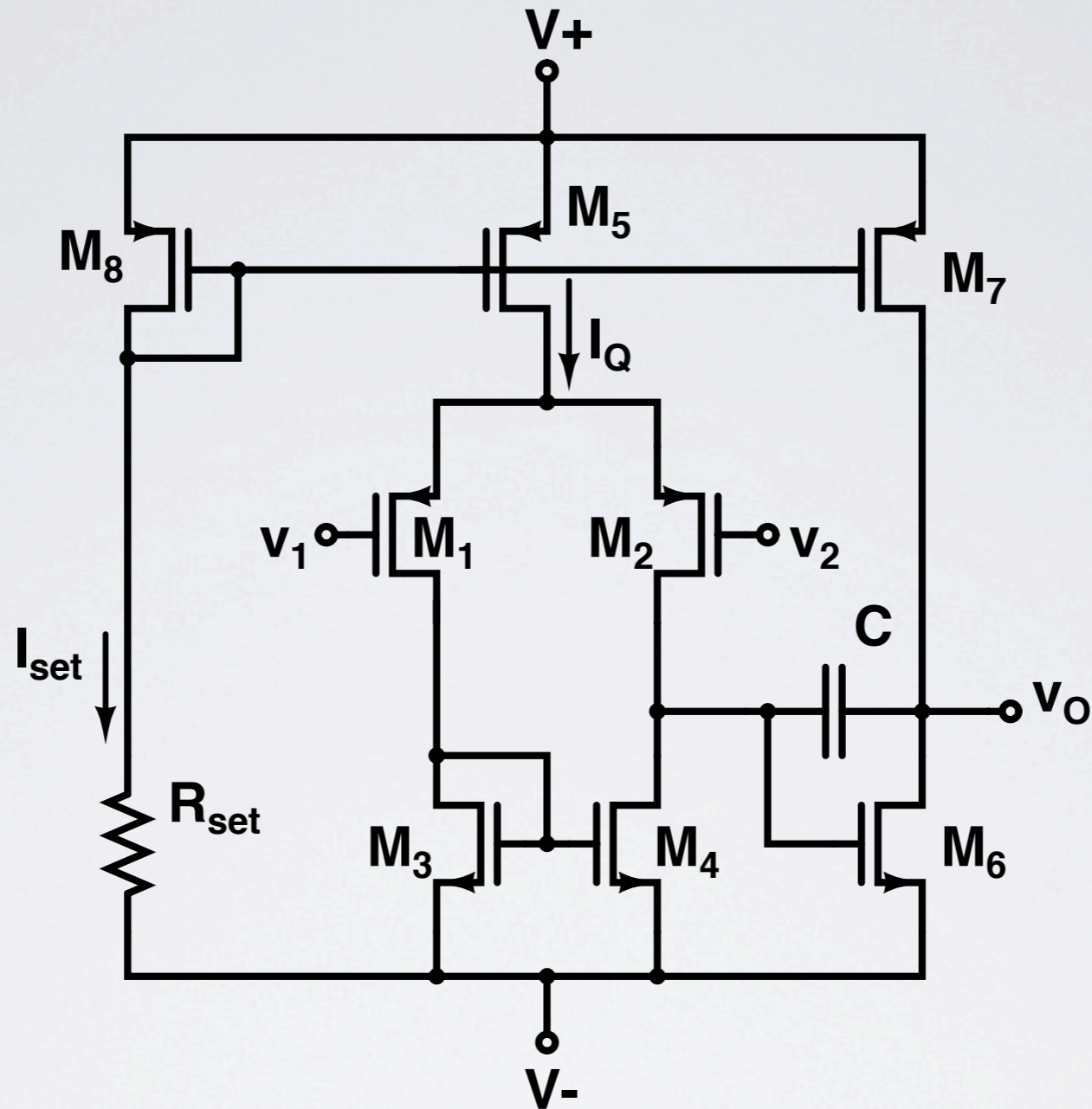


# CMOS OPAMPS

INEL4202 Electronics II









Example 13.8: Find DC bias current when  $V_{TN}=0.5V$ ,  $\frac{1}{2}\mu_n C_{ox}=20\mu A/V^2$ ,  $\lambda_n=0.02V^{-1}$ ,  $V_{TP}=-0.5V$ ,  $\frac{1}{2}\mu_p C_{ox}=10\mu A/V^2$ ,  $\lambda_p=0.02V^{-1}$ ,  $R_{SET}=225k\Omega$ ,  $(W/L)_3=(W/L)_4=6.25$ ,  $(W/L)_{OTHER}=12.5$ ,  $V_+=5V$ ,  $V_-=-5V$ . (ANSWER:  $I_{REF}=39.7\mu A$ )

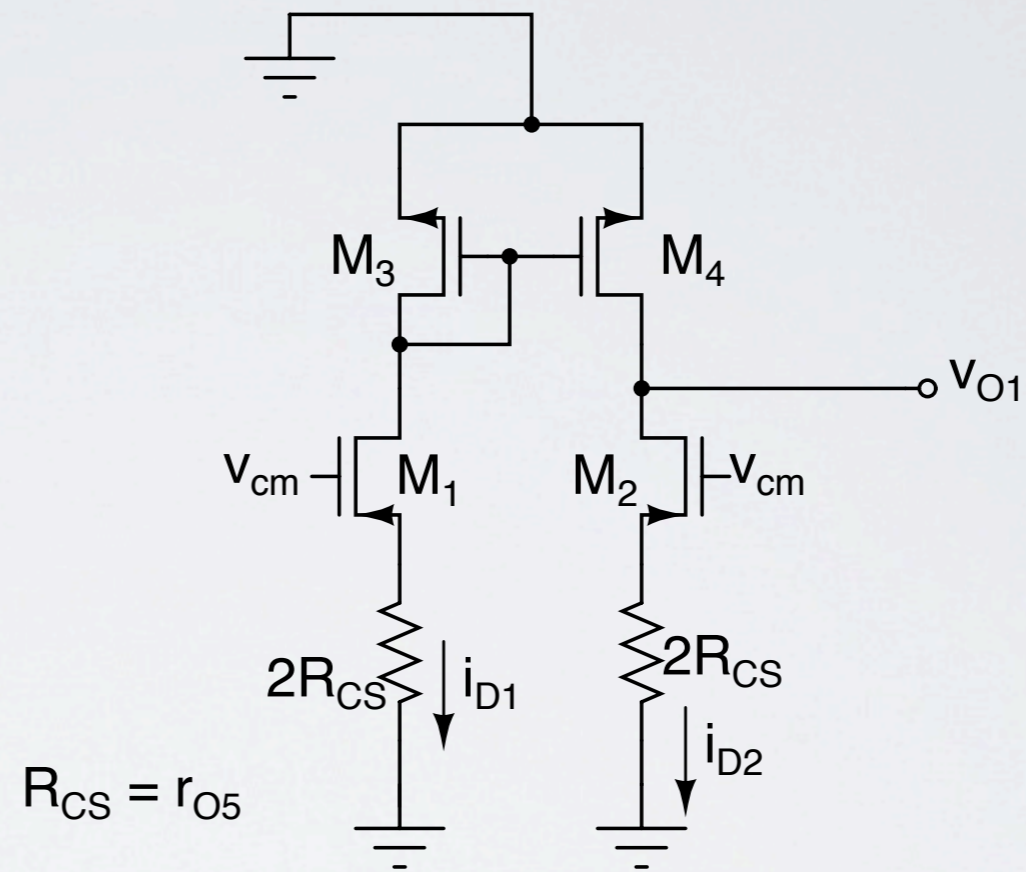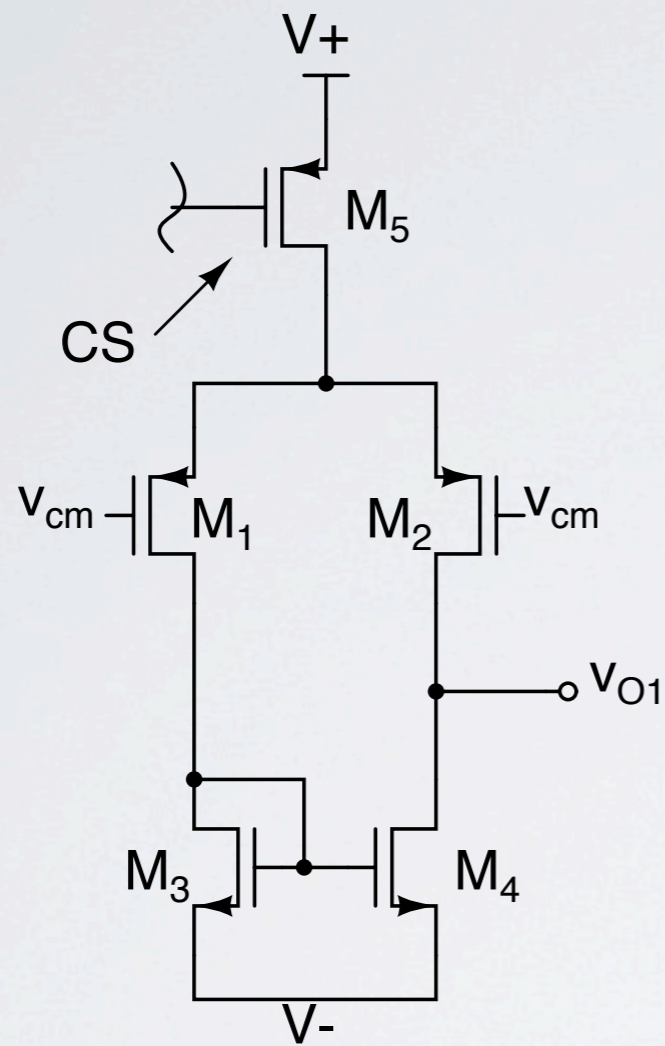Example 13.9: Find gain. (ANSWER:  $A_v=(125)(125)=15,625$ )

$A_{CM}$  for differential stage with active load due to and error  $\epsilon$  in  $K$  ( for example,  $(W/L)_1 = (1 + \epsilon) (W/L)_2$ )



$$R_{CS} = r_{O5}$$

small-signal equivalent ckt.  
 $i_{D1}$  is the incremental drain current


$A_{CM}$  for differential stage with active load due to and error  $\epsilon$  in  $K$  (for example,  $(W/L)_1 = (1 + \epsilon) (W/L)_2$ )

$$\begin{aligned}
 i_{d,1} &= g_{m1} v_{gs,1} \\
 v_{gs,1} &= v_{g,1} - v_{s,1} \\
 v_{g,1} &= v_{cm} \\
 v_{s,1} &= 2R_{CS} \times i_{d,1} \\
 i_{d,1} &= g_{m1} (v_{cm} - 2R_{CS} \times i_{d,1}) \\
 i_{d,1} (1 + g_{m1} 2R_{CS}) &= g_{m1} v_{cm} \\
 i_{d,1} &= \frac{g_{m1} v_{cm}}{1 + g_{m1} 2R_{CS}} \\
 i_{d,2} &= \frac{g_{m2} v_{cm}}{1 + g_{m2} 2R_{CS}} \\
 g_{m1} &= g_{m2} (1 + \epsilon) \\
 i_{o,1} &= i_{d,1} - i_{d,2} = \frac{g_{m2} (1 + \epsilon) v_{cm}}{1 + g_{m2} (1 + \epsilon) 2R_{CS}} - \frac{g_{m2} v_{cm}}{1 + g_{m2} 2R_{CS}} \\
 v_{o,1} &= i_{o,1} (r_{o4} || r_{o2})
 \end{aligned}$$

If  $2g_{m2}\epsilon R_{CS} \ll 1$ , (or equivalently,  $\epsilon \ll \frac{1}{2g_{m2}R_{CS}}$ )


$$\begin{aligned}
 i_{o,1} &\simeq \frac{g_{m2}\epsilon v_{cm}}{1 + g_{m2} 2R_{CS}} \\
 A_{cm,1} &= \frac{v_{o,1}}{v_{cm}} = \frac{g_{m2}\epsilon (r_{o4} || r_{o2})}{1 + g_{m2} 2R_{CS}} \Rightarrow CMRR = \frac{1 + g_{m2} 2R_{CS}}{\epsilon}
 \end{aligned}$$

# Three-stage cmos opamp

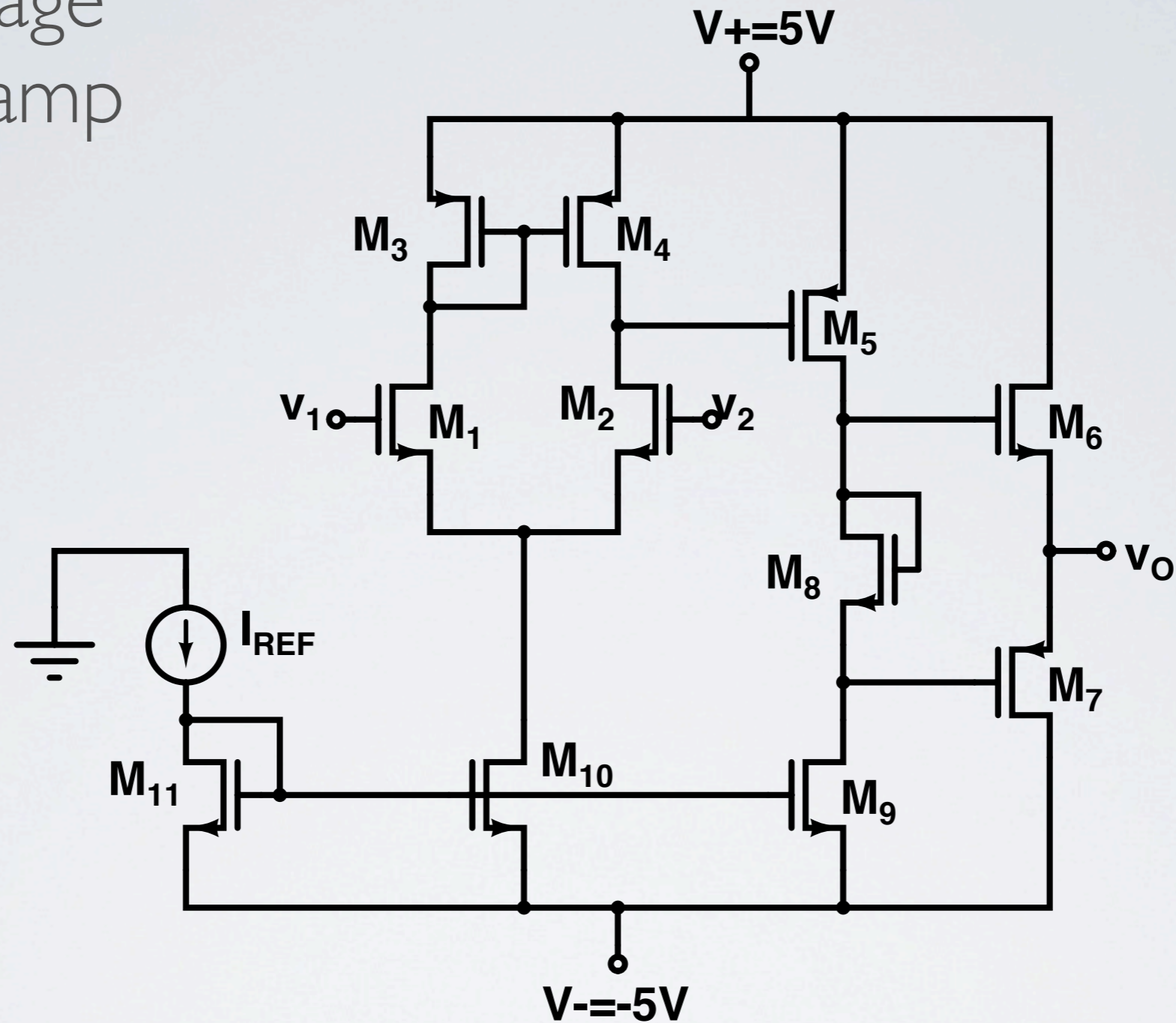


**Example 13.10:** Find DC and AC characteristics.  $V_{TN}=0.7V$ ,  $k_n'=80\mu A/V^2$ ,  $\lambda_n=0.01V^{-1}$ ,  $V_{TP}=-0.7V$ ,  $k_p'=40\mu A/V^2$ ,  $\lambda_p=0.015V^{-1}$ ,  $I_{REF}=160\mu A$ ,  $(W/L)_1=(W/L)_2=15/1$ ,  $(W/L)_3=(W/L)_4=40/1$ ,  $(W/L)_5=80/1$ ,  $(W/L)_6=25/1$ ,  $(W/L)_7=50/1$ ,  $(W/L)_9=(W/L)_{10}=(W/L)_{11}=20/1$ . Select  $(W/L)_8$  so that  $V_{GS6}=V_{GS7}=0.85V$ .

# Three-stage cmos opamp

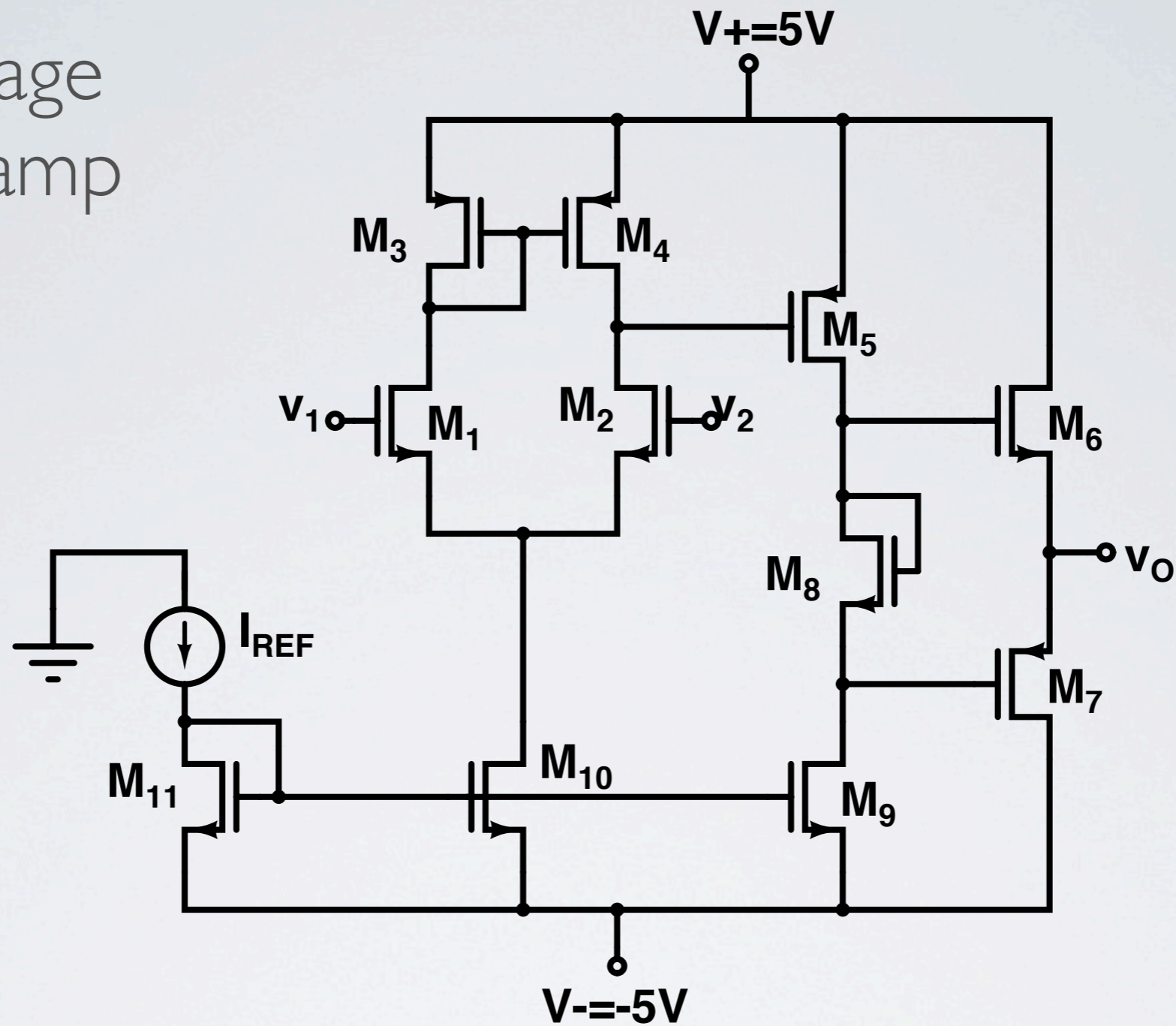

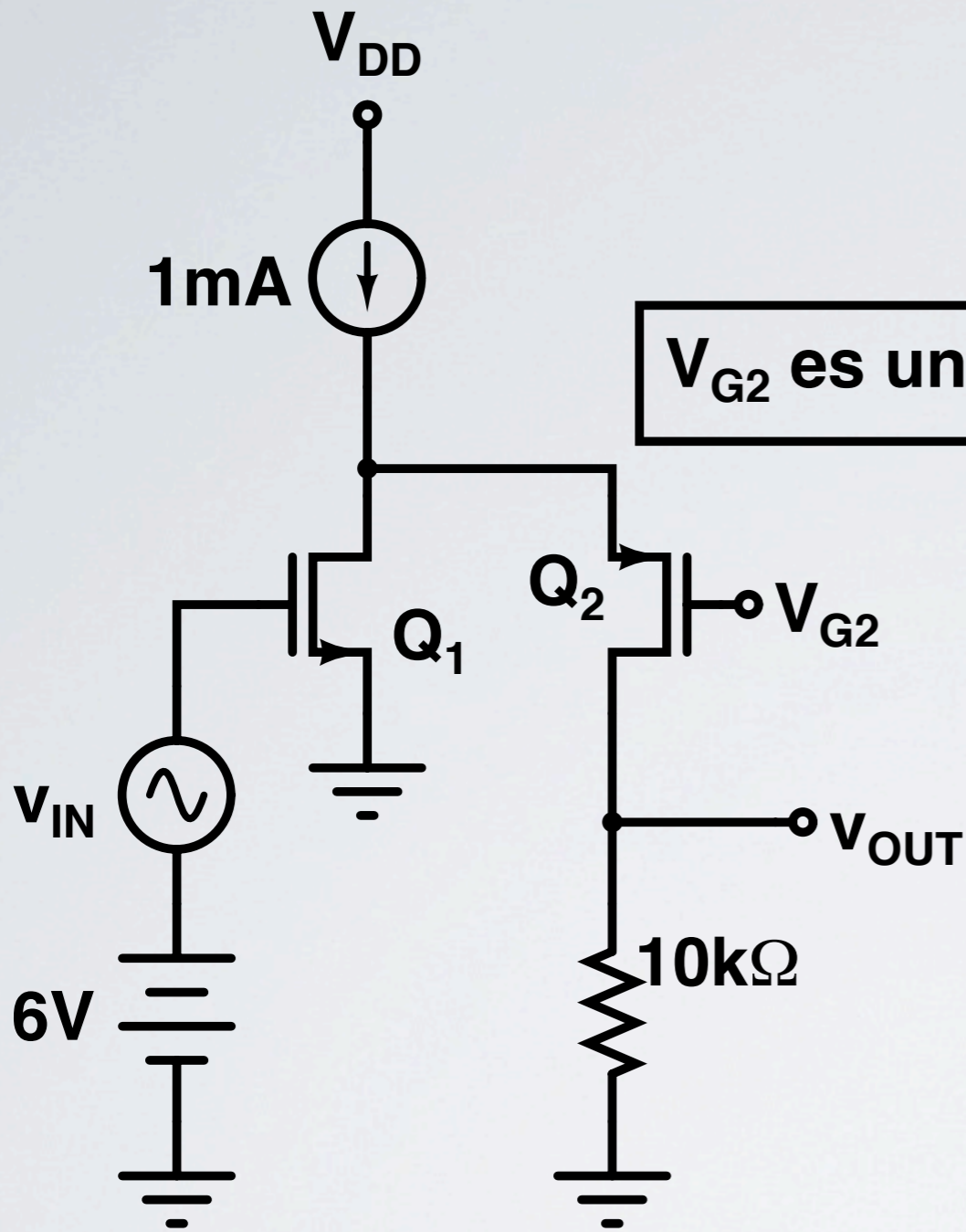
**Example:** Find DC and AC characteristics.  $V_{TN}=0.7V$ ,  $k_n'=80\mu A/V^2$ ,  $\lambda_n=0.01V^{-1}$ ,  $V_{TP}=-0.7V$ ,  $k_p'=40\mu A/V^2$ ,  $\lambda_p=0.015V^{-1}$ ,  $I_{REF}=160\mu A$ ,  $(W/L)_1=(W/L)_2=15/1$ ,  $(W/L)_3=(W/L)_4=40/1$ ,  $(W/L)_5=80/1$ ,  $(W/L)_6=25/1$ ,  $(W/L)_7=50/1$ ,  $(W/L)_9=(W/L)_{10}=(W/L)_{11}=20/1$ . Select  $(W/L)_8$  so that  $V_{GS6}=V_{GS7}=0.85V$ .

**ANSWER:**  $(W/L)_8 = 4$ ;  $I_{D6}=I_{D7}=22.5\mu A$ ;  $A_v=(219)(-253)=-55407 V/V$ .



$$K_{n,p} = 20\text{mA/V}$$


$$V_{Tn} = -V_{TP} = 1\text{V}$$

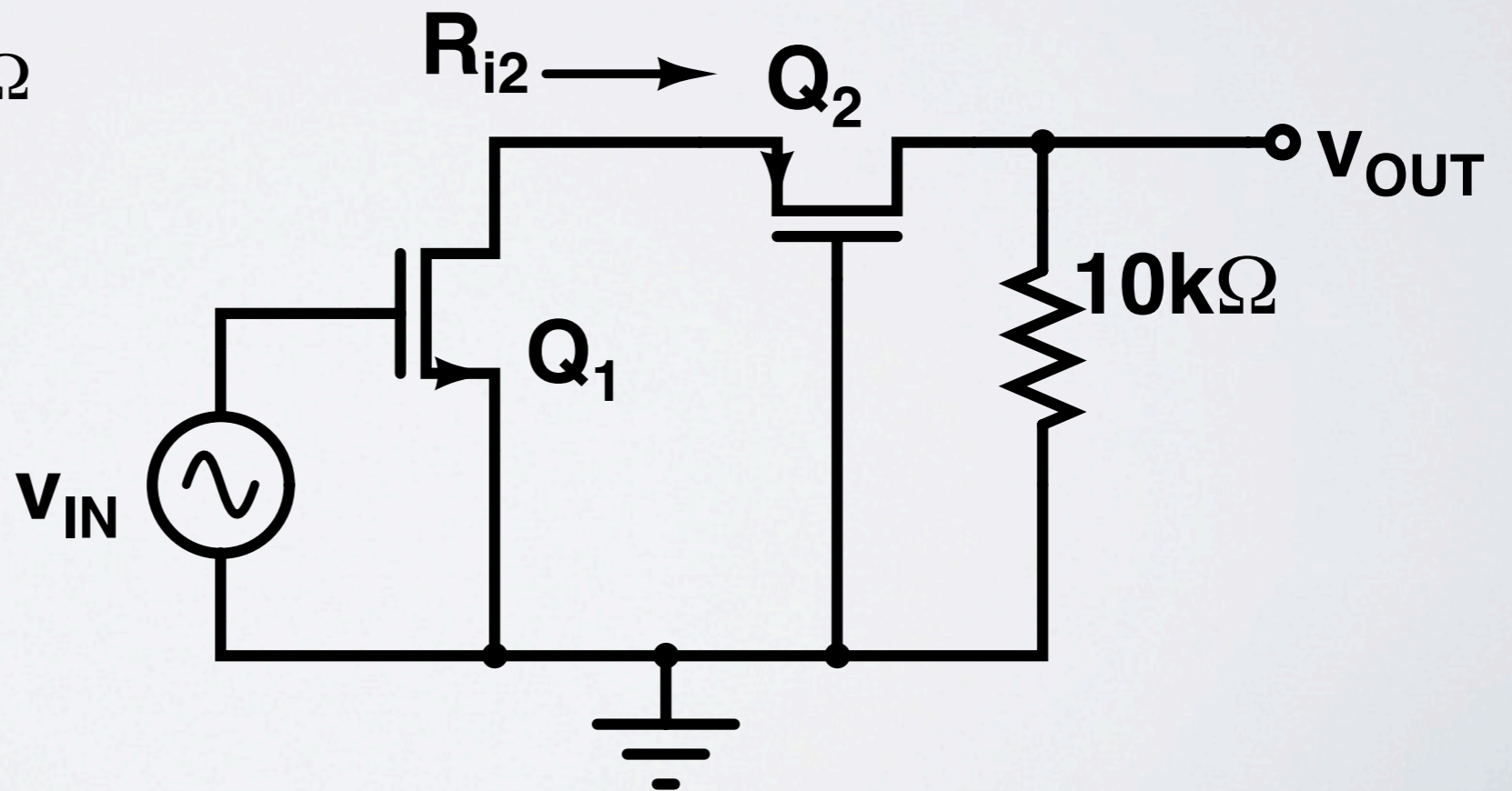

For the following CMOS amplifier, where  $V_{b1}$  and  $V_{b2}$  are DC voltages for proper operation of the circuit:

- identify the negative and the positive terminals
- find the expression for the differential gain  $A_{id} = V_{out}/V_{id}$
- find the expression for the differential input resistance  $R_{ind}$
- find the expression for the output resistance  $R_{out}$

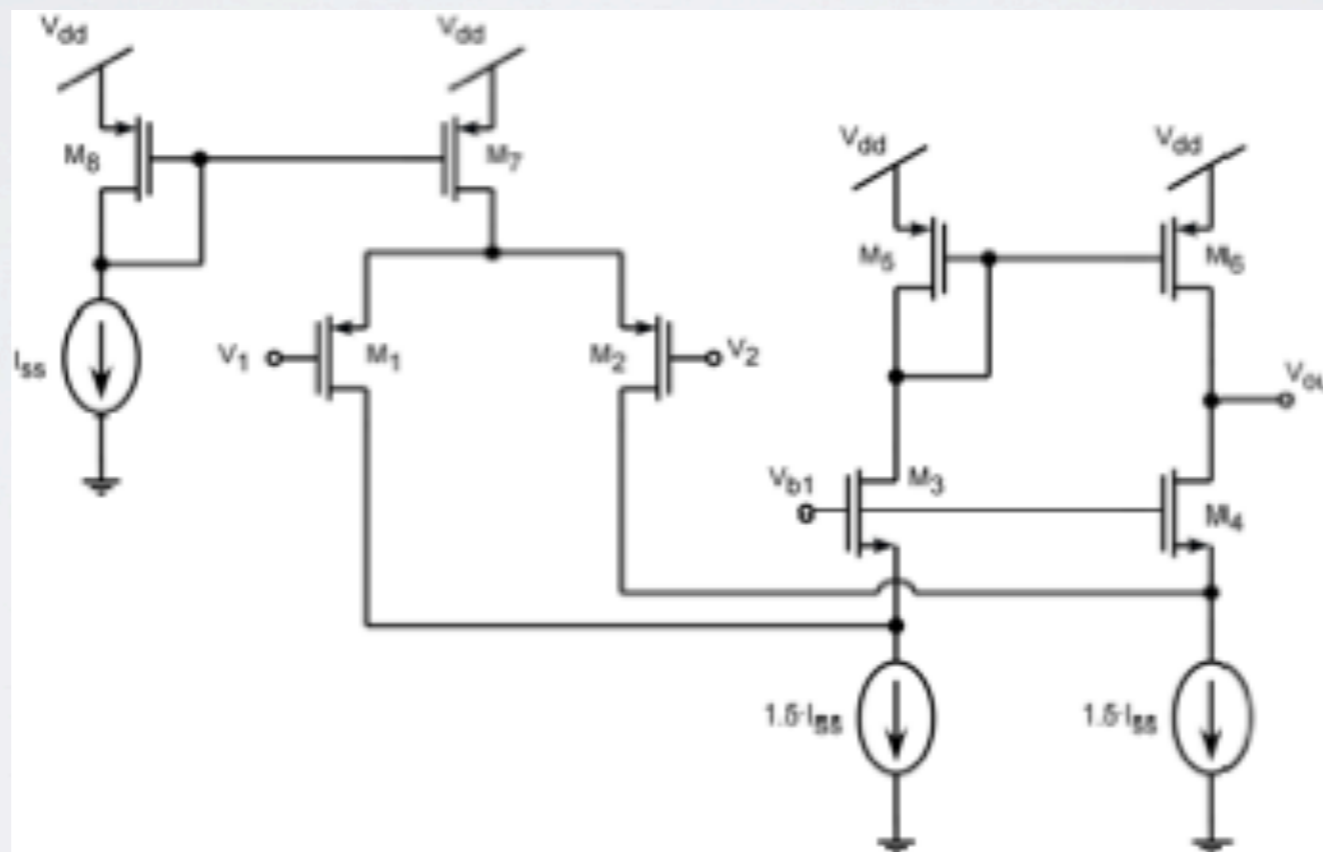Assume:  $I_{ss}$  = ideal current source




III. For the following CMOS amplifier, where  $V_{b1}$  and  $V_{b2}$  are DC voltages for proper operation of the circuit:

- identify the negative and the positive terminals
- find the expression for the differential gain  $A_{id} = V_{out}/V_{id}$
- find the expression for the differential input resistance  $R_{ind}$
- find the expression for the output resistance  $R_{out}$

Assume:  $I_{ss}$  = ideal current source

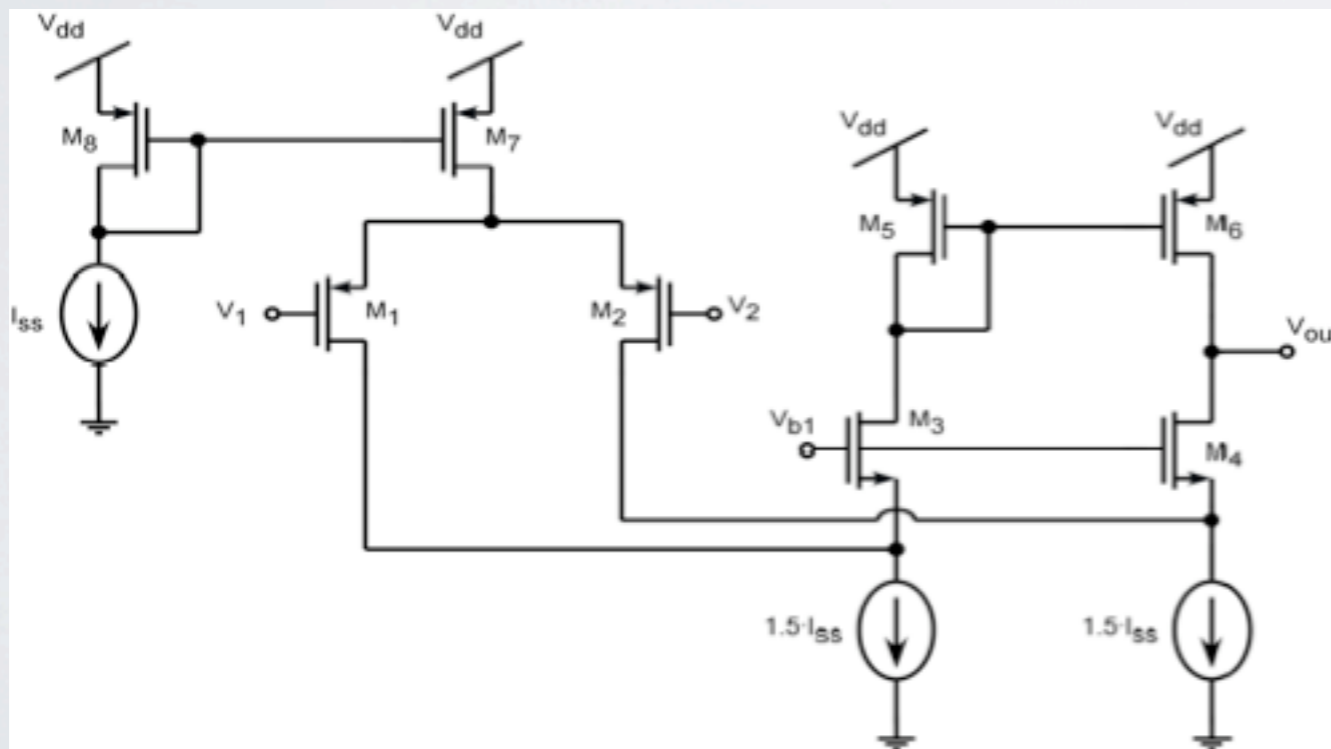a)  
 $v_1 \uparrow \Rightarrow i_{d1} \uparrow \Rightarrow i_{d5} \downarrow \Rightarrow i_{d6} \downarrow$   
 $\therefore v_1$  is + ;  $v_2$  is -




$$\begin{aligned}
 \text{b) } A_{id} &= \frac{v_{OUT}}{v_{id}} = g_{m1} R_O \\
 R_O &= r_{O6} \parallel r_{O4} (1 + g_{m4} r_{O2}) \\
 g_{m1} &= 2\sqrt{K_P I_{SS}/2} & g_{m4} &= 2\sqrt{K_N I_{SS}} \\
 r_{O6} &= \frac{1}{\lambda_{P6} I_{SS}} & r_{O2} &= \frac{2}{\lambda_{P2} I_{SS}} \\
 r_{O4} &= \frac{1}{\lambda_{N4} I_{SS}}
 \end{aligned}$$

$$\text{c) } R_{ind} = \infty$$
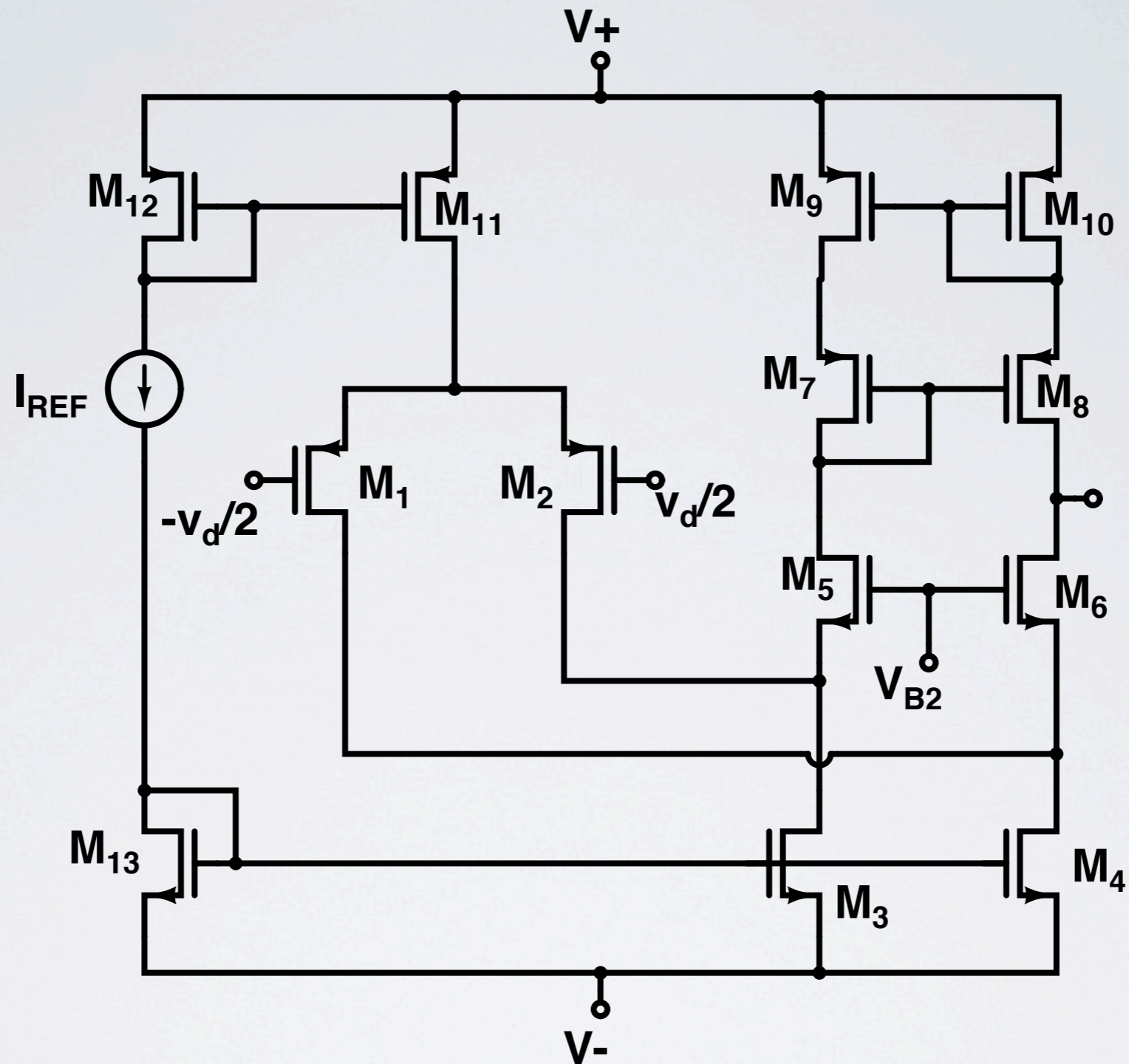
$$\begin{aligned}
 \text{d) } R_O &= r_{O6} \parallel r_{O4} (1 + g_{m4} r_{O2}) \\
 g_{m1} &= 2\sqrt{K_P I_{SS}/2} & g_{m4} &= 2\sqrt{K_N I_{SS}} \\
 r_{O6} &= \frac{1}{\lambda_{P6} I_{SS}} & r_{O2} &= \frac{2}{\lambda_{P2} I_{SS}} \\
 r_{O4} &= \frac{1}{\lambda_{N4} I_{SS}}
 \end{aligned}$$





Example:  $I_{REF} = 100\mu A$ ,  $k_n' = 80\mu A/V^2$ ,  $K_p' = 40\mu A/V^2$ ,  $(W/L) = 25$ ,  $\lambda_n = \lambda_p = 0.02V^{-1}$ .  
 Find voltage gain. (ANSWER:  $A_d = 32000$ )