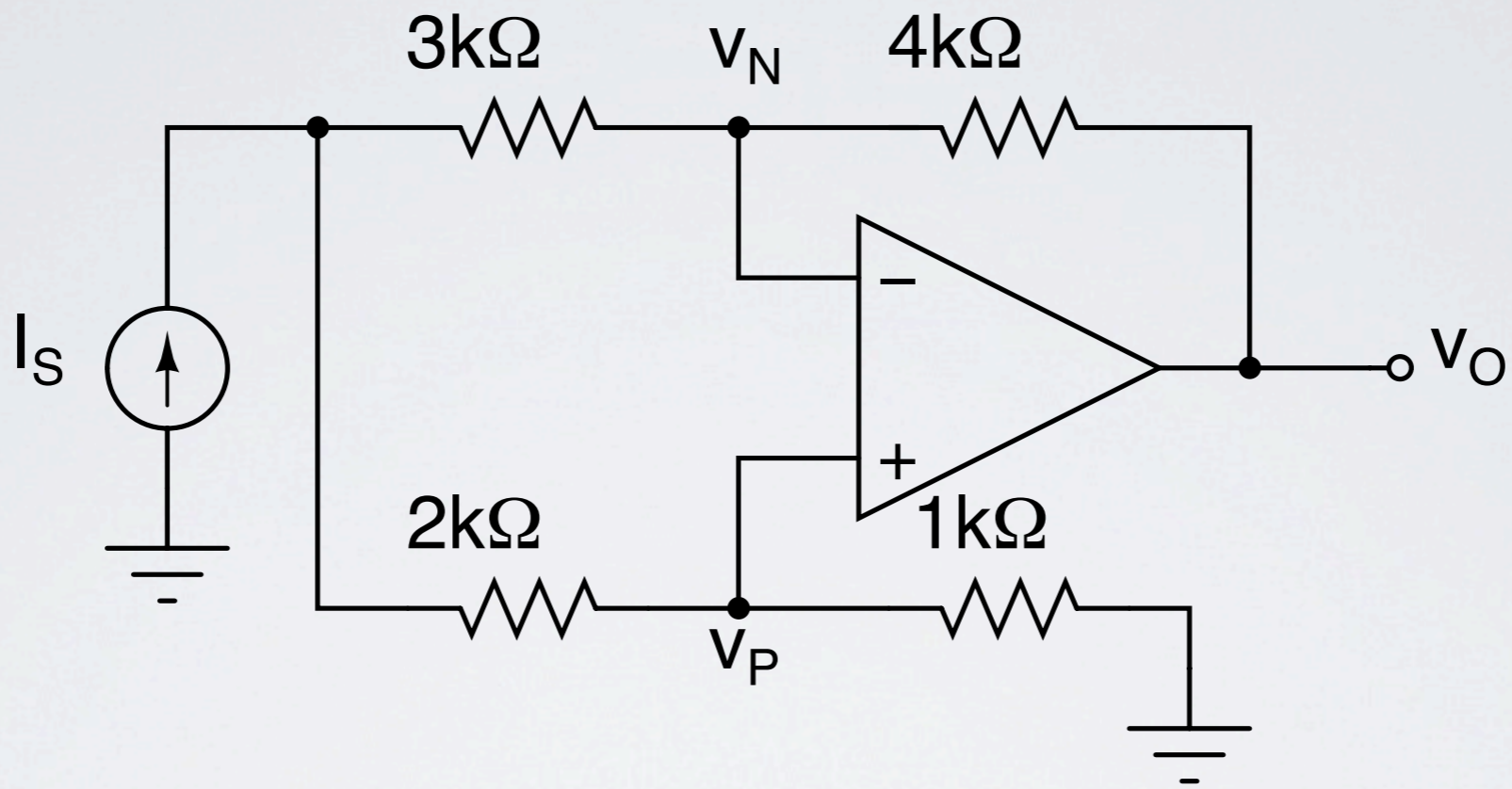


REVIEW PARTIAL EXAM 3


INEL 4202 Electronics II
Spring 2013

TOPICS

17 (3/19)	Operational amplifiers, Summers, integrators, inverting and non-inverting amplifiers	2.1- 2.4	2(1, 2, 8, 9, 11, 12, 16, 20, 22, 30, 44, 46, 49, 60, 62, 72, 74)
18 (3/21)	Integrators and differentiators, Applications	2.5	2.79, 2.80
19 (4/2)	Current sources	7.(4,5)	7.(46, 47, 48, 55, 56, 58, 67, 70, 76, 77, 78)
20 (4/4)	The differential amplifier	8.(1-3, 5)	8.(1, 2, 9, 25, 27, 29, 32, 33, 53, 60, 61, 62, 63, 64, 85, 91, 94, 102)
21 (4/9)	DC analysis of the 741 opamp	12.(3,4)	12.(23, 24, 25, 28, 29, 37, 39)
22 (4/11)	AC analysis of the 741 op-amp	12.5	12.(42, 43, 47, 50)
23 (4/18)	Frequency response and slew rate	12.6	12.(59, 62, 63)
24 (4/23)	CMOS opamp DC and AC analysis	12.1	12.(2, 3, 5, 6)
25 (4/25)	Freq. resp. and slew rate of CMOS opamp		12.(9, 10, 11)
26 (4/30)	Folded cascode opamp	12.2	12.(15, 16, 18, 19)



$$\beta = 100$$

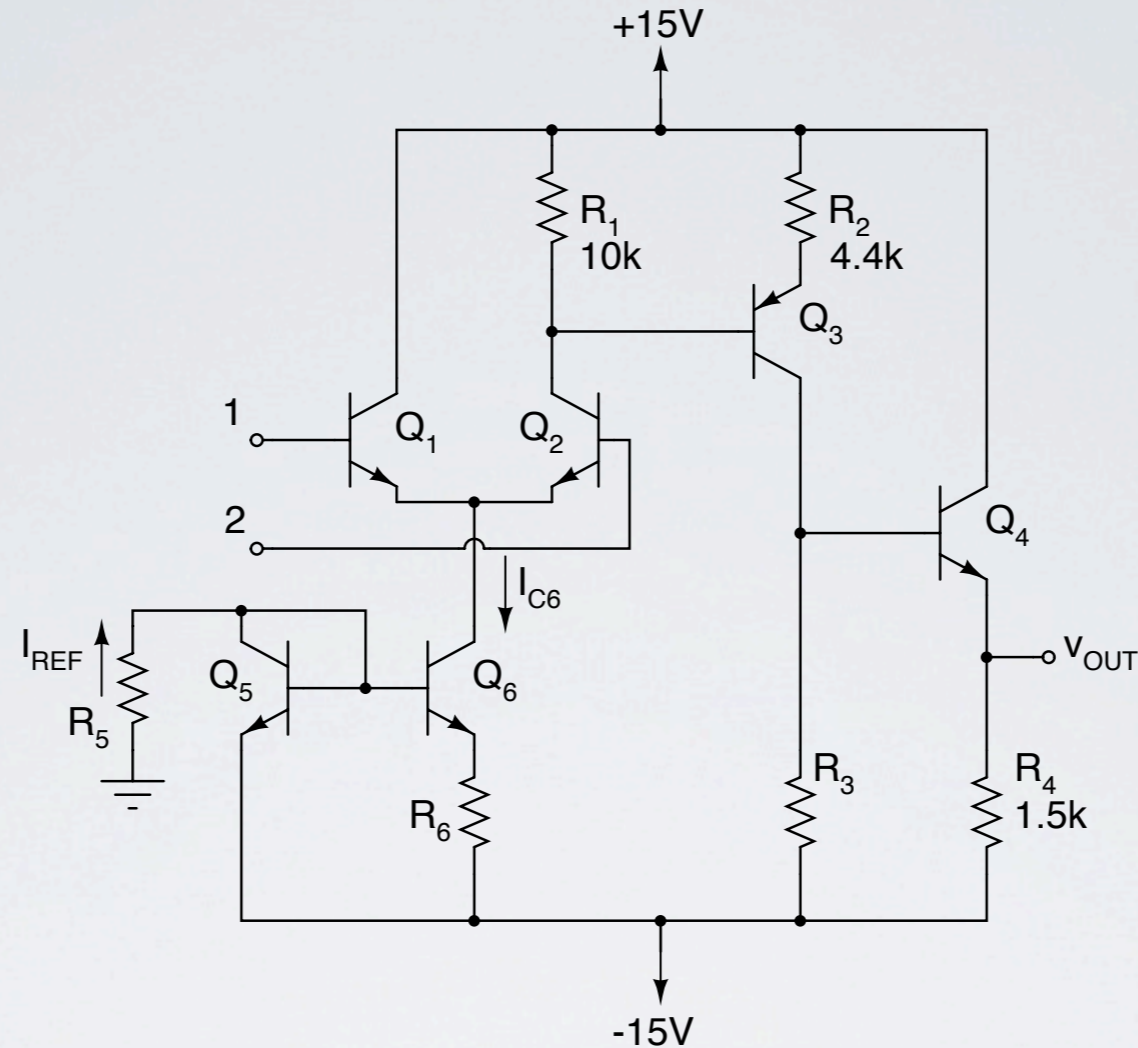

1. Assuming $R_5 = 50k\Omega$, $R_3 = 10k\Omega$, $R_6 = 0$, and that the area of Q_6 equals 5 times the area of Q_5 , find:
 - (a) the differential gain $A_d = \frac{v_{OUT}}{v_1 - v_2}$ (40 points)
 - (b) the input resistance R_{in} seen by differential signals between terminals 1 and 2. (15 points)
 - (c) the output resistance R_{out} at the output terminal. (15 points)
2. Assuming $I_{C6} = 1mA$, select R_3 so that $v_{OUT} \approx 0V$ when $v_1 = v_2 = 0V$. (15 points)
3. Select R_5 and $R_6 \neq 0$ such that $i_{C6} = I_{REF}/5 = 0.2mA$ and equal areas for Q_5 and Q_6
4. Find the Common-mode rejection ratio (CMRR) for your selection of R_6 in the previous problem. Assume $V_A = 100V$. (15 points)

1. (a) To find the gain, we need to determine the bias currents.

$$I_{REF} = \frac{15 - 0.7}{R_5} = \frac{14.3V}{50K} = 286 \mu A$$

$$I_{C6} = 5 \times I_{REF} = 1.43 \text{ mA}$$

$$I_{C2} = \frac{1}{2} I_{C6} = 0.715 \text{ mA}$$

$$\therefore V_{C2} = 15 - 10K (0.715 \text{ mA}) = 7.85V$$

$$I_{C3} = \frac{15V - (V_{C2} + 0.7)}{4.4K\Omega} = \frac{15 - (7.85 + 0.7)}{4.4K} = 1.47 \text{ mA}$$

$$\therefore V_{B4} = -15 + (1.47 \text{ mA})(R_3) = -15 + (1.47 \text{ mA})(10K) = -0.37V$$

$$I_{E4} = \frac{V_{B4} - 0.7 + 15}{1.5K} = 9.3 \text{ mA}$$

From this we can find the g_m 's

$$g_{m2} = \frac{0.715 \text{ mA}}{25 \text{ mV}} = 0.0286 \text{ A/V}$$

$$g_{m3} = \frac{1.47 \text{ mA}}{25 \text{ mV}} = 0.0588 \text{ A/V}$$

$$g_{m4} = \frac{9.3 \text{ mA}}{25 \text{ mV}} = 0.372 \text{ A/V}$$

The load at the collector of C_2 is

$$R_{C2} = R_C \parallel (R_{E3} + (\beta + 1) 4.4K) \\ = 10K \parallel \left[\frac{100(25)}{1.47} + 101(4.4K) \right] = 9.78K\Omega$$

$$\therefore \frac{V_{C2}}{V_1 - V_2} = + \frac{1}{2} g_{m2} R_{C2} = \frac{1}{2} (0.0286 \text{ A/V})(9.78K\Omega) = 140 \text{ V/V}$$

$$\frac{v_{c3}}{v_{c2}} = \frac{-g_{m3} R_{c3}}{1 + g_{m3} R_2}$$

$$R_{c3} = R_3 // (r_{\pi 4} + 101 \times 1.5k\Omega) = 10k // \left(\frac{100}{0.372} + 151.5k \right) \\ = 10k // (151.8k\Omega) = 9.38k\Omega \quad \leftarrow$$

$$\frac{v_{c3}}{v_{c2}} = \frac{-0.0588 \times 9.38k\Omega}{1 + 0.0588 \times 4.4k} = -2.12 \text{ V/V} \quad \leftarrow$$

$$\frac{v_{e4}}{v_{c3}} = \frac{+g_{m4} R_4}{1 + g_{m4} R_4} = \frac{0.372(1500)}{1 + 0.372 \times 1500} = 0.998 \quad \leftarrow$$

$$A_d = (+140 \text{ V/V}) (-2.12 \text{ V/V}) (0.998 \text{ V/V}) = \boxed{-296.3 \text{ V/V}} \quad \leftarrow$$

$$(b) R_{in} = 2r_{\pi} = 2 \times \frac{100}{g_{m2}} = 2 \times \frac{100}{0.0286 \text{ A/V}} = \boxed{7k\Omega}$$

$$(c) R_{out} = 1.5k // \frac{r_{\pi 4} + R_3}{101} = 1.5k // \frac{\frac{100}{0.372} + 10k\Omega}{101} = \boxed{95.2\Omega}$$

$$(2) \text{ if } I_{C6} = 1 \text{ mA}, I_{C2} = 0.5 \text{ mA}, v_{c2} = 10 \text{ V}; I_{C3} = \frac{15 - 10.7}{4.4k} = 0.98 \text{ mA}$$

$$\text{For } v_{out} = 0, v_{c3} = +0.7 \text{ V}; \therefore R_3 = \frac{15.7 \text{ V}}{0.98 \text{ mA}} = \boxed{16k\Omega}$$

$$3) R_5 = (15 \text{ V} - 0.7) / 1 \text{ mA} = 14.3k; R_6 = (V_T / I_{C6}) * \ln(I_{REF} / I_{C6}) = (0.025 \text{ V} / 0.2 \text{ mA}) \ln(5) = 201 \text{ Ohms}$$

$$4) R_{c5} = r_{o6} (1 + g_{m6} \times R_6) = (100 \text{ V} / 0.2 \text{ mA}) \{ 1 + (0.2 \text{ mA} / 0.025 \text{ V}) 201 \} = 1.3 \text{ MOhms}$$

$$|A_{CM}| = g_{m2} R_{c2} / (1 + 2g_{m2} R_{c5}) = R_{c2} / 2R_{c5} = 10k / 2.6M = 0.00192 \text{ V/V}$$

$$\text{Re-calculate } A_{dm} \text{ with the new } I_{C6} = 0.2 \text{ mA} \text{ and calc. } CMRR = 20 \times \log(|A_{dm} / A_{cm}|)$$

