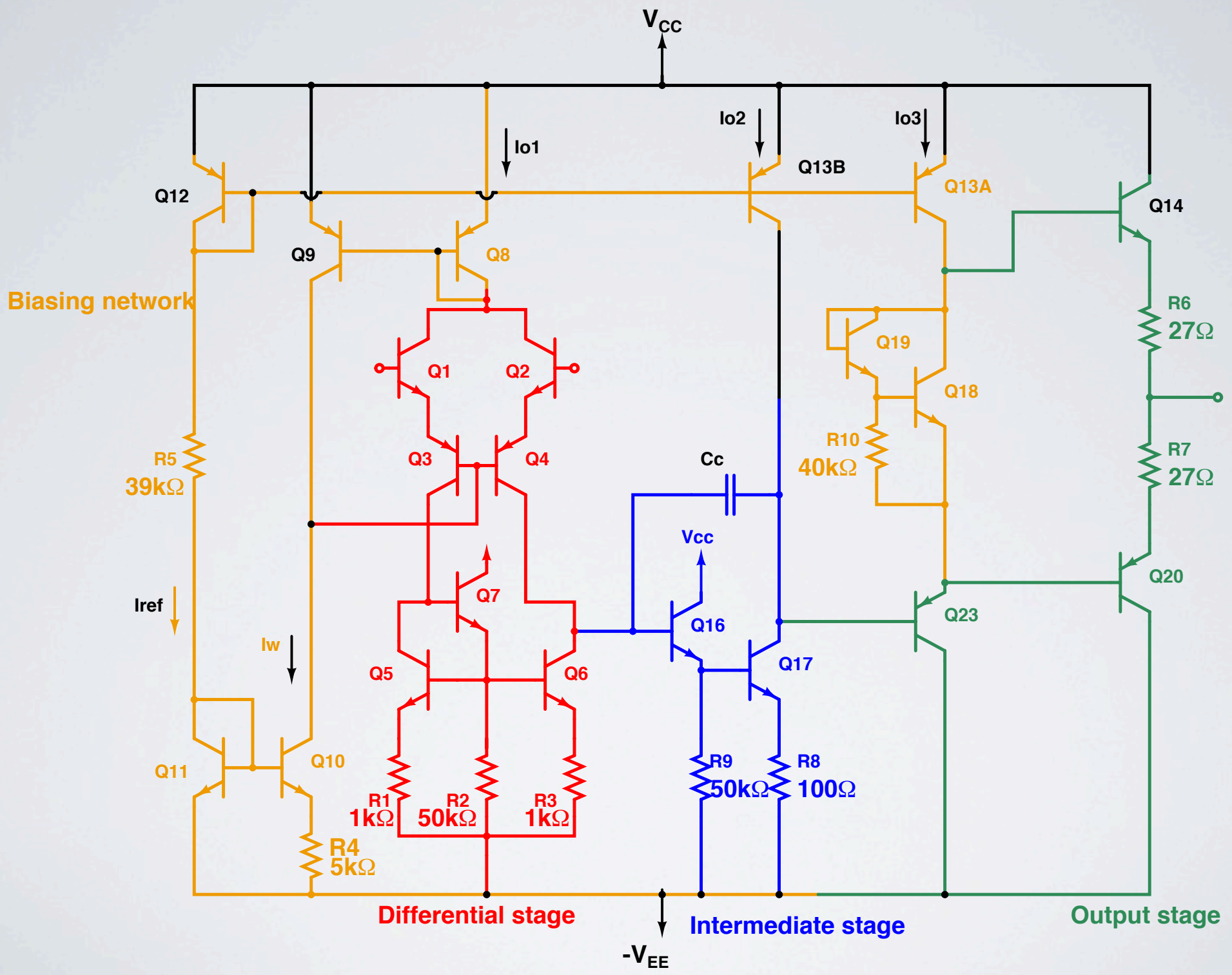


# ANALYSIS OF THE UA741

INEL 4202 - Electronics II



- Standard npn transistors:  $I_S = 10^{-14}A$        $\beta = 200$        $V_A = 125V$
- Standard pnp transistors:  $I_S = 10^{-14}A$        $\beta = 50$        $V_A = 50V$
- $Q_{13A}$ :  $I_{SA} = 0.25 \times 10^{-14}A$
- $Q_{13B}$ :  $I_{SB} = 0.75 \times 10^{-14}A$


## DC Quantities



- |    |             |    |                |
|----|-------------|----|----------------|
| 1. | $I_W$       | 5. | Bias current   |
| 2. | $I_{C,7}$   | 6. | Offsets        |
| 3. | $I_{E,16}$  | 7. | CM input range |
| 4. | $V_{BE,19}$ |    |                |


Textbook results for dc collector currents



**TABLE 9.1** Dc Collector Currents of the 741 Circuit ( $\mu\text{A}$ )


$Q_1$	9.5	$Q_8$	19	$Q_{13B}$	550	$Q_{19}$	15.8
$Q_2$	9.5	$Q_9$	19	$Q_{14}$	154	$Q_{20}$	154
$Q_3$	9.5	$Q_{10}$	19	$Q_{15}$	0	$Q_{21}$	0
$Q_4$	9.5	$Q_{11}$	730	$Q_{16}$	16.2	$Q_{22}$	0
$Q_5$	9.5	$Q_{12}$	730	$Q_{17}$	550	$Q_{23}$	180
$Q_6$	9.5	$Q_{13A}$	180	$Q_{18}$	165	$Q_{24}$	0
$Q_7$	10.5						

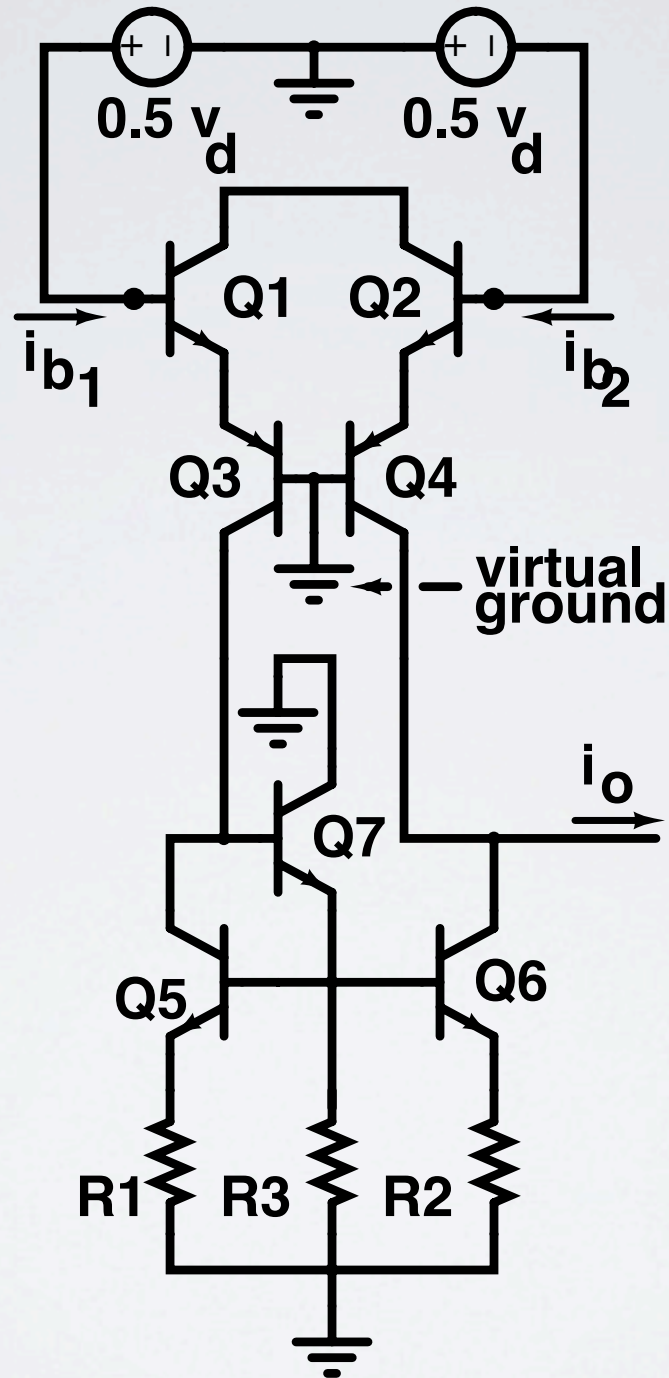

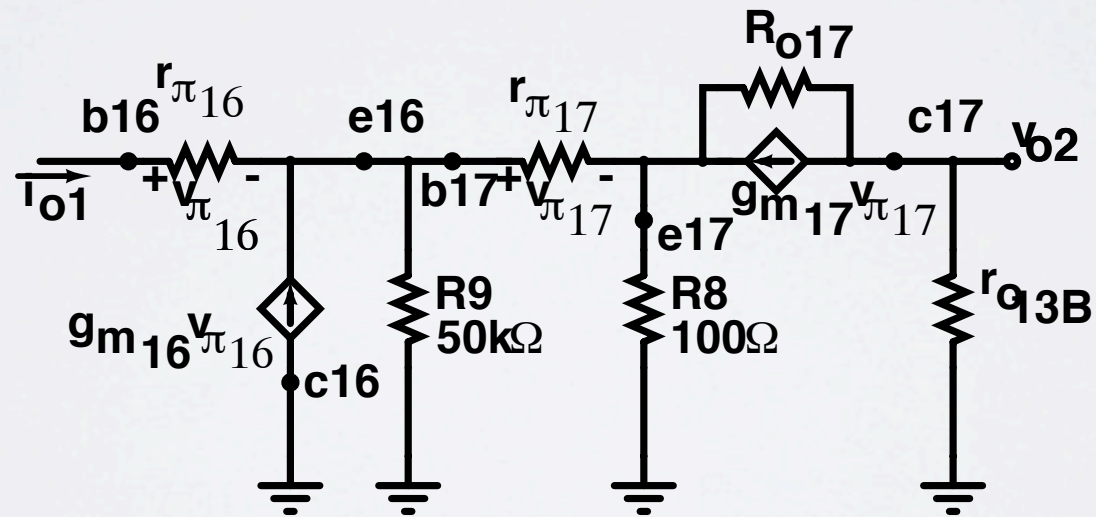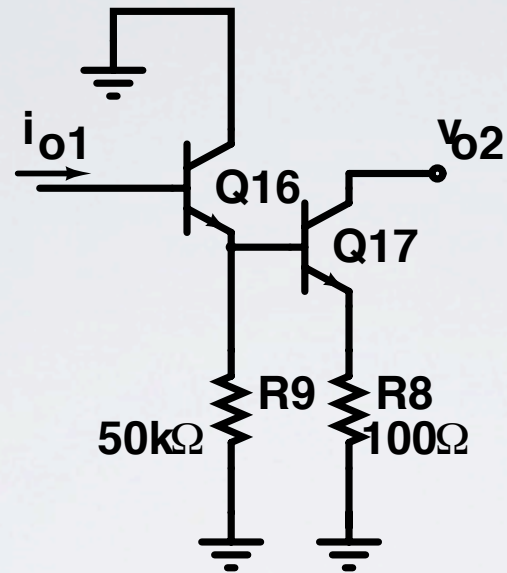


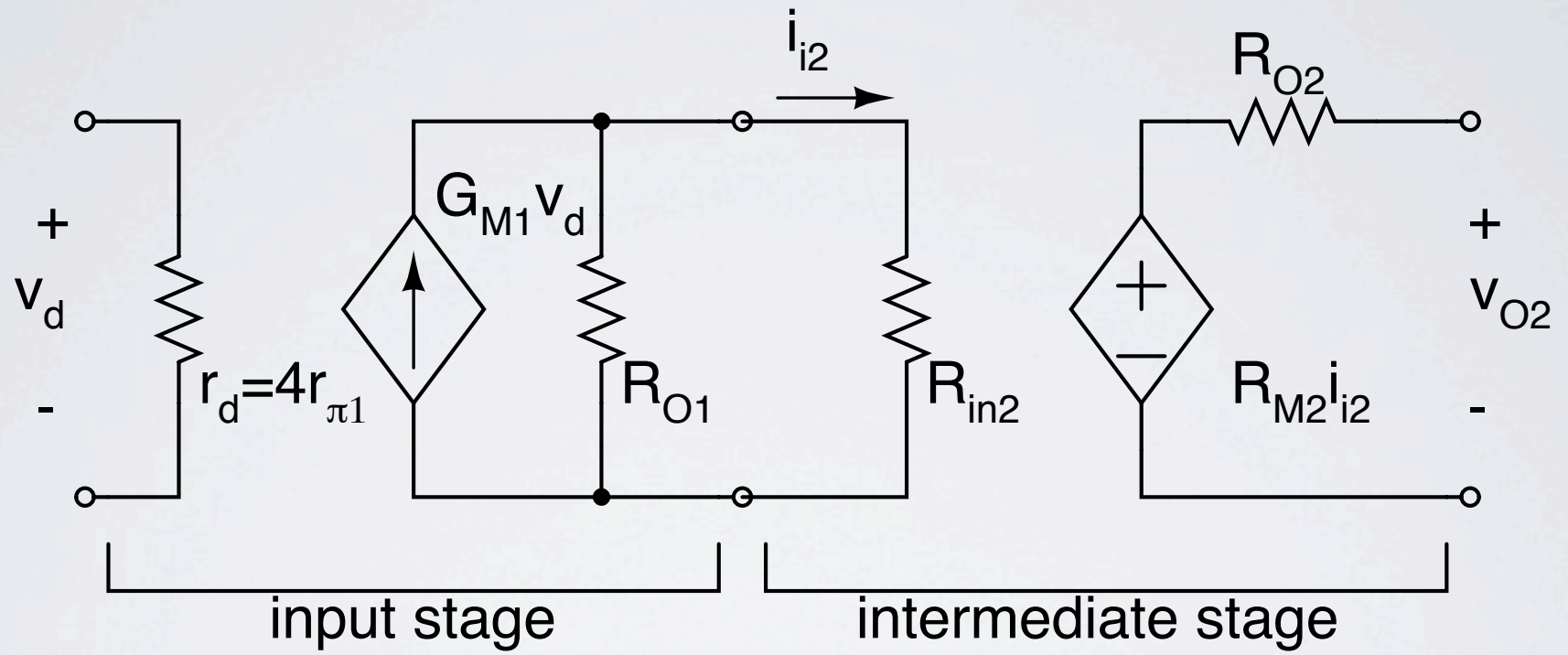

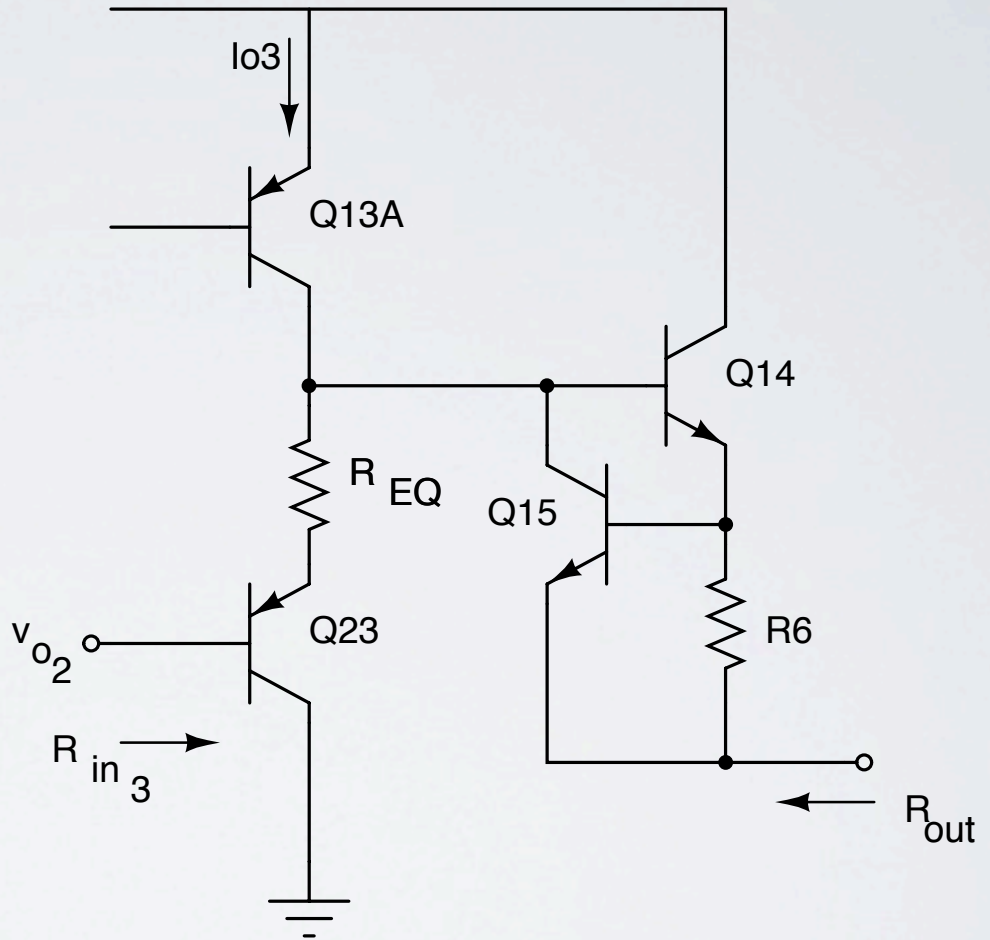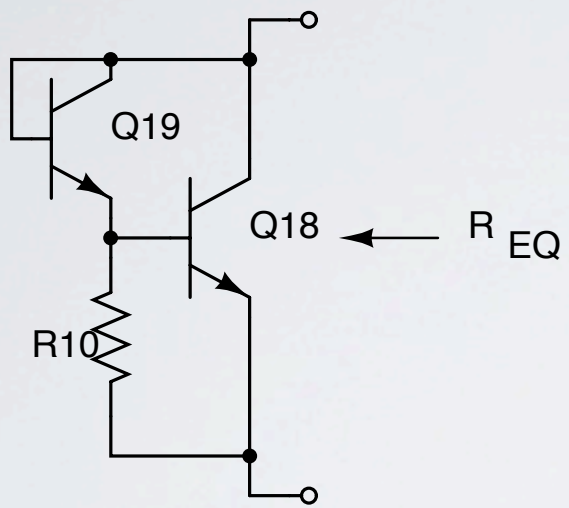


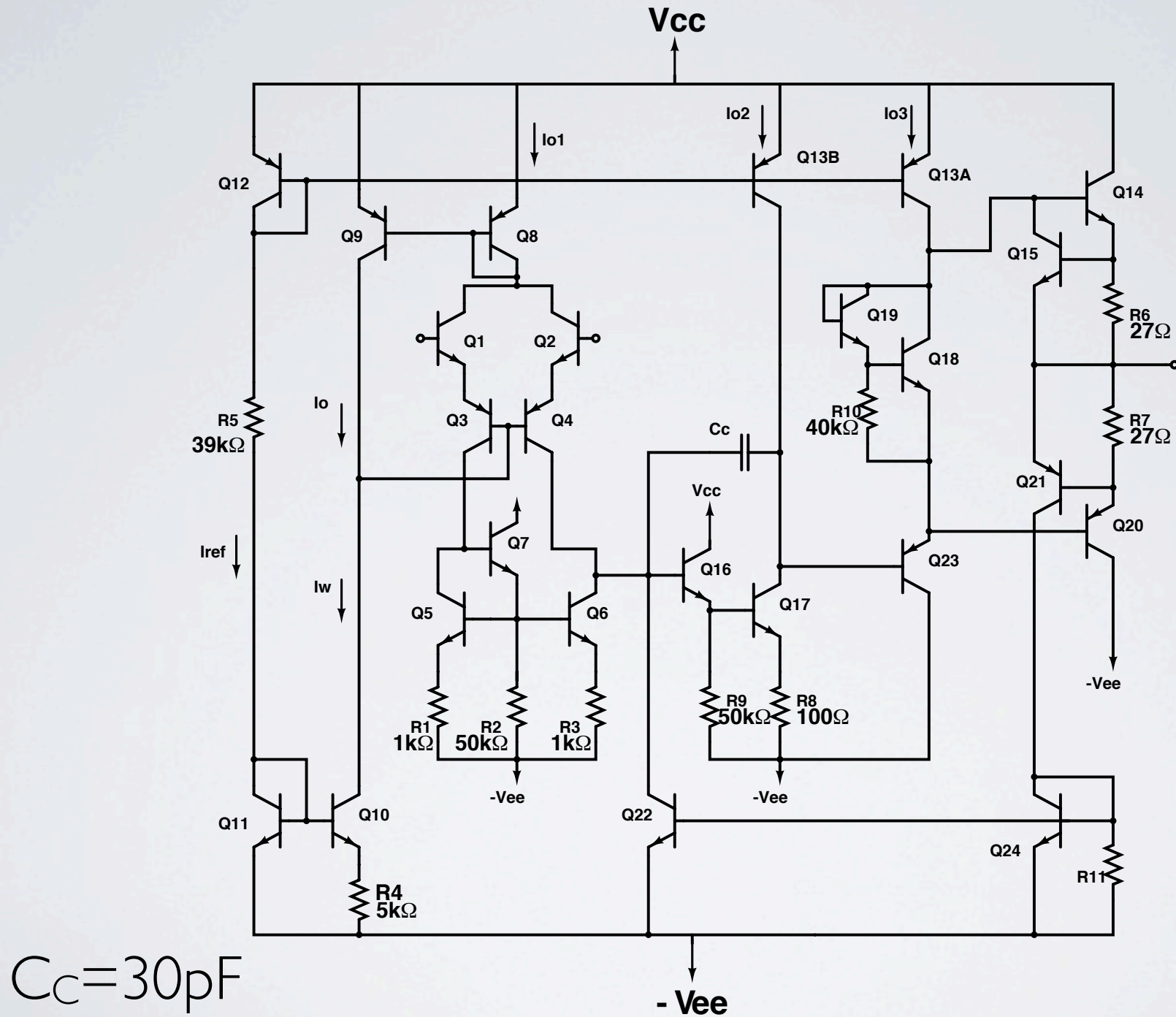

$C_c = 30pF$

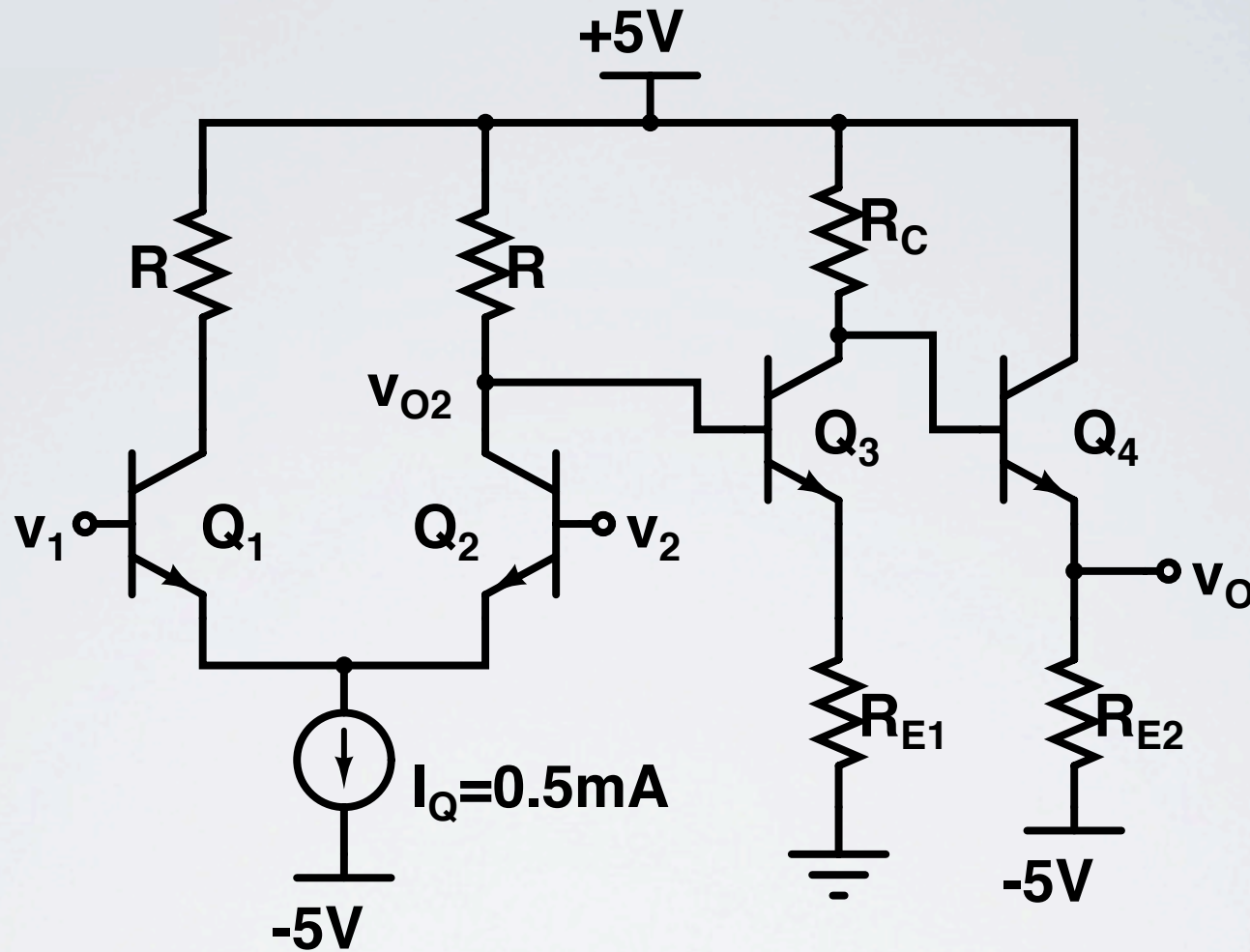

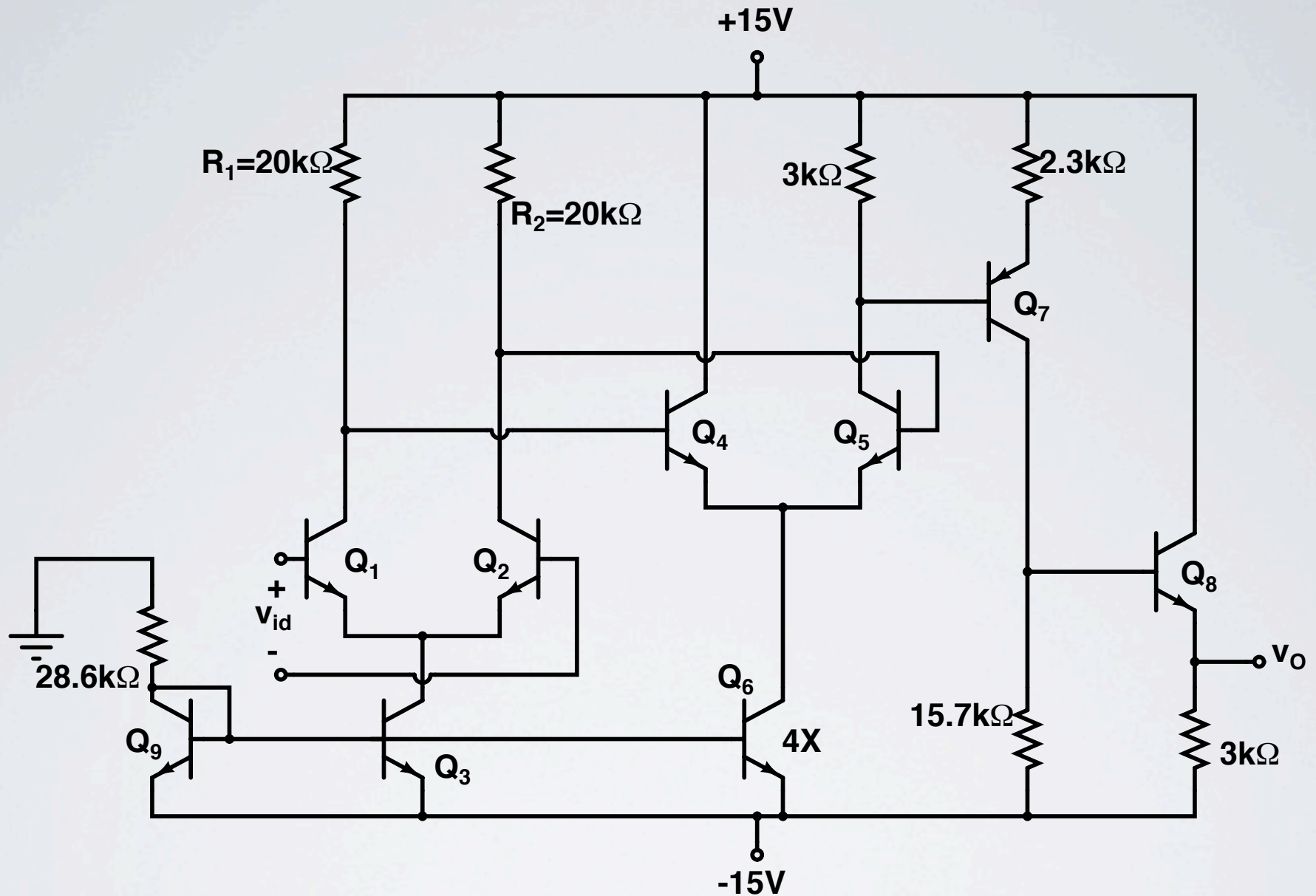Assume  $h_{FE} = 100$ ,  $V_{BE} = 0.7\text{V}$ ,  $V_A = \infty$ ,  $R_{O(CS)} = 100\text{k}\Omega$  (a) For  $v_1 = v_2 = 0\text{V}$ , design so that  $v_{O2} = 2\text{V}$ ,  $v_{C3} = 3\text{V}$ ,  $I_{CQ3} = 0.5\text{mA}$ ,  $I_{CQ4} = 3\text{mA}$ ; (b) Find  $A_{d1} = v_{O2}/v_d$  &  $A_d = v_O/v_d$ ; c) Find  $A_{cm1} = v_{O2}/v_{cm}$  and  $A_{cm} = v_O/v_{cm}$ , and the overall CMRR



Assume  $h_{FE} = 100$ ,  $V_{BE(ON)} = 0.7\text{V}$ . Find: (a) (dc)  $I_C, V_C, V_E$  for all Q's, (b) Power dissipated at DC, (c) input bias current, (d) CM voltage range, (e)  $A_d = v_O/v_{id}$