

Memory Circuits

Latches and flip-flops

INEL 4207 - Fall 2011

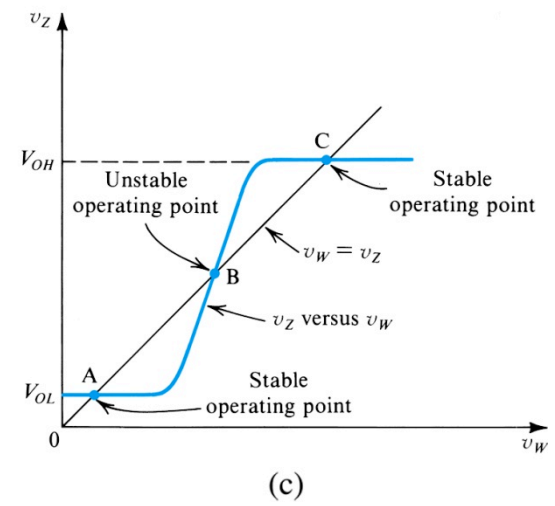
 
 


Figure 16.1 (a) Basic latch. (b) The latch with the feedback loop opened. (c) Determining the operating point(s) of the latch.


 


Figure 16.2

 

(a)

R	S	Q_{n+1}
0	0	Q_n
0	1	1
1	0	0
1	1	Not used

(b)

Figure 16.3 (a) The set/reset (SR) flip-flop and (b) its truth table.

 


Fig. 16.4 CMOS implementation of a clocked SR flip-flop. The clock signal is denoted by ϕ .



- 1. Assume $Q=0$, $Q'=1$**
- 2. Clock and S go high**
- 3. Q' is pulled down**
- 4. Inv $Q_3/Q_4 \rightarrow$ reaches transition point ($V_{DD}/2$)**
- 5. Inv $Q_3/Q_4 \rightarrow$ regenerative action forces Q_3 into cutoff**
- 6. Inv $Q_1/Q_2 \rightarrow$ reaches transition point ($V_{DD}/2$)**
- 7. Regenerative action keeps Q' low even if S goes low**

Example 1

The CMOS SR flip-flop in Fig. 16.4 is fabricated in a 0.18- μm process for which $\mu_n C_{ox} = 4 \mu_p C_{ox} = 300 \mu\text{A/V}^2$, $V_{tn} = |V_{tp}| = 0.5\text{V}$, and $V_{DD} = 1.8\text{V}$. The inverters have $(W/L)_n = 0.27\mu\text{m}/0.18\mu\text{m}$ and $(W/L)_p = 4 (W/L)_n$. The four NMOS transistors in the set-reset circuit have equal W/L ratios.

- (a) Determine the minimum value required for this ratio to ensure that the flip-flop will switch.
- (b) Also, determine the minimum width the set pulse must have for the case in which the W/L ratio of each of the four transistors in the set-reset circuit is selected at twice the minimum value found in (a). Assume that the total capacitance at each of the Q and \bar{Q} nodes and ground is **20fF**.

Assume that initially $Q = 0, Q' = 1$

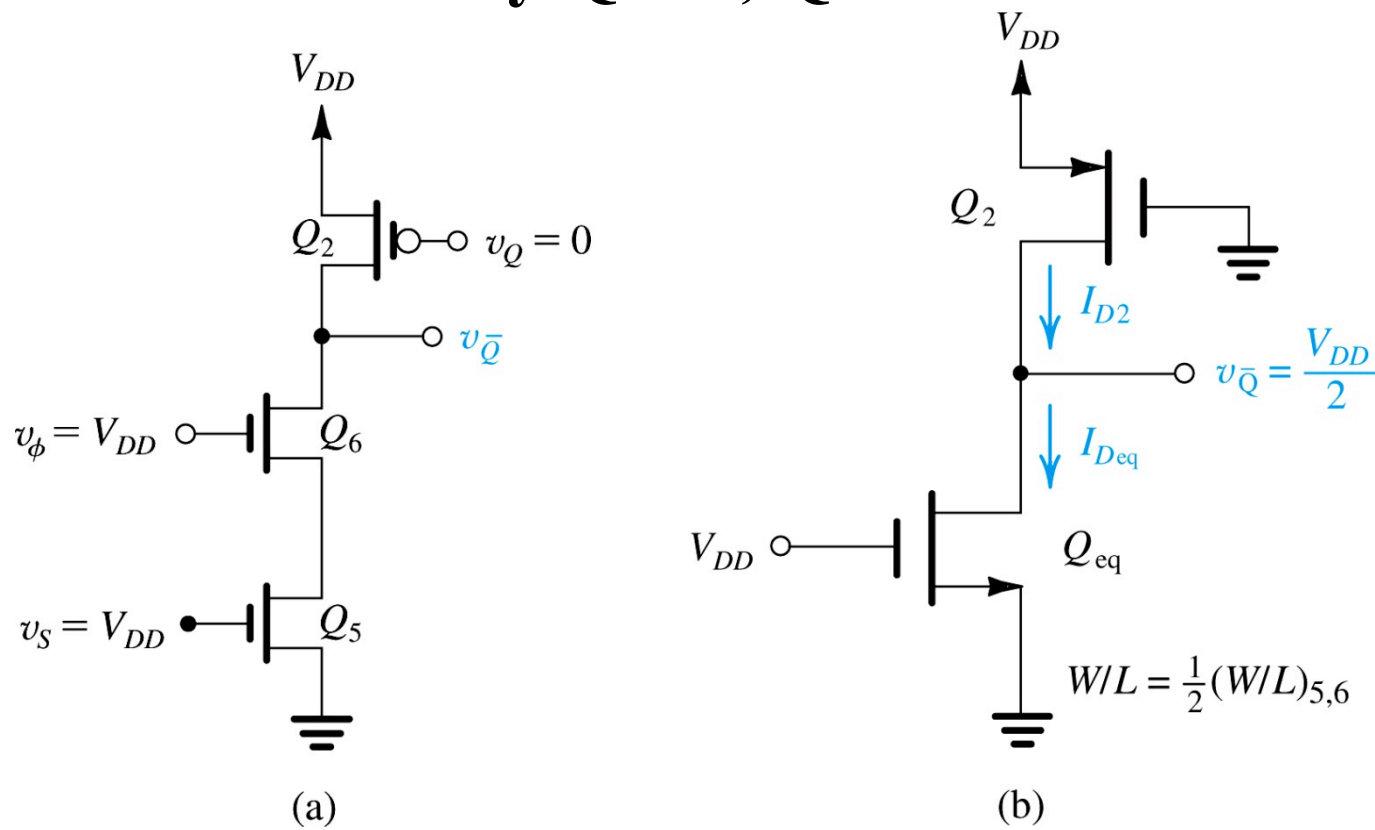


Figure 16.5 (a) The relevant portion of the flip-flop circuit of Fig. 16.4 for determining the minimum W/L ratios of Q_5 and Q_6 needed to ensure that the flip-flop will switch. (b) The circuit in (a) with Q_5 and Q_6 replaced with their equivalent transistor Q_{eq} , at the point of switching.

Assume that initially $Q = 0$, $Q' = 1$

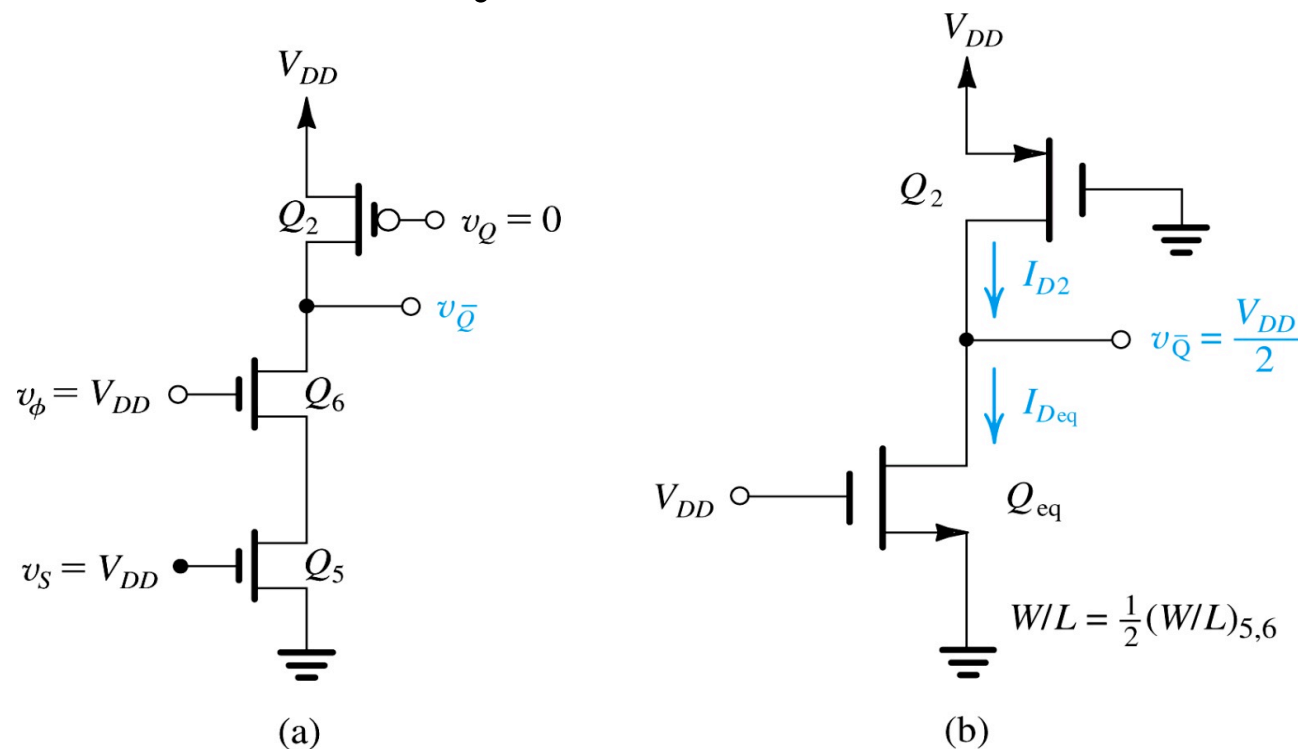


Figure 16.5 (a) The relevant portion of the flip-flop circuit of Fig. 16.4 for determining the minimum W/L ratios of Q_5 and Q_6 needed to ensure that the flip-flop will switch. (b) The circuit in (a) with Q_5 and Q_6 replaced with their equivalent transistor Q_{eq} , at the point of switching.

(a) ANSWER: $(W/L)_5 = (W/L)_6 = 0.54\mu\text{m}/0.18\mu\text{m}$

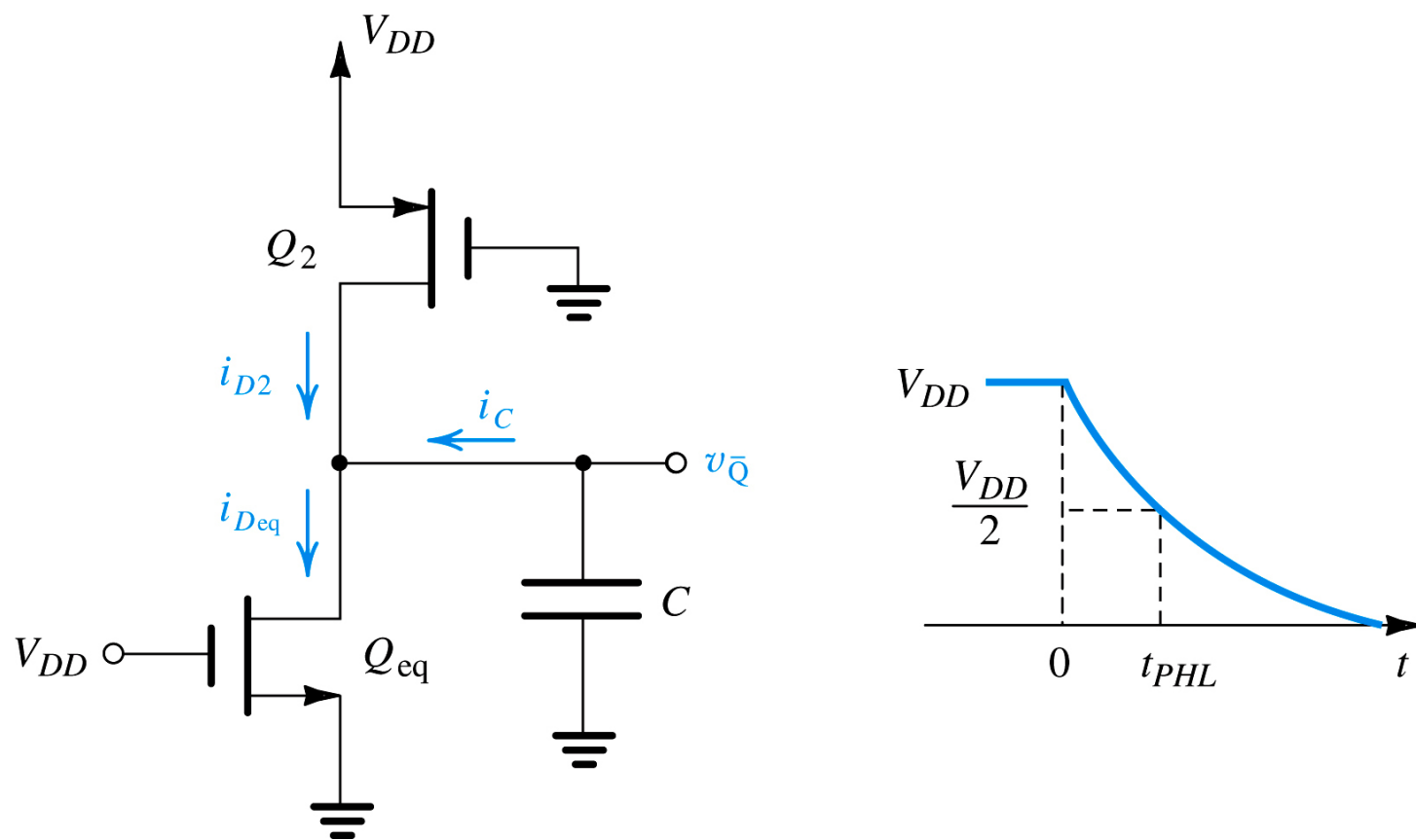


Figure 16.6 Determining the time t_{PHL} for $v_{\bar{Q}}$ to fall from V_{DD} to $V_{DD}/2$.

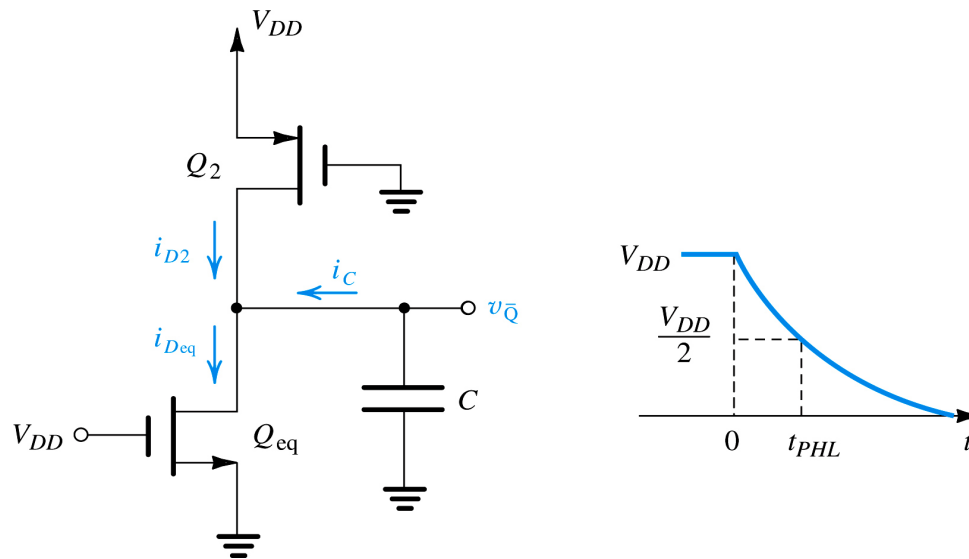


Figure 16.6 Determining the time t_{PHL} for $v_{\bar{Q}}$ to fall from V_{DD} to $V_{DD}/2$.

(b) ANSWER: Add t_{PHL} for Q1-Q2 and t_{PHL} for Q3-Q4. Set $(W/L)_5 = (W/L)_6 = (W/L)_7 = (W/L)_8 = 1.08\mu\text{m}/0.18\mu\text{m}$.

For Q1-Q2, use $i_C = i_{D,eq} - i_{D2}$. At $t=0$, $v_{Q'} = V_{DD}$ and Q_2 is off, Q_{eq} is saturated and $i_C = 760.5\mu\text{A}$. At $t=t_{PHL}$, $v_{Q'} = V_{DD}/2$ and $i_{D2} = 344.25\mu\text{A}$, $i_{Deq} = 688.5\mu\text{A}$ and $i_C = 344.25\mu\text{A}$. $i_{Cav} = 552.4\mu\text{A}$, $t_{PHL} = 32.6\text{ps}$

For Q3-Q4, you can use the formulas from ch. 14 that use α to get $t_{PLH} = 49.5\text{ps}$.

$$T_{\min} = t_{PHL} + t_{PLH}$$

 


Figure 16.7 A simpler CMOS implementation of the clocked SR flip-flop. This circuit is popular as the basic cell in the design of static random-access memory (SRAM) chips.



 


Figure 16.8 A block diagram representation of the D flip-flop.

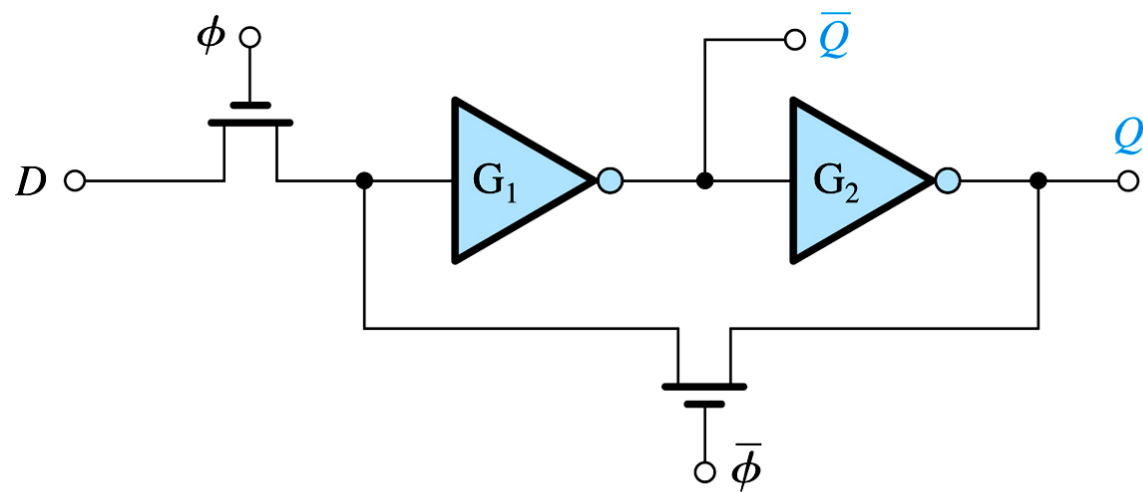

(a)

 

(b)

Figure 16.9 A simple implementation of the D flip-flop. The circuit in (a) utilizes the two-phase non-overlapping clock whose waveforms are shown in (b).

 
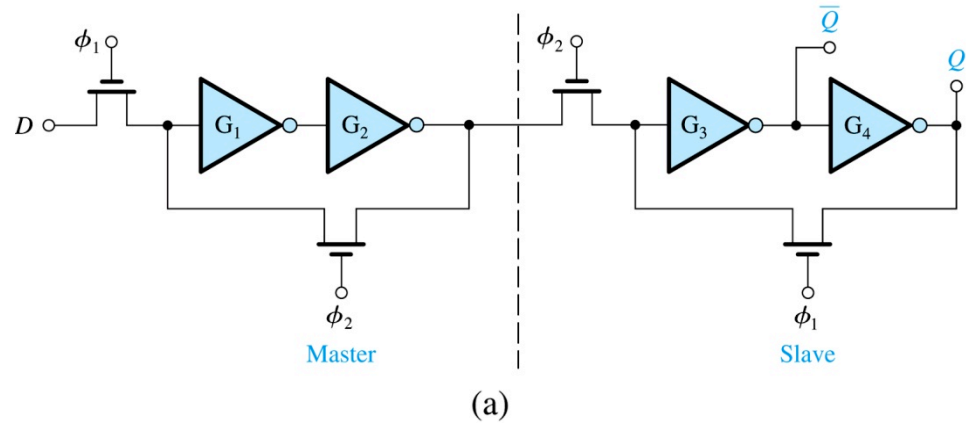


Figure 16.10 (a) A master–slave D flip-flop. The switches can be, and usually are, implemented with CMOS transmission gates. (b) Waveforms of the two-phase nonoverlapping clock required.