
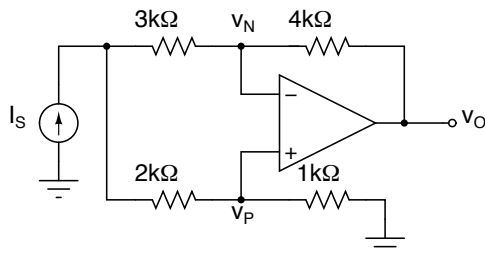


INEL 5207 Analog System Design with Operational Amplifiers
 Spring 2007 Exam #1 Prof. Manuel Toledo
 Univ. of Puerto Rico at Mayaguez

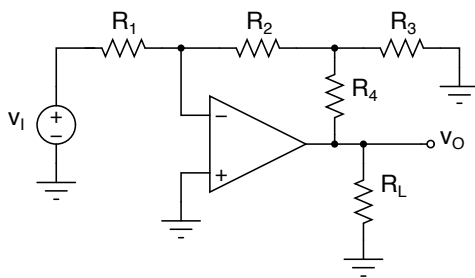1. For the following circuit, find v_N , v_P and v_O if $I_S = 1\text{mA}$. Assume an ideal opamp. (25 pts)



2. Use the following circuit to design an amplifier with a gain of -100V/V . You should select the resistors so that the maximum opamp output sink/source current of 20mA is not exceeded when a $\pm 100\text{mV}$ input voltage is applied. The opamp can be assumed otherwise ideal. Use $R_L = 1\text{k}\Omega$. (40 pts)



- ~~3. For the amplifier designed in problem 2, determine the actual gain if the opamp exhibits an open loop gain of $5,000\text{V/V}$. Otherwise the opamp can be considered ideal, with $r_O = 0$ and $r_d = \infty$. Use the resistor values that you found in problem 2. (35 pts)~~