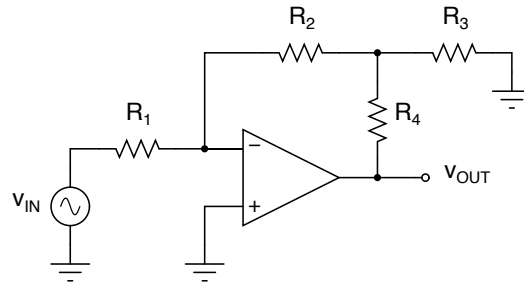


INEI 5207 Analog System Design with Operational Amplifiers
 Fall 2005 Exam #2 Prof. Manuel Toledo
 Univ. of Puerto Rico at Mayaguez

1. The following circuit's op amp has a constant GBP of 3MHz. and is otherwise ideal. Find the circuit's closed-loop bandwidth, f_{bw} , if all resistors are $1M\Omega$. Notice that this is an inverting configuration. (25 pts)



2. Using uA741 op amps, design an amplifier with gain equal to $\pm 1000V/V$ and a $44kHz$ bandwidth. Use as many inverting stages as needed. Besides the finite GBP, the op amp can be considered ideal. (25 pts)
3. For a single-stage non-inverting amplifier with a $100V/V$ gain, find the size of the largest step input that will not produce a slew-rate limited output if a uA741 op amp is used. Besides slew-rate limitations, the op amp can be considered ideal. (25 pts)
4. ~~An op amp that has two poles at 100kHz and a unity gain frequency of 1MHz is used to construct the circuit described in problem 3. Find the phase margin of the circuit. (25 points)~~