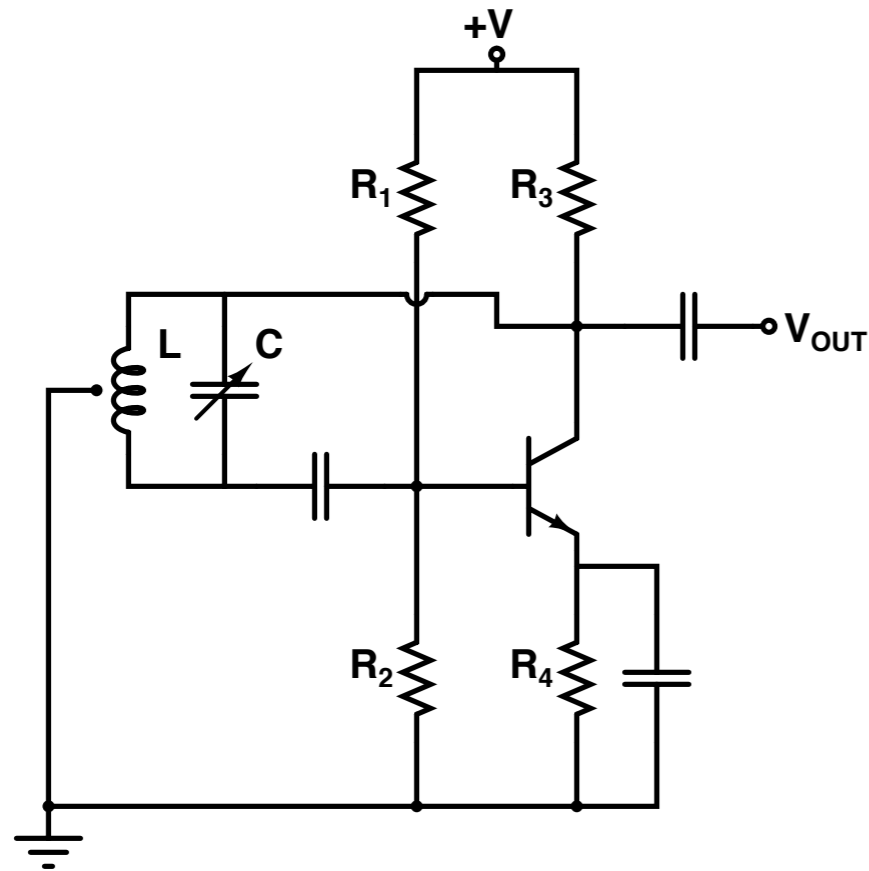


# V-F & F-V Converters

INEL 5205 Instrumentation

- frequency is easily measured
- frequency can be measured with high precision
- frequency is robust to interference, voltage drops and other factors that affect amplitude


# Hartley Osc.



$C =$  Capacitive sensor

$$f = \frac{1}{\sqrt{LC}}$$



# LM131/LM231 Converter

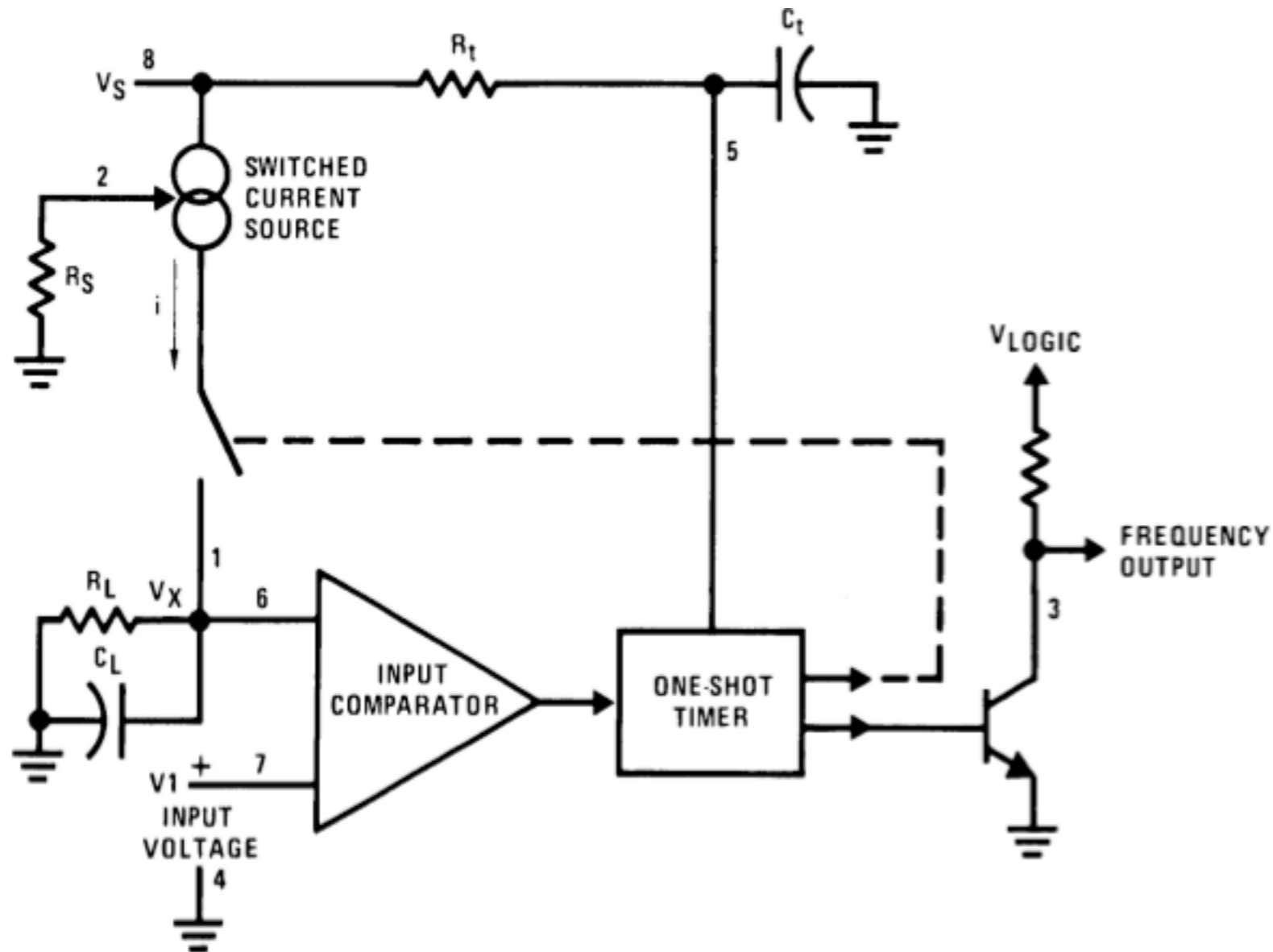

00568004

**FIGURE 2. Simplified Block Diagram of Stand-Alone Voltage-to-Frequency Converter and External Components**

# Functional Block Diagram

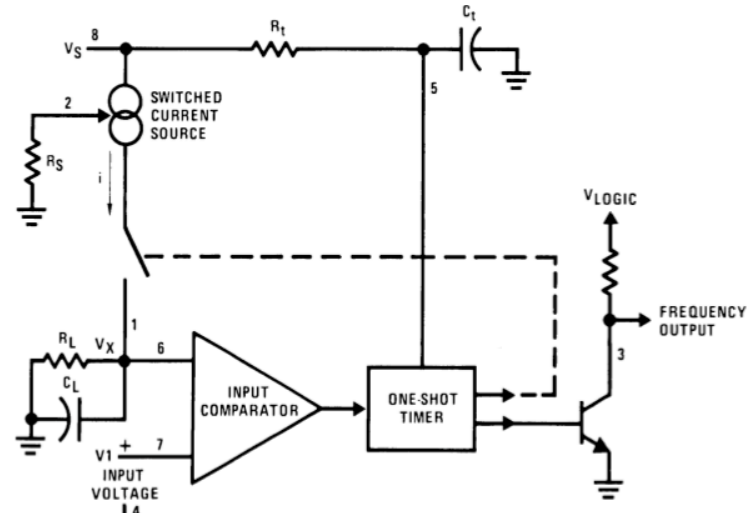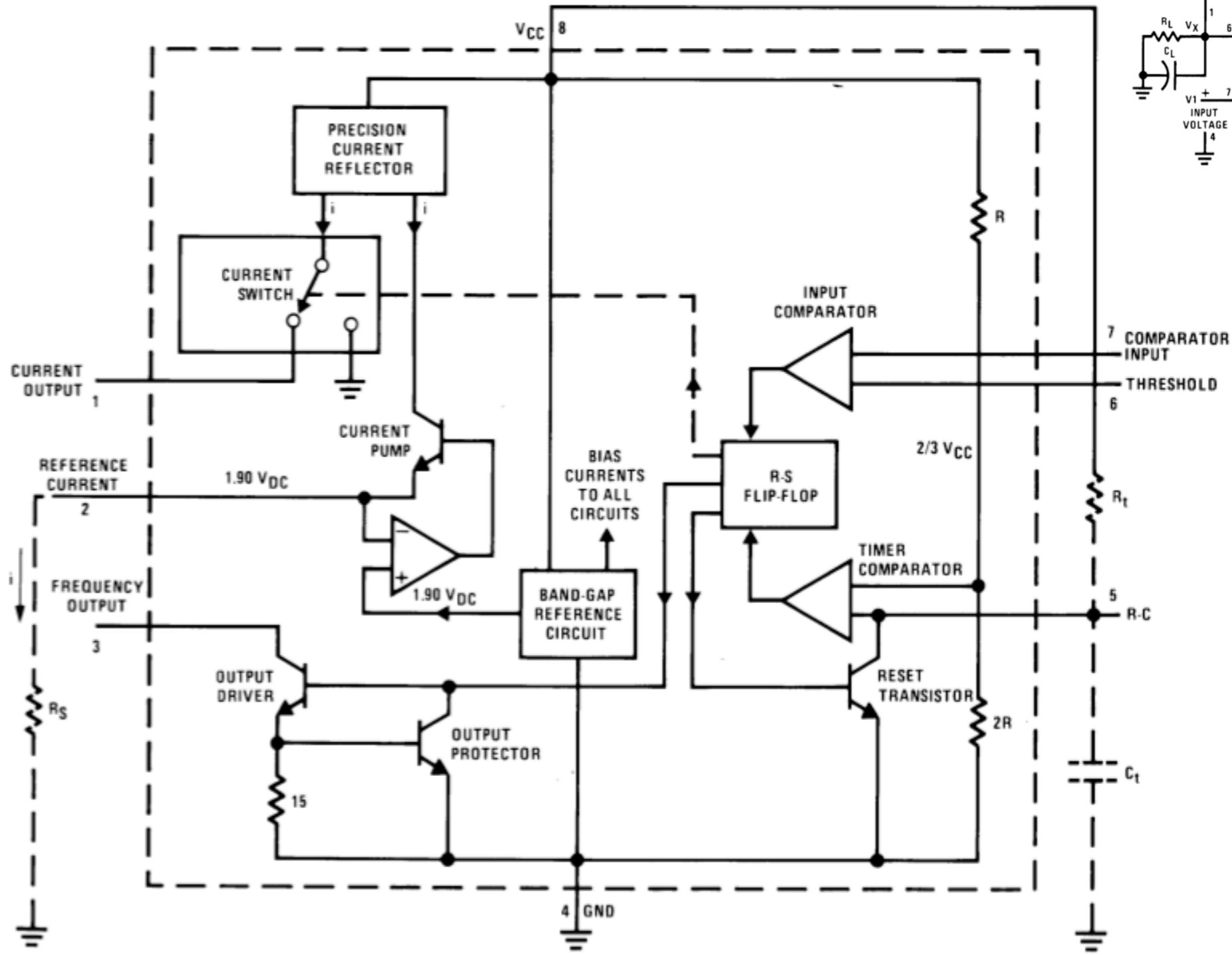


00568004

Pin numbers apply to 8-pin packages only.


00568002

FIGURE 1.

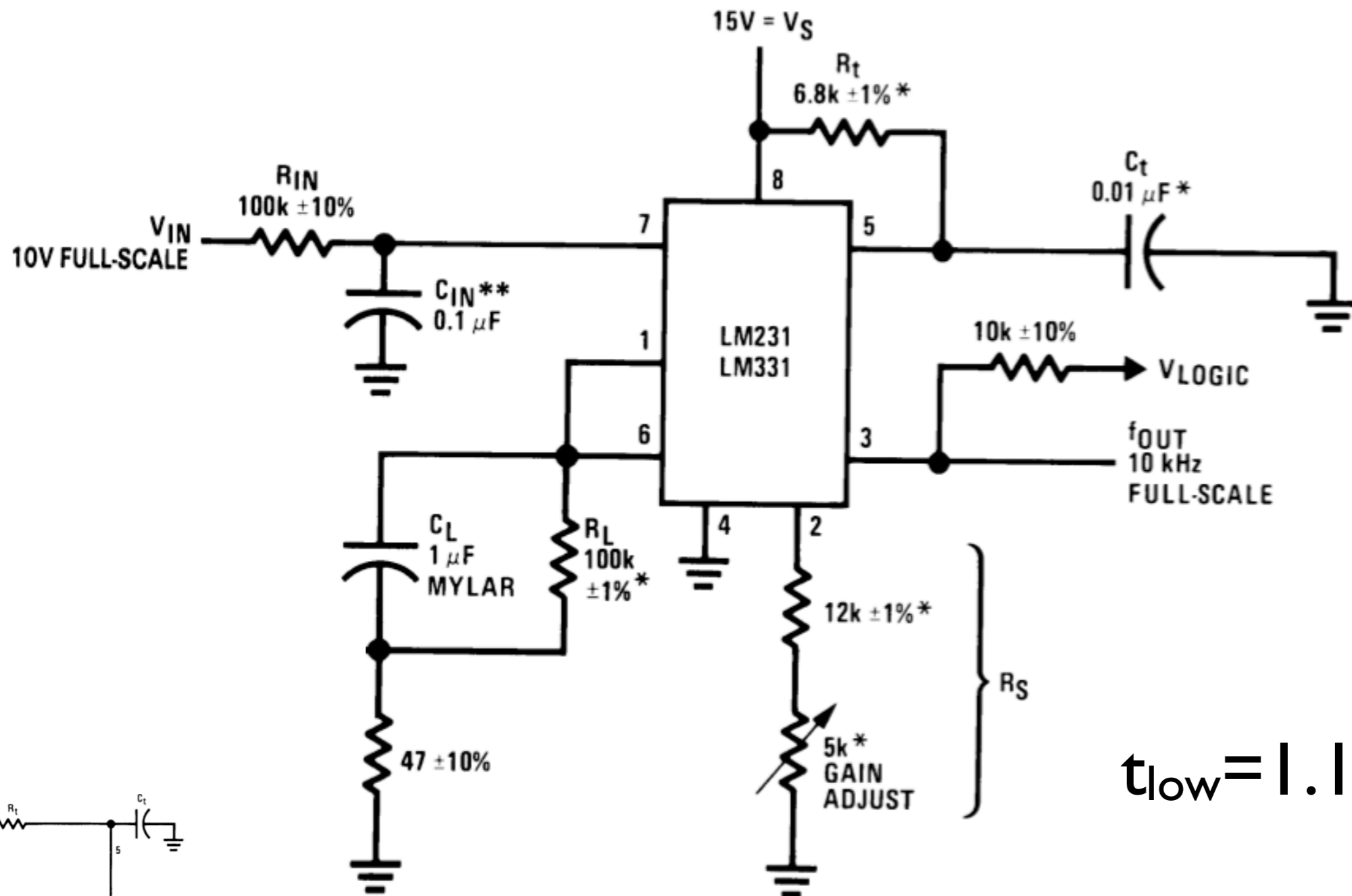

$$t_{low} = 1.1 R_t C_t$$

00568001

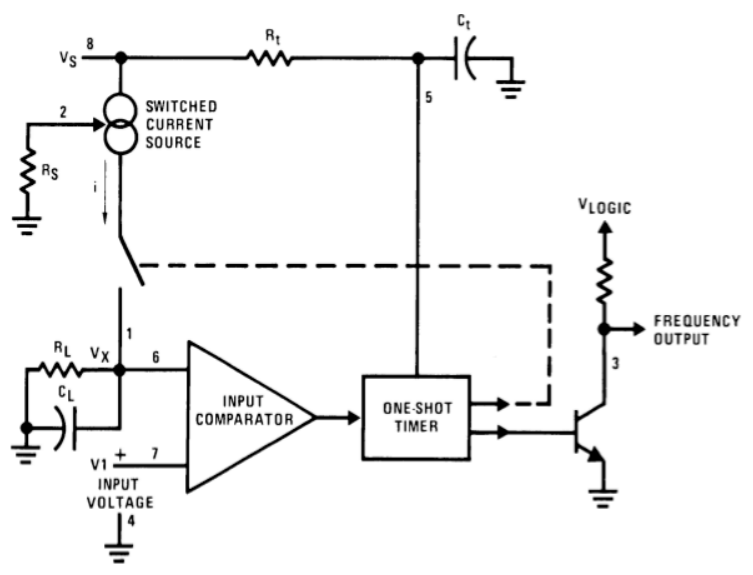

$$f_{OUT} = \frac{V_{IN}}{2.09 V} \cdot \frac{R_S}{R_L} \cdot \frac{1}{R_t C_t}$$


$$f_{out} = 1000 V_{in}$$

for gain adj = 2.5k

**Example 4-11: Design a V-to-f converter that will output a 20kHz signal when  $V_{in, max} = 5V$ . If  $V_{in, min} = 1V$ , what is the frequency range?**

**Example: Use a V-to-f converter and a counter to build an 8-bit ADC with a conversion rate of 100Hz and an input voltage range of 0 to 1V**
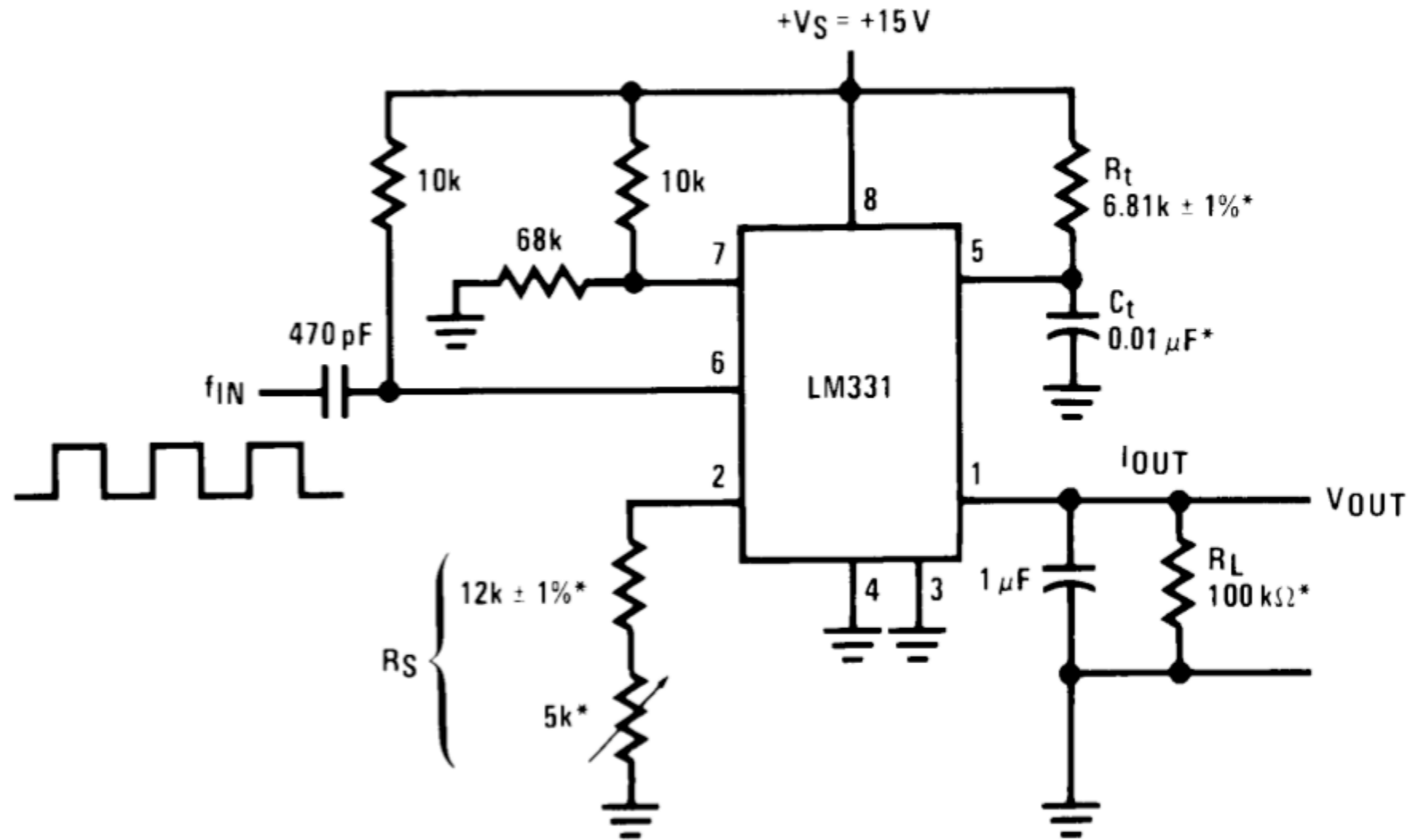
# F-to-V Conversion using the LM131/LM231/LM331



00568007

$$V_{OUT} = f_{IN} \times 2.09\text{V} \times \frac{R_L}{R_S} \times (R_t C_t)$$