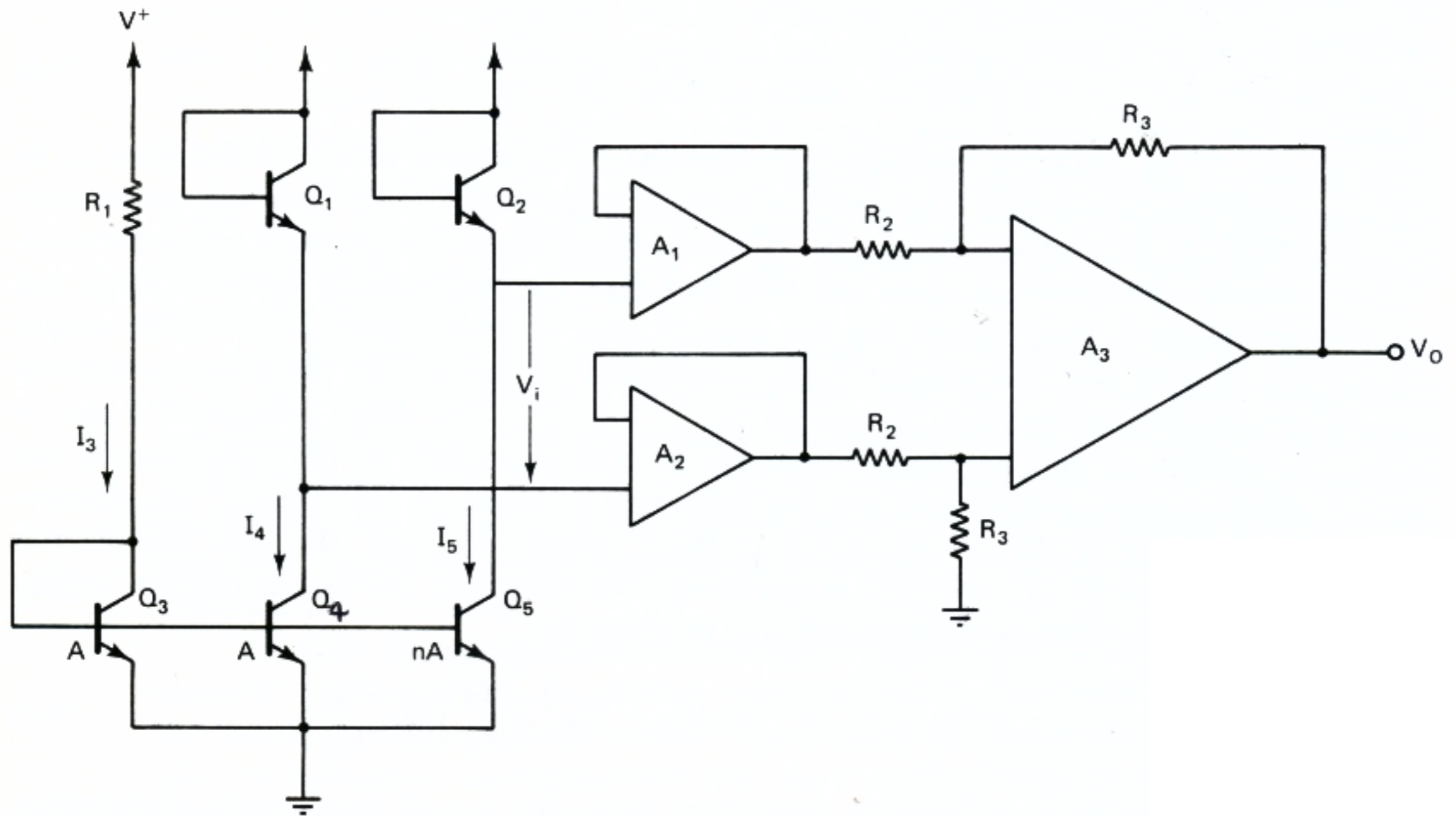


SENSORES DE TEMPERATURA ICS

INEL 5205 - Instrumentación



V_0 es proporcional a T absoluta

$$V_{BE5} = V_{BE4}$$

$$I_2 = I_5 = nI_4 = nI_1$$

$$\frac{I_2}{I_1} = \frac{I_5}{I_4} = n$$

$$v_i = V_+ - v_{BE1} - (V_+ - v_{BE2}) = v_{BE2} - v_{BE1}$$

$$I_1 = I_s \exp(v_{BE1}/V_T)$$

$$I_2 = I_s \exp(v_{BE2}/V_T)$$

$$\frac{I_2}{I_1} = n = \exp\left(\frac{v_{BE2} - v_{BE1}}{V_T}\right)$$

$$v_i = V_T \ln(n)$$

$$v_o = \frac{R_3}{R_2} \ln(n) V_T = \left(\frac{k R_3}{q R_2} \ln(n)\right) T = TC \times T$$

$$TC = \frac{dv_o}{dT} = \frac{k R_3}{q R_2} \ln(n)$$

For $TC = 1\text{mV}/^\circ\text{C} = 1\text{mV}/^\circ\text{K}$, at $T = 25^\circ\text{C} = 298^\circ\text{K}$

$$\frac{kT}{q} = 25.678\text{mV}$$

$$\frac{k}{q} = \frac{25.678\text{mV}}{298^\circ\text{K}}$$

and

$$TC = 1\text{mV}/^\circ\text{K} = \frac{25.678\text{mV}}{298^\circ\text{K}} \frac{R_3}{R_2} \ln(n)$$

Select n to some reasonable number, like $n = 2$, and

$$\frac{R_3}{R_2} = \frac{1\text{mV}/^\circ\text{K}}{\ln(2)} \frac{298^\circ\text{K}}{25.678\text{mV}} = \boxed{16.74}$$

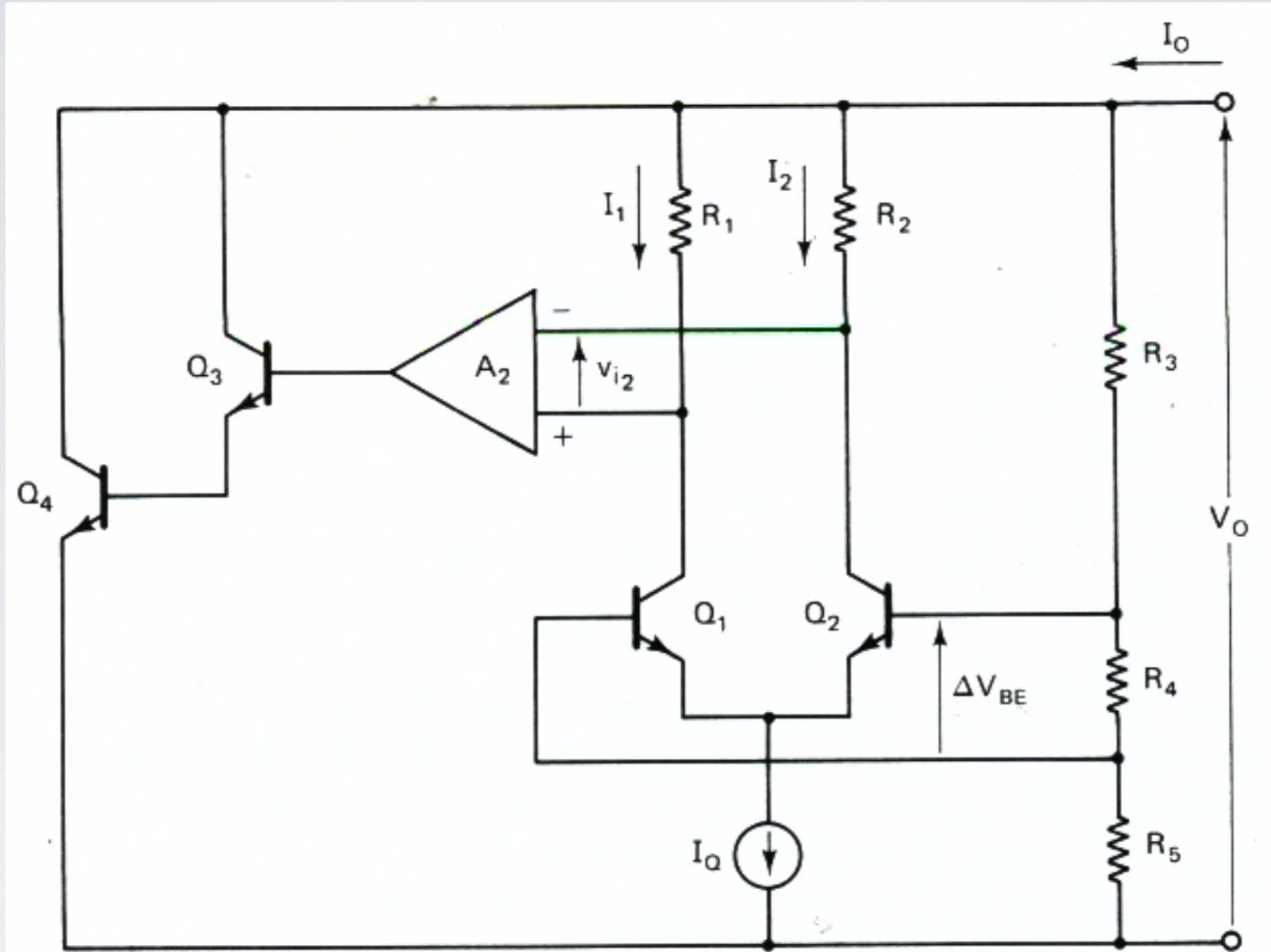


Figure 9.2 Two-terminal VPTAT temperature sensor.

V_O es proporcional a T absoluta

$$v_p = v_n \Rightarrow I_1 R_1 = I_2 R_2 \Rightarrow \frac{I_2}{I_1} = \frac{R_1}{R_2}$$

$$\frac{I_2}{I_1} = \frac{R_1}{R_2} = \exp\left(\frac{v_{BE2} - v_{BE1}}{V_T}\right)$$

$$v_{BE2} - v_{BE1} = V_T \ln\left(\frac{R_1}{R_2}\right)$$

Neglecting base currents,

$$v_{BE2} - v_{BE1} = V_T \ln\left(\frac{R_1}{R_2}\right) = V_{R4} = \frac{R_4}{R_3 + R_4 + R_5} v_o$$

$$v_o = \left(\frac{R_3 + R_4 + R_5}{R_4} \ln\left(\frac{R_1}{R_2}\right) \frac{k}{q}\right) T$$

$$TC = \frac{R_3 + R_4 + R_5}{R_4} \ln\left(\frac{R_1}{R_2}\right) \frac{k}{q}$$

For $TC = 10\text{mV}/^\circ\text{K}$ and using $\frac{R_1}{R_2} = 10$,

$$10\text{mV}/^\circ\text{K} = \frac{R_3 + R_4 + R_5}{R_4} \ln(10) \frac{25.678\text{mV}}{298^\circ\text{K}}$$


$$R_3 + R_5 = 49.4R_4$$

Assign $I_{R3} = 1\mu\text{A}$, $V_{B2} = 1.0\text{V}$ and $v_o = 2.98\text{V}$ at $T = 298^\circ\text{K}$. Then

$$R_5 + R_4 = \frac{1\text{V}}{1\text{mA}} = 1\text{k}\Omega \quad R_3 + R_4 + R_5 = 2.98\text{k}\Omega$$

$$\boxed{R_3 = 1.98\text{k}\Omega} \quad R_5 = 49.4R_4 - 1.98\text{k}\Omega = 1\text{k}\Omega - R_4$$
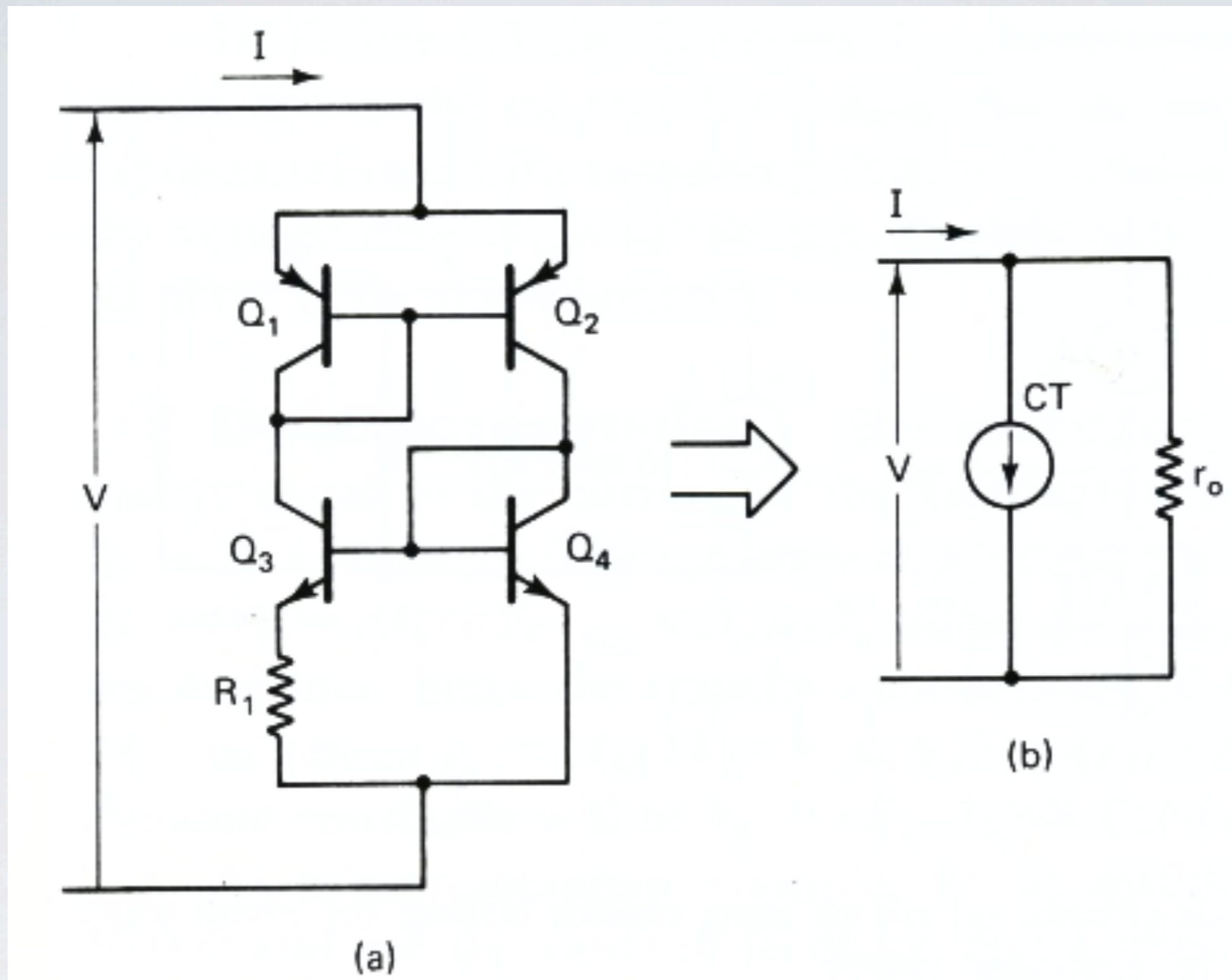
$$\boxed{R_4 = 2.98\text{k}\Omega \div 50.4 = 59\Omega} \Rightarrow \boxed{R_5 = 941\Omega}$$



I es proporcional a T absoluta

$$I_1 = I_2 = I_3 = I_4$$

$$r = A_3/A_4$$

$$\frac{I_3}{A_3} = J_3 = J_S \exp(v_{BE3}/V_T)$$

$$\frac{I_4}{A_4} = J_4 = J_S \exp(v_{BE4}/V_T)$$

$$\frac{I_4}{A_4} \div \frac{I_3}{A_3} = \frac{I_4 A_3}{I_3 A_4} = 1 \times r = \exp((v_{BE4} - v_{BE3})/V_T)$$

$$v_{BE4} - v_{BE3} = I_1 R_1 = V_T \ln(r)$$

$$I_0 = 2I_1 = \left(\frac{2 \ln(r) k}{R_1 q} \right) T = TC \times T$$

$$TC = \frac{2 \ln(r) k}{R_1 q}$$

For $TC = 1.0 \mu A/^\circ K$ and selecting $r = 8$,

$$R_1 = \frac{2 \ln(8)}{1 \mu A/^\circ K} \frac{25.678 mV}{298^\circ K} = \boxed{358.4 \Omega}$$