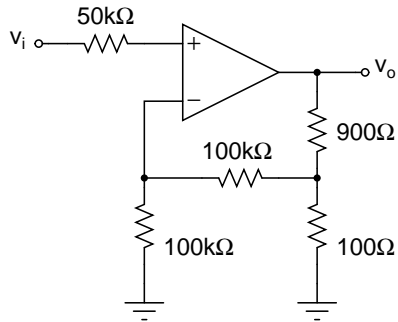



Operational Amplifiers Practice Problems

1. The operational amplifier in the following circuit is ideal.




Find the circuit's gain $A_v = \frac{v_o}{v_i}$.

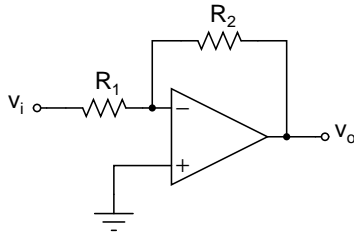2. The amplifier shown in the following sketch has a voltage gain $A_v = -100$ and input resistance $R_{in} = 10\text{k}\Omega$.




Determine R_1 and R_2 assuming an ideal operational amplifier.

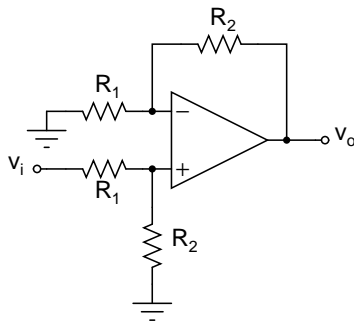3. The amplifier shown in the following sketch has a voltage gain $A_v = +100$ and input resistance $R_{in} = 10\text{k}\Omega$.




Determine R_1 and R_2 assuming an ideal operational amplifier.

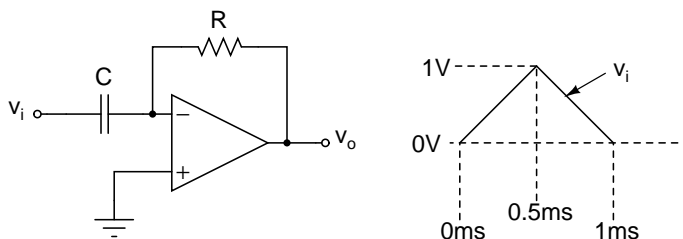4. For the circuit shown in the following sketch, $R = 1\text{k}\Omega$ and $C = 1\mu\text{F}$. The opamp is ideal.




Draw the output waveform when the input voltage is the one shown on the right hand side of the figure.

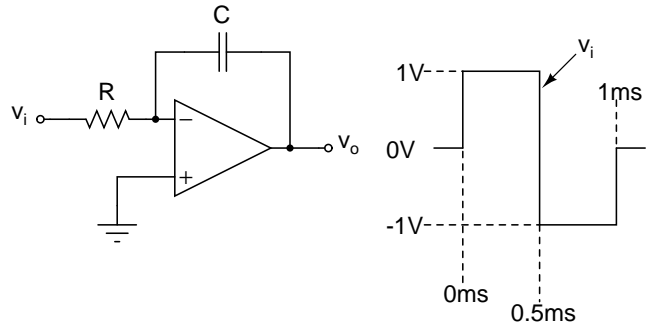5. For the circuit shown in the following sketch, $R = 1k\Omega$ and $C = 1\mu F$.




Draw the output waveform when the input voltage is the one shown on the right hand side of the figure.

6. For the following circuit

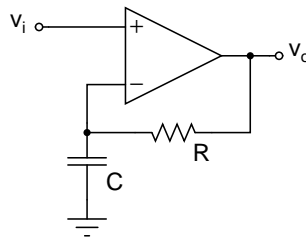


- (a) Derive an expression for v_o in terms of v_i and the component values. Notice that v_i does not need to be sinusoidal.
- (b) Find an expression for v_o in terms of the Laplace operator s , valid when v_i is sinusoidal.

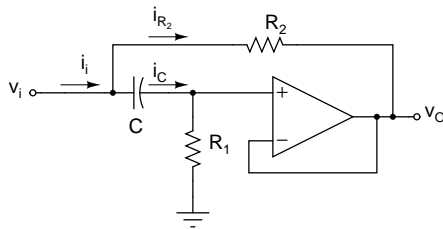
7. Determine the input impedance $Z_{in} = \frac{v_i}{i_i}$ for the following circuit. Assume an ideal opamp.



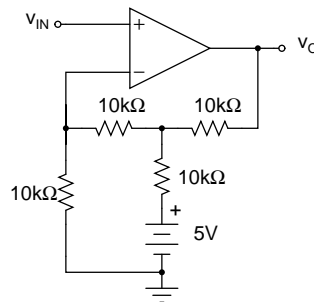
8. Find v_O in terms of v_{IN} for the following circuit.



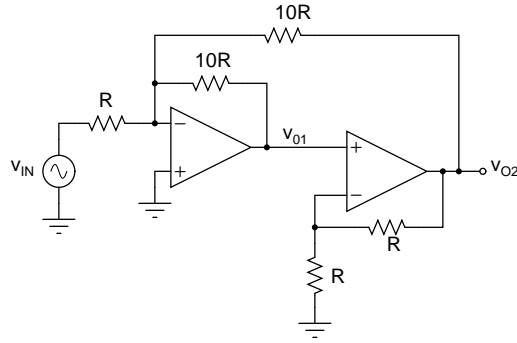9. Find $\frac{v_{O1}}{v_{IN}}$ and $\frac{v_{O2}}{v_{IN}}$ for the following circuit.



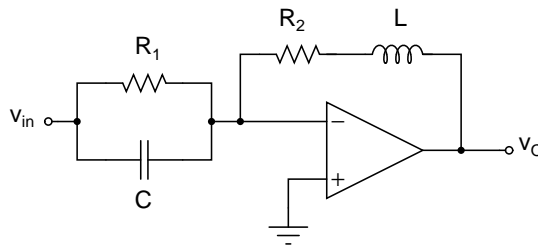10. For the following circuit, express the output voltage v_O as a differential equation of v_{in} in terms of the component values.



11. Assuming ideal operation of the amplifiers ($A_v = \infty$), find the expression for I_L in terms of the differential voltage $v_2 - v_1$ and the resistors R_x , R_1 , and R_2 .

