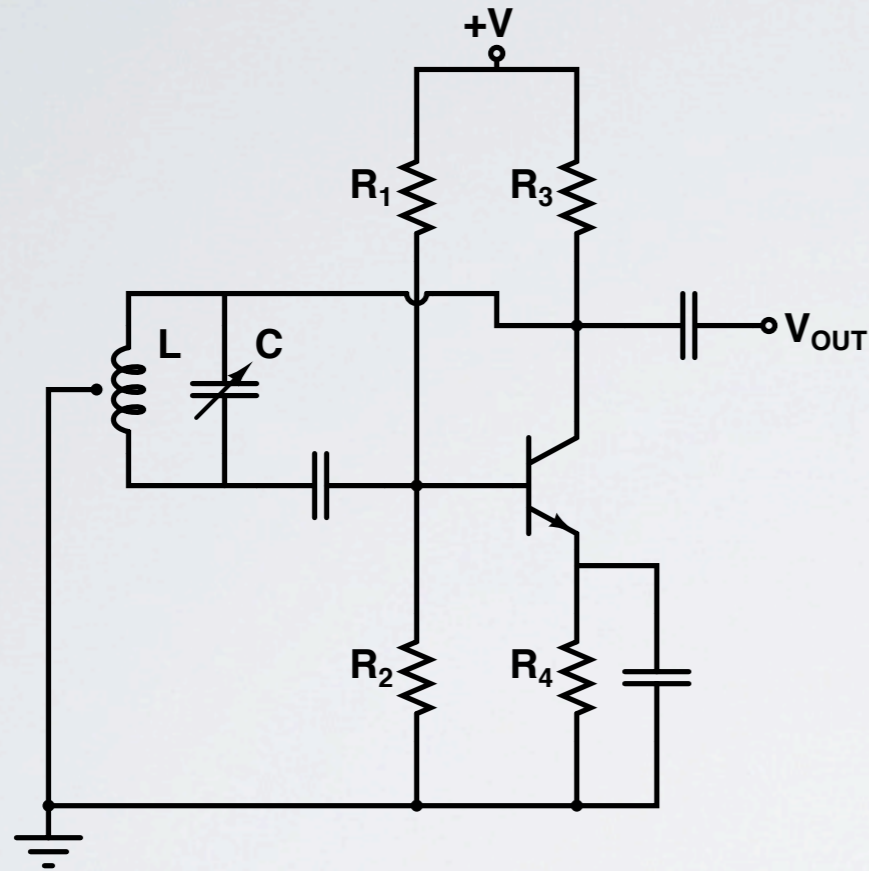


V-F & F-V CONVERTERS

INEL 5205 Instrumentation

- frequency is easily measured
- frequency can be measured with high precision
- frequency is robust to interference, voltage drops and other factors that affect amplitude


Hartley Osc.



$C =$ Capacitive sensor

$$f = \frac{1}{\sqrt{LC}}$$

LM131/LM231 Converter

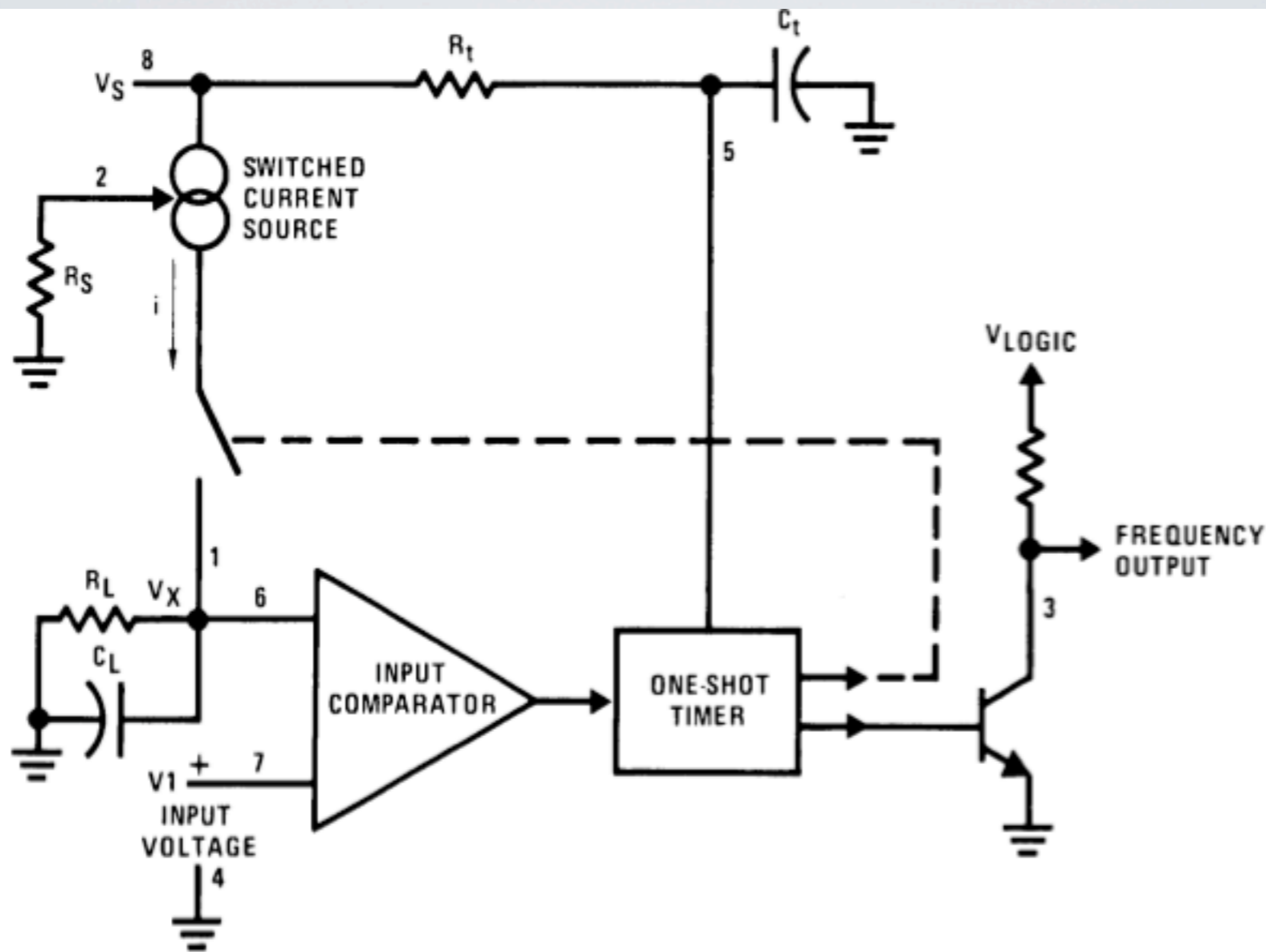

00568004

FIGURE 2. Simplified Block Diagram of Stand-Alone Voltage-to-Frequency Converter and External Components

The voltage comparator compares a positive input voltage, V_{IN} , at pin 7 to the voltage, V_x , at pin 6. If $V_{IN} > V_x$

- The comparator will trigger the 1-shot timer.
- The output of the timer will turn ON both the frequency output transistor and the switched current source for a period $t = 1.1 \times R_t C_t$.
- During this period, the current i will flow out of the switched current source and provide a fixed amount of charge, $Q = i \times t$, into the capacitor, C_L .
- This will normally charge V_x up to a higher level than V_{IN} .

At the end of the timing period $1.1 \times R_t C_t$



- the timer will reset itself, and the current i will turn OFF,
- Now there is no current flowing from pin 1, and
 - the capacitor C_L will be gradually discharged by R_L until $V_x < V_{IN}$
 - then the comparator will trigger the timer and start another cycle.

Current flowing into C_L : $I_{AVE} = i \times (1.1 \times R_t C_t) \times f$

Current flowing out of C_L : $V_x / R_L \approx V_{IN} / R_L$.

If V_{IN} is doubled, the frequency will double to maintain this balance. Even a simple V-to-F converter can provide a frequency precisely proportional to its input voltage over a wide range of frequencies.

Functional Block Diagram

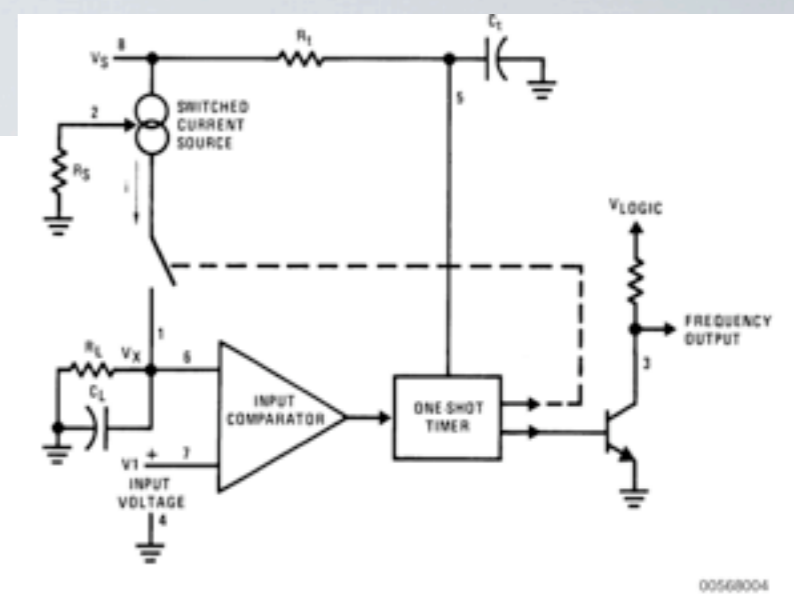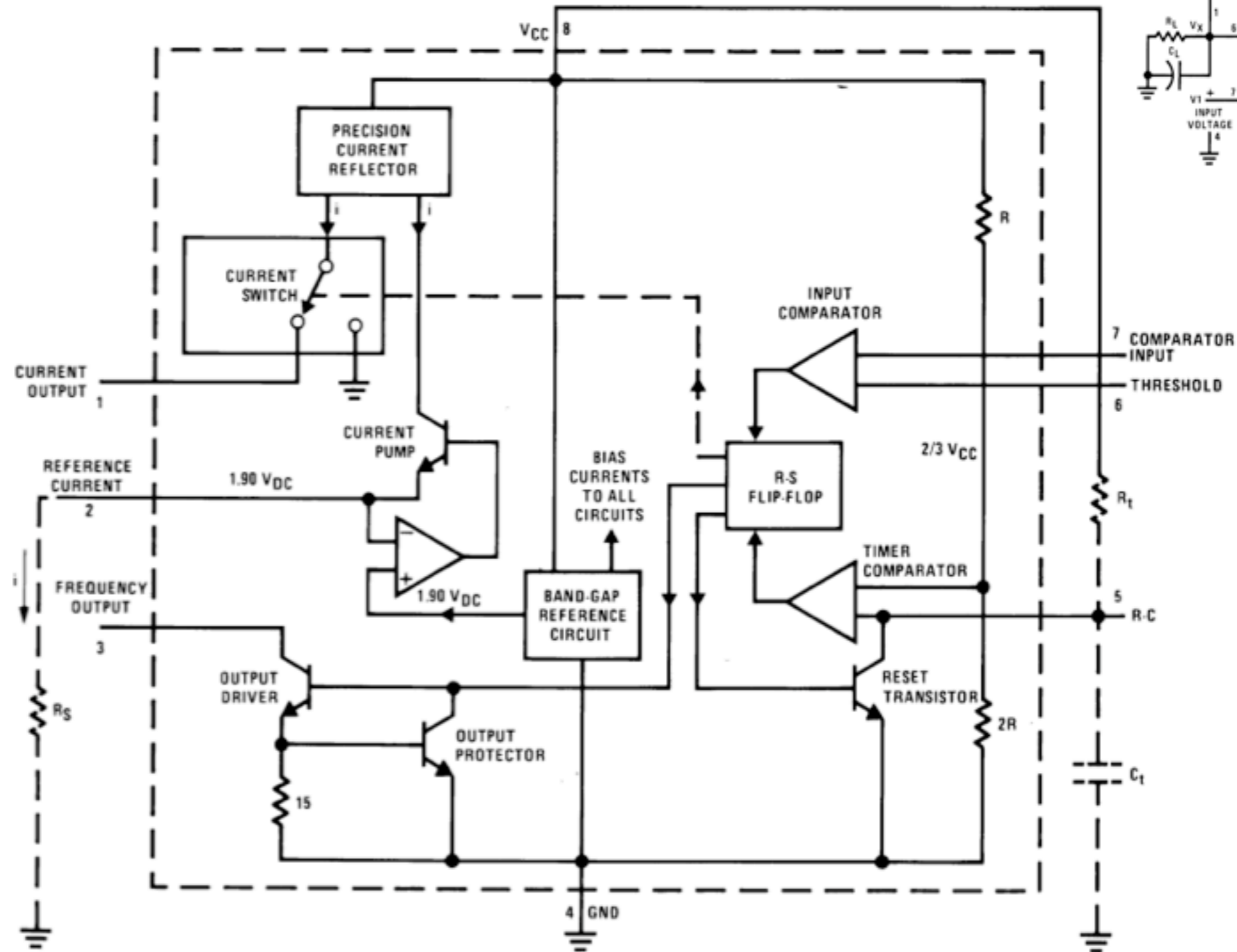


Pin numbers apply to 8-pin packages only.

FIGURE 1.


00568002

00568004

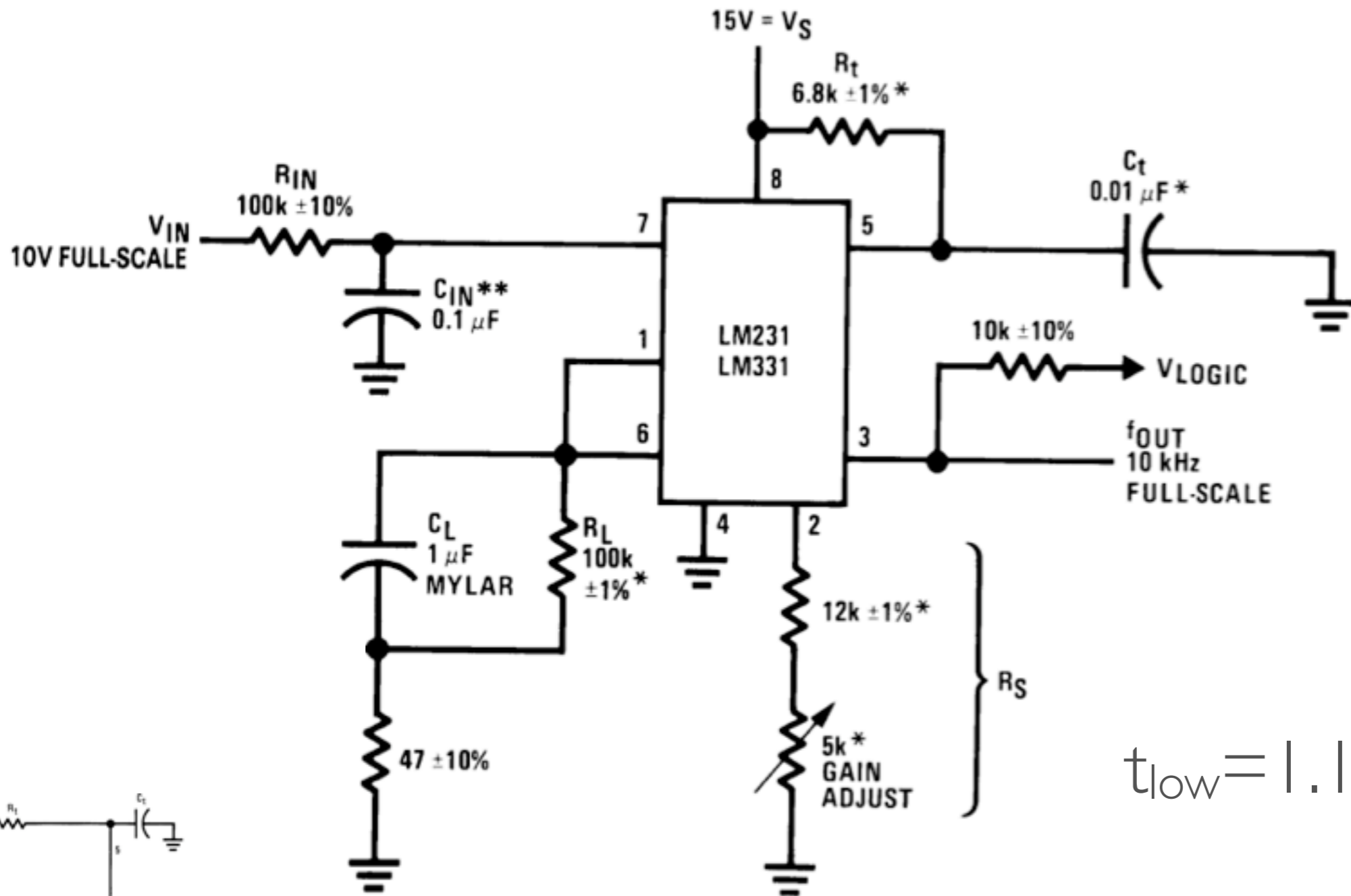

$$t_{low} = 1.1 R_t C_t$$

00568001

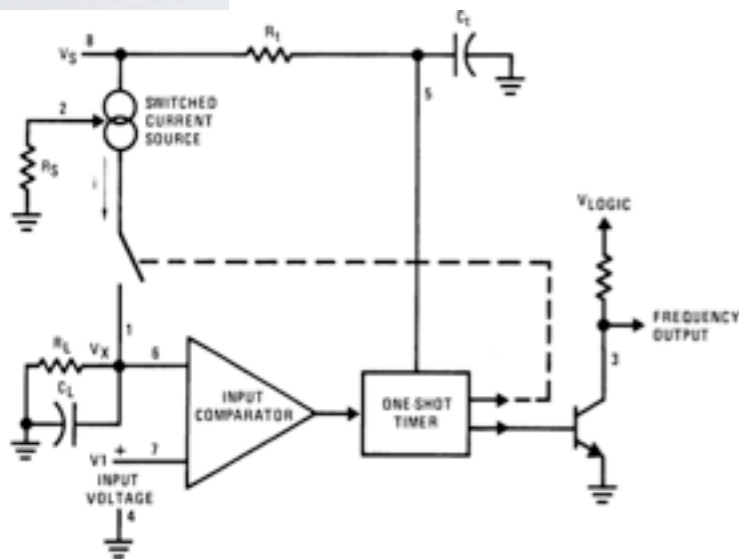

00568004


$$f_{OUT} = \frac{V_{IN}}{2.09 V} \cdot \frac{R_S}{R_L} \cdot \frac{1}{R_t C_t}$$


$f_{out} = 1000 V_{in}$
for gain adj = 2.5k

Example 4-11: Design a V-to-f converter that will output a 20kHz signal when $V_{in, max} = 5V$. If $V_{in, min} = 1V$, what is the frequency range?



Example: Use a V-to-f converter and a counter to build an 8-bit ADC with a conversion rate of 100Hz and an input voltage range of 0 to 1V

VCO

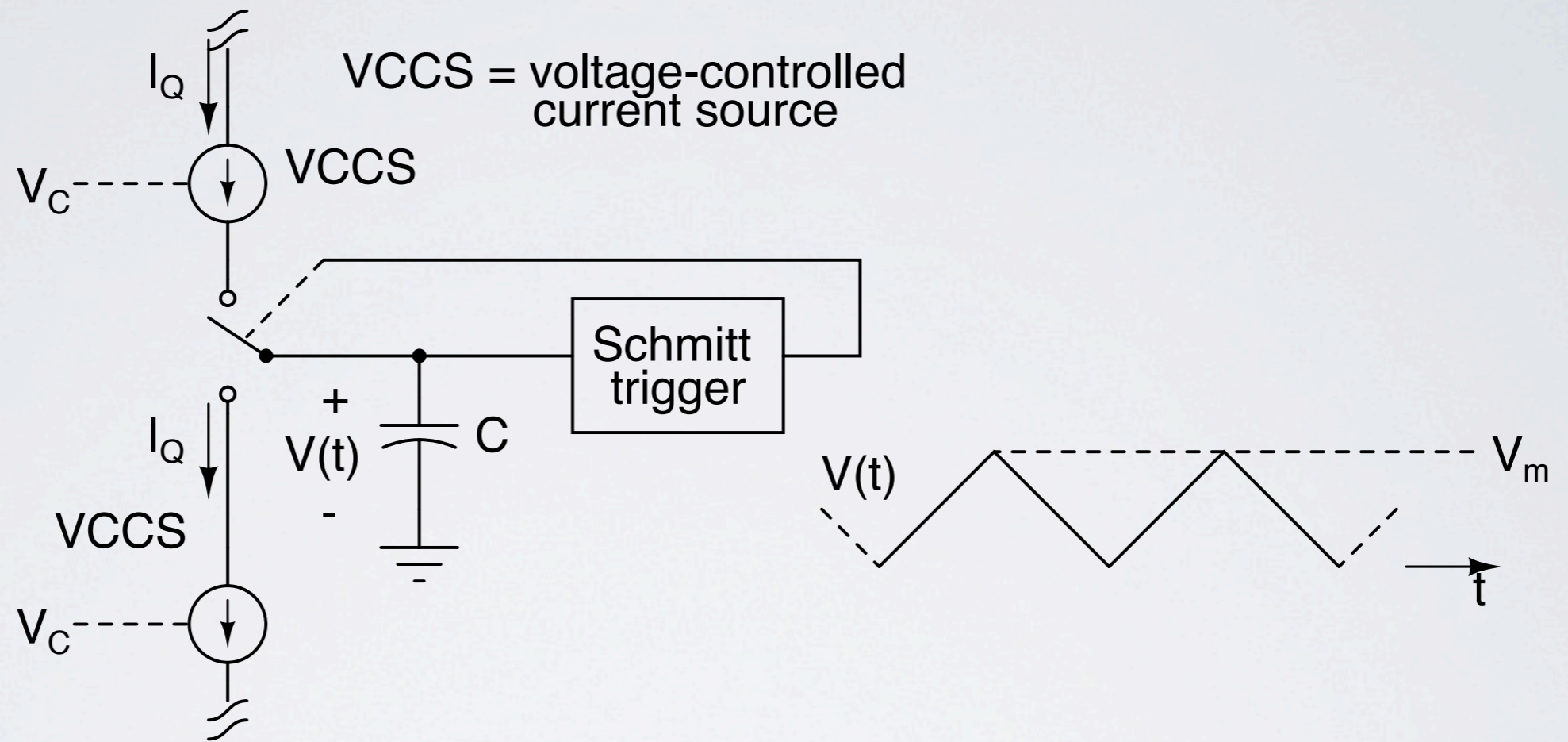


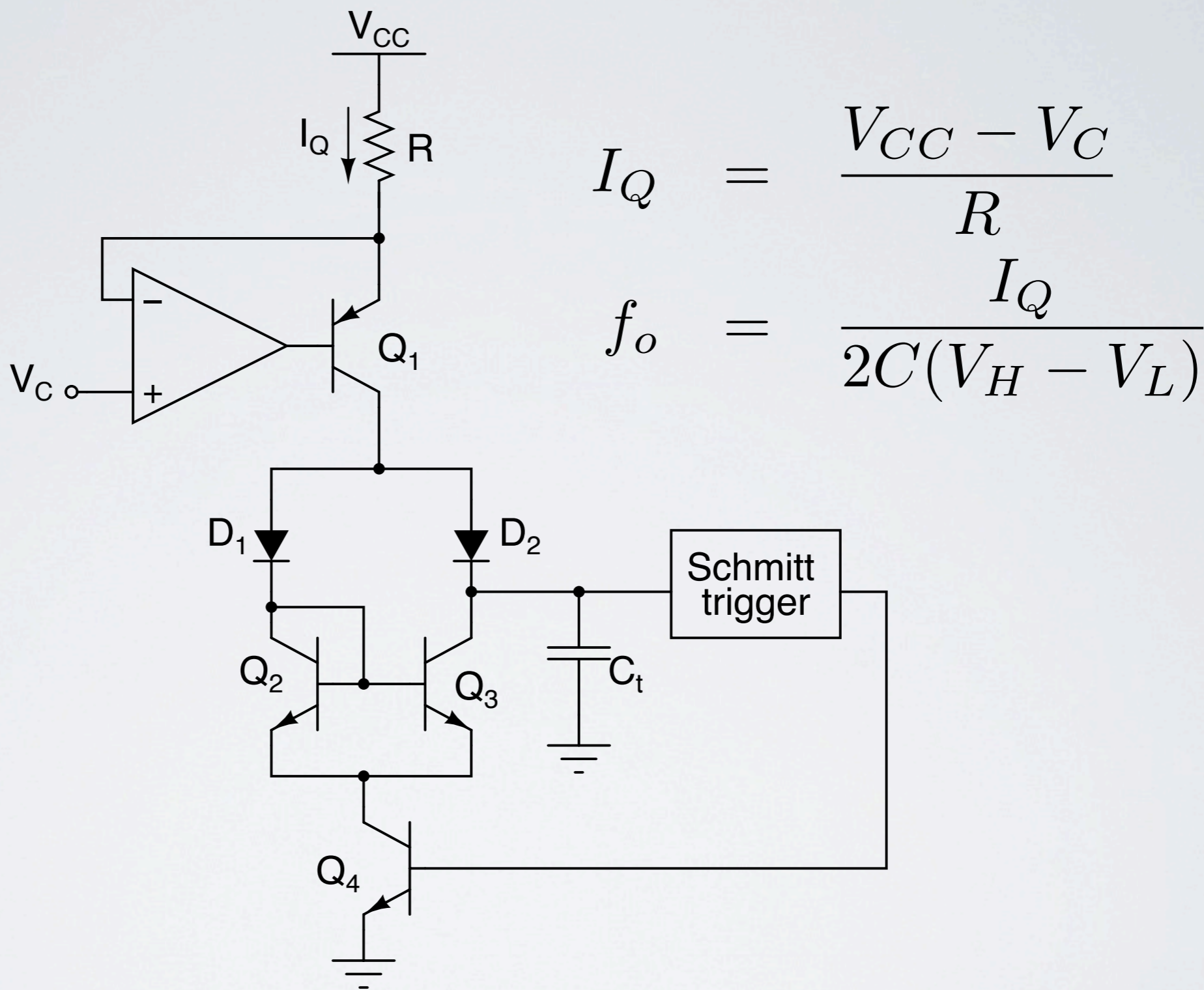

Schmitt Trigger

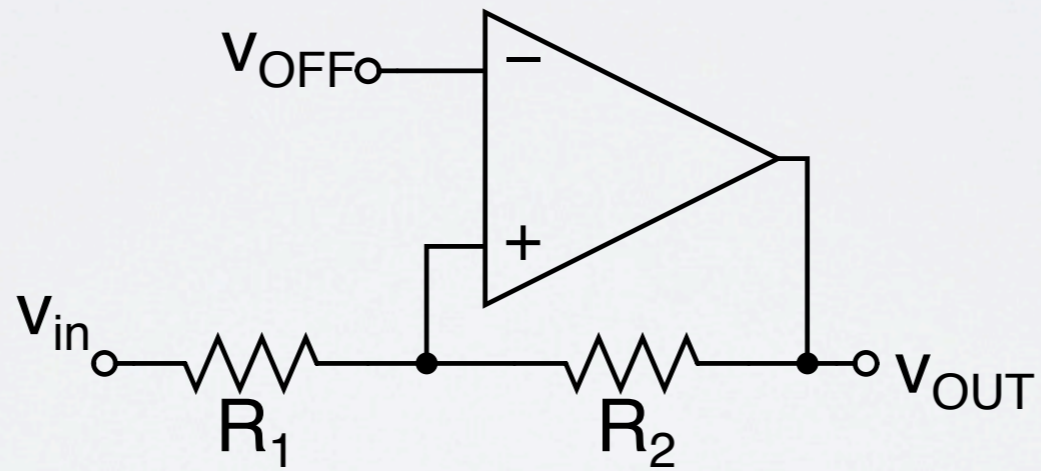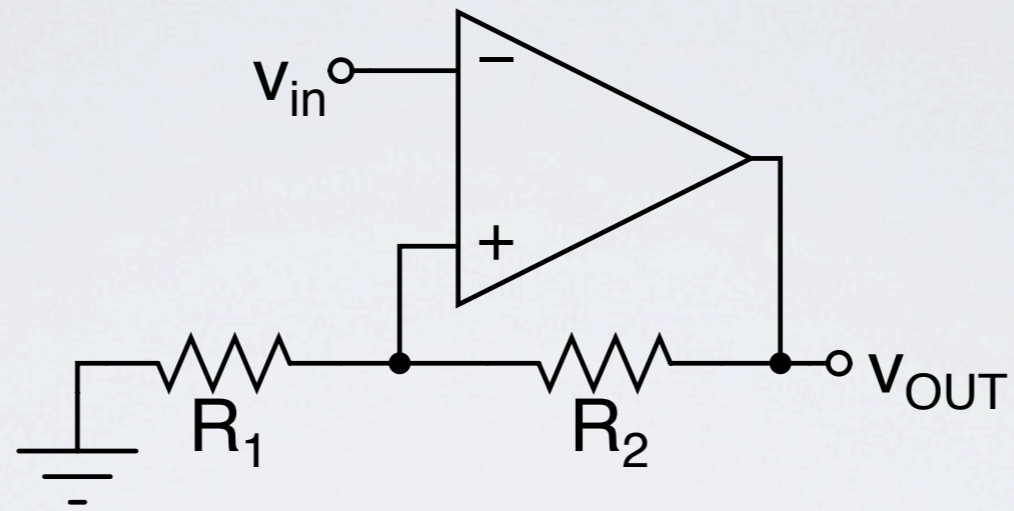


555 Timer

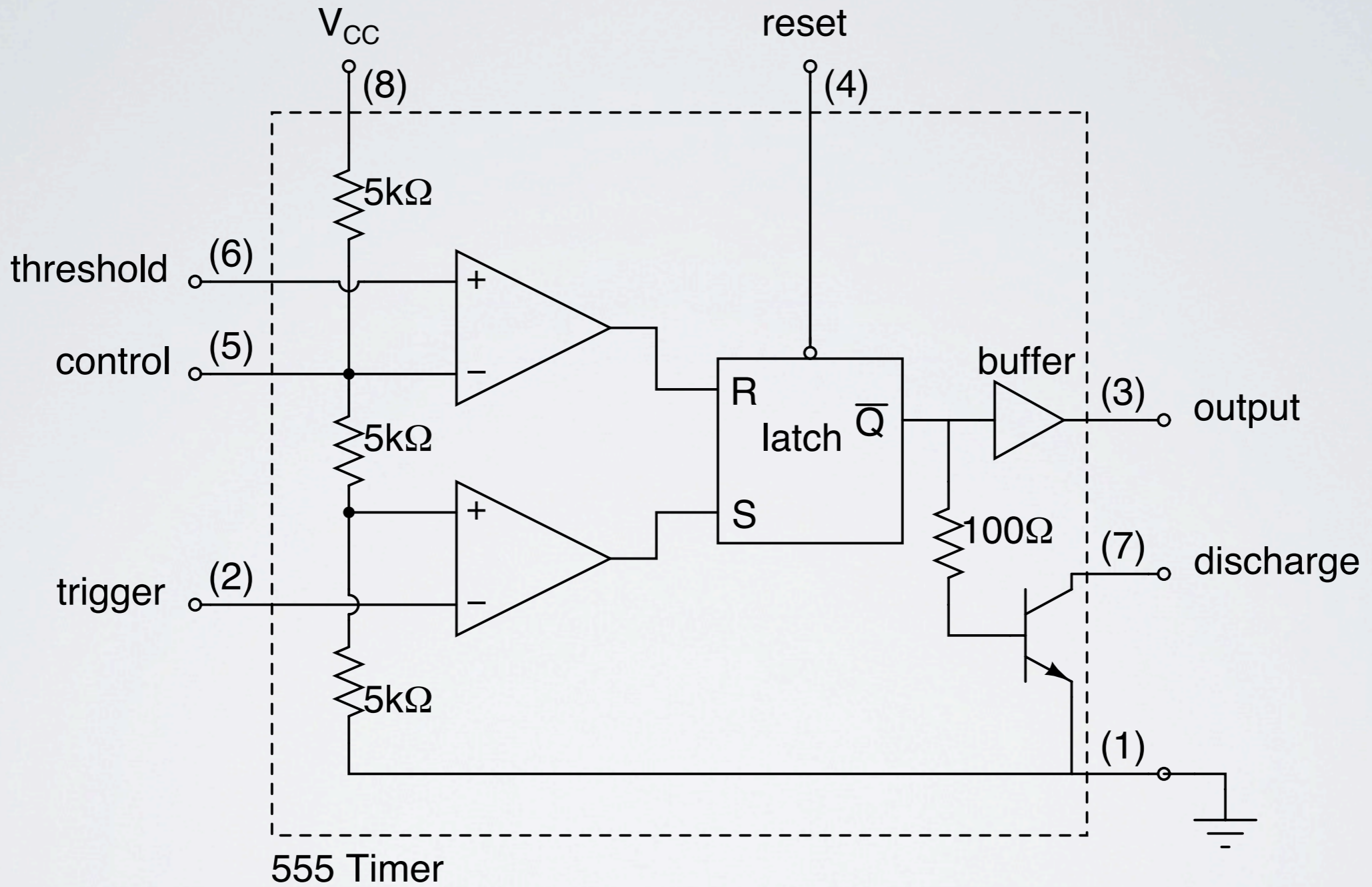


Monostable Multivibrator (one shot)

$$T = RC \ln 3 = 1.1RC$$


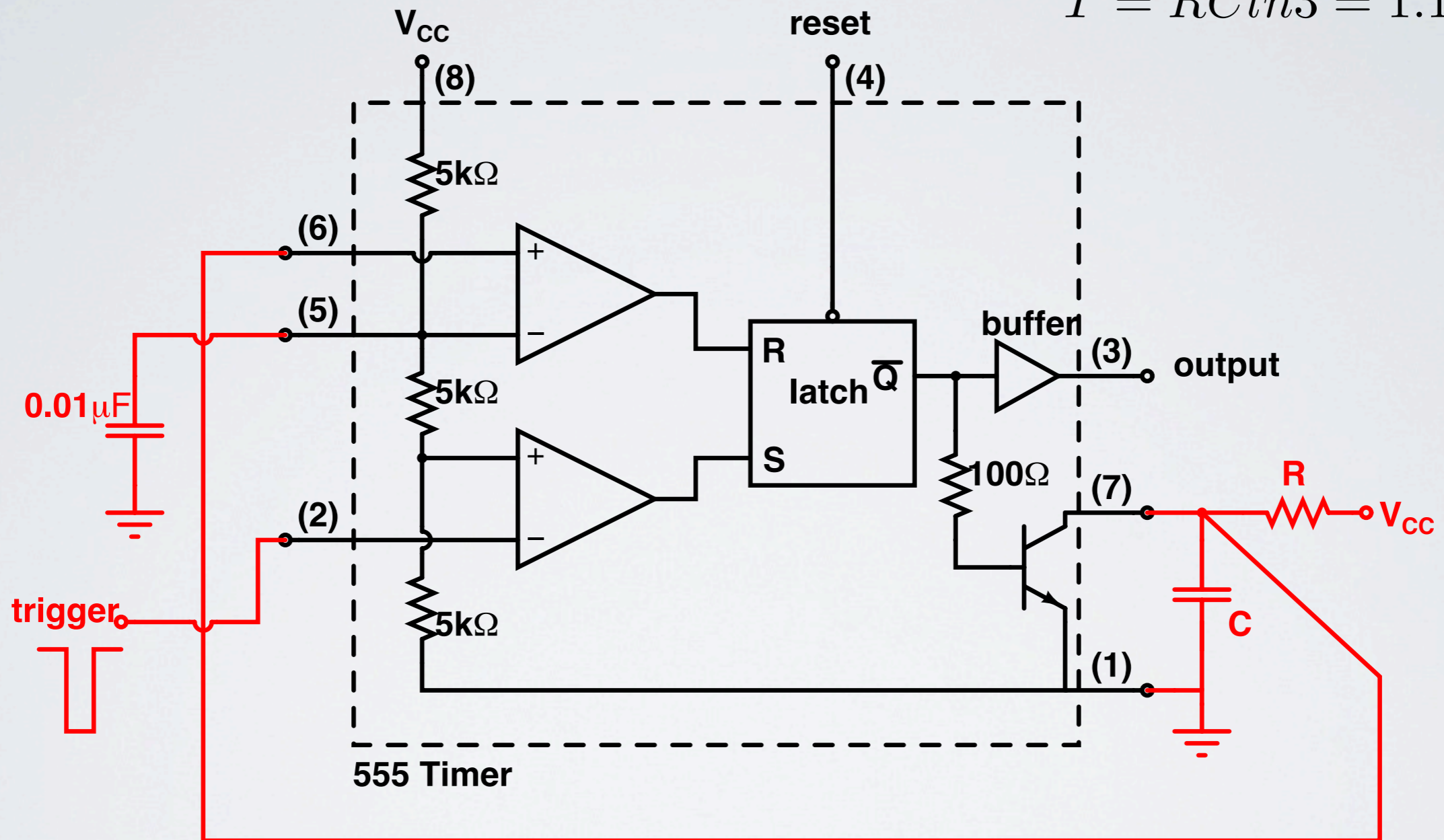


Astable Multivibrator

$$f = \frac{1}{0.693(R_A + 2R_B)C}$$

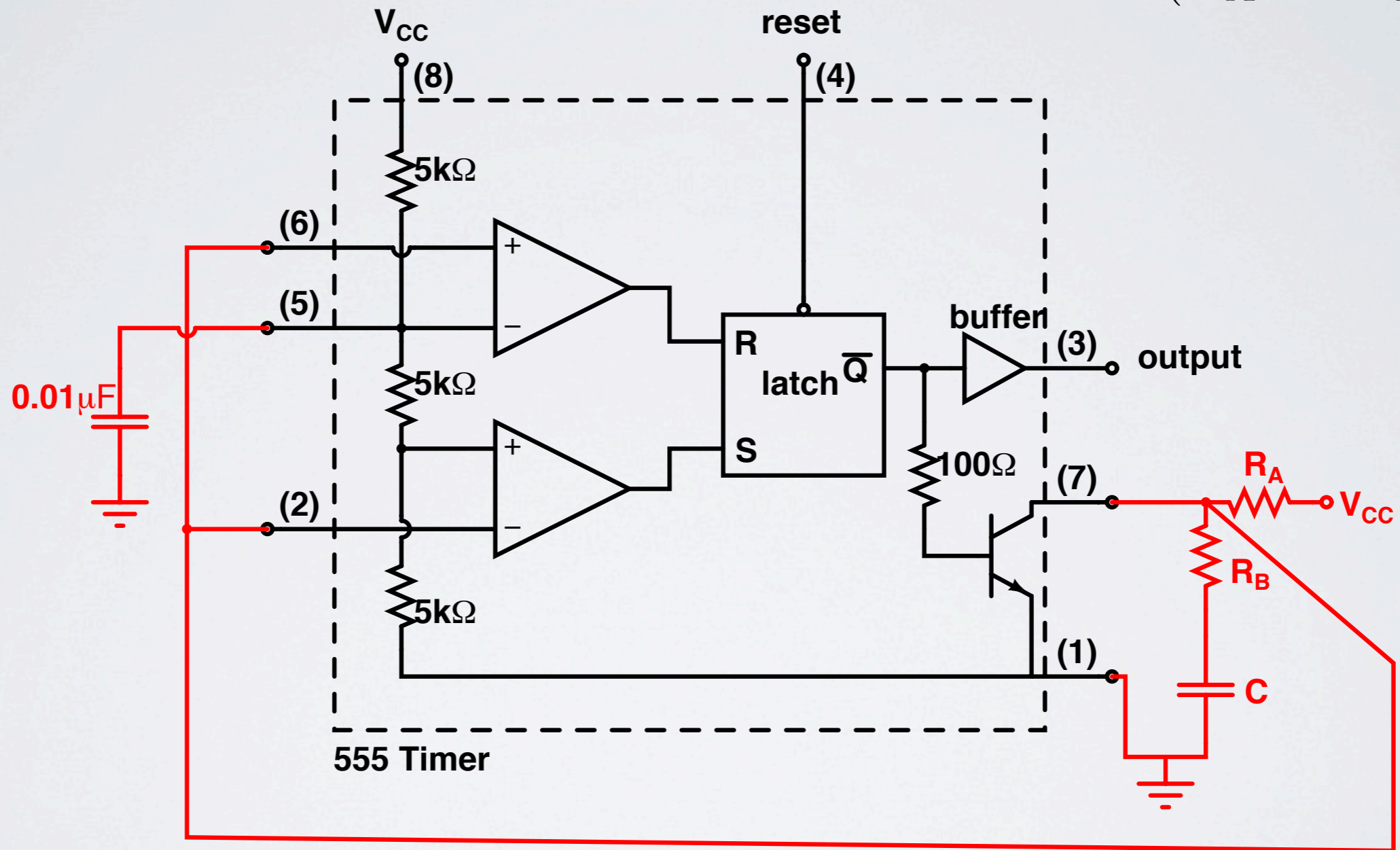

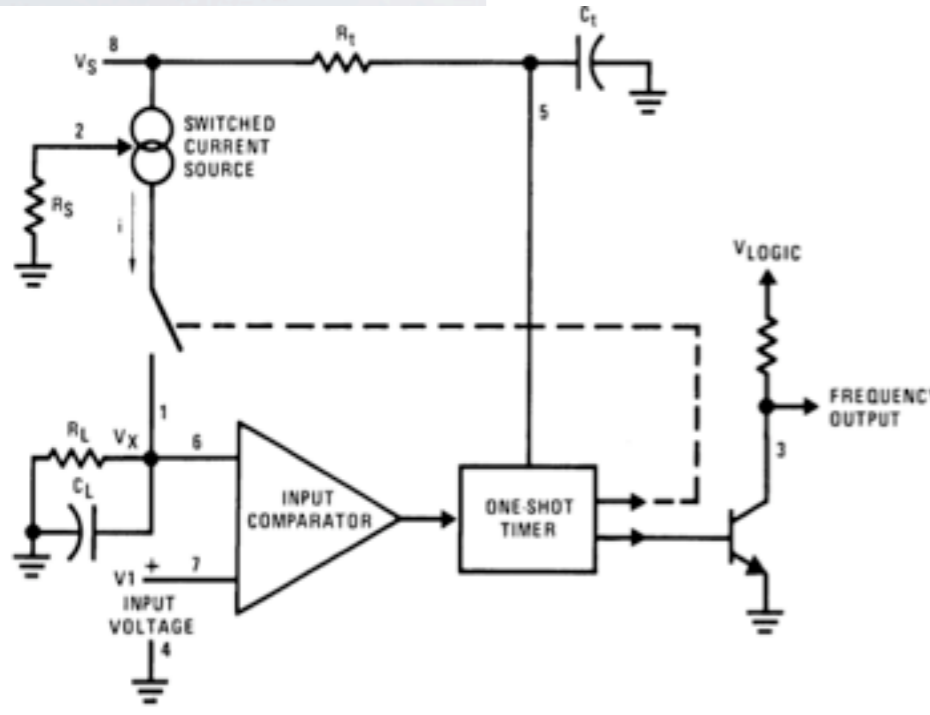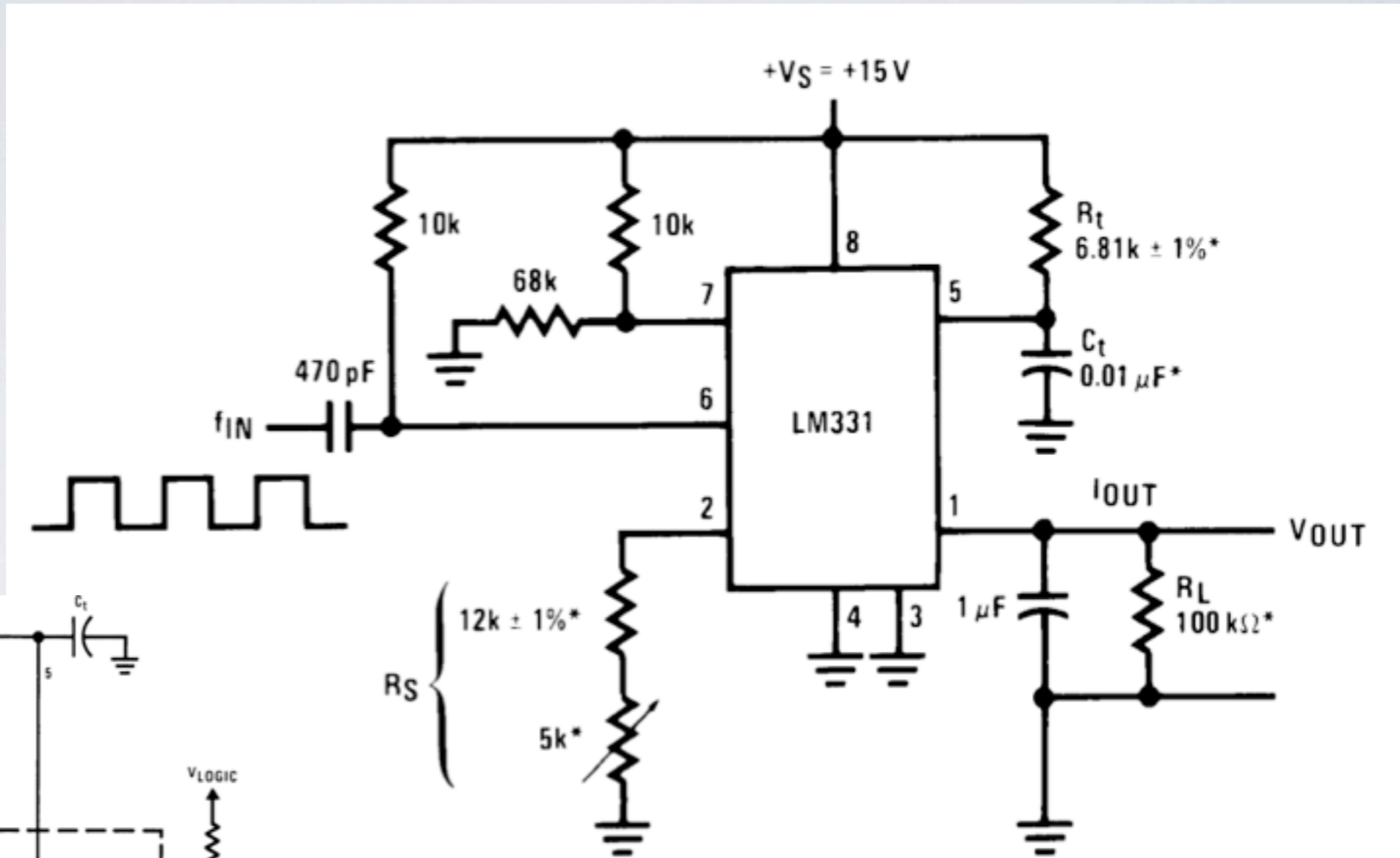F-to-V Conversion using the LM131/LM231/LM331



$$V_{OUT} = f_{IN} \times 2.09V \times \frac{R_L}{R_S} \times (R_t C_t)$$

00568007