
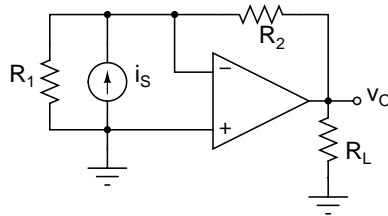


1. For the circuit shown below, a power supply of  $\pm 15V$  is used. The opamp utilizes a bias current  $I_Q = 50mA$  and exhibits a short-circuit current  $I_{ss} = 20mA$  but can otherwise be considered ideal). If  $i_S = 1mA$ ,  $R_2 = 10k\Omega$  and  $R_1 = R_L = 1k\Omega$ , determine the following quantities:

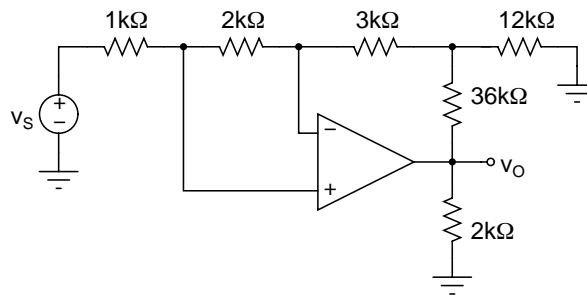
- (a) output voltage  $v_O$ ,
- (b) opamp output current and direction,
- (c) power dissipated by the opamp,
- (d) power dissipated by the whole circuit.



2. Assuming the opamp of the following circuit has an open-loop gain  $a = 3000V/V$ ,  $r_d = \infty$  and  $r_o = 0$ , find the voltage gain  $A_v = \frac{v_O}{v_S}$  for the following circuit.



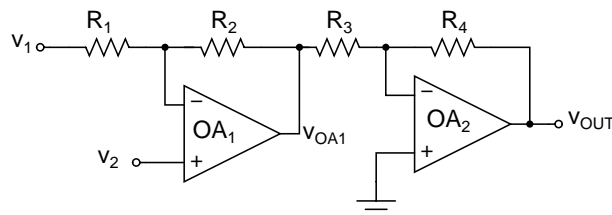- 3. For the circuit shown in problem 2, determine the loop gain  $T$  using the same parameters for the opamp.
- 4. Show that the result obtain in problem 2 is consistent with the feedback formula  $A_V = A_{ideal} \frac{1}{1+T}$ .
- 5. For the following circuit,



let both  $v_1$  and  $v_2$  be connected to ground and consider only the effect of each transistor's bias current  $I_B$ . Assume that current  $I_B$  flows into the + and - inputs of each opamp and that the opamps are matched (i.e. identical).

- (a) Find the relationship between the resistance values that causes the cancelation of the error due to the bias current. Consider only the resistors shown in the above figure.
- (b) Determine the worse-case error due to the offset voltage  $|V_{OS}| \leq 1mV$  if  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$  are chosen so that: (i) the overall voltage gain is  $+25V/V$ ; (ii) the input is  $v_1$  and (iii) no resistor is less than  $1k\Omega$ ; and (iv) the relationship found in part (a) is satisfied.