

INEL 5207 - Spring 2009  
Solutions to review problems

1. For the circuit shown below, a power supply of  $\pm 15V$  is used. The opamp utilizes a bias current  $I_Q = 50mA$  and exhibits a short-circuit current  $I_{ss} = 20mA$  but can otherwise be considered ideal. If  $i_S = 1mA$ ,  $R_2 = 10k\Omega$  and  $R_1 = R_L = 1k\Omega$ , determine the following quantities:

- (a) output voltage  $v_O$ ,

ANSWER:  $v_O = -i_S R_2 = -1mA \times 10k\Omega = -10V$

- (b) opamp output current and direction,

ANSWER: A current of  $10V/1k\Omega = 10mA$  flows upward through  $R_L$ . The opamp output current is  $i_S + i_L = 11mA$  flowing into the opamp.


- (c) power dissipated by the opamp,

ANSWER: Since  $i_S = I_{ss}$ , the opamp won't limit the current. Thus


$$P_{opamp} = I_Q \times 30V + (-10V - (-15V))i_O = 50mA \times 30V + 11mA \times 5V = 1555mW$$

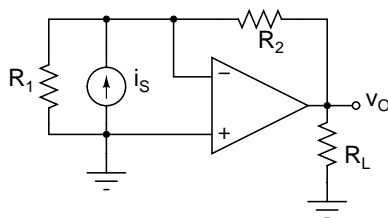- (d) power dissipated by the whole circuit.

$$P_{total} = P_{opamp} + i_L^2 R_L + i_S^2 R_2 = 1555mW + 110mW = 1660mW$$



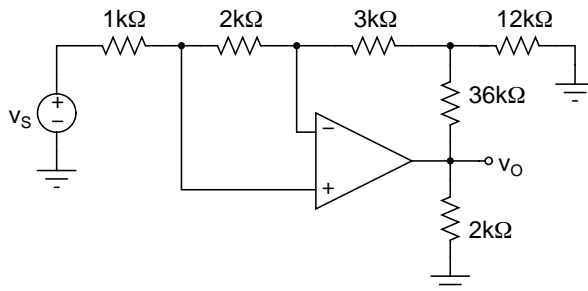2. Assuming the opamp of the following circuit has an open-loop gain  $a = 3000V/V$ ,  $r_d = \infty$  and  $r_o = 0$ , find the voltage gain  $A_v = \frac{v_O}{v_S}$  for the following circuit.



ANSWER: Let  $v_A$  be the voltage at the node common to the  $3k$ ,  $12k$  and  $36k$  resistors.

$$\begin{aligned}
 i_{2k} &= \frac{v_d}{2k} = i_{1k} = i_{3k} \\
 v_A &= v_S - i_{2k} \times 6k = v_S - 3v_d \\
 i_{12k} &= v_A/12k \rightarrow \\
 v_O &= v_A - (i_{2k} - i_{12k})36k \\
 &= v_S - 3v_d - 36 \left( \frac{v_d}{2} - \frac{v_S}{12} + \frac{3v_d}{12} \right) \\
 &= v_S - 3v_d - 18v_d + 3v_S - 9v_d \\
 &= 4v_S - 30v_d = 4v_S - \frac{30v_O}{3000} = 4v_S - 0.01 \times v_O \\
 \frac{v_O}{v_S} &= \frac{4}{1.01}
 \end{aligned}$$

3. For the circuit shown in problem 2, determine the loop gain  $T$  using the same parameters for the opamp.

ANSWER:


$$\begin{aligned}
 \beta &= \frac{2}{6} \times \frac{12 \parallel 6}{12 \parallel 6 + 36} = \frac{1}{3} \times \frac{4}{40} = \frac{1}{30} \\
 T &= a\beta = \frac{3000}{30} = 100V/V
 \end{aligned}$$

4. Show that the result obtain in problem 2 is consistent with the feedback formula  $A_V = A_{ideal} \frac{1}{1+\frac{1}{T}}$ .

ANSWER:

$$\begin{aligned}
 A_{ideal} &= \frac{v_S + 36 \times v_S/12}{v_S} = 4V/V \\
 A_V &= 4V/V \times \frac{1}{1 + \frac{1}{100}} = \frac{4}{1.01}
 \end{aligned}$$

5. For the following circuit,

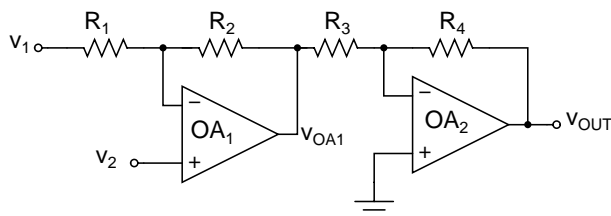


let both  $v_1$  and  $v_2$  be connected to ground and consider only the effect of each transistor's bias current  $I_B$ . Assume that current  $I_B$  flows into the + and - inputs of each opamp and that the opamps are matched (i.e. identical).

- (a) Find the relationship between the resistance values that causes the cancelation of the error due to the bias current. Consider only the resistors shown in the above figure.

ANSWER:

The circuit looks as follows:

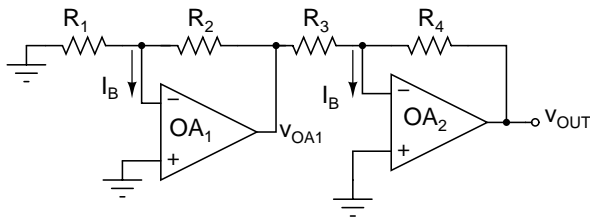

So  $v_{OA1} = i_B R_2$  and  $i_{R3} = \frac{R_2}{R_3} I_B$ . If  $i_{R3} = I_B$ , then no current flows through  $R_4$  and  $v_{OUT} = 0$ . So the relationship that we are seeking is

$$\boxed{R_2 = R_3}$$

- (b) Determine the worse-case error due to the offset voltage  $|V_{OS}| \leq 1mV$  if  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$  are chosen so that: (i) the overall voltage gain is  $25V/V$ ; (ii) the input is  $v_1$  and (iii) no resistor is less than  $1k\Omega$ ; and (iv) the relationship found in part (a) is satisfied.

ANSWER:

To have an overall gain of  $25V/V$ , select  $R_1 = 1k\Omega$ ,  $R_2 = R_3 = 5k\Omega$  and  $R_4 = 25k\Omega$ .

The first stage  $V_{OS}$  will be amplified by a factor  $6 \times 5 = 30$ . The gain for the second stage  $V_{OS}$  is 6. Thus

$$\boxed{E_O = 36mV}$$