
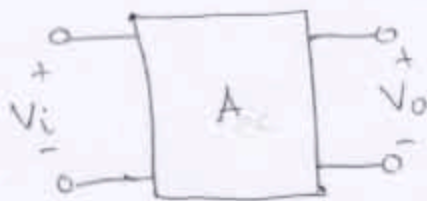


Intro

two-port device

if  $A$  is independent of  $v_i \rightarrow$  linear amplifier

voltage amplifier

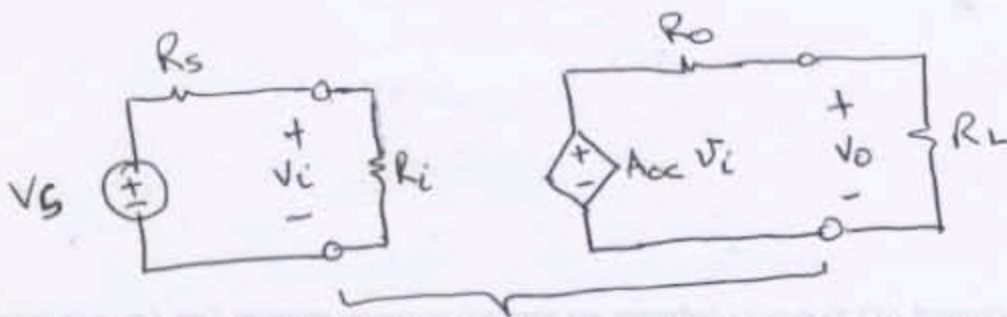


voltage amp.

$$v_o = A_{oc} v_i \frac{R_L}{R_L + R_o} ; v_i = \frac{R_i}{R_i + R_S} v_S$$

$$v_o = A_{oc} \frac{R_i}{R_i + R_S} \frac{R_L}{R_L + R_o} v_S$$
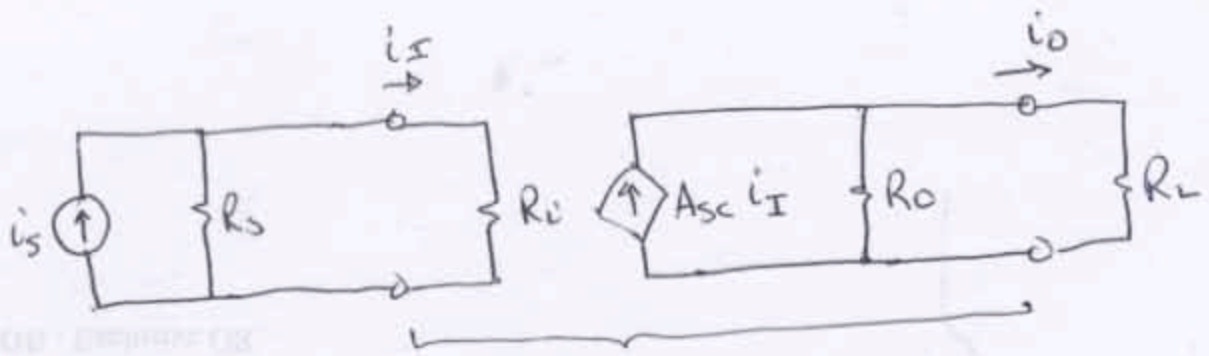
$$\text{gain} = A = \frac{v_o}{v_S} = A_{oc} \underbrace{\frac{R_i}{R_i + R_S}}_{\text{input loading}} \underbrace{\frac{R_L}{R_L + R_o}}_{\text{output loading}}$$



Current Amp.

$$i_o = A_{sc} i_I \frac{R_o}{R_o + R_L} ; i_I = i_s \frac{R_s}{R_s + R_i}$$

$$A_i = \frac{i_o}{i_s} = A_{sc} \frac{R_s}{R_s + R_i} \frac{R_o}{R_o + R_L}$$

The are also:

Transconductance amplifier  $\rightarrow v_i, i_o$

Transresistance amplifier  $\rightarrow i_I, v_o$

### OP AMP




Typical numbers (741)

$$r_d = 2M\Omega$$




$$r_o = 75\Omega$$

$$a = 200 \text{ V/mV}$$

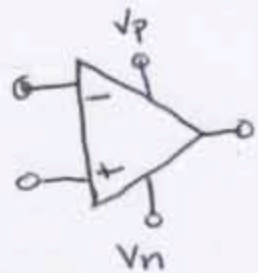

# Basic config.

non-inverting.

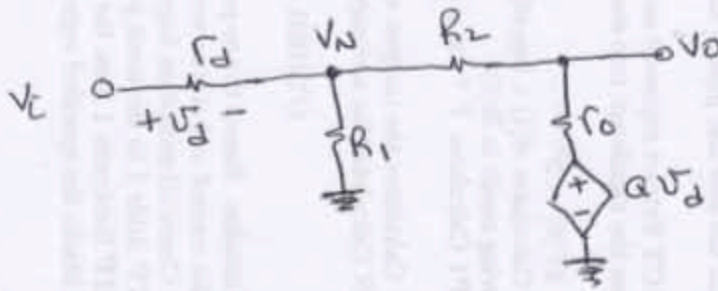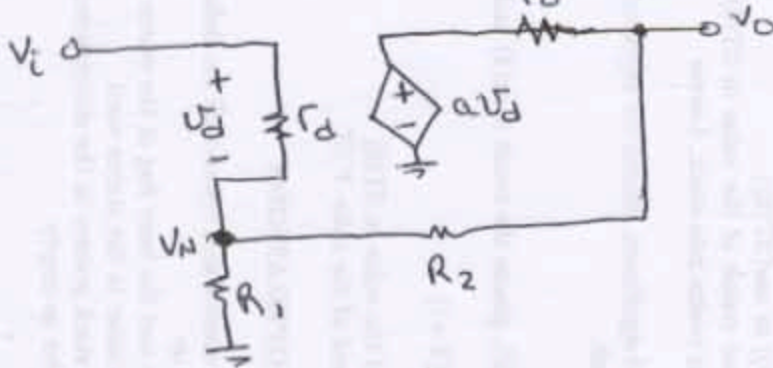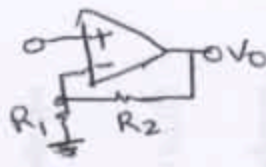

KCL at  $V_n$ :

$$\frac{V_i - V_n}{r_d} = \frac{V_n}{R_1} + \frac{V_n - V_o}{R_2} \quad (1)$$

KCL at  $V_o$ :

$$\frac{V_n - V_o}{R_2} = \frac{V_o - aV_d}{r_o} \quad (2)$$

$$V_d = V_i - V_n$$

from (2)

$$r_o V_n - r_o V_o = R_2 V_o - a(V_i - V_n) R_2$$

$$r_o V_n - r_o V_o = R_2 V_o - aR_2 V_i + aR_2 V_n$$

$$V_n (r_o - aR_2) = (r_o + R_2) V_o - aR_2 V_i$$

$$V_n = \frac{aR_2 V_i - (r_o + R_2) V_o}{aR_2 - r_o}$$

Let  $r_o \ll R_2 \ll aR_2$

$$v_N \approx \frac{aR_2 v_i - R_2 v_o}{aR_2} = v_i - v_o/a$$

From ①

$$\frac{1}{r_d} v_i - \frac{1}{r_d} v_N = \frac{1}{R_1} v_N + \frac{1}{R_2} v_N - \frac{1}{R_2} v_o$$

$$\frac{1}{r_d} v_i = v_N \left( \frac{1}{r_d} + \frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{1}{R_2} v_o$$

if  $r_d \gg R_1, R_2$ ,  $\frac{1}{r_d} \ll \frac{1}{R_1}, \frac{1}{R_2}$

$$\therefore \frac{1}{r_d} v_i \approx v_N \left( \frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{1}{R_2} v_o$$

$$= v_N \left( 1 + \frac{R_2}{R_1} \right) - v_o$$

$$= \left( 1 + \frac{R_2}{R_1} \right) v_i - \left( 1 + \frac{R_2}{R_1} \right) \left( \frac{1}{a} \right) v_o - v_o$$

$$\left( \frac{1}{r_d} - 1 - \frac{R_2}{R_1} \right) v_i \approx - \left( 1 + \frac{R_2}{R_1} \right) v_i = - \left( 1 + \frac{R_2}{R_1} \right) \left( \frac{1}{a} \right) v_o - v_o$$

$$\boxed{\frac{v_o}{v_i} = \frac{1 + R_2/R_1}{1 + \left( 1 + R_2/R_1 \right) \left( \frac{1}{a} \right)}}$$



This shows the effect of having a finite open loop-gain.

Example:  $R_2 = 100R_1$ ;  $1/a = 1/10^4$  (very small)

$$\frac{v_o}{v_i} = \frac{101}{1 + \frac{101}{10^4}} = \frac{101}{1.0101} = 99.99$$

about 1% error in gain.

inv. amp.

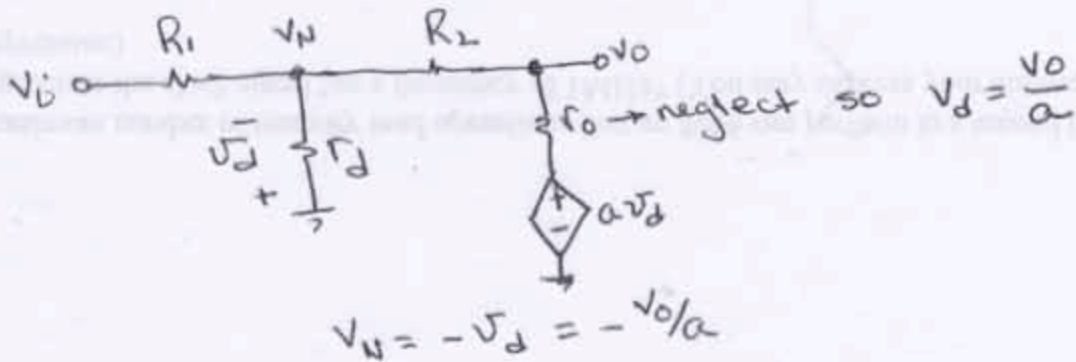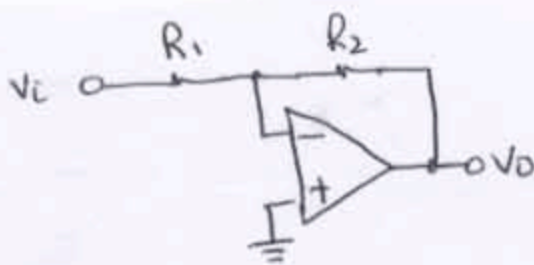

$$\frac{v_i + v_o/a}{R_1} + \frac{v_o/a}{r_d} = \frac{-v_o/a - v_o}{R_2} = \frac{-v_o(1 + 1/a)}{R_2}$$

$$\frac{v_i}{R_1} = -v_o \left( \frac{1}{aR_1} + \frac{1}{a r_d} + \frac{1}{R_2} + \frac{1}{aR_2} \right)$$

$$= -v_o \left[ \frac{1}{R_2} + \frac{1}{a} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{r_d} \right) \right]$$

$$= -\frac{v_o}{R_2} \left( 1 + \frac{R_2}{a} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{r_d} \right) \right)$$

$$\boxed{\frac{v_o}{v_i} = -\frac{R_2}{R_1} \frac{1}{1 + (1 + R_2/R_1 + R_2/r_d)/a}}$$