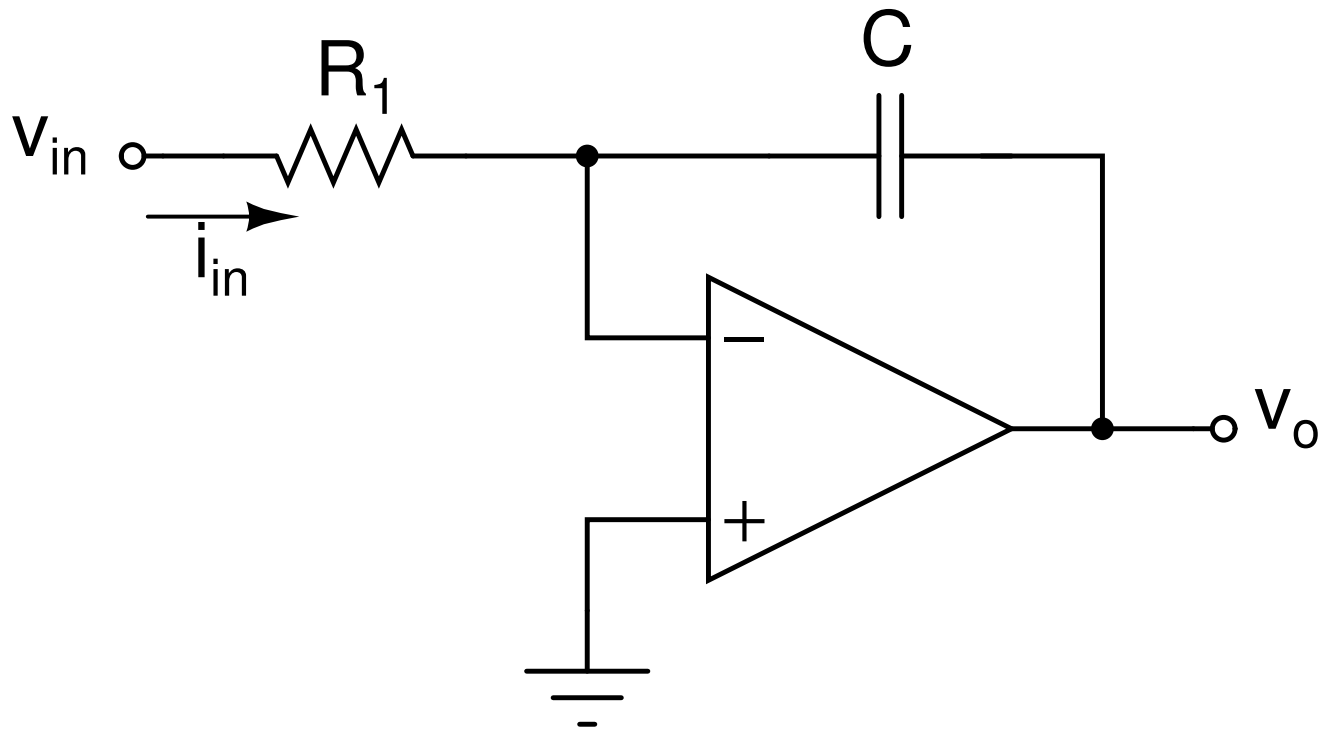



# Filters

INEL 5207 - Spring 2011


# Integrator




# Low-pass filter

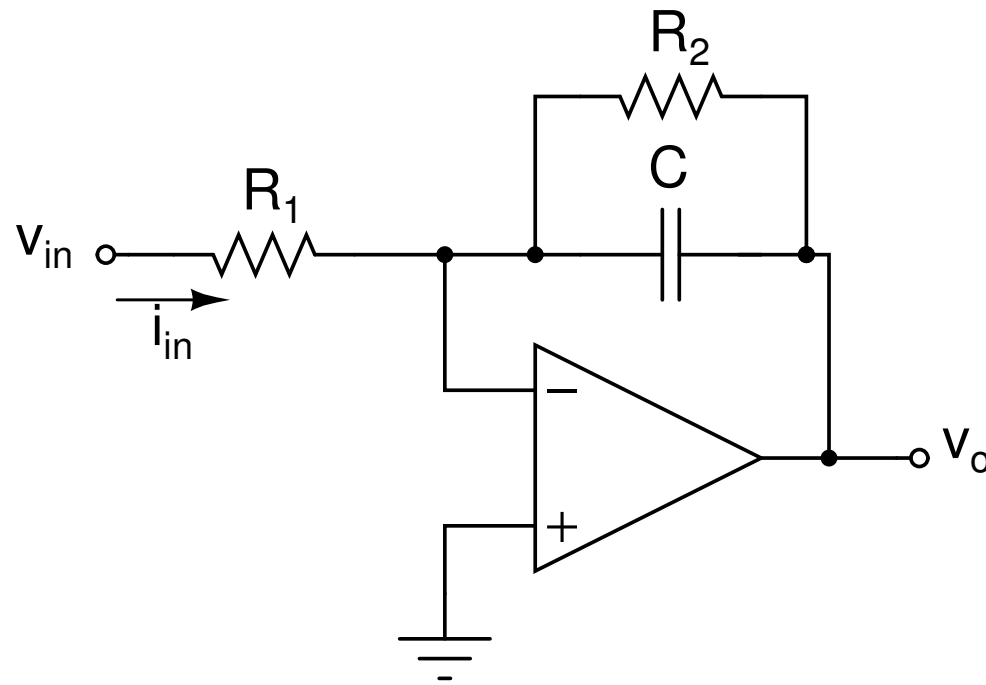

# Differentiator

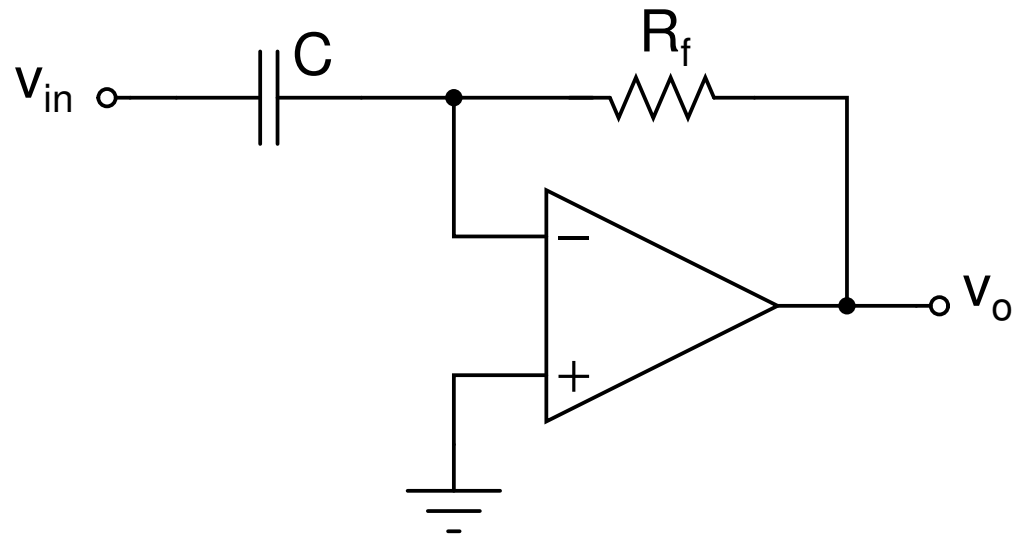


# high-pass filter

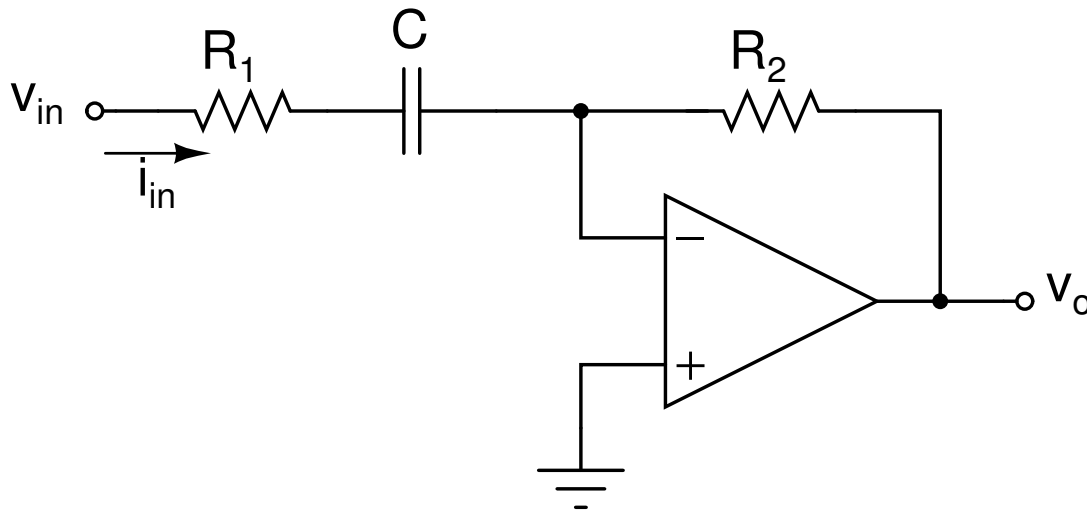




# Phono pre-amp

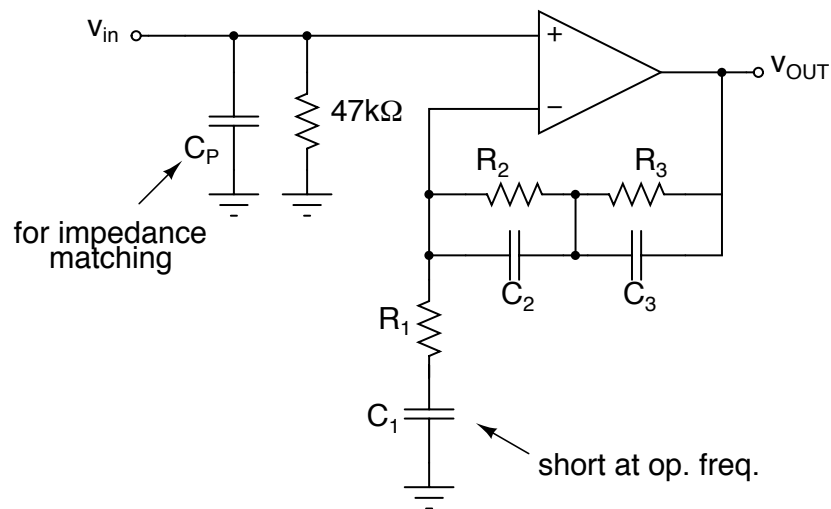
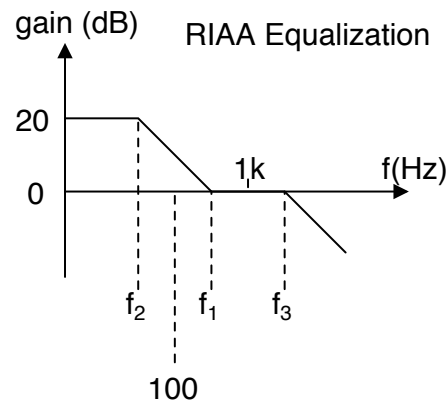
$$f_1 = 500\text{Hz}, f_2 = 50\text{Hz}, f_3 = 2122\text{Hz}$$



shift by 30-40dB for moving magnet cartridge, 50-60dB for moving-coil cartridge

$$H(jf) \simeq 1 + \frac{R_2 + R_3}{R_1} \frac{1 + jf/f_1}{(1 + jf/f_2)(1 + jf/f_3)}$$

$$f_1 = \frac{1}{2\pi(R_2 \parallel R_3)(C_2 + C_3)}$$

$$f_2 = \frac{1}{2\pi R_2 C_2} \quad f_3 = \frac{1}{2\pi R_3 C_3}$$

## 2<sup>nd</sup> order filters

$$H(s) = \frac{N(s)}{(s/\omega_0)^2 + 2\zeta(s/\omega_0) + 1}$$

$\omega_0$  = undamped natural frequency

$\zeta$  = damping ratio

$\zeta > 1$	Overdamp: Real, neg. poles. Response shows decaying exponentials
$0 < \zeta < 1$	Underdamped: poles are complex conj. Response is a damped sinusoid
$\zeta = 0$	Undamped: Poles on imag. axis. Response shows sustained oscillations.
$\zeta < 0$	Unstable: rhp poles. Filters must have $\zeta < 0$ .

Let  $s \rightarrow j\omega$ ,

$$H(j\omega) = \frac{N(j\omega)}{1 - j(\omega/\omega_0)^2 + (j\omega/\omega_0)/Q}$$

$$Q \equiv \frac{1}{2\zeta}$$

Low-pass

$$H_{LP}(j\omega) = \frac{1}{1 - j(\omega/\omega_0)^2 + (j\omega/\omega_0)/Q}$$

- For  $\omega \ll \omega_0$  :  $|H_{LP}| = 1 = 0dB$ .
- For  $\omega \gg \omega_0$  :  $|H_{LP}| = \frac{1}{(\omega/\omega_0)^2} = -40dB/dec$ .
- For  $\omega = \omega_0$  :  $|H_{LP}| = Q$


Largest  $Q$  before the onset of peaking:  $\frac{1}{\sqrt{2}}$

For  $Q > \frac{1}{\sqrt{2}}$

$$\frac{\omega_{peak}}{\omega_0} = \sqrt{1 - \frac{1}{2Q^2}}$$

$$|H_{LP}|_{max} = \frac{Q}{\sqrt{1 - \frac{1}{4Q^2}}}$$

## 2<sup>nd</sup> order Response

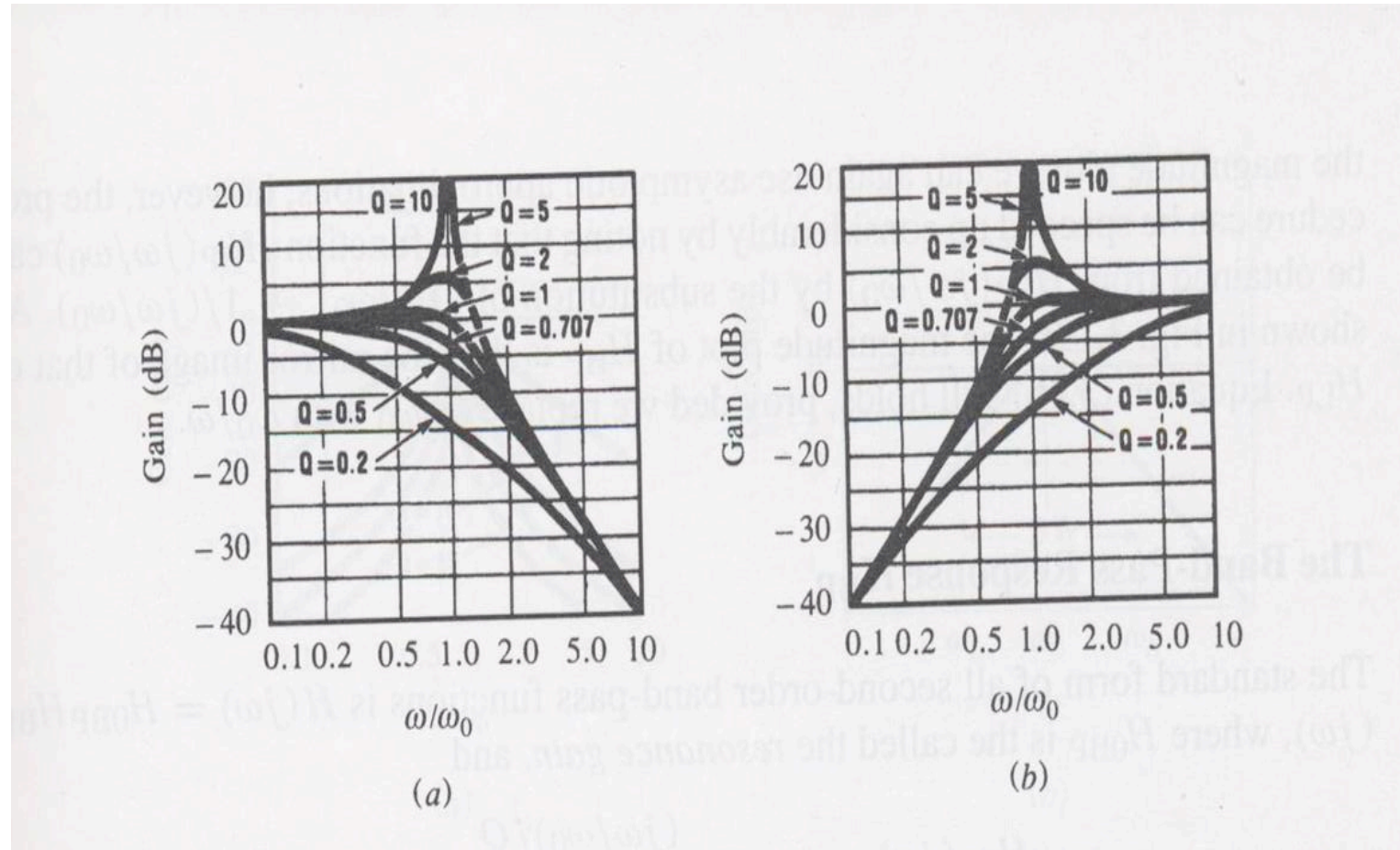

Lowpass and highpass

## High-pass

$$H_{HP}(j\omega) = \frac{-(\omega/\omega_0)^2}{1 - j(\omega/\omega_0)^2 + (j\omega/\omega_0)/Q}$$

## Band-pass


$$H_{BP}(j\omega) = \frac{j(\omega/\omega_0)/Q}{1 - j(\omega/\omega_0)^2 + (j\omega/\omega_0)/Q}$$

- $j(\omega/\omega_0)/Q \rightarrow$  zero at origin.
- For  $\omega \ll \omega_0$  :  $|H_{BP}| \simeq (\omega/\omega_0)/Q = (\frac{\omega}{\omega_0})_{dB} - Q_{dB}$ .
- For  $\omega \gg \omega_0$  :  $|H_{BP}| \simeq -(\frac{\omega}{\omega_0})_{dB} - Q_{dB}$ .
- For  $\omega = \omega_0$  :  $|H_{LP}| = 0$


$$\begin{aligned} BW &= \omega_H - \omega_L \\ &= \omega_0 \left( \sqrt{1 - \frac{1}{4Q^2}} - \frac{1}{2Q} \right) - \omega_0 \left( \sqrt{1 - \frac{1}{4Q^2}} + \frac{1}{2Q} \right) \end{aligned}$$

$$\omega_0 = \sqrt{\omega_L \omega_H}$$

$$Q = \omega_0 / BW$$

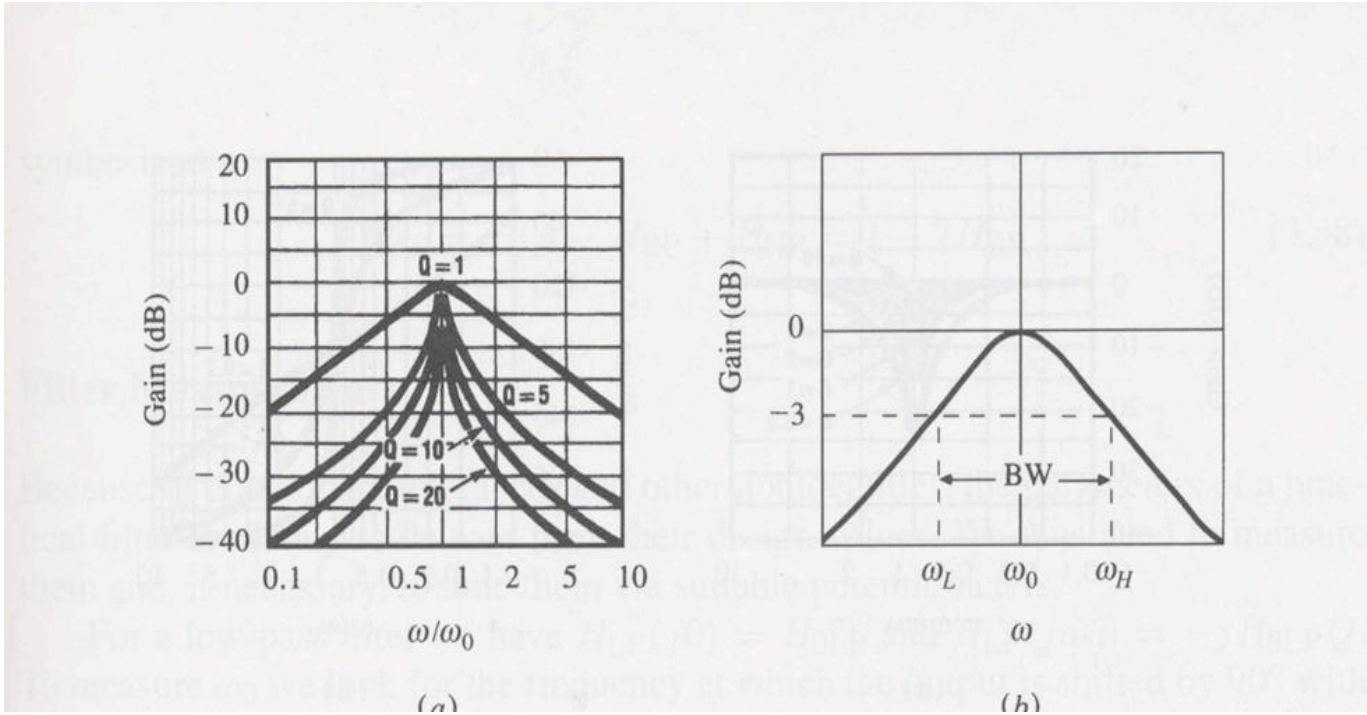

# Bandpass

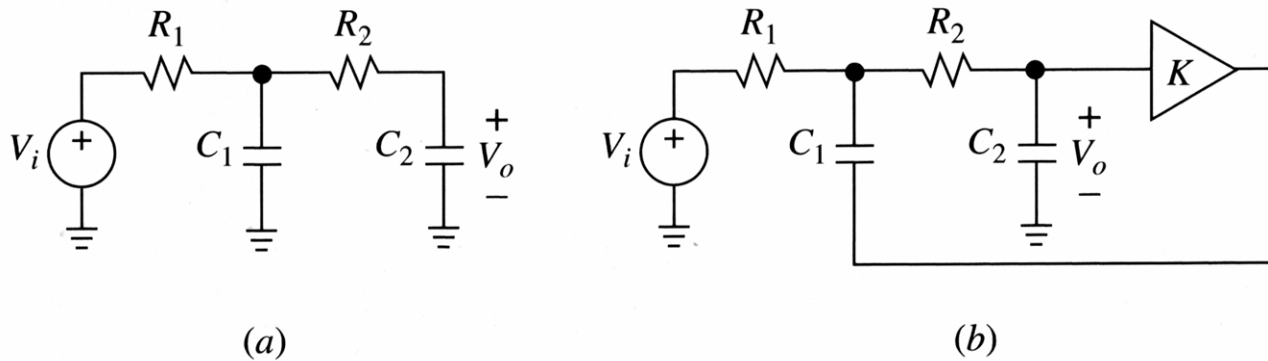

**FIGURE 3.22**

(a) Passive and (b) active realization of a second-order low-pass filter.

For (a)  $Q \leq 0.5$

Textbook

$$Z_1 = R_1$$


$$Z_2 = R_2$$

$$Z_3 = 1/sC_1$$

$$Z_4 = 1/sC_2$$

$$K = A_{v0}$$

## Sallen-Key (KRC) Filter

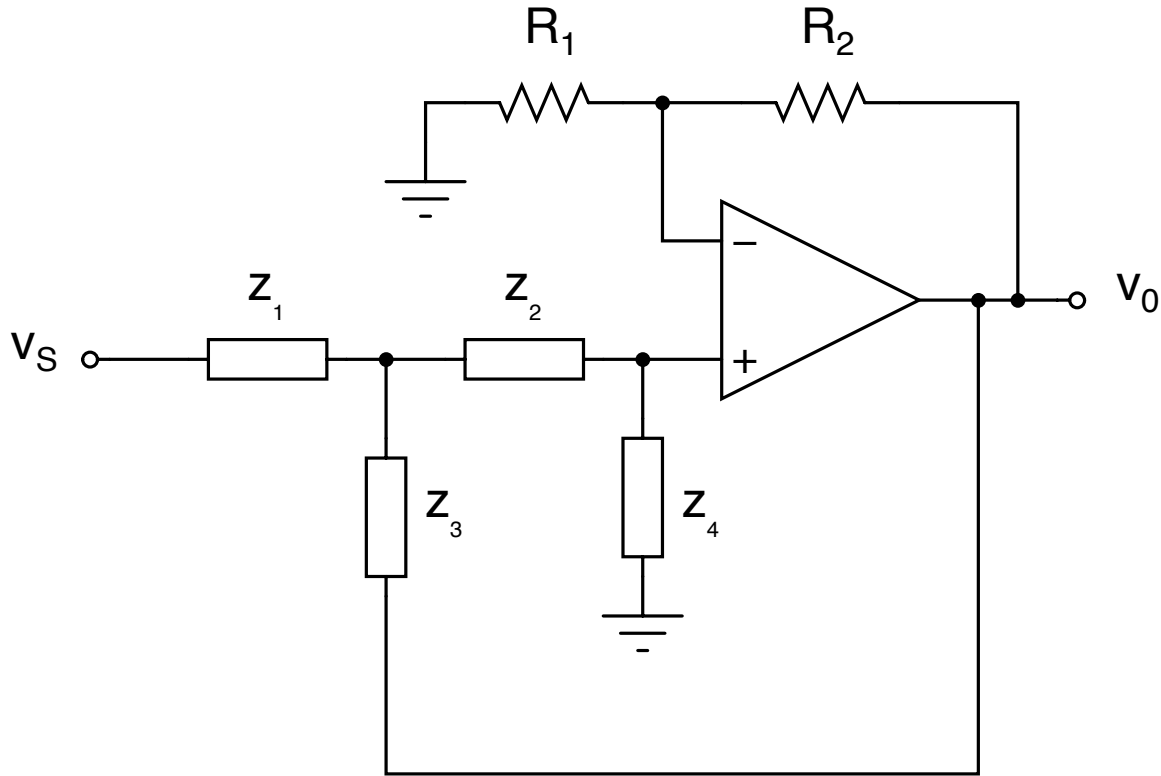

$$v_+ = \frac{z_4}{z_2 + z_4} \left( \frac{z_3(z_2 + z_4)}{z_1(z_2 + z_3 + z_4) + z_3(z_2 + z_4)} v_S + \frac{z_1(z_2 + z_4)}{z_3(z_1 + z_2 + z_4) + z_1(z_2 + z_4)} v_O \right)$$

Setting  $v_+ = V_O/A_{v0}$  and rearranging gives

$$\frac{v_O}{A_{v0}} = \frac{z_3 z_4}{z_1(z_2 + z_3 + z_4) + z_3(z_2 + z_4)} v_S + \frac{z_1 z_4}{z_3(z_1 + z_2 + z_4) + z_1(z_2 + z_4)} v_O$$

or

$$\left(1 - \frac{z_1 z_4}{z_3(z_1 + z_2 + z_4) + z_1(z_2 + z_4)}\right) v_O = \frac{z_3 z_4}{z_1(z_2 + z_3 + z_4) + z_3(z_2 + z_4)} v_S$$

which, after rearranging yields

$$\frac{v_O}{v_S} = \frac{z_3 z_4}{z_3(z_1 + z_2 + z_4) + z_1 z_2 + z_1 z_4(1 - A_{v0})} A_{v0}$$

where  $A_{v0} = 1 + R_2/R_1$ .

Component choices are for the *equal component* design

To obtain a Sallen-Key filter, let  $z_1 = z_2 = R$  and  $z_3 = z_4 = \frac{1}{sC}$ . Then

$$\frac{v_O}{v_S} = \frac{\frac{1}{s^2 C^2}}{\frac{1}{sC}(2R + \frac{1}{sC}) + R^2 + \frac{R}{sC}(1 - A_{v0})} A_{v0}$$

which can be rearranged to obtain

$$\frac{v_O}{v_S} = \frac{A_{v0}}{s^2 (RC)^2 + (3 - A_{v0})(RC)s + 1}$$

Letting  $RCs$  represent a scaled frequency  $s' = j\omega'$ ,

$$\frac{v_O}{v_S} = \frac{A_{v0}}{s'^2 + (3 - A_{v0})s' + 1}$$

whose denominator is of the form


$$s^2 + 2\zeta s + 1$$

$$Q = 3 - A_{v0}$$

Example: Design an equal-component low-pass filter with  $f_0 = 1kHz$  and  $Q = 5$ .

Example: Modify the design to get a dc gain of 0dB.


# Unity-gain option

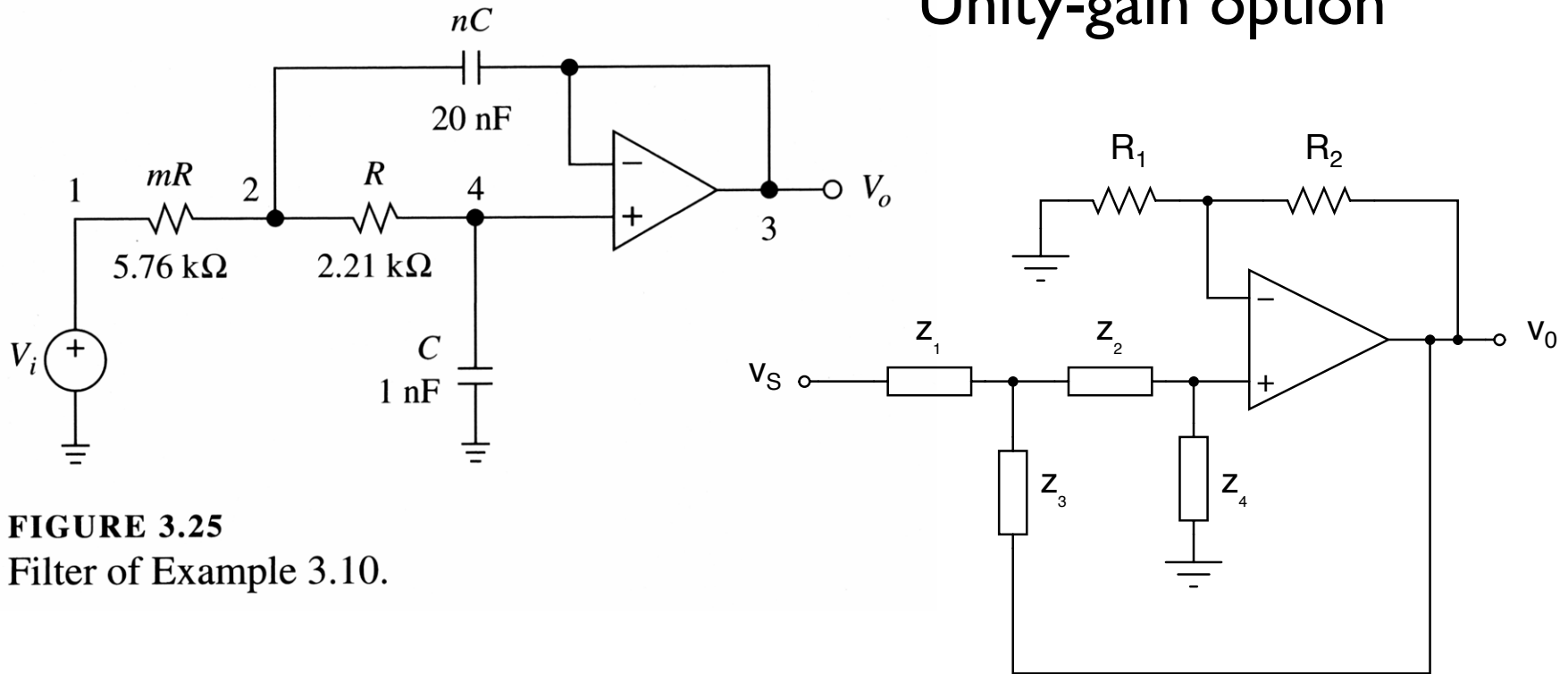


**FIGURE 3.25**  
Filter of Example 3.10.

$$\frac{v_O}{v_S} = \frac{z_3 z_4}{z_3(z_1 + z_2 + z_4) + z_1 z_2 + z_1 z_4(1 - A_{v0})} A_{v0}$$

$$z_1 = mR \quad z_2 = R \quad z_3 = 1/nsC \quad z_4 = 1/sC$$

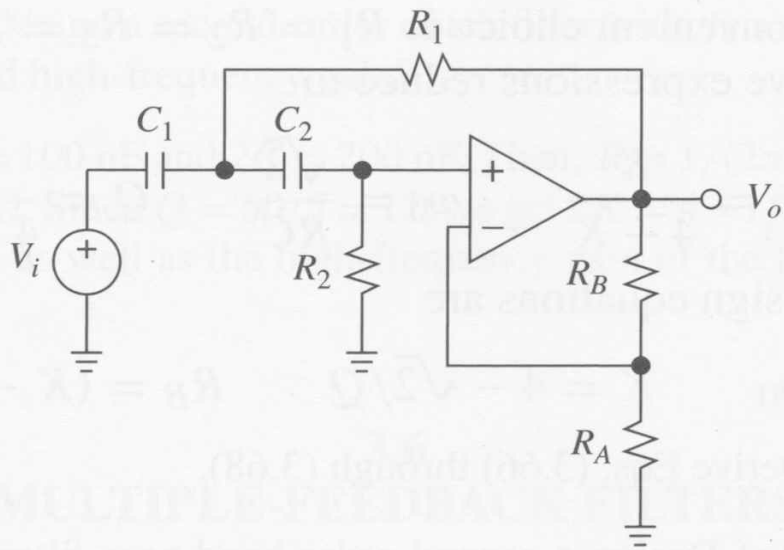


**FIGURE 3.27**  
High-pass *KRC* filter.

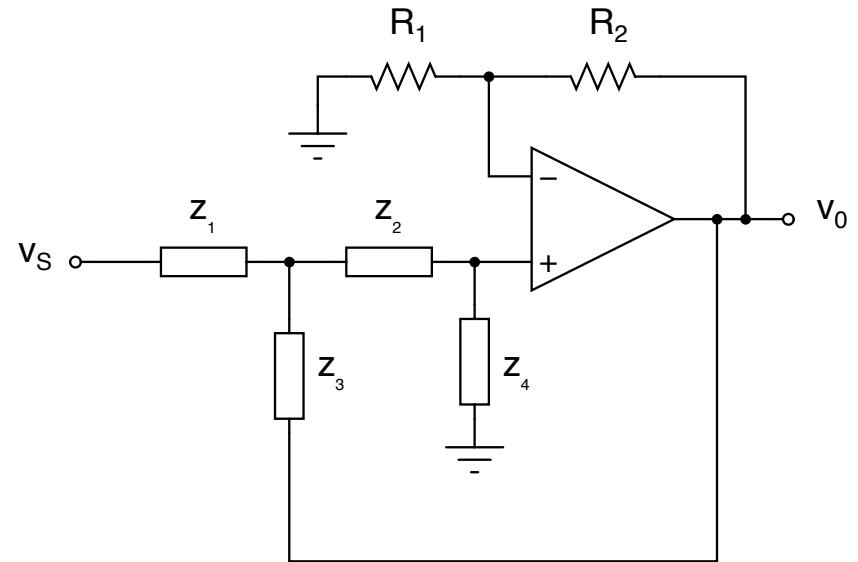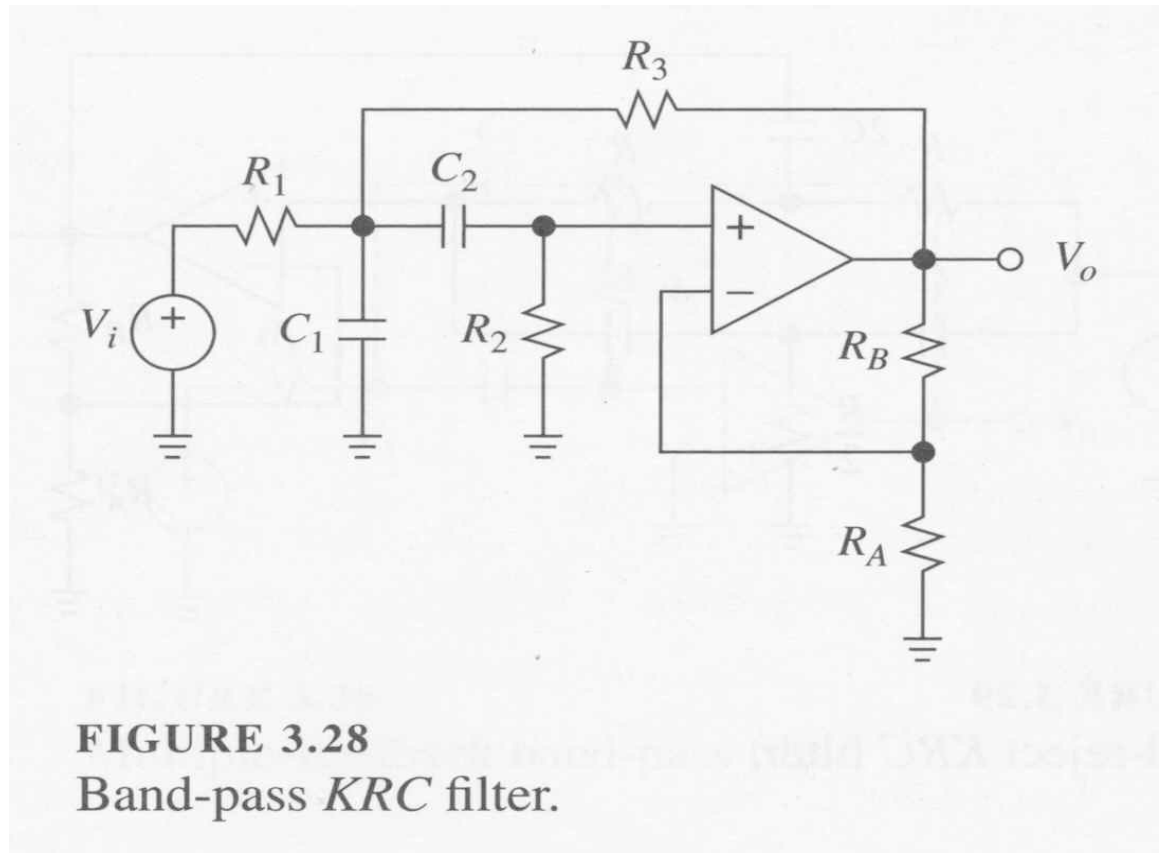

$$\frac{v_O}{v_S} = \frac{z_3 z_4}{z_3(z_1 + z_2 + z_4) + z_1 z_2 + z_1 z_4(1 - A_{v0})} A_{v0}$$

$$z_1 = 1/sC_1 \quad z_2 = 1/sC_2 \quad z_3 = R_1 \quad z_4 = R_2$$




Band-Pass KRC:  $V_O/V_i = H_{0BP}H_{BP}$  where  $H_{BP}$  is given in slide 12 and, for  $Q > \sqrt{2}/3$ ,  $R_1 = R_2 = R_3 = R$  and  $C_1 = C_2 = C$ ,

$$H_{0BP} = \frac{K}{4 - K} \quad \omega_0 = \frac{\sqrt{2}}{RC} \quad Q = \frac{\sqrt{2}}{4 - K}$$

Design equations:

$$RC = \sqrt{2}/\omega_0 \quad K = 4 - \sqrt{2}/Q \quad R_B = (K - 1)R_A$$

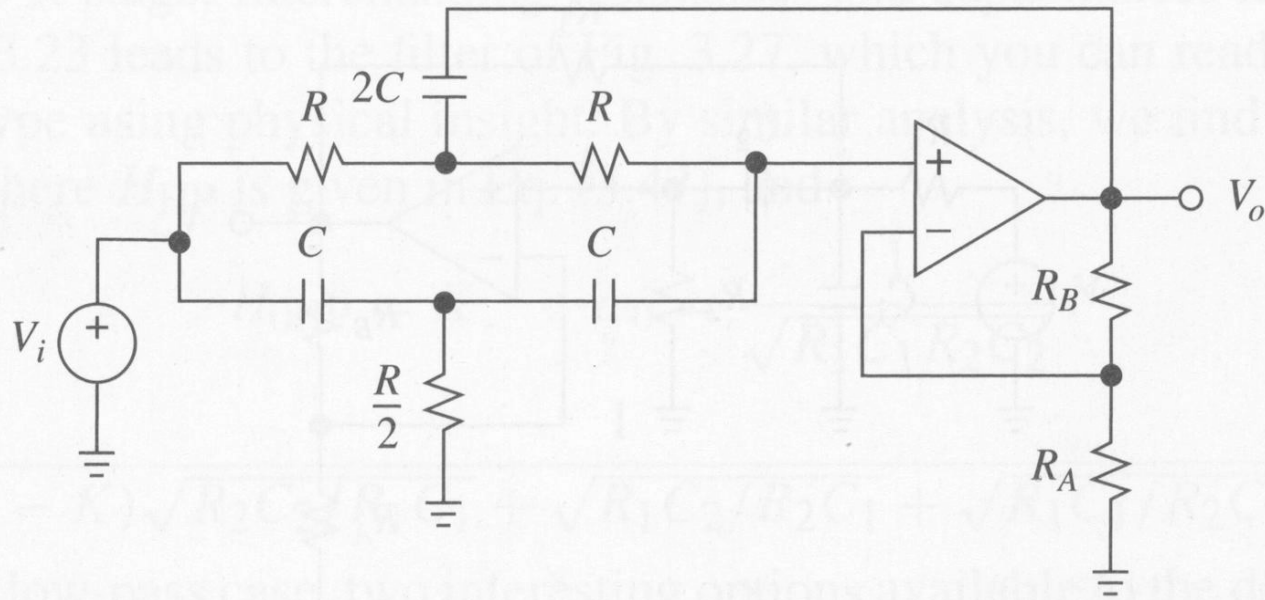

**FIGURE 3.29**  
Band-reject *KRC* filter.

### Band Reject (Notch) Filter

$$H_N(j\omega) = \frac{1 - (\omega/\omega_0)^2}{1 - (\omega/\omega_0)^2 + j(\omega/\omega_0)/Q}$$

$$V_O/V_i = H_{0N}H_N \quad H_{0N} = K \quad \omega_0 = \frac{1}{RC} \quad Q = \frac{1}{4 - 2K}$$