

AMPLIFIER INPUT AND OUTPUT IMPEDANCES

INEL 5207 - SPRING 2008

ECE DEPT. UPRM

EQUIVALENT IMPEDANCES

- OPAMP GAIN INTRODUCES A POLE IN THE CIRCUIT'S EQUIVALENT INPUT & OUTPUT IMPEDANCES
- THIS MEANS THAT THE SOURCE/LOAD WILL SEE A COMPLEX EQUIVALENT QUANTITY I.E. AN IMPEDANCE INSTEAD OF A RESISTANCE
- THUS THE LOADING AT THE INPUT/OUTPUT CAN POTENTIALLY AFFECT THE FREQUENCY RESPONSE
- NOTICE THAT THIS IS INDEPENDENT OF THE OPAMP COMMON-MODE AND -DIFFERENTIAL-MODE PARASITIC CAPACITANCES

INPUT-SERIES

$$a = \frac{a_0}{1 + j \frac{f}{f_b}}$$


$$Z_{IN} = (1 + T)r_d = \left(1 + \frac{\beta a_0}{1 + j \frac{f}{f_b}}\right) r_d$$

$$= \frac{1 + \beta a_0 + j \frac{f}{f_b}}{1 + j \frac{f}{f_b}} r_d$$

$$= \frac{1 + j \frac{f}{(1 + \beta a_0) f_b}}{1 + j \frac{f}{f_b}} (1 + \beta a_0) r_d$$

$$\approx \frac{1 + j \frac{f}{\beta a_0 f_b}}{1 + j \frac{f}{f_b}} (1 + \beta a_0) r_d$$
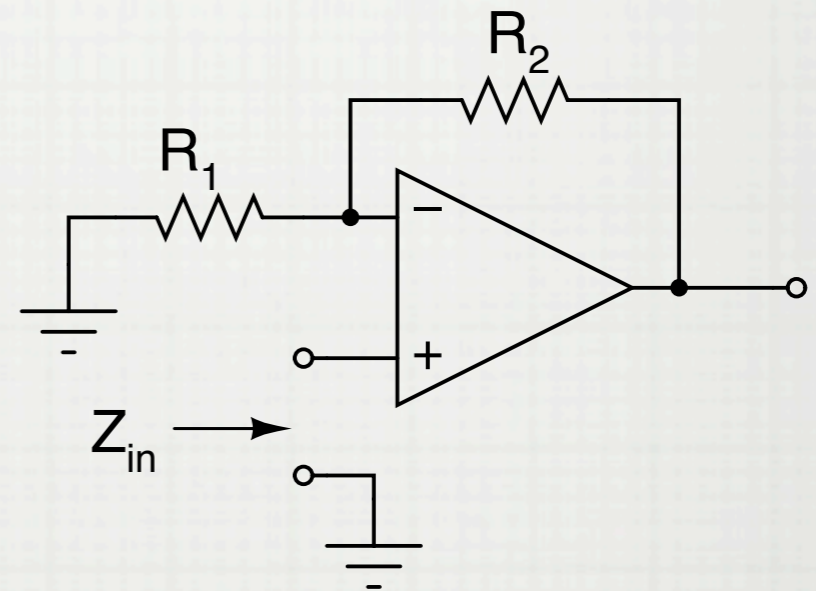
$$= \frac{1 + j \frac{f}{f_B}}{1 + j \frac{f}{f_b}} R_d$$




$$f_B = \beta f_t = \beta a_0 f_b$$

$$R_d = (1 + \beta a_0) r_d$$

INPUT-SERIES
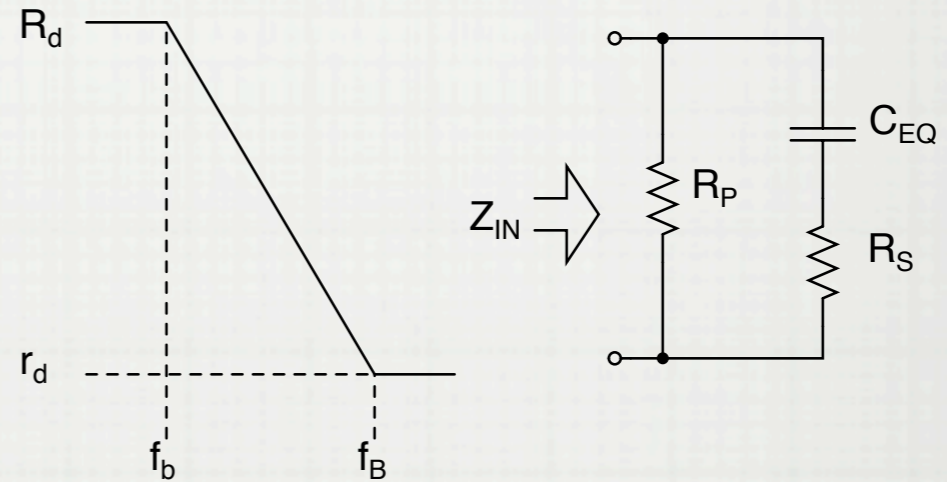
$$Z_{IN} = \frac{1 + j \frac{f}{f_B}}{1 + j \frac{f}{f_b}} R_d$$





$$R_P = R_d$$

$$R_S = r_d$$

$$C_{EQ} = \frac{1}{2\pi r_d f_B} = \frac{1}{2\pi r_d \beta f_t}$$

OUTPUT-SERIES

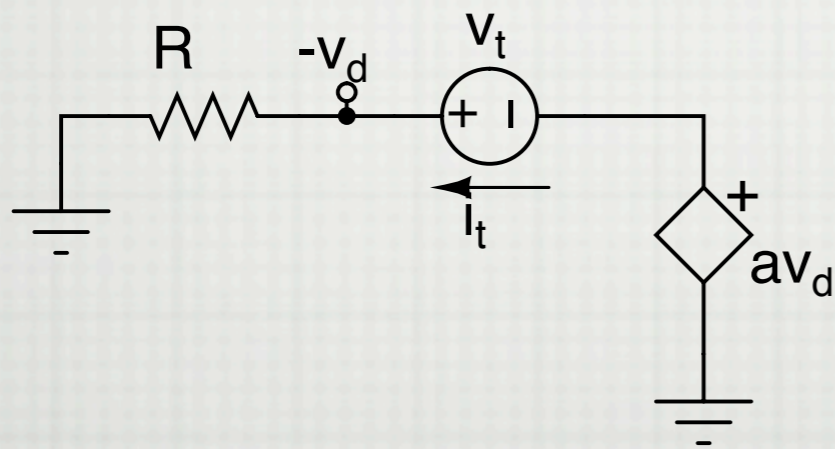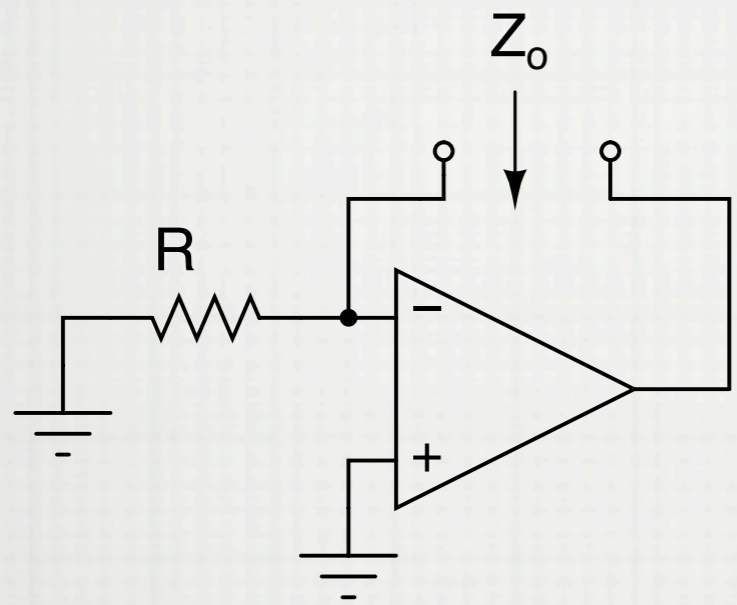

$$i_t = -\frac{v_d}{R} \Rightarrow v_d = -i_t R$$

$$v_t = (1 + a)v_d = -(1 + a)Ri_t$$

$$a = \frac{a_0}{1 + j\frac{f}{f_b}}$$


$$Z_{EQ} = -\left(1 + \frac{a_0}{1 + j\frac{f}{f_b}}\right) R$$

$$= -\left(\frac{1 + j\frac{f}{f_b(1+a_0)}}{1 + j\frac{f}{f_b}}\right) (1 + a_0) R$$

$$\approx -\left(\frac{1 + j\frac{f}{a_0 f_b}}{1 + j\frac{f}{f_b}}\right) (1 + a_0) R$$

$$\approx -\left(\frac{1 + j\frac{f}{f_t}}{1 + j\frac{f}{f_b}}\right) (1 + a_0) R$$



OUTPUT-SERIES

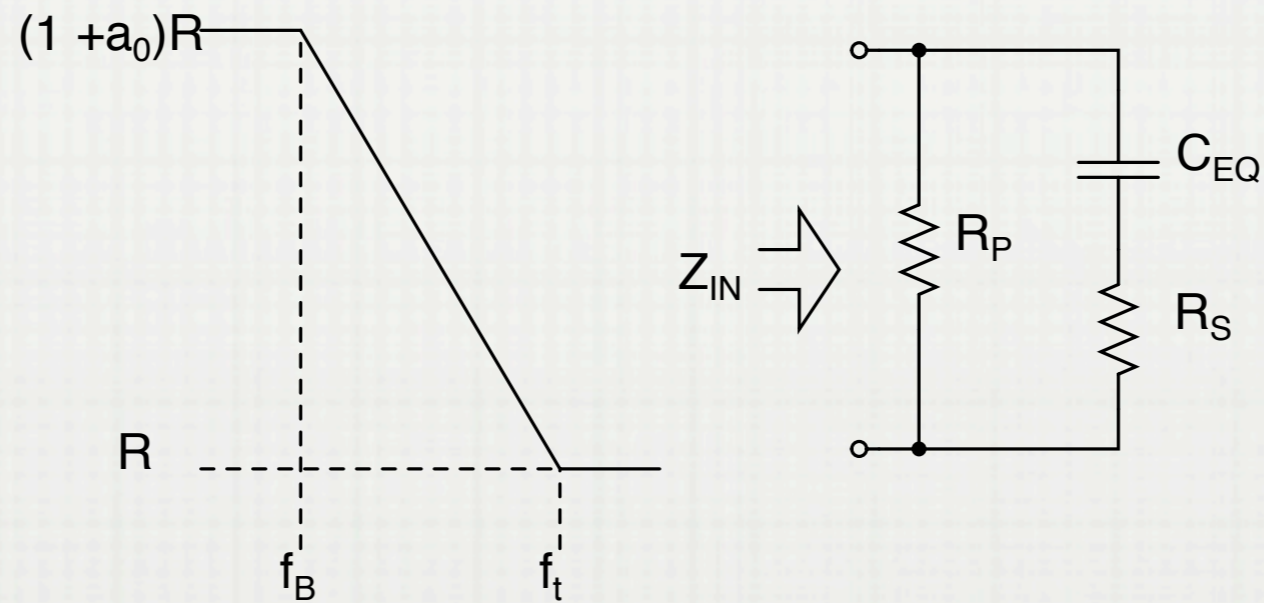

$$Z_{EQ} \approx - \left(\frac{1 + j \frac{f}{f_t}}{1 + j \frac{f}{f_b}} \right) (1 + a_0) R$$

$$R_P = (1 + a_0)R \quad R_S = R \quad C_{EQ} = \frac{1}{2\pi f_t R}$$



OUTPUT-SHUNT

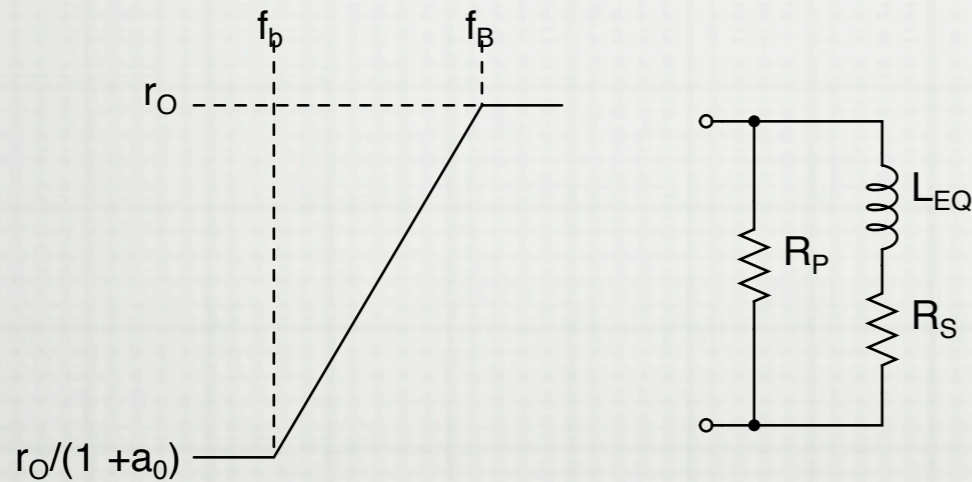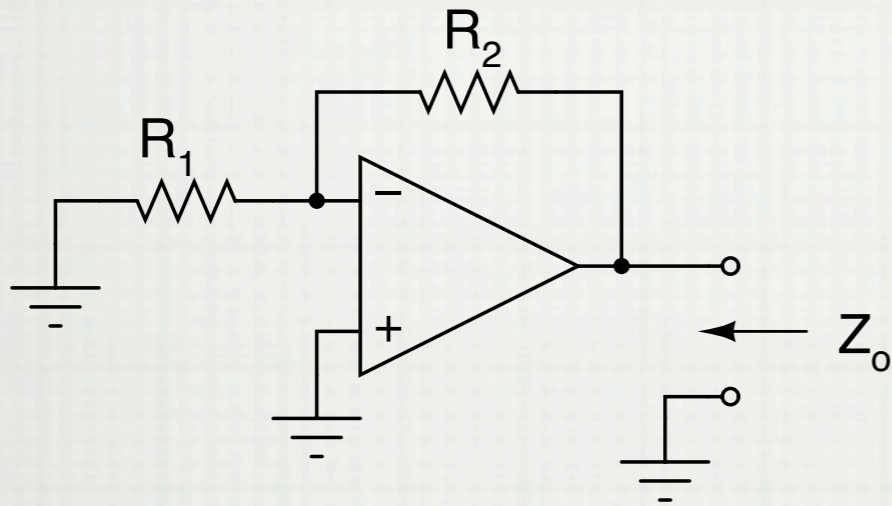

$$R_S = \frac{r_O}{1 + a_0} \quad R_P = r_0 \quad L_{EQ} = \frac{r_O}{2\pi f_B}$$

$$\begin{aligned} Z_O &= \frac{r_O}{1 + \beta a} = \frac{r_O}{1 + \frac{\beta a_0}{1 + jf/f_b}} \\ &= \frac{(1 + jf/f_b) r_O}{1 + jf/f_b + \beta a_0} \\ &= \frac{1 + jf/f_b}{1 + jf/(1 + \beta a_0) f_b} \frac{r_O}{1 + \beta a_0} \\ &\approx \frac{1 + jf/f_b}{1 + j \frac{f}{\beta a_0 f_b}} \frac{r_O}{1 + \beta a_0} \\ &\approx \frac{1 + jf/f_b}{1 + j \frac{f}{\beta f_t}} \frac{r_O}{1 + \beta a_0} \\ &\approx \frac{1 + j \frac{f}{f_b}}{1 + j \frac{f}{f_B}} \frac{r_O}{1 + \beta a_0} \end{aligned}$$

INPUT-SHUNT

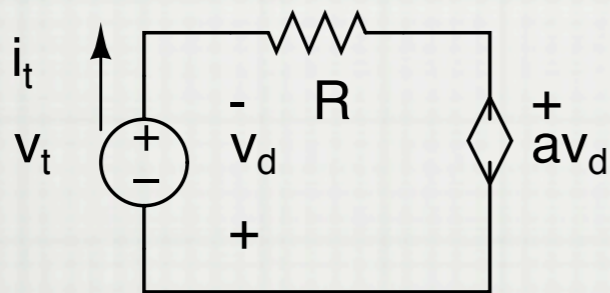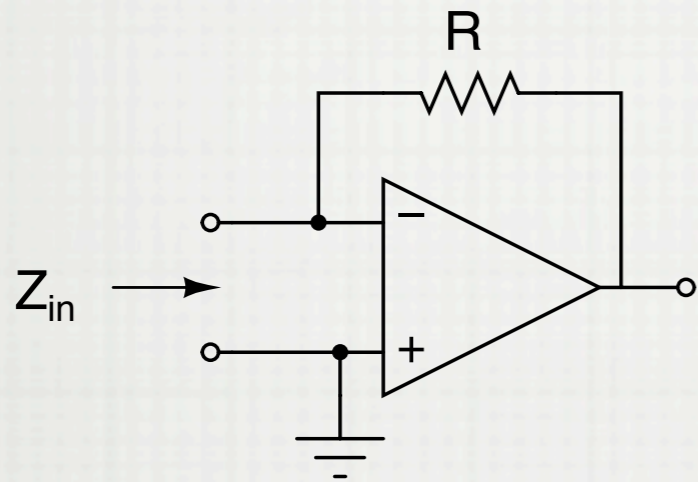


$$v_t = i_t R - a v_t$$

$$v_t(1 + a) = i_t R$$

$$\frac{v_t}{i_t} = Z_{EQ} = \frac{R}{1 + a}$$

$$\begin{aligned} Z_{EQ} &= \frac{R}{1 + \frac{a_0}{1 + j \frac{f}{f_b}}} \\ &= \frac{1 + j \frac{f}{f_b}}{1 + a_0 + j \frac{f}{f_b}} R \\ &= \frac{1 + j \frac{f}{f_b}}{1 + j \frac{f}{(1 + a_0) f_b}} \frac{R}{1 + a_0} \\ &\approx \frac{1 + j \frac{f}{f_b}}{1 + j \frac{f}{a_0 f_b}} \frac{R}{1 + a_0} \\ &\approx \frac{1 + j \frac{f}{f_b}}{1 + j \frac{f}{f_t}} \frac{R}{1 + a_0} \end{aligned}$$

INPUT-SHUNT

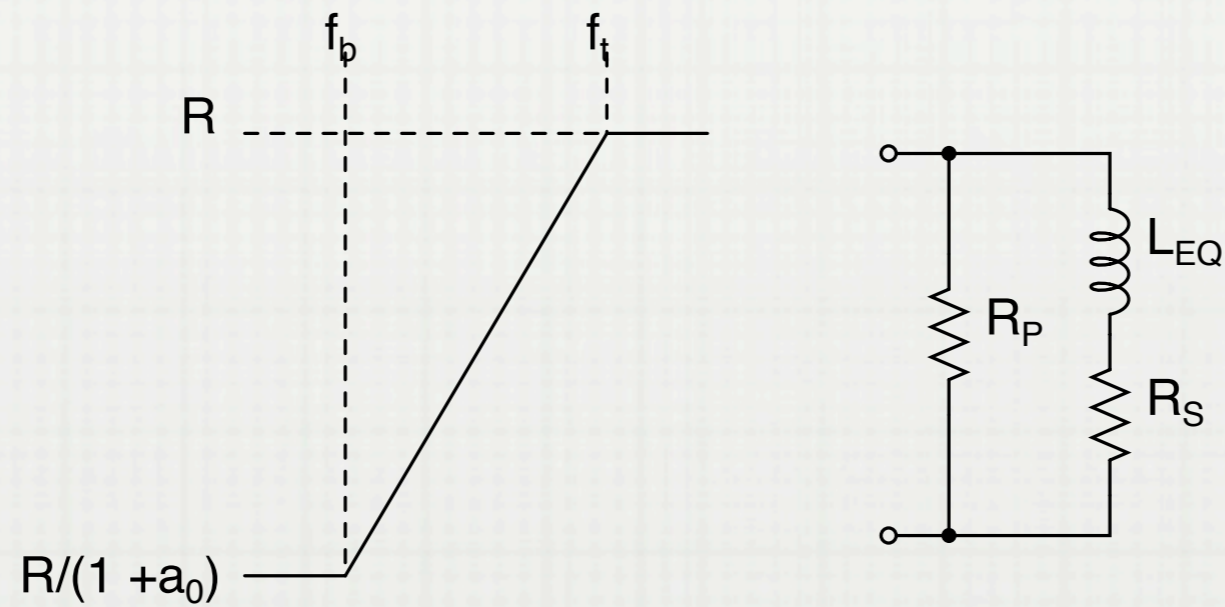

$$R_P = R \quad R_S = \frac{R}{1 + a_0} \quad L_{EQ} = \frac{R}{2\pi f_t}$$