

- 6.41 If the total energy stored in the circuit in Fig. P6.41 is 80 mJ, what is the value of L ?


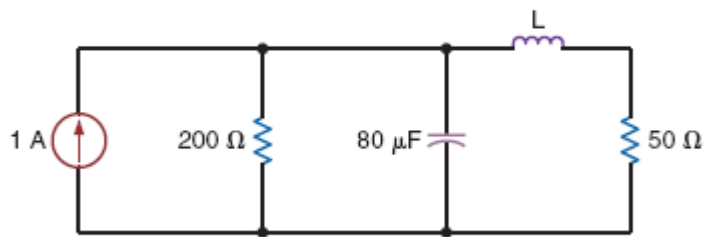


Figure P6.41


SOLUTION:

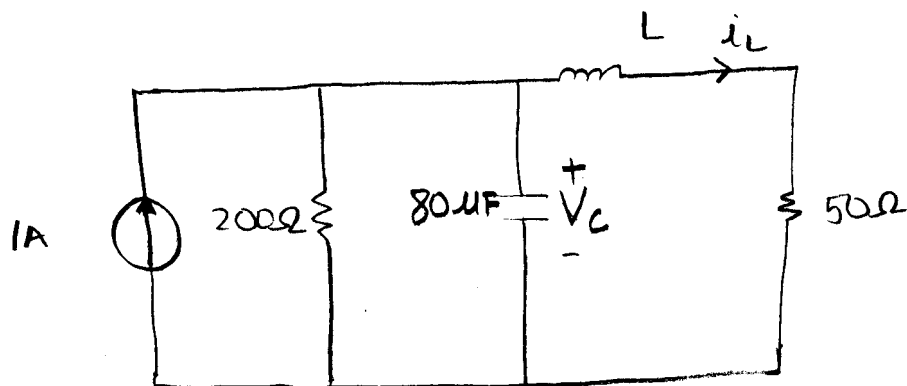

$$i_C = C \frac{dv_C}{dt} = 0, \quad v_C \text{ is a constant}$$

$$v_L = L \frac{di_L}{dt} = 0, \quad i_L \text{ is a constant}$$

Redraw the circuit as:

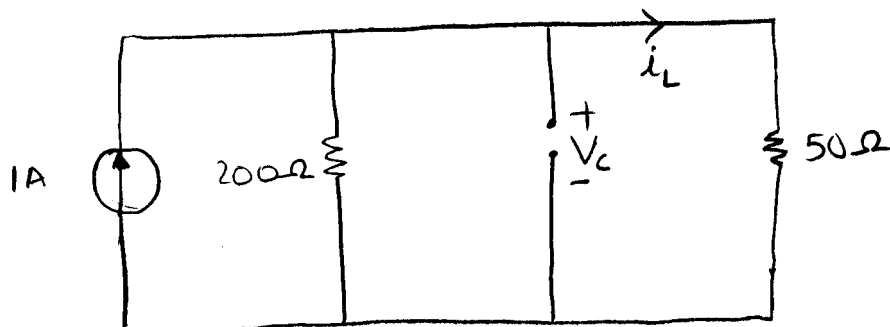

$$R_{eq} = 200 \parallel 50 = \frac{200(50)}{200+50}$$

$$R_{eq} = 40 \Omega$$

$$V_c = (1)(40) \quad V_c = 40V$$

$$W_c = \frac{1}{2} C V_c^2$$

$$W_c = \frac{1}{2} (80 \mu) (40)^2$$

$$W_c = 64 mJ$$

$$i_L = \left(\frac{200}{200+50} \right) (1)$$

$$i_L = 0.8 A$$

$$W_L = \frac{1}{2} L i_L^2$$

$$L = \frac{2 W_L}{i_L^2}$$

$$W_{total} = W_L + W_c$$

$$W_L = 80m - 64m$$

$$W_L = 16mJ$$

$$L = \frac{2(16m)}{(0.8)^2}$$

$$L = 50mH$$