

$$\frac{C dv_o(t)}{dt} = \frac{v_s - v_o}{5k} \quad ; \quad \frac{dv_o(t)}{dt} + \frac{v_o(t)}{125} = \frac{v_s(t)}{125} \quad ; \quad \frac{dv_o(t)}{dt} + 8v_o(t) = 8v_s(t)$$

$$\boxed{\frac{dv_o(t)}{dt} + 8v_o(t) = 48e^{-2t}}$$

ecuación diferencial que describe el sistema (I)

Natural (complem. sol) must satisfy

$$\frac{dv_{oc}(t)}{dt} + 8v_{oc}(t) = 0 \quad ; \quad .$$

$$\frac{dv_{oc}(t)}{dt} = -8v_{oc}(t) \quad ; \quad \int \frac{dv_{oc}(t)}{v_{oc}(t)} = \int -8 dt$$

$$\boxed{v_{oc}(t) = e^{-8t} K_2}$$

Forced response (particular sol.)

$$\frac{dv_{op}(t)}{dt} + 8v_{op}(t) = 48e^{-2t}$$

$v_{op}(t)$ & its derivative must have the form e^{-2t}

$$\text{Assume } \boxed{v_{op} = K_1 e^{-2t}}$$

$$\text{TOTAL SOL: } v_{oc}(t) = K_1 e^{-2t} + K_2 e^{-8t}$$

Now, substitute v_{op} in (I);

$$\frac{d(K_1 e^{-2t})}{dt} + 8(K_1 e^{-2t}) = 48e^{-2t} \quad ; \quad [K_1(-2) + 8K_1] e^{-2t} = 48e^{-2t}$$

$$\boxed{K_1 = 8}$$

$$\text{TOTAL SOLUTION: } v_o(t) = 8e^{-2t} + K_2 e^{-8t}$$

Use initial condit to determine K_2 : $v_o(0) = -18$


$$v_o(0) = -18 = 8e^0 + K_2 e^0$$

$$\boxed{K_2 = -26}$$

$$\boxed{v_o(t) = 8e^{-2t} - 26e^{-8t}} \quad t \geq 0$$

for $i(t)$:

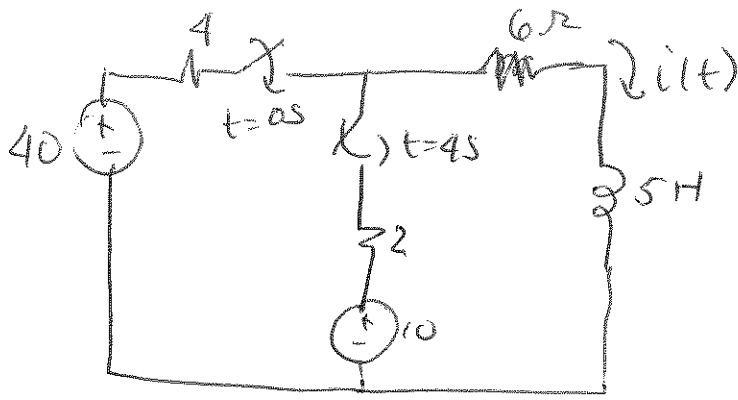
$$i(t) = \frac{C dv_o(t)}{dt} = 25 \times 10^{-6} \frac{d}{dt} [8e^{-2t} - 26e^{-8t}] = -0.4e^{-2t} + 5.2e^{-8t} \text{ mA } t > 0$$



find $i(t)$

$$i(t) = \begin{cases} 0 & \forall t \leq 0 \\ 4(1 - e^{-2t}) & \forall 0 \leq t \leq 4 \\ 2.72 + 1.273e^{-1.4667(t-4)} & \forall t \geq 4 \end{cases}$$

For $t \leq 4$

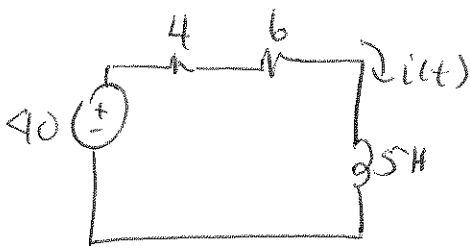

$$i(0) = 0$$


$$i(\infty) = \frac{40}{10} = 4A$$

$$\tau = \frac{L}{R_{eq}} = \frac{5}{10} = \frac{1}{2}$$

$$i(t) = 2i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

$$i(t) = 4(1 - e^{-2t}) \quad \forall 0 \leq t \leq 4$$

For $t \geq 4$

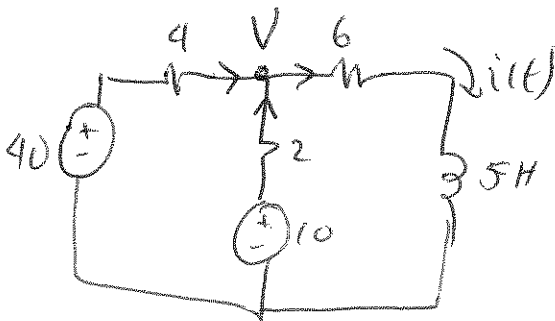

$$i(0) = i(4) = 4A$$


$$i(\infty) = ? ; i(\infty) = i(4)$$

$$i(\infty) = ? ; \frac{40 - V}{4} + \frac{10 - V}{2} = \frac{V}{6} ; V = \frac{180}{11} V$$

$$i(\infty) = \frac{V}{6} = \frac{180}{66} = 2.727A$$

$$\tau = (4 \parallel 2) + 6 = \frac{22}{3} \Omega$$

$$i(t) = 2.72 + 1.273e^{-1.4667(t-4)}$$

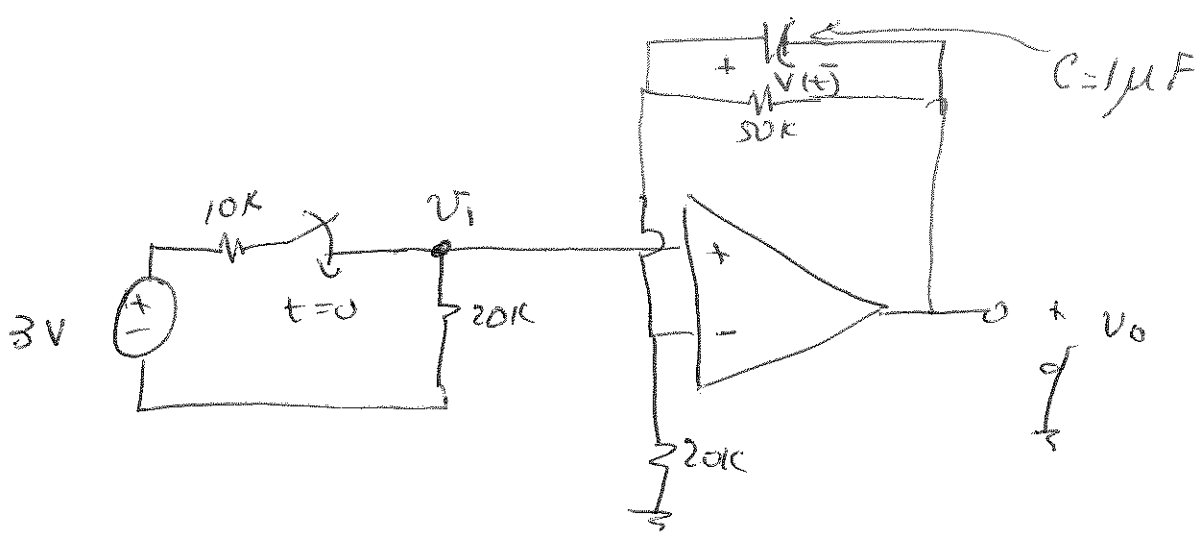

find $v(t)$:

$$\boxed{v(0^-) = 0}$$

$$v(0^+) = v(0^-) = 0$$

$$v(\infty) = ?$$

$$v_o(\infty) = \left(1 + \frac{50}{20}\right) v_i = 7 v_i$$

$$v_i = 3 \left(\frac{20}{30}\right) = 2V \quad ; \quad v_o(\infty) = \left(1 + \frac{50}{20}\right) 2 = 7V$$

divisor de voltaje

But, $v = v_i - v_o$:

$$\boxed{v(\infty) = 2 - 7 = -5}$$

$$\tau = RC = (1 \times 10^{-6})(50k\Omega) = 0.05$$

$$v(t) = -5 + [0 - (-5)] e^{-t/0.05} = -5 (1 - e^{-20t}) V \quad \# \underline{\underline{t > 0}}$$