

INEL 3105 Lecture #18

Note Title

11/10/2009

Factores:

$$v(t) = V_m \cos(\omega t + \theta) \rightarrow \hat{V} = V_m \angle \theta$$

$$= V_m e^{j\theta}$$

$$= V_m \cos \theta + j V_m \sin \theta$$

$$V_m = \sqrt{V_m^2 \cos^2 \theta + V_m^2 \sin^2 \theta} = V_m \sqrt{\cos^2 \theta + \sin^2 \theta} = V_m$$


Ejemplo: Evaluar los fasores de:

① $10 \cos(\omega t + 15^\circ)$

② $5 \sin(\omega t + 5^\circ)$

③ $-10 \cos(\omega t + 90^\circ)$; usando como base cos;

① $10 \angle 15^\circ$

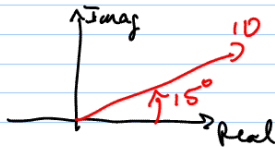


$$10 \angle 15^\circ = 10 e^{j15^\circ} = 10 \cos 15^\circ + j 10 \sin 15^\circ$$

② $5 \sin(\omega t + 5^\circ) = 5 \cos(\omega t + 5^\circ - 90^\circ)$

$$5 \cos(\phi - 90^\circ) = 5 \cos \phi \cos 90^\circ + 5 \sin \phi \sin 90^\circ$$

$$= 5 \sin \phi = 5 \sin(\omega t + 5^\circ)$$
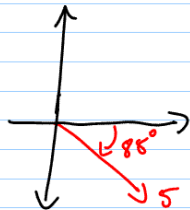
$$5 \angle -90^\circ = 5 \angle -85^\circ = 5 e^{-j85^\circ} = 5 e^{-j \frac{85}{180} \pi}$$



③ $-10 \cos(\omega t + 90^\circ) \rightarrow -10 \angle 90^\circ = -10 e^{j(\pi/2)}$

$$-10 = 10 \angle 180^\circ = 10 e^{j\pi}$$


$$-10 e^{j\pi/2} = 10 e^{j\pi} e^{j\pi/2} = 10 e^{j(3\pi/2)}$$



Números complexos: parte real & parte imaginária

$$j = \sqrt{-1}$$

$$z = x + jy$$

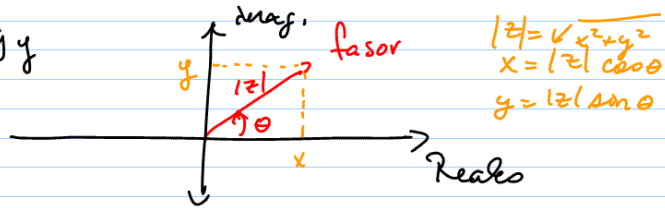

$$|z| = \sqrt{x^2 + y^2}$$

$$x = |z| \cos \theta$$

$$y = |z| \sin \theta$$

$$z = |z| \cos \theta + j |z| \sin \theta$$

$$= |z| \{ \cos \theta + j \sin \theta \}$$

Euler: $e^{j\theta} = \cos \theta + j \sin \theta$

$$z = |z| e^{j\theta} \leftarrow \text{forma polar}$$

$$|z| = \sqrt{x^2 + y^2} \quad \tan \theta = \frac{y}{x}$$

$$z = x + jy \leftarrow \text{forma rectangular}$$

Álgebra de #s Complexos:

① Soma: $z = z_1 \pm z_2$; $z_1 = x_1 + jy_1$, $z_2 = x_2 + jy_2$

$$z = (x_1 \pm x_2) + j(y_1 \pm y_2) = Z e^{j\theta}$$

$$|z| = \sqrt{(x_1 \pm x_2)^2 + (y_1 \pm y_2)^2} \quad ; \quad \theta = \tan^{-1} \frac{y_1 \pm y_2}{x_1 \pm x_2}$$

② Multiplicação: $z = z_1 z_2$; $z_1 = |z_1| e^{j\theta_1}$; $|z_1| = \sqrt{x_1^2 + y_1^2}$; $\theta_1 = \tan^{-1} \left(\frac{y_1}{x_1} \right)$
 $z_2 = |z_2| e^{j\theta_2}$; $|z_2| = \sqrt{x_2^2 + y_2^2}$; $\theta_2 = \tan^{-1} \left(\frac{y_2}{x_2} \right)$

$$z = z_1 z_2 = |z_1| e^{j\theta_1} |z_2| e^{j\theta_2}$$

$$= |z_1| |z_2| e^{j(\theta_1 + \theta_2)} = Z e^{j\theta} \rightarrow \theta = \theta_1 + \theta_2$$

$$|z| = |z_1| |z_2|$$

(3) División: $z = \frac{z_1}{z_2} = \frac{|z_1| e^{j\theta_1}}{|z_2| e^{j\theta_2}} = \frac{|z_1|}{|z_2|} e^{j\theta_1} e^{-j\theta_2}$

$$z = \frac{|z_1|}{|z_2|} e^{j(\theta_1 - \theta_2)} = z e^{j\theta} \rightarrow \theta = \theta_1 - \theta_2$$

↓

$$|z| = \frac{|z_1|}{|z_2|}$$

Ejemplo: $z = z_1 + \frac{z_2}{z_3} z_4$

$$\begin{aligned} z_1 &= 4e^{j45^\circ} \\ z_2 &= 2e^{j90^\circ} \\ z_3 &= 8e^{j53^\circ} \\ z_4 &= 4 + j3 \end{aligned}$$

Solución: $\frac{z_2}{z_3} = \frac{2e^{j90^\circ}}{8e^{j53^\circ}} = \frac{1}{4} e^{j(90-53)^\circ} = \frac{1}{4} e^{j37^\circ}$

$$\left(\frac{z_2}{z_3}\right) z_4 = \frac{1}{4} e^{j37^\circ} (4 + j3) ; \quad z_4 = \sqrt{4^2 + 3^2} e^{j \tan^{-1}\left(\frac{3}{4}\right)} = 5 e^{j37^\circ}$$

$$\begin{aligned} \frac{z_2}{z_3} z_4 &= \frac{1}{4} e^{j37^\circ} 5 e^{j37^\circ} = \frac{5}{4} e^{j74^\circ} = \frac{5}{4} [\cos 74^\circ + j \sin 74^\circ] \\ &= -0.344 + j1.20 \quad (\text{en forma rectangular}) \end{aligned}$$

$$z_1 = 4 \left[4 \cos 45^\circ + j \sin 45^\circ \right] = 4 \left[\frac{\sqrt{2}}{2} + j \frac{\sqrt{2}}{2} \right] = 2\sqrt{2} + j2\sqrt{2}$$

$$z = 2\sqrt{2} + j2\sqrt{2} - 0.344 + j1.20 = 3.17 + j4.028 ; \quad |z| = \sqrt{3.17^2 + 4.028^2} = 5.13$$

← 3.17 ← 4.028

$$\theta = \tan^{-1}\left(\frac{4.028}{3.17}\right) = 51.8^\circ$$

$$z = 5.13 e^{j51.7^\circ} \quad \leftarrow \text{en forma polar}$$

Fasores:

$$v(t) = V_m \cos(\omega t + \theta)$$


$$= \operatorname{Re} \left\{ V_m e^{j(\omega t + \theta)} \right\}$$

↑
operador de parte real.

$$= \operatorname{Re} \left\{ \underbrace{V_m \cos(\omega t + \theta)}_{\text{real}} + j \underbrace{V_m \sin(\omega t + \theta)}_{\text{imaginario}} \right\} = V_m \cos(\omega t + \theta)$$

$$V_m e^{j(\omega t + \theta)} = \underbrace{V_m e^{j\theta}}_{\text{fasor de } \uparrow} e^{j\omega t} = \hat{V} = V_m e^{j\theta}$$

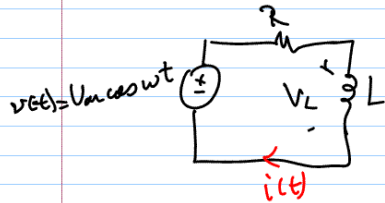Ejemplo: Evaluar $i(t)$ en régimen permanente



Solución:

$$-v(t) + R i(t) = -L \frac{di(t)}{dt}$$

$$v(t) = V_m e^{j\omega t}$$

$$i(t) = I_m e^{j(\omega t + \phi)}$$

$$L \frac{d}{dt} [I_m e^{j(\omega t + \phi)}] + R I_m e^{j(\omega t + \phi)} = V_m e^{j\omega t}$$

$$L I_m j\omega e^{j(\omega t + \phi)} + R I_m e^{j(\omega t + \phi)} = V_m e^{j\omega t}$$

$$j\omega L I_m e^{j\omega t} e^{j\phi} + R I_m e^{j\omega t} e^{j\phi} = V_m e^{j\omega t}$$

$$j\omega L I_m e^{j\phi} + R I_m e^{j\phi} = V_m$$

↑ ↑ fasor de $i(t) = \hat{I}$

$$j\omega L \hat{I} + R \hat{I} = V_m$$

$$\hat{I} \{R + j\omega L\} = V_m ; \hat{I} = \frac{V_m}{R + j\omega L} = \frac{V_m e^{j0}}{\sqrt{R^2 + L^2 \omega^2} e^{j \tan^{-1}(\frac{\omega L}{R})}}$$

$$= \frac{V_m}{\sqrt{R^2 + L^2 \omega^2}} e^{j(0 - \tan^{-1}(\frac{\omega L}{R}))}$$

$$\hat{I} = \frac{V_m}{\sqrt{R^2 + L^2 \omega^2}} e^{-j \tan^{-1}(\frac{\omega L}{R})} = I_m e^{j\phi}$$

$$I_m = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \quad \phi = -\tan^{-1}\left(\frac{\omega L}{R}\right)$$

$$V_m e^{j\omega t} \rightarrow i(t) = I_m e^{j(\omega t + \phi)}$$

$$V_m \cos \omega t \rightarrow i(t) = I_m \cos(\omega t + \phi) \\ = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos\left(\omega t - \tan^{-1}\left(\frac{\omega L}{R}\right)\right)$$

excitación: $v(t) = V_m e^{j(\omega t + \theta_v)} \leftarrow \text{Re}[v(t)]$

respuesta: $x(t) = X_m e^{j(\omega t + \theta_x)} \leftarrow \text{Re}[x(t)]$


excitación: $v(t) = V_m \cos(\omega t + \theta_v)$

respuesta: $x(t) = X_m \cos(\omega t + \theta_x)$

Faseor de $v(t) = V_m e^{j\theta_v} = \hat{V} = V_m e^{j(\omega t + \theta_v)}$
amplitud ángulo de fase

produce el faseor $\hat{X} = X_m e^{j\theta_x}$; $x(t) = X_m e^{j(\omega t + \theta_x)}$

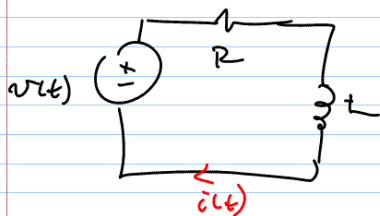ejemplo: Eval $i(t)$ en régimen permanente



$$v(t) = V_m \cos \omega t = V_m e^{j\omega t}$$

$$v(t) = Ri + L \frac{di(t)}{dt}$$

$$i(t) = I_m e^{j(\omega t + \theta)}; \text{ Faseor de } i(t) = \hat{I} = I_m e^{j\theta}$$


$$V_m e^{j\omega t} = R I_m e^{j\omega t} e^{j\theta} + j\omega L I_m e^{j\omega t} e^{j\theta}$$

$$V_m = R I_m e^{j\theta} + j\omega L I_m e^{j\theta}$$

$$\hat{V} = R\hat{I} + j\omega L\hat{I}$$

unidades de ohmios

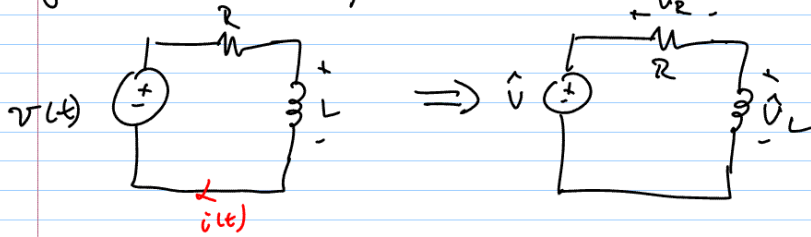$j\omega L =$ Resistencia equivalente en un inductor ; Impedancia = Z_L



$$v_R(t) = Ri(t)$$

$$\hat{V}_R = R\hat{I}$$

$$v_L(t) = L \frac{di(t)}{dt} \Rightarrow \hat{V}_L = j\omega L \hat{I}$$

$\frac{d}{dt} = j\omega$

Suma de voltajes fase por fase "KVL"

$$\hat{V} - \hat{V}_R - \hat{V}_L = 0 ; \hat{V} = R\hat{I} + j\omega L\hat{I}$$

$$\hat{I} = \frac{\hat{V}}{R + j\omega L} ; \hat{I} = \frac{\hat{V}}{\hat{Z}} ; \hat{Z} = R + j\omega L$$


$$\hat{Z} = R + j\omega L = |z| e^{j\theta_z}$$

$$|z| = \sqrt{R^2 + \omega^2 L^2}$$

$$\theta_z = \tan^{-1}\left(\frac{\omega L}{R}\right)$$

$$\hat{I} = \frac{\hat{V}}{|z| e^{j\theta_z}} = \frac{V_m}{|z|} e^{-j\theta_z} ; \hat{I} = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} e^{-j \tan^{-1}\left(\frac{\omega L}{R}\right)} = I_m e^{j\phi}$$

Inductores:

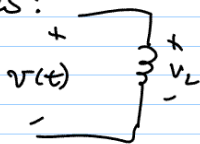

$$\oint \mathbf{E} \cdot d\mathbf{l} = 0 ; -v(t) + 0 = -L \frac{di(t)}{dt} \Rightarrow v(t) = L \frac{di(t)}{dt}$$

$$V_m e^{j\omega t} e^{j\phi} = L \frac{d}{dt} [I_m e^{j\omega t} e^{j\phi}]$$

$$= L I_m e^{j\phi} j\omega e^{j\omega t}$$

$$V_m e^{j\phi} = j\omega L I_m e^{j\phi}$$

$$\hat{V} = j\omega L \hat{I}_L ; \hat{I}_L = I_m e^{j\phi}$$

$$\hat{V}_L = j\omega L \hat{I}_L \rightarrow \text{impedancia inductiva } Z_L = j\omega L$$

$$V_L = Z_L \hat{I}_L$$

$$V_m e^{j\theta_v} = j\omega L I_m e^{j\theta_i}$$

$$V_m e^{j\theta_v} = \omega L I_m e^{j\theta_i} e^{j\pi/2}$$

$$= \omega L I_m e^{j(\theta_i + \pi/2)}$$

$$j = |j| e^{j\pi/2} ; |j| = 1$$

$$\angle j = \tan^{-1}\left(\frac{1}{0}\right) = 90^\circ = \pi/2$$

$$j = e^{j\pi/2}$$

$$V_m = \omega L I_m$$

$$\theta_v = \theta_i + \pi/2$$

V_L "leads" I_m by $\pi/2$